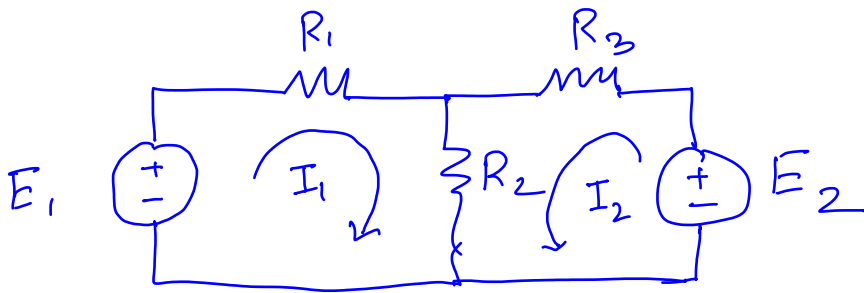


## Quick Recap

Superposition Theorem  $\rightarrow$



$$E_1 = I_1 R_1 + (I_1 + I_2) R_2$$

$$E_2 = I_2 R_3 + (I_1 + I_2) R_2$$

$$A x = b$$

$$A = \begin{bmatrix} R_1 + R_2 & R_2 \\ R_2 & R_2 + R_3 \end{bmatrix}$$


$$x = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$b = \begin{bmatrix} E_1 \\ E_2 \end{bmatrix}$$


$$b = \underbrace{\begin{bmatrix} E_1 \\ 0 \end{bmatrix}}_{b_1} + \underbrace{\begin{bmatrix} 0 \\ E_2 \end{bmatrix}}_{b_2}$$

$$A x = b = b_1 + b_2$$
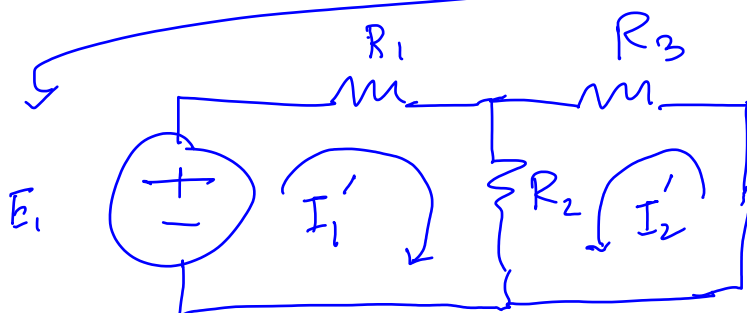
$$x = \underbrace{A^{-1} b_1}_{x_1} + \underbrace{A^{-1} b_2}_{x_2}$$



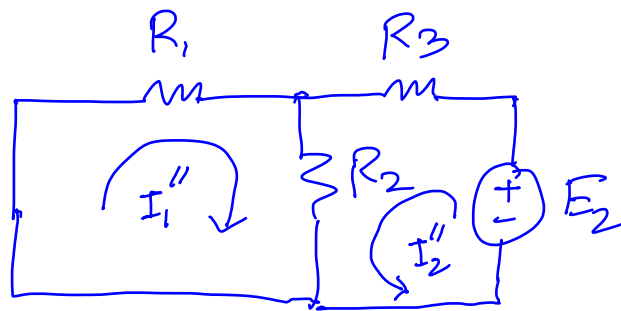
$$x_1 = \begin{bmatrix} I_1' \\ I_2' \end{bmatrix}$$




$$\mathcal{R}_2 = \begin{bmatrix} I_1'' \\ I_2'' \end{bmatrix}$$

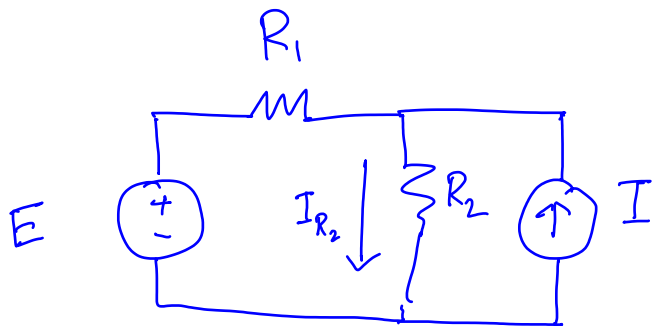
$$\left. \begin{aligned} I_1 &= I_1' + I_1'' \\ I_2 &= I_2' + I_2'' \end{aligned} \right\}$$



$$I_{R_2} = ?$$

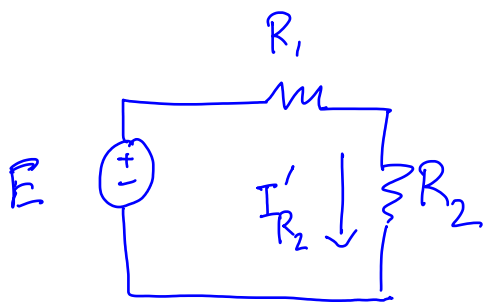

$$I'_{R_2} = \frac{E}{R_1 + R_2}$$

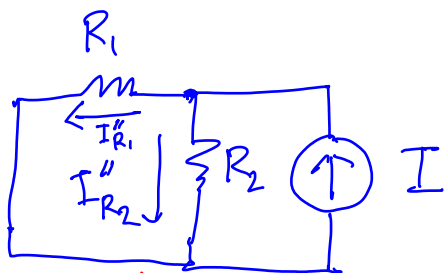

$$I = I''_{R_1} + I''_{R_2}$$

$$\underline{I''_{R_1}} \cdot R_1 = \underline{I''_{R_2}} \cdot R_2$$

$$I''_{R_2} + \frac{R_2}{R_1} I''_{R_2} = I$$


$$\Rightarrow I''_{R_2} = \frac{R_1 I}{R_1 + R_2}$$

*Total current*  $\rightarrow$   $I_{R_2} = I'_{R_2} + I''_{R_2}$


*Current due to E*  $\rightarrow$

*Current due to I*  $\rightarrow$
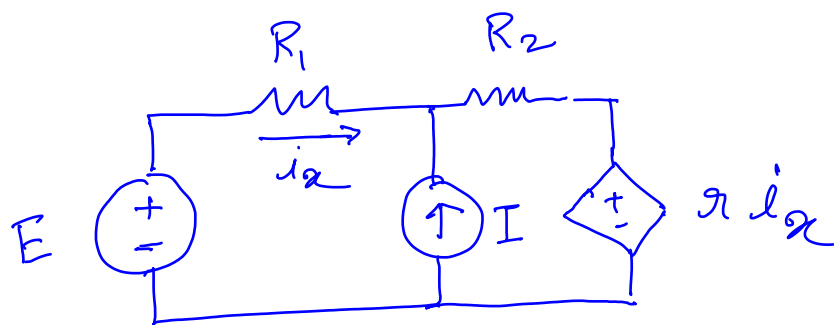
$$= \frac{E}{R_1 + R_2} + \frac{R_1 I}{R_1 + R_2}$$




$$\pi i_x = ?$$

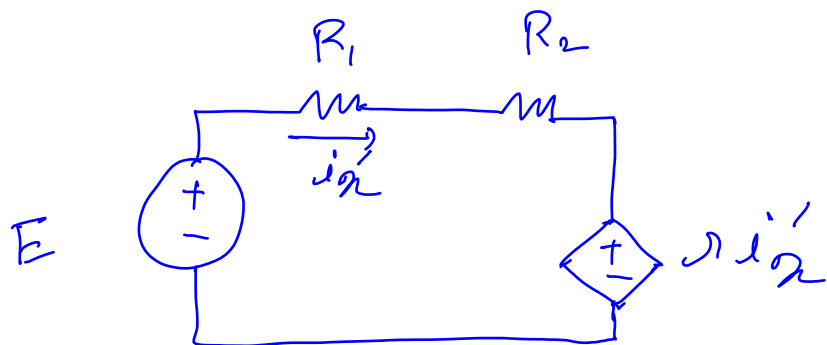

$$i'_x = \frac{E - \pi i'_x}{R_1 + R_2}$$

↓  
solve for  $i'_x$

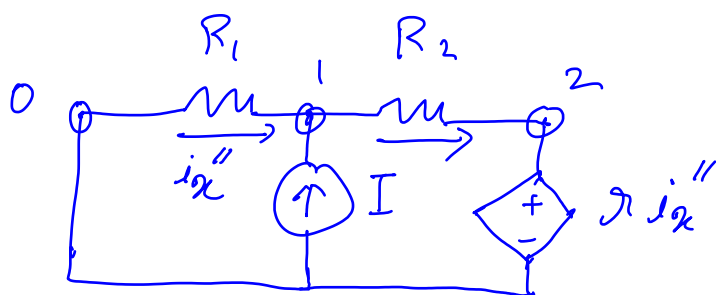

KCL at node 1

$$i''_x + I = \frac{V_1 - V_2}{R_2}$$

$$i''_x = -\frac{V_1}{R_1}$$


$$V_2 = \pi i''_x$$

solve for  $i''_x$


Total current  
→  
Current due to E  
→  
current due to I  
→

$$i_x = i'_x + i''_x$$


## Thevenin's Theorem / Norton's Theorem

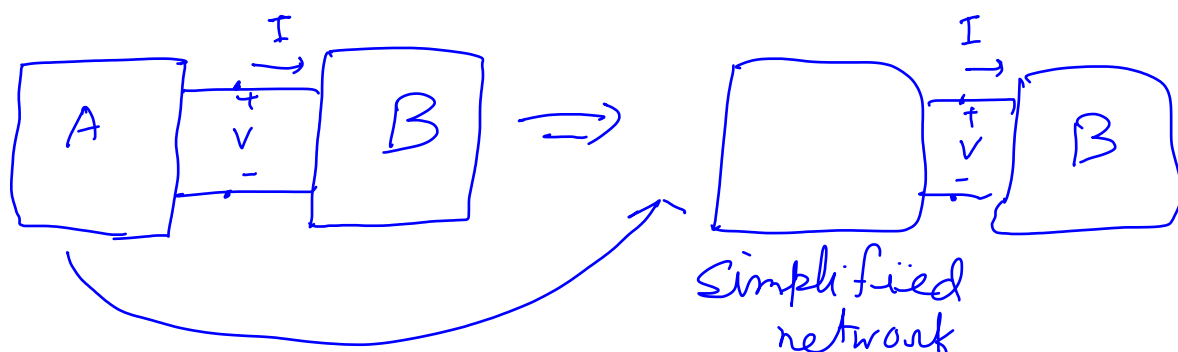

## Thevenin Equivalent of Network A

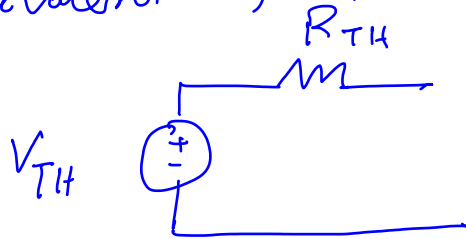

## Norton Equivalent of Network A

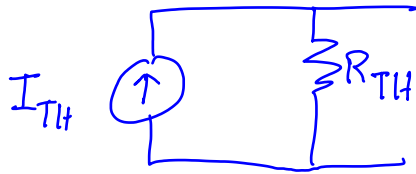

$$V_{TH} = I_{TH} \cdot R_{TH}$$


## Properties of Network A

- 1) It should be a linear network
- 2) Voltage sources or current sources can be present.
- 3) There should be no controlled-source coupling with network B.

## Properties of Network B

- 1) It can be linear or non-linear
- 2) There should not be any coupling via controlled sources with network A.


## How to Compute $V_{TH}$

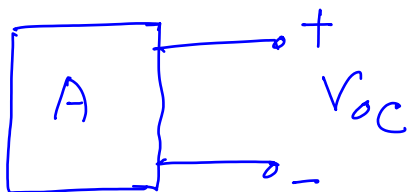

Remove network B and compute  $V_{OC}$

$$V_{TH} = V_{OC}$$


## How to Compute $I_{TH}$

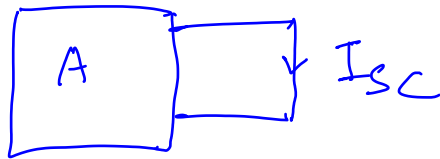



Remove network B, short-circuit the terminal and compute  $I_{sc}$

$$I_{TH} = I_{sc}$$

## How to compute $R_{TH}$

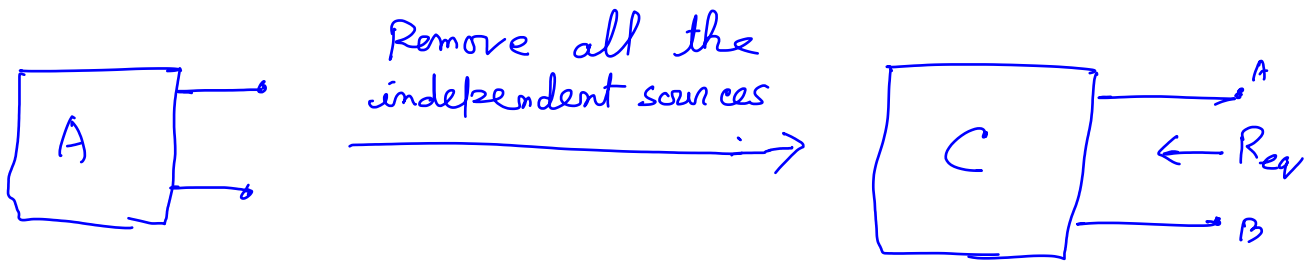

$$R_{TH} = R_{eq}$$

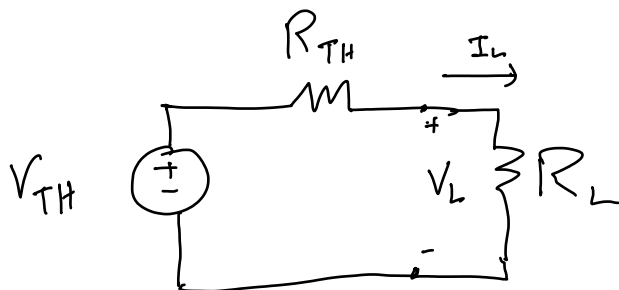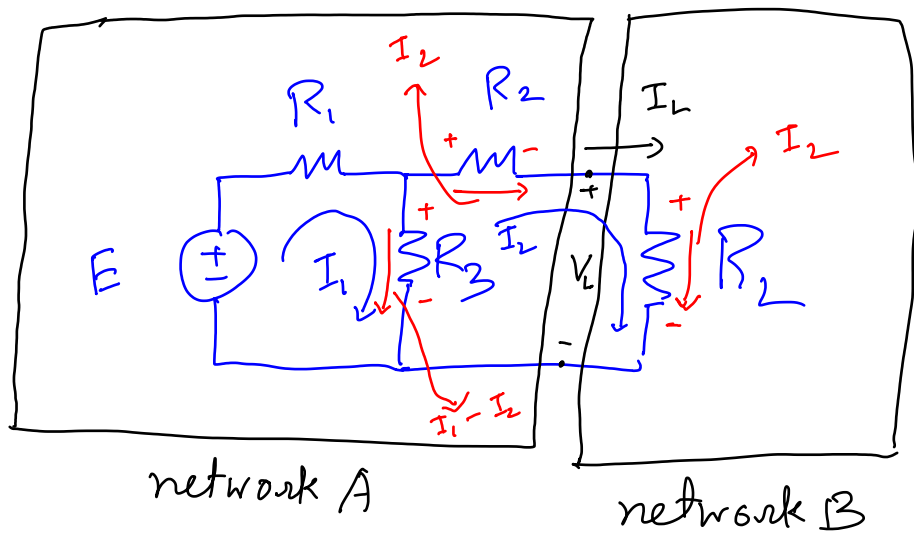

$$E = I_1 R_1 + (I_1 - I_2) R_3$$

$$(I_1 - I_2) R_3 = I_2 (R_2 + R_L)$$

$$I_L = I_2$$


$$I_1 R_3 = I_2 (R_3 + R_2 + R_L)$$

$$\begin{aligned} E &= I_1 (R_1 + R_3) - I_2 R_3 \\ &= \frac{R_1 + R_3}{R_3} \cdot (R_3 + R_2 + R_1) \cdot I_2 - I_2 R_3 \end{aligned}$$


$$I_2 \left( \frac{(R_1 + R_3)(R_3 + R_2 + R_L)}{R_3} - R_3 \right) = E$$

$$I_L = I_2 = \frac{E \cdot R_3}{R_1 R_2 + R_1 R_2 + R_1 R_L + R_3 R_2 + R_3 R_L} \}$$

Thevenin Equivalent Circuit,

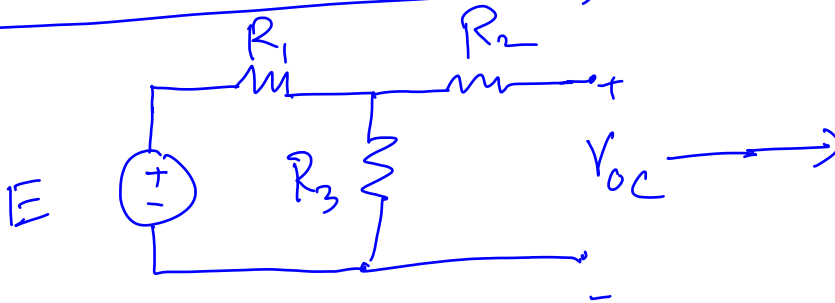


= network A

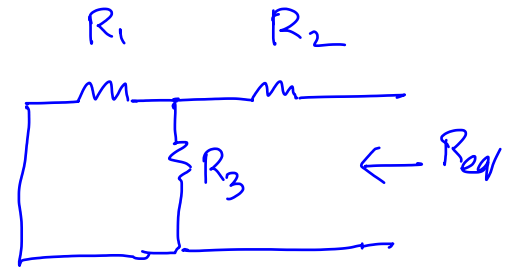

network C

$$R_{TH} = R_2 + \frac{R_1 R_3}{R_1 + R_3}$$
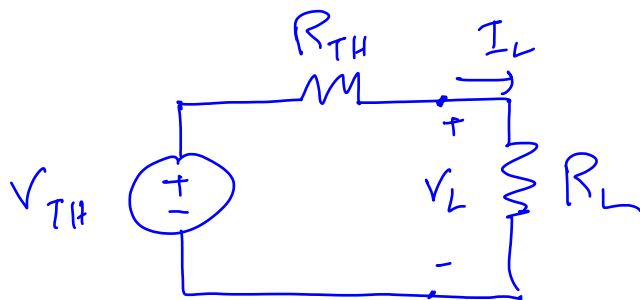
$$V_{TH} = V_{OC} = \frac{R_3 E}{R_1 + R_3} \quad \checkmark$$



$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$= \frac{E R_3 / (R_1 + R_3)}{R_2 + \frac{R_1 R_3}{R_1 + R_3} + R_L}$$

$$= \frac{E R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3 + R_1 R_L + R_3 R_L}$$



