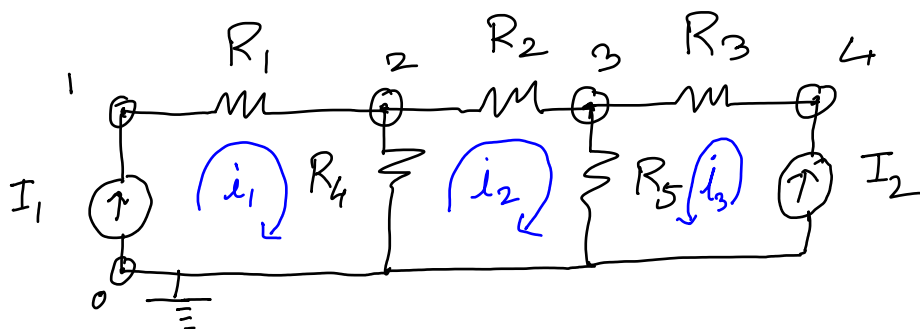


Quick Recap

"b" \rightarrow no. of branches
 "n" \rightarrow no. of nodes


(n-1) variables to do node analysis
 (b-n+1) variables to do loop analysis



(circuit)


$$i_1 = I_1$$

$$i_3 = I_2$$

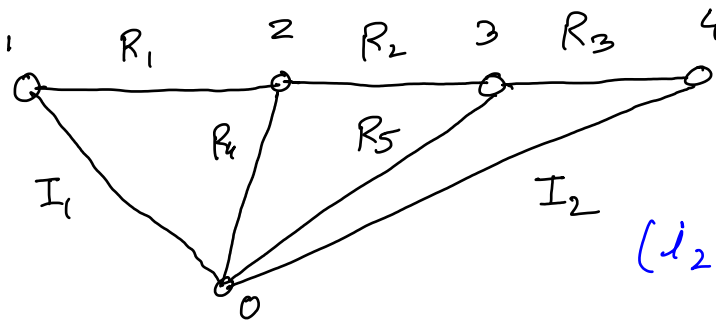


(graph)
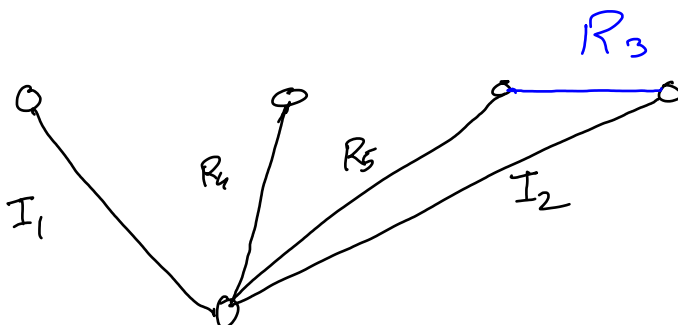
$$(i_2 - i_1) R_4 + i_2 R_2 + (i_2 + i_3) R_5 = 0$$



(tree)

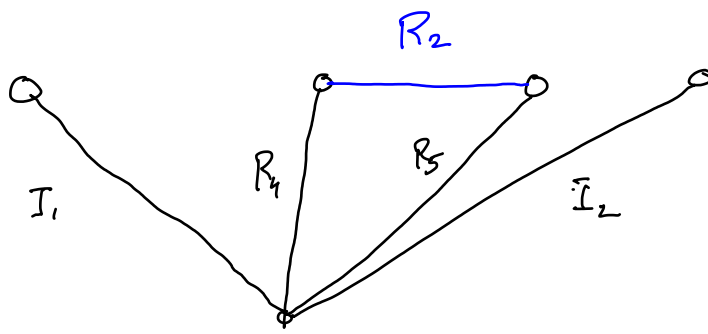


Mesh \rightarrow a loop which does not contain any other loop.


Loops $\rightarrow 6$

Meshs $\rightarrow 3$

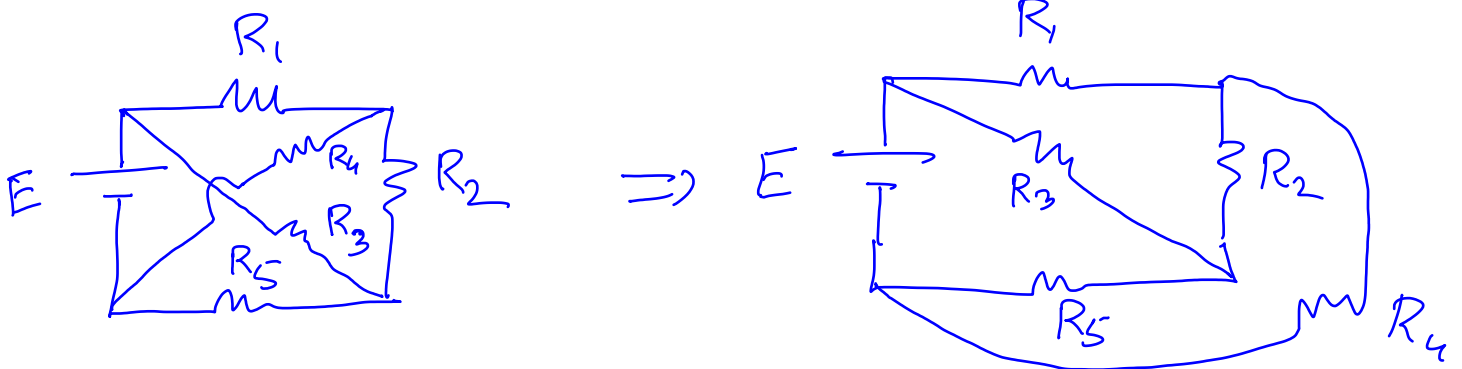For planar circuits, use Mesh currents as independent variables --




(planar)

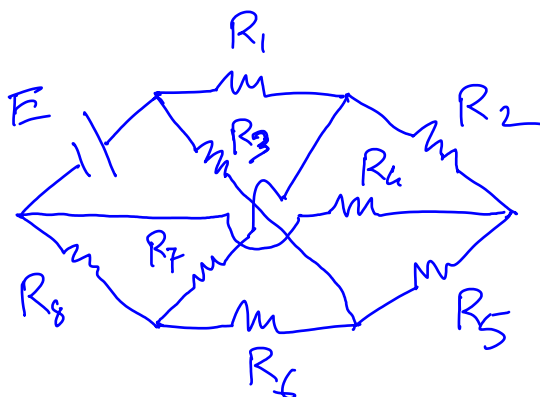

(non-planar)

Node Analysis

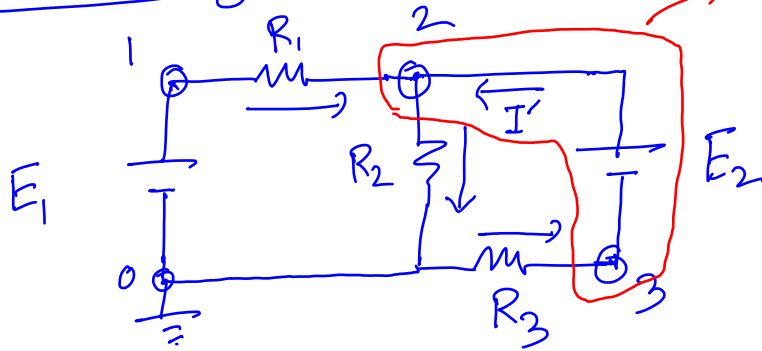

$$V_1, V_2, V_3$$

$$V_1 = E_1$$


$$V_2 - V_3 = E_2$$

$$\left. \begin{aligned} \frac{V_1 - V_2}{R_1} + I' &= \frac{V_2}{R_2} \\ -\frac{V_3}{R_3} &= I' \end{aligned} \right\} \text{Combine}$$

$$\frac{V_1 - V_2}{R_1} - \frac{V_3}{R_3} = \frac{V_2}{R_2}$$

✓ } — (eq. using super node)

Mesh Analysis

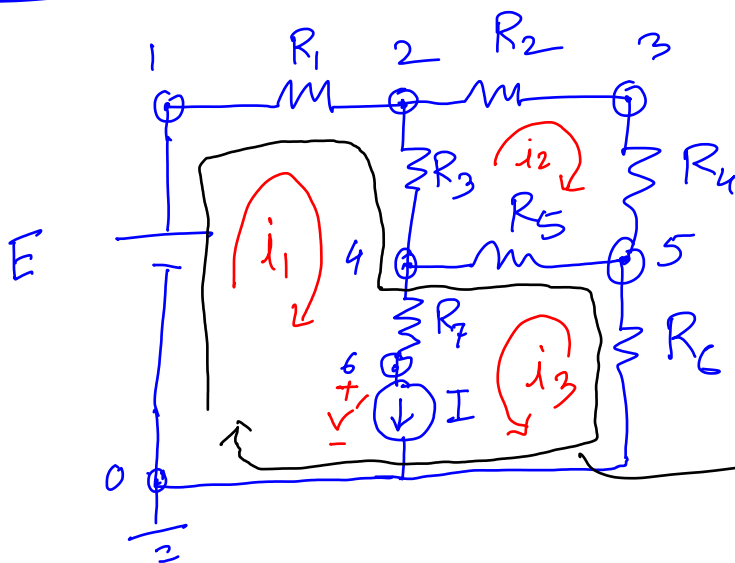

$$b = 9$$

$$n = 7$$

$$b - n + 1 = 3$$

(Super Mesh)

KVL will lead to eq. (5).

KVL at Mesh 1,

$$E = i_1 R_1 + (i_1 - i_2) R_3 + (i_1 + i_2) R_7 + V' \quad \text{--- (1)}$$

$$(i_2 - i_1) R_3 + i_2 R_2 + i_2 R_4 + (i_2 + i_3) R_5 = 0 \quad \text{--- (2)}$$

$$(i_3 + i_1) R_2 + V' + i_3 R_6 + (i_3 + i_2) R_5 = 0 \quad \text{--- (3)}$$

Adding (1) and (3),

$$\checkmark \quad E + i_3 R_6 + (i_3 + i_2) R_5 = i_1 R_1 + (i_1 - i_2) R_3 \quad \text{--- (5)}$$

$$i_1 + i_3 = I \quad \text{--- (4)}$$

Use (2), (4) and (5) to solve for i_1 , i_2 and i_3 .

