
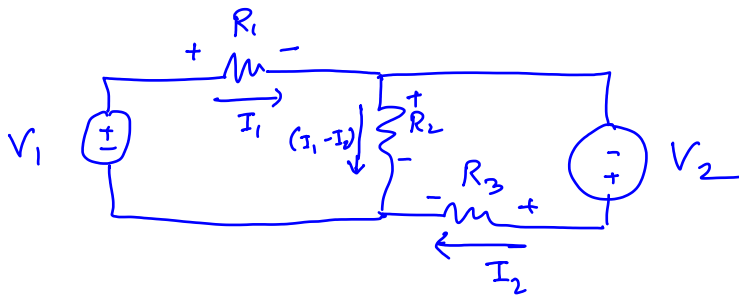


Quick Recap

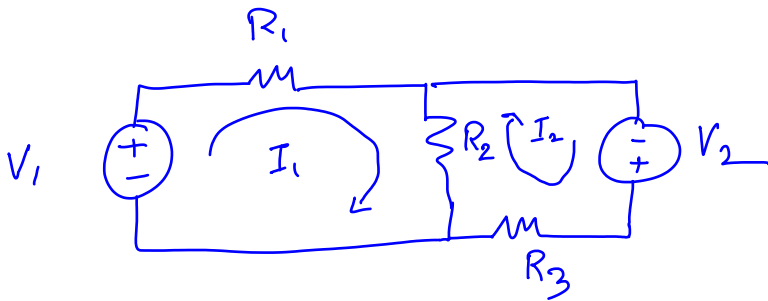

$$V_1 - V_{R_1} - V_{R_2} = 0$$

$$V_2 - V_{R_3} + V_{R_2} = 0$$

$$V_{R_1} = I_1 R_1$$


$$V_{R_2} = (I_1 - I_2) R_2$$

$$V_{R_3} = I_2 R_3$$

Capacitors

$$Q = C V$$

↪ Capacitance

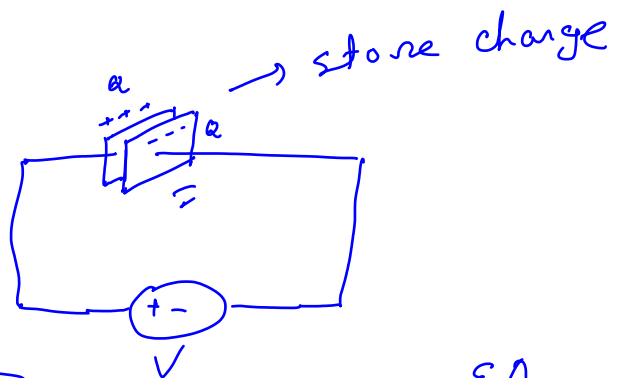

$$I = \frac{dq}{dt} = C \frac{dv}{dt}$$

$$C = \frac{\epsilon A}{d}$$


$\epsilon \rightarrow$ permittivity

$A \rightarrow$ area of the plate

$d \rightarrow$ distance between the plates

unit of capacitance Farad = $\frac{\text{Coulomb}}{\text{volt}}$ }

Capacitor Charging →

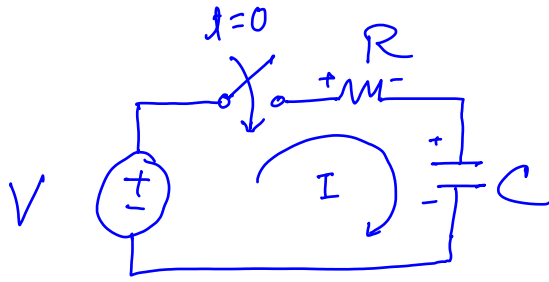

$$V = V_R + V_C$$

$$V = IR + V_C$$

$$= CR \frac{dV_C}{dt} + V_C$$

$$V = RC \frac{dV_C}{dt} + V_C$$

$$\Rightarrow \int_0^{V_C} \frac{dV_C}{V - V_C} = \int_0^t \frac{1}{RC} dt$$

$$\Rightarrow -\ln\left(\frac{V - V_C}{V}\right) = \frac{t}{RC}$$


$$\Rightarrow \frac{V - V_C}{V} = e^{-t/RC}$$

$$\Rightarrow V_C = V - V e^{-t/RC}$$

$$V_C = V(1 - e^{-t/RC}) \quad \forall t \geq 0$$

$$\text{at } t=0 \quad V_C = 0$$

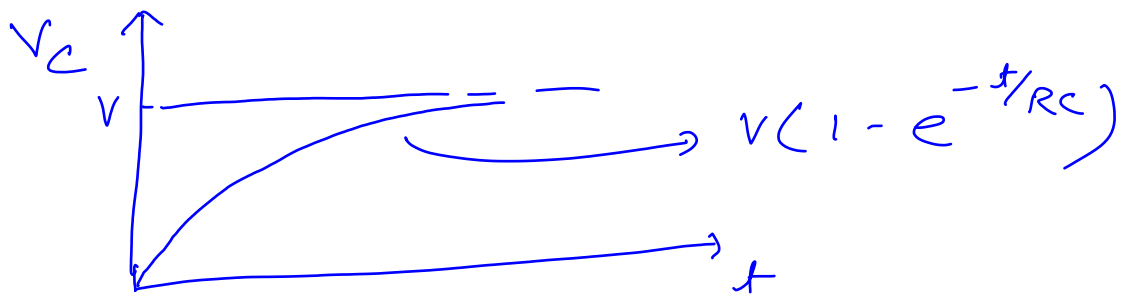at $t \rightarrow \infty$ $V_C \rightarrow V$ at $t \rightarrow \infty$ the capacitor is fully charged.




$$I = C \frac{dV_C}{dt} = \frac{CV}{RC} e^{-t/RC} = \frac{V}{R} e^{-t/RC}$$


at $t=0$ the ^{discharged} capacitor acts as a short circuit

at $t \rightarrow \infty$ the capacitor acts as an open circuit.

Capacitor discharging

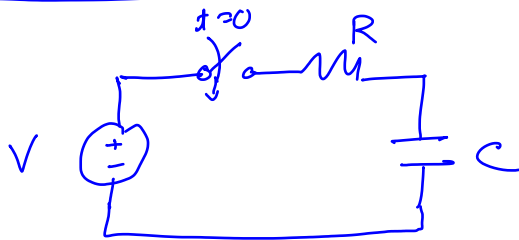

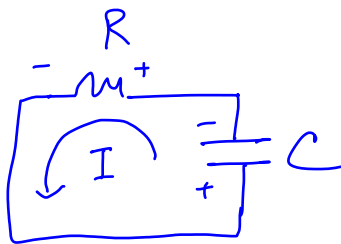After a very long time remove the voltage source and connect the R and C together.



$$V_R + V_C = 0$$

$$V_R = IR, \quad I = C \frac{dV_C}{dt}$$


$$IR + V_C = 0$$

$$RC \frac{dV_C}{dt} + V_C = 0$$

$$\int_{V_C(0)=V}^{V_C} \frac{dV_C}{V_C} = \int_0^t -\frac{1}{RC} dt$$

$$\ln \frac{V_C}{V} = -\frac{t}{RC}$$
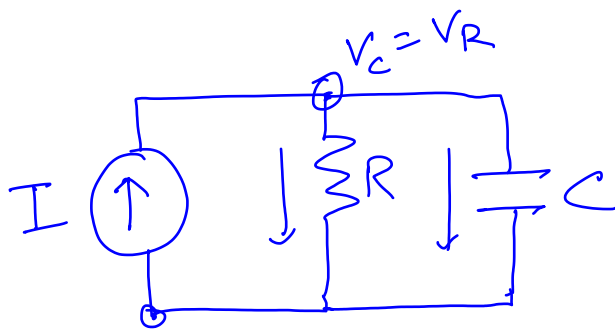
$$\Rightarrow V_C = V e^{-t/RC} \quad (\text{discharging})$$



$$I = \frac{V_C}{R} + C \frac{dV_C}{dt}$$

$$\Rightarrow \int_0^{V_C} \frac{dV_C}{IR - V_C} = \int_0^t \frac{1}{RC} dt$$

$$\Rightarrow -\ln \frac{IR - V_C}{IR} = \frac{t}{RC}$$

$$\Rightarrow IR - V_C = IR e^{-t/RC}$$

$$\Rightarrow V_C = IR (1 - e^{-t/RC})$$

$$I_C = C \frac{dV_C}{dt} = \frac{IR C}{RC} e^{-t/RC} = I e^{-t/RC}$$

