

Tutorial - I solutions

Q1

3. Determine the angle by which v_1 leads i_1 if $v_1 = 10 \cos(10t - 45^\circ)$ and i_1 is equal to (a) $5 \cos 10t$; (b) $5 \cos(10t - 80^\circ)$; (c) $5 \cos(10t - 40^\circ)$; (d) $5 \cos(10t + 40^\circ)$; (e) $5 \sin(10t - 19^\circ)$.

Solⁿ :

$$v_1 = 10 \cos(10t - 45^\circ)$$

converting v_1 into phasor Domain

$$v_1 = 10 \angle -45^\circ$$

(taking $\cos(100t)$ as reference)

* For any Signal : $x = A \cos(\omega t + \phi)$

its phasor : $X = A \angle \phi$

(a) $i_1 = 5 \cos(10t)$ $\xrightarrow[\text{phasor}]{\sim}$ $I_1 = 5 \angle 0^\circ$

For angle between v_1 and i_1 : $\frac{v_1}{I_1} = \frac{10 \angle -45^\circ}{5 \angle 0^\circ}$
 $= 2 \angle -45^\circ$

$\therefore v_1$ leads i_1 by angle of -45°

$$(b) \quad i_1 = 5 \cos(10t - 80^\circ) \quad (\text{Phasor}) \quad I_1 = 5 \angle -80^\circ$$

For angle between v_1 and i_1 :

$$\begin{aligned} \frac{v_1}{I_1} &= \frac{16 \angle -45^\circ}{5 \angle -80^\circ} \\ &= 2 \angle (-45^\circ - (-80^\circ)) \\ &= 2 \angle (-45^\circ + 80^\circ) \\ &= 2 \angle 35^\circ \end{aligned}$$

$\therefore v_1$ leads i_1 by angle : 35°

$$(c) \quad i_1 = 5 \cos(10t - 40^\circ) \quad (\text{Phasor}) \quad I_1 = 5 \angle -40^\circ$$

For angle between v_1 and i_1 :

$$\begin{aligned} \frac{v_1}{I_1} &= \frac{16 \angle -45^\circ}{5 \angle -40^\circ} \\ &= 2 \angle (-45^\circ - (-40^\circ)) \\ &= 2 \angle (-45^\circ + 40^\circ) \\ &= 2 \angle -5^\circ \end{aligned}$$

$\therefore v_1$ leads i_1 by angle : -5°

$$(d) \quad i_1 = 5 \cos(10t + 40^\circ) \quad (\text{Phasor}) \quad I_1 = 5 \angle +40^\circ$$

For angle between v_1 and i_1 :

$$\frac{v_1}{I_1} = \frac{16 \angle -45^\circ}{8 \angle +40^\circ}$$

$$= 2 \angle (-45^\circ - (+40^\circ))$$

$$= 2 \angle (-45^\circ - 40^\circ)$$

$$= 2 \angle -85^\circ$$

$\therefore v_1$ leads i_1 by angle : -85°

$$(e) \quad i_1 = 5 \sin(10t - 15^\circ) \quad (\text{Phasor}) \quad I_1 = 5 \angle -105^\circ$$

$$= 5 \cos(10t - 15^\circ - 90^\circ)$$

For angle between v_1 and i_1 :

$$\frac{v_1}{I_1} = \frac{16 \angle -45^\circ}{8 \angle -105^\circ}$$

$$= 2 \angle (-45^\circ - (-105^\circ))$$

$$= 2 \angle (-45^\circ + 105^\circ)$$

$$= 2 \angle 60^\circ$$

$\therefore v_1$ leads i_1 by angle : 60°

Q2

5. Determine which waveform in each of the following pairs is lagging: (a) $\cos 4t$, $\sin 4t$; (b) $\cos(4t - 80^\circ)$, $\cos(4t)$; (c) $\cos(4t + 80^\circ)$, $\cos 4t$; (d) $-\sin 5t$, $\cos(5t + 2^\circ)$; (e) $\sin 5t + \cos 5t$, $\cos(5t - 45^\circ)$.

Solⁿ : (a) $\cos 4t$, $\sin 4t = \cos(4t - 90^\circ)$

$\brace{}$ phasor

$1 L 0^\circ$, $1 L -90^\circ$

From the above $\sin 4t$ is lagging wrt $\cos 4t$ by 90°

(b) $\cos(4t - 80^\circ)$, $\cos(4t)$

$\brace{}$ phasor

$1 L -80^\circ$, $1 L 0^\circ$

From the above $\cos(4t - 80^\circ)$ is lagging wrt $\cos 4t$ by 80°

(c) $\cos(4t + 80^\circ)$, $\cos 4t$

$\brace{}$ phasor

$1 L 80^\circ$, $1 L 0^\circ$

From the above $\cos 4t$ is lagging wrt $\cos(4t + 80^\circ)$ by 80°

(d) $-\sin 5t = \cos(5t + 90^\circ)$, $\cos(5t + 2^\circ)$

$\brace{}$ phasor

$1 L 90^\circ$, $1 L 2^\circ$

$$* \quad \frac{1 \angle 50^\circ}{1 \angle 2^\circ} = 1 \angle 50^\circ - 2^\circ = 1 \angle 48^\circ$$

$\therefore \cos(st + 2^\circ)$ is lagging wrt $-\sin st$ by 88°

(e) $\sin st + \cos st$, $\cos(st - 45^\circ)$

$$\underbrace{\sin st + \cos st}_{\text{Phasor}} , \underbrace{\cos(st - 45^\circ)}_{\text{}}$$

$$\underbrace{1 \angle -90^\circ + 1 \angle 0^\circ}_{\text{}} , 1 \angle -45^\circ$$


$$1(-j) + 1 = 1-j = \sqrt{1^2 + 1^2} \angle \phi = \sqrt{2} \angle -45^\circ$$

$$\therefore \phi = -\tan^{-1}\left(\frac{1}{1}\right) = -45^\circ$$

* For any complex number : $z = x + jy$

Phasor form : $\sqrt{x^2 + y^2} \angle \phi$

$$\text{Let } \theta = \tan^{-1}\left(\frac{|y|}{|x|}\right)$$

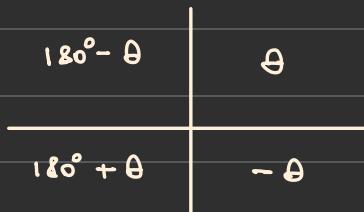

$$\therefore 1 \angle -45^\circ, 1 \angle -45^\circ$$

\therefore No pairs are leading / lagging

Q3

 $\circ - j$

20. Perform the indicated operations, and express the answer in both rectangular and polar forms:

$$(a) \frac{2+j3}{1+8\angle 90^\circ} - 4; (b) \left(\frac{10\angle 25^\circ}{5\angle -10^\circ} + \frac{3\angle 15^\circ}{3-j5} \right) j2;$$

(a)

$$\frac{2+j3}{1+8\angle 90^\circ} = \frac{2+j3}{1+8j}$$

$$j = 1 \angle 90^\circ$$

$$-j = 1 \angle -90^\circ$$

$$\therefore 2+3j = \sqrt{2^2+3^2} \angle \tan^{-1}\left(\frac{3}{2}\right)$$

$$= \sqrt{13} \angle 56.30^\circ$$

$$2+3j \approx 3.60 \angle 56.30^\circ$$

$$\therefore 1+8j = \sqrt{1^2+8^2} \angle \tan^{-1}\left(\frac{8}{1}\right) = \sqrt{65} \angle 82.87^\circ$$

$$= 8.06 \angle 82.87^\circ$$

⇒

$$\frac{2+3j}{1+8j} - 4 = \frac{2+3j - 4 - 32j}{1+8j} = -\frac{2-29j}{1+8j}$$

$$= 3.6 \angle 183.18^\circ$$

In rectangular form: $3.6 (\cos(183.18^\circ) + j \sin(183.18^\circ))$

$$= 3.6 (-0.998 - j 0.055)$$

$$= -3.6 - j 0.2$$

$$\begin{aligned}
 (b) & \left(\frac{\frac{2}{3} \angle 25^\circ}{8 \angle -10^\circ} + \frac{3 \angle 15^\circ}{3-j5} \right) j2 \\
 & = \left(1.638 + j1.147 + \frac{3 \angle 15^\circ}{5.83 \angle -59.03^\circ} \right) j2 \\
 & = (1.638 + j1.147 + 0.514 \angle 74.03^\circ) j2 \\
 & = (1.775 + j1.641) j2 \\
 & = -3.282 + j3.558 \\
 & = 4.32 \angle 111.56^\circ
 \end{aligned}$$

In rectangular form: $4.32 (\cos(111.56^\circ) + j \sin(111.56^\circ))$

$$\begin{aligned}
 & = -1.58 + j4.02
 \end{aligned}$$

Q4

26. Transform each of the following into phasor form: (a) $11 \sin 100t$; (b) $11 \cos 100t$; (c) $11 \cos(100t - 90^\circ)$; (d) $3 \cos 100t - 3 \sin 100t$.

Solⁿ: (a) $11 \sin 100t \rightsquigarrow 11 \angle -90^\circ$

$$\begin{aligned}
 & = 11 \cos(100t - 90^\circ)
 \end{aligned}$$

(b) $11 \cos 100t \rightsquigarrow 11 \angle 0^\circ$

$$(c) \quad 11 \cos(100t - 90^\circ) \quad \text{at } 11 \angle -90^\circ$$

$$\begin{aligned}
 (d) \quad 3 \cos 100t - \underbrace{3 \sin 100t}_{\cos(100t - 90^\circ)} &= 3 \angle 0^\circ - 3 \angle -90^\circ \\
 &= 3 - (3 \angle -90^\circ) \\
 &= 3 + 3^\circ \\
 &= 3\sqrt{2} \angle 45^\circ \left(\frac{3}{3}\right) \\
 &= 3\sqrt{2} \angle 45^\circ
 \end{aligned}$$

Q5

39. Determine the equivalent admittance of the following, assuming an operating frequency of 1000 rad/s: (a) 25 Ω in series with 20 mH; (b) 25 Ω in parallel with

$$\begin{aligned}
 \text{soln: } (a) \quad \text{---} \quad 25 \Omega \quad 20 \text{mH} \rightarrow \quad j\omega L = j(1000)(20 \times 10^{-3}) \\
 &= 20j^\circ
 \end{aligned}$$

$$Z_{eq.} = 25 + 20j^\circ$$

$$\begin{aligned}
 \text{admittance } Y_{eq.} &= \frac{1}{Z_{eq.}} = \frac{1}{25 + 20j^\circ} = 0.031 \angle -38.65^\circ \text{ Siemens} \\
 &= (0.024 - 0.015j) \text{ Siemens}
 \end{aligned}$$

(b)




$$\begin{aligned}
 \frac{1}{Z_{eq.}} &= \frac{1}{25} + \frac{1}{20j^\circ} = \frac{20j^\circ + 25}{500j^\circ}, \quad Y_{eq} = \frac{20j^\circ + 25}{500j^\circ} = 64 \angle -51.3^\circ \text{ mS}
 \end{aligned}$$

Q6


 $125 \mu\text{F}$ in series, but $\omega = 4 \text{ krad/s}$.

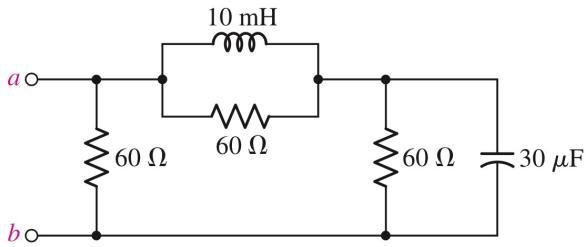43. Calculate the equivalent impedance seen at the open terminals of the network shown in Fig. 10.56 if f is equal to (a) 1 Hz; (b) 1 kHz; (c) 1 MHz; (d) 1 GHz; (e) 1 THz.



■ FIGURE 10.56

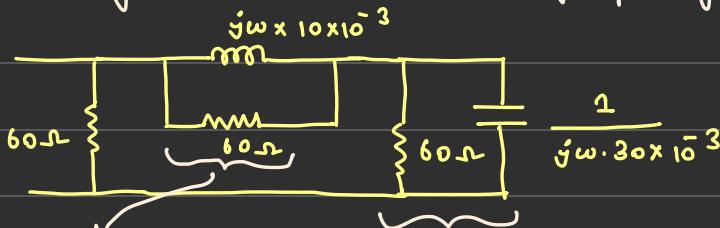solⁿ : converting the circuit into frequency domain



$$Z_2 = \frac{60 \times j\omega \times 10^{-2}}{60 + j\omega \times 10^{-2}}$$

$$Z_1 = \frac{60 \times \frac{1}{j\omega \cdot 30 \times 10^{-3}}}{60 + \frac{1}{j\omega \cdot 30 \times 10^{-3}}}$$

(a) $f = 1 \text{ Hz} \rightsquigarrow \omega = 2\pi f = 2\pi \text{ rad/sec}$


$$\Rightarrow Z_1 = \frac{\frac{30}{60} \times 10}{\frac{1}{2\pi j \times 2 \times 10^{-2}}} = -j \frac{10^4}{\frac{1}{2\pi j \times 3 \times 10^{-2}}} = \frac{60 + \frac{100}{2\pi j \times 3}}{60 + \frac{100}{2\pi j \times 3}}$$

$$Z_1 = \frac{-j \times 10^4}{\frac{60 + \frac{100}{2\pi j} \times 3}{60 - 5.30j}} = \frac{-0.31j \times 10^4}{60 - 5.30j}$$

$$\therefore Z_1 = \frac{-8100j}{60 - 5.30j} = 51.46 \angle -84.35^\circ$$


$$Z_2 = \frac{60 \times j\omega 10^{-2}}{60 + j\omega 10^{-2}} = \frac{60 \times 10^{-2}j}{60 + j10^{-2}} = \frac{0.6j}{60 + 0.01j}$$

$$= 0.01 \angle 89.99^\circ$$

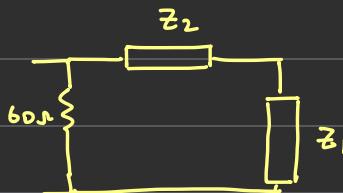

$$\begin{aligned} Z_{eq} &= 60 \parallel (Z_1 + Z_2) \\ &= 60 \parallel (51.45 \angle -84.35^\circ) \\ &= \frac{60 \times 51.45 \angle -84.35^\circ}{60 + 51.45 \angle -84.35^\circ} \\ &= \frac{3087 \angle -84.35^\circ}{82.41 \angle -38.45^\circ} \end{aligned}$$

$$Z_{eq} = 37.45 \angle -46.48^\circ$$

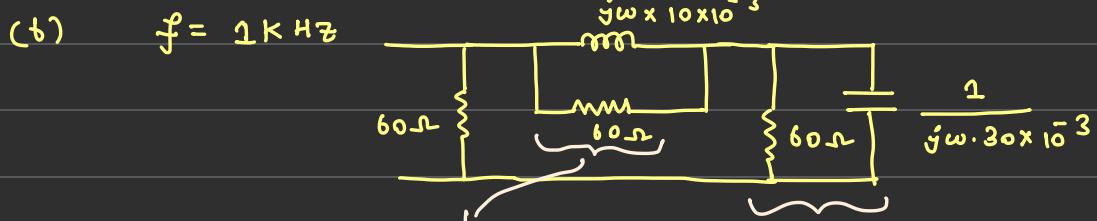

$$Z_2 = \frac{60 \times j\omega \cdot 10^{-2}}{60 + j\omega \cdot 10^{-2}}$$

$$Z_1 = \frac{60 \times \frac{1}{j\omega \cdot 30 \times 10^{-3}}}{60 + \frac{1}{j\omega \cdot 30 \times 10^{-3}}}$$

$$\begin{aligned} Z_1 &= \frac{60 \times \frac{1}{30j}}{60 + \frac{1}{30j}} = \frac{-2j}{60 - 0.03j} \\ &= 0.033 \angle -89.57^\circ \end{aligned}$$

$$Z_2 = \frac{6j}{60 + 0.1j} = 0.057 \angle 89.50^\circ$$


$$\therefore Z_{eq} = 60 \parallel (0.057 \angle 89.50^\circ)$$

$$= \frac{60 \times 0.057 \angle 89.50^\circ}{60 + 0.057 \angle 89.50^\circ}$$

$$= \frac{3.42 \angle 89.50^\circ}{60 \angle 0.05^\circ}$$

$$Z_{eq} = 0.057 \angle 89.77^\circ$$
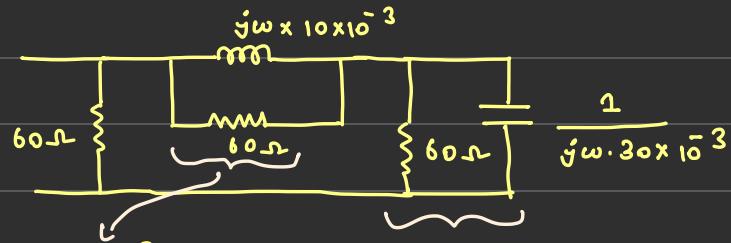
$$(c) f = 1 \text{ MHz} \\ = 10^6 \text{ Hz}$$



$$Z_2 = \frac{60 \times j\omega \cdot 10^{-2}}{60 + j\omega \cdot 10^{-2}}$$

$$Z_1 = \frac{60 \times \frac{1}{j\omega \cdot 30 \times 10^{-3}}}{60 + \frac{1}{j\omega \cdot 30 \times 10^{-3}}}$$

$$\therefore Z_1 = \frac{\frac{60^2}{j \times 10^6 \times 10^{-3} \times 30}}{60 + \frac{1}{j \times 10^6 \times 10^{-3} \times 30}} = \frac{-2 \times 10^3 j}{60 - j \frac{100}{3}} = 29.13 \angle -60.94^\circ$$

$$\therefore Z_2 = \frac{60 \times j \times 10^6 \times 10^{-2}}{60 + j \times 10^6 \times 10^{-2}} = \frac{6 \times 10^5 j}{60 + j \times 10^4} = 59.9 \angle 0.21^\circ$$

$$\therefore Z_{eq.} = 60 \parallel (78.18 \angle -18.73^\circ)$$


$$= \frac{60 \times 78.18 \angle -18.73^\circ}{60 + 78.18 \angle -18.73^\circ}$$

$$= \frac{4620 \angle -18.73^\circ}{136.37 \angle -10.60^\circ}$$

$$Z_{eq.} = 4825.03 \angle -18.5^\circ \Omega$$

$$(d) f = 1 \text{ GHz}$$

$$= 10^9 \text{ Hz}$$

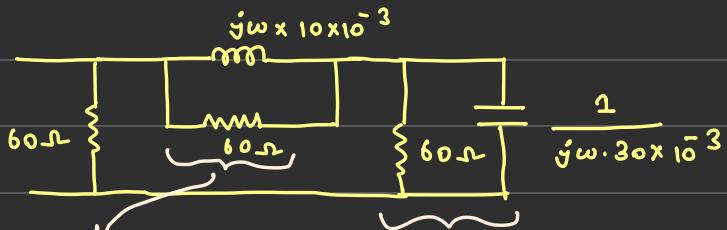

$$Z_2 = \frac{60 \times j\omega \times 10^{-2}}{60 + j\omega \times 10^{-2}}$$

$$Z_1 = \frac{60 \times \frac{1}{j\omega \cdot 30 \times 10^{-3}}}{60 + \frac{1}{j\omega \cdot 30 \times 10^{-3}}}$$

$$\therefore Z_1 = \frac{\frac{60^2}{j \times 10^9 \times 30 \times 10^{-3}}}{60 + \frac{1}{j \times 10^9 \cdot 30 \times 10^{-3}}} = \frac{-2 \times 10^6 j}{60 - \frac{10^7}{3} j} = \frac{1}{3} \times 10^{-7} \angle -89.5^\circ \Omega$$


$$\therefore Z_2 = \frac{6 \times 10^6 j}{60 + 10^7 j} = 60 \times 10^{-7} \angle 3.43^\circ$$

$$\therefore Z_{eq} = 60 \parallel (5.99 \times 10^{-3} \angle 3.43^\circ)$$

$$= \frac{60 \times 5.99 \times 10^{-3} \angle 3.43^\circ}{60 + 5.99 \times 10^{-3} \angle 3.43^\circ}$$

$$Z_{eq} = 5.98 \times 10^{-3} \angle 3.42 \Omega$$
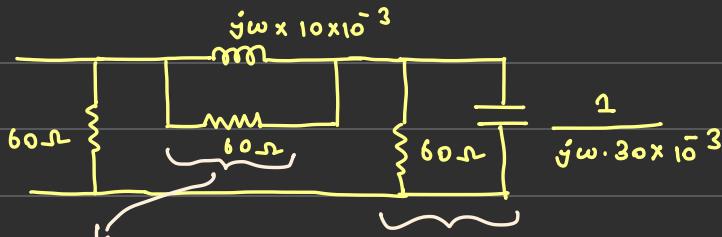
$$(e) f = 1 \text{ T.Hz} \\ = 10^{12} \text{ Hz}$$



$$Z_2 = \frac{60 \times j\omega 10^{-2}}{60 + j\omega 10^{-2}}$$

$$Z_1 = \frac{60 \times \frac{1}{j\omega \cdot 30 \times 10^{-3}}}{60 + \frac{1}{j\omega \cdot 30 \times 10^{-3}}}$$

$$\begin{aligned} Z_1 &= \frac{\frac{60^2}{j \times 10^{12} \times 30 \times 10^{-3}}}{60 + \frac{1}{j \times 10^{12} \cdot 30 \times 10^{-3}}} &= \frac{-2 \times 10^9 j}{60 - \frac{10^{10}}{3} j} \\ &\approx \frac{-2 \times 10^9 j}{60} \end{aligned}$$

$$\approx -\frac{1}{3} \times 10^{10} \angle 90^\circ$$

$$\approx \frac{10^{10}}{3} \angle -90^\circ \approx 3.33 \times 10^9 \angle -90^\circ$$


$$Z_2 = \frac{6 \times 10^9 j}{60 + 10^{10} j} \approx 60 \times 10^{-7} \angle 3.43^\circ \Omega$$

$$Z_{eq.} = 60 \parallel (5.99 \times 10^6 \angle 3.42^\circ)$$

$$= \frac{60 \times 5.99 \times 10^6 \angle 3.42^\circ}{60 + 5.99 \times 10^6 \angle 3.42^\circ}$$

$$Z_{eq} \approx 5.28 \times 10^6 \angle 3.41^\circ \Omega$$

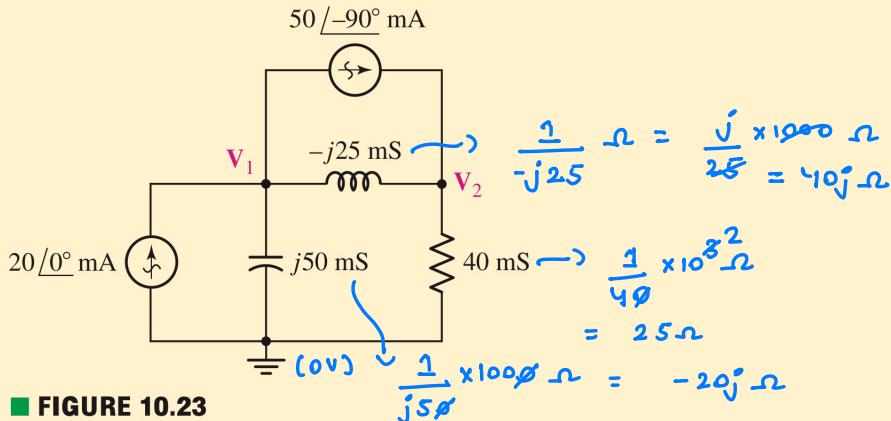10.12 Use nodal analysis on the circuit of Fig. 10.23 to find V_1 and V_2 .



Sol^m : modal at V_1 :

$$-20 \angle 0^\circ \times 10^{-3} + \frac{V_1}{-20j} + \frac{V_1 - V_2}{40j} + 50 \angle -90^\circ \times 10^{-3} = 0$$

$$\Rightarrow \frac{V_1}{20j} - \frac{V_2}{40j} = 20 \times 10^{-3} + 50j \times 10^{-3}$$

$$\Rightarrow -20 \times 10^{-3} + V_1 \left[-\frac{1}{20j} + \frac{1}{40j} \right] - \frac{V_2}{40j} + 50(-j) \times 10^{-3} = 0$$

$$\Rightarrow -20 \times 10^{-3} - 50j \times 10^{-3} = - \left[V_1 \left[-\frac{1}{20j} + \frac{1}{40j} \right] - \frac{V_2}{40j} \right]$$

$$\Rightarrow -40j \times 10^{-3} [20 + 50j] = V_1 + V_2 \quad -(1)$$

modal at V_2

$$V_2 \left(\frac{-j}{40} + \frac{1}{25} \right) - \frac{V_1}{40j} = -50 \times 10^{-3} j$$

after solving,

$$-5v_1 + (5+8j)v_2 = 10 \quad -(2)$$

from eqn (1) & (2)

$$v_1 = 0.9756 + 0.4195j$$

$$v_2 = 1.0244 - 1.2195j$$

In polar form

$$v_1 = 1.062 \angle 23.27^\circ V$$

$$v_2 = 1.593 \angle -50^\circ V$$

Q6

10.13 Use mesh analysis on the circuit of Fig. 10.25 to find \mathbf{I}_1 and \mathbf{I}_2 .

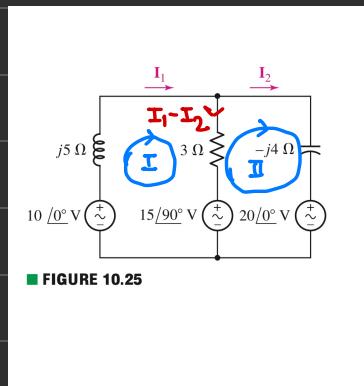


FIGURE 10.25

$$\text{So, by KVL in Mesh I: } -10 \angle 0^\circ + I_1(5 \angle 90^\circ) + 3(I_1 - I_2) + 15 \angle 90^\circ = 0$$
$$\Rightarrow I_1(3 + 5j) - 3I_2 = 10 - 15j - (1)$$

$$\text{I}_1 (3 + 5j) - 3 \text{I}_2 = 10 - 15j$$

$$\underline{\underline{\text{KVL II}}} : -3(\text{I}_1 - \text{I}_2) - 4j\text{I}_2 + 20 - 15j = 0$$

$$\Rightarrow -3\text{I}_1 + (3 - 4j)\text{I}_2 = -20 + 15j \quad -(2)$$

By cramer's rule

$$\Delta = \begin{vmatrix} 3+5j & -3 \\ -3 & 3-4j \end{vmatrix}$$

$$= (3+5j)(3-4j) - 9$$

$$\Delta = 20 + 3j$$

$$\Delta_1 = \begin{vmatrix} 10 - 15j & -3 \\ -20 + 15j & 3 - 4j \end{vmatrix} = (10 - 15j)(3 - 4j) + 3(-20 + 15j)$$

$$= -30 - 85j - 60 + 45j$$

$$\Delta_1 = -90 - 40j$$

$$\Delta_2 = \begin{vmatrix} 3+5j & 10 - 15j \\ -3 & -20 + 15j \end{vmatrix} = -185 - 55j + 3(10 - 15j)$$

$$= -105 - 100j$$

$$\therefore I_1 = \frac{\Delta_1}{\Delta} = \frac{-90 - 40j}{20 + 3j} = -4.69 - 1.25j$$

$$\therefore I_1 = 4.87 \angle -164.6^\circ A$$

$$\therefore I_2 = \frac{\Delta_2}{\Delta} = \frac{-105 - 100j}{20 + 3j} = 7.17 \angle -144.9^\circ$$

$$\therefore I_2 = 7.17 \angle -144.9^\circ A$$