
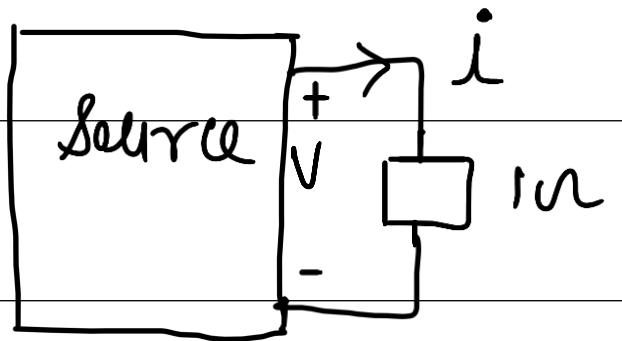


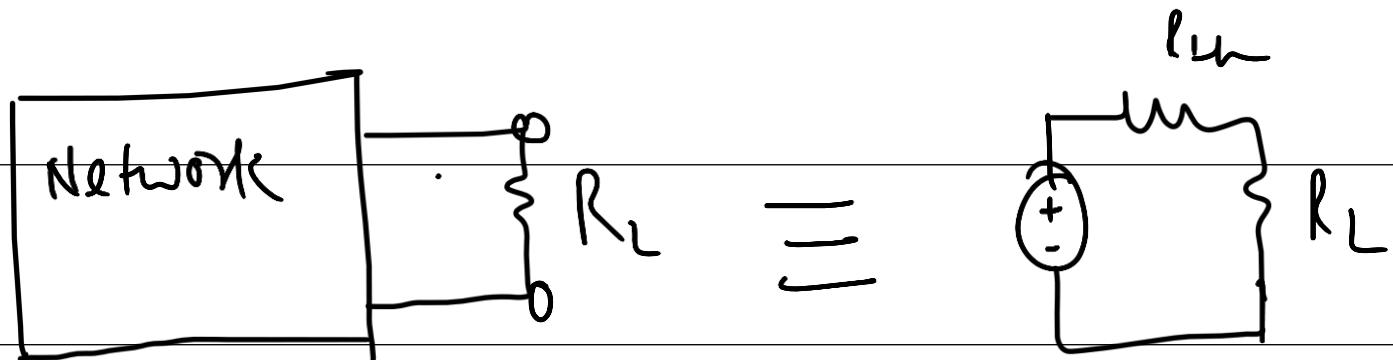Q-1 As shown in the figure, a  $1\Omega$  resistor is connected to a source that has a load line  $v+i=100$ , the current through the resistance is ?



Sol<sup>n</sup>: Any two terminal bilateral linear DC circuits can be replaced by an equivalent circuit consisting of a voltage source and a series resistor.




Given : Load line equation =  $V + i = 100$

To obtain open-circuit voltage ( $V_{th}$ ) put  $i=0$  in load line equation

$$\Rightarrow V_{th} = 100V$$

To obtain short-circuit current ( $i_{sc}$ ) put  $V=0$  in load line equation  $i_{sc} = 100A$

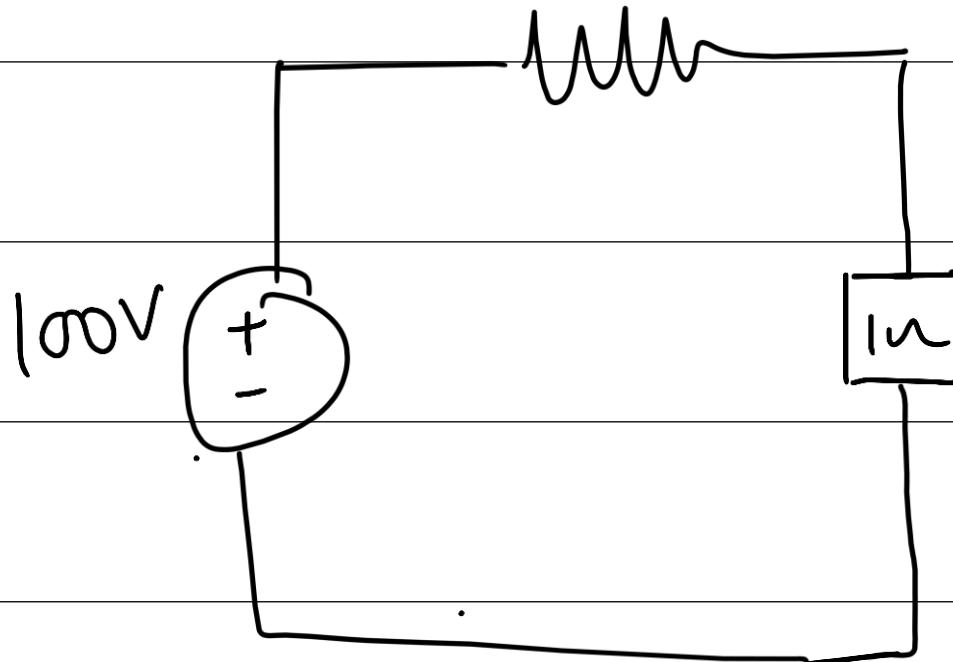
$$\text{so, } R_{th} = \frac{V_{th}}{i_{sc}} = \frac{100}{100} = 1\Omega$$



$$\text{Current } (i) = \frac{100}{2} = 50\text{A} \quad \underline{\text{Ans}}$$


$$V_3 = 1.5 \angle 17^\circ V$$

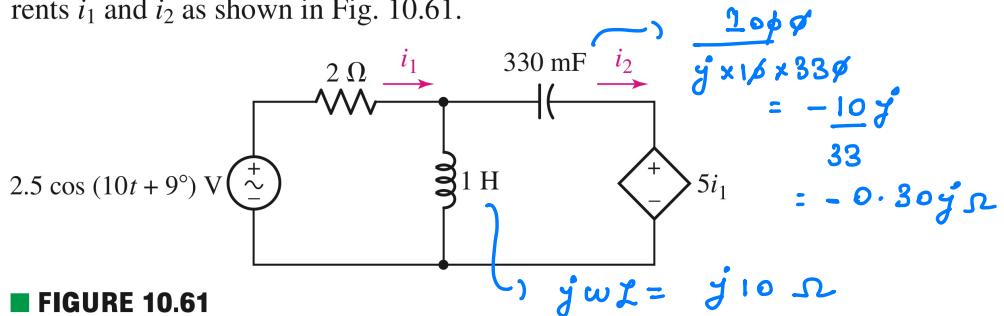52. Employ phasor analysis techniques to obtain expressions for the two mesh currents  $i_1$  and  $i_2$  as shown in Fig. 10.61.



■ FIGURE 10.61

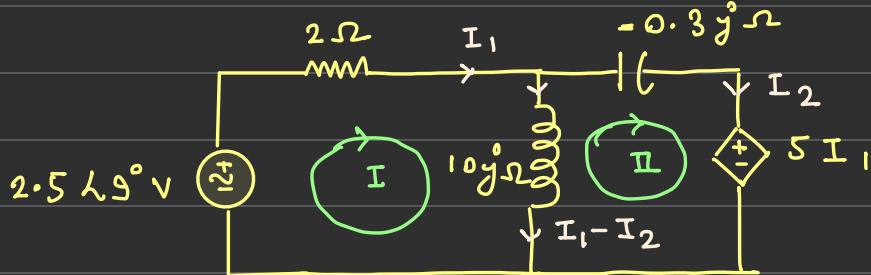Sol<sup>n</sup> : converting into phasor domain  
 $\omega = 10 \text{ rad/s}$



mesh analysis :

$$(I) \quad -2.5 \angle 9^\circ + 2I_1 + (I_1 - I_2)(10j) = 0$$

$$\Rightarrow -2.46 - 0.351j + (2+10j)I_1 - 10jI_2 = 0$$

$$\Rightarrow (2+10j)I_1 - 10jI_2 = 2.46 + 0.351j \quad -(1)$$

$$(II) \quad 5I_1 - 10j(I_1 - I_2) - 0.3jI_2 = 0$$

$$\Rightarrow (5-10j)I_1 + 9.7jI_2 = 0 \quad -(2)$$

solving the equations by cramer's rule

$$\Delta = \begin{vmatrix} 2+10j & -10j \\ 5-10j & 5+7j \end{vmatrix} = (2+10j)(5+7j) + 10j(5-10j)$$

$$= -97 + 19.4j + 50j \\ + 100$$

$$\Delta = 3 + 69.4j$$

$$\Delta_1 = \begin{vmatrix} 2.46 + 0.39j & -10j \\ 0 & 5+7j \end{vmatrix}$$

$$\Delta_1 = -3.78 + 23.86j$$

$$\Delta_2 = \begin{vmatrix} 2+10j & 2.46 + 0.39j \\ 5-10j & 0 \end{vmatrix} = - (16.2 - 22.65j)$$

$$\Delta_2 = -16.2 + 22.65j$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-3.78 + 28.86j}{3 + 69.4j}$$

$$= (0.34 + 0.069j) A$$

$$I_1 = 0.35 \angle 11.48^\circ A$$

In time domain:

$$i_1(t) = 0.35 \cos(10t + 11.48^\circ) A$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-16.2 + 22.65j}{3 + 69.4j}$$

$$= (0.31 + 0.24j) A$$

$$I_2 = 0.4 \angle 38.04^\circ A$$

In time domain:


$$i_2(t) = 0.4 \cos(10t + 38.04^\circ) A$$

70. Use  $\omega = 1 \text{ rad/s}$ , and find the Norton equivalent of the network shown in Fig. 10.74. Construct the Norton equivalent as a current source  $I_N$  in parallel with a resistance  $R_N$  and either an inductance  $L_N$  or a capacitance  $C_N$ .


Sol<sup>m</sup> :

$$\omega = 1 \text{ rad/s}$$

$$V_{OC} = 1 \angle 0^\circ \text{ V}$$

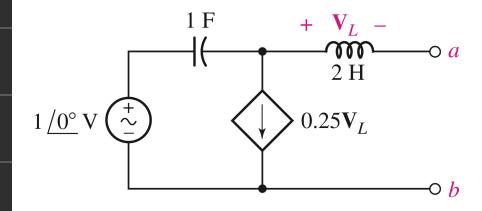

Finding short circuit current

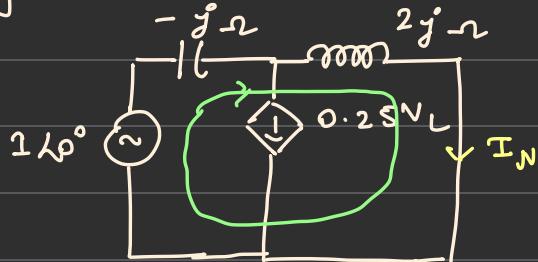

$$KVL : 1 \angle 0^\circ = -j(0.25I_N(j^2) + I_N) + 2jI_N$$


$$1 \angle 0^\circ = (0.5 + j)I_N$$

$$I_N = 0.4 - j 0.8 = 0.89 \angle -63.43^\circ \text{ A}$$

$$\therefore Z_N = \frac{V_{OC}}{I_N} = 0.5 + j = \frac{1}{\frac{1}{R} + \frac{1}{jX}}$$

$$\Rightarrow R = 2.5 \Omega, X = 1.25$$

$$L = 1.25 \text{ H}$$

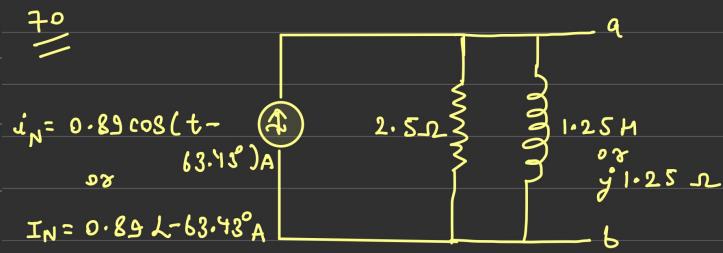

value, redesign the circuit to achieve a corner frequency of 2 kHz.

80. Design a purely passive network (containing only resistors, capacitors, and inductors) which has an impedance of  $(22 - j7)/5/8^\circ \Omega$  at a frequency of  $f = 100 \text{ MHz}$ .


Sol<sup>n</sup>: one of the possible combinations

$$Z = \frac{22 - j7}{5 \angle 8^\circ} = 4.618 \angle -25.65^\circ = (4.162 \angle -j2) \Omega$$

•  $Z$  is constructed using a series combination of single resistor, capacitor and an inductor

$$R = 4.16 \Omega, -j2 = j\omega L - \frac{j}{\omega C}, \text{ setting } L = 200 \text{ mH}$$

$$\Rightarrow C = 0.12 \mu\text{F}$$

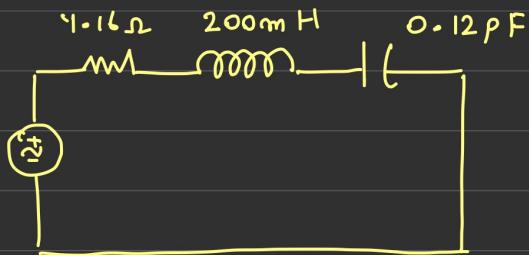

$$f = 100 \text{ MHz} = 100 \times 10^6 \text{ Hz}$$

$$= 10^8 \text{ Hz}$$

$$\omega = 2\pi f = 2\pi \times 10^8 \text{ Hz}$$

## Tutorial-2

1. Given,  $V_1 = 10 \angle -80^\circ V$


$$V_2 = 4 \angle 0^\circ V$$

$$V_3 = 2 \angle -23^\circ V$$

$$Z_1 = j30\Omega = 30 \angle 90^\circ \Omega$$

$$Z_2 = 55\Omega = 55 \angle 0^\circ \Omega$$
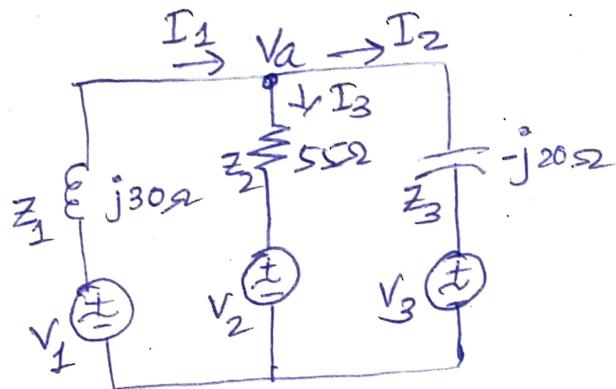
$$Z_3 = -j20\Omega = 20 \angle -90^\circ \Omega$$



Apply KCL at node ' $V_a$ :

$$I_1 = I_2 + I_3 \quad \text{---(1)}$$

$$\Rightarrow \frac{V_1 - V_a}{Z_1} = \frac{V_a - V_3}{Z_3} + \frac{V_a - V_2}{Z_2}$$

$$\Rightarrow \frac{10 \angle -80^\circ - V_a}{30 \angle 90^\circ} = \frac{V_a - 2 \angle -23^\circ}{20 \angle -90^\circ} + \frac{V_a - 4 \angle 0^\circ}{55 \angle 0^\circ}$$

$$\Rightarrow \frac{10 \angle -80^\circ}{30 \angle 90^\circ} - \frac{V_a}{30 \angle 90^\circ} = \frac{V_a}{20 \angle -90^\circ} - \frac{2 \angle -23^\circ}{20 \angle -90^\circ} + \frac{V_a}{55 \angle 0^\circ} - \frac{4 \angle 0^\circ}{55 \angle 0^\circ}$$

$$\Rightarrow V_a \left[ \frac{1}{30 \angle 90^\circ} + \frac{1}{20 \angle -90^\circ} + \frac{1}{55 \angle 0^\circ} \right] = \frac{10 \angle -80^\circ}{30 \angle 90^\circ} + \frac{2 \angle -23^\circ}{20 \angle -90^\circ} + \frac{4 \angle 0^\circ}{55 \angle 0^\circ}$$

$$\Rightarrow V_a (0.018 + j0.0167) = -0.216 + j0.0342$$

$$\Rightarrow V_a = \frac{-0.216 + j0.0342}{0.018 + j0.0167}$$

$$\Rightarrow V_a = -5.502 + j7.004 = 8.91 \angle 128.15^\circ \quad \text{---(2)}$$

$$I_1 = \frac{V_1 - V_a}{Z_1} = \frac{10 \angle -80^\circ - 8.91 \angle 128.15^\circ}{30 \angle 90^\circ}$$

$$\Rightarrow I_1 = 0.61 \angle -156.45^\circ A = -0.56 - j 0.24 A$$

(3)

$$I_2 = \frac{V_a - V_3}{Z_3} = \frac{8.91 \angle 128.15^\circ - 2 \angle -23^\circ}{20 \angle -90^\circ}$$

$$\Rightarrow I_2 = 0.54 \angle -136.4^\circ A = -0.39 - j 0.37 A$$

(4)


2) Given,  $C = 250 \text{ mF} \Rightarrow$

$$Z_C = -j0.2 \Omega$$

$$L = 70 \text{ mH}, Z_L = j1.4 \Omega$$

$$V_{S1} = 9 \cos(20t) V = 9 V$$
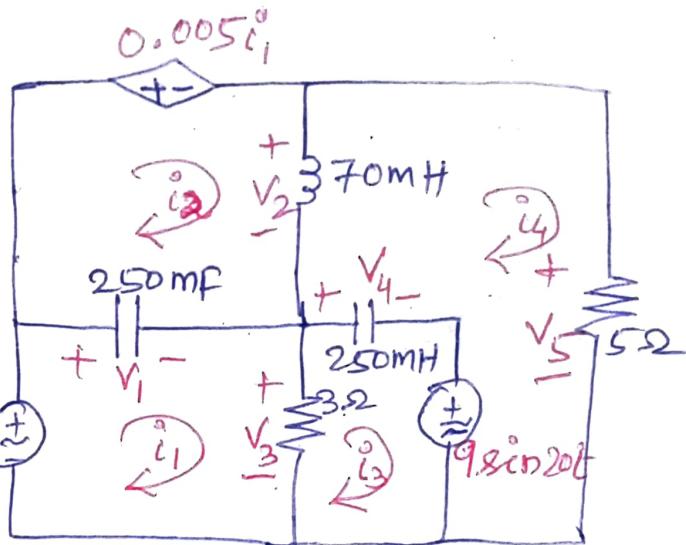
$$V_{S2} = 9 \sin(20t) V = -j9 V \quad 9 \cos 20t V$$



### Mesh-1

$$\text{Apply KVL, } -9 + V_1 + V_3 = 0$$

$$\Rightarrow -9 + Z_C(I_1 - I_2) + Z_R(I_1 - I_3) = 0$$

$$\Rightarrow -9 - j0.2(I_1 - I_2) + 3(I_1 - I_3) = 0$$

$$\Rightarrow (3 - j0.2)I_1 + j0.2I_2 - 3I_3 = 9$$

— (1)

### Mesh-2

$$\text{Apply KVL, } 0.005I_1 + V_2 - V_1 = 0$$

$$\Rightarrow 0.005I_1 + (I_2 - I_4)(j1.4) - (I_1 - I_2)(-j0.2) = 0$$

$$\Rightarrow (0.005 + j0.2)I_1 + j1.02I_2 - j1.4I_4 = 0$$

— (2)

### Mesh-3 Apply KVL, $-j9 - V_3 + V_4 = 0$

$$\Rightarrow -j9 - (I_1 - I_3)3 + (I_3 - I_4)(-j0.2) = 0$$

$$\Rightarrow -3I_1 + (3 - j0.2)I_3 + j0.2I_4 = j9$$

— (3)

### Mesh-4 Apply KVL,

$$V_5 - (-j9) - V_4 - V_2 = 0$$

$$\Rightarrow 5I_4 + j9 - (I_3 - I_4)(-j0.2) - (I_2 - I_4)(j1.4) = 0$$

$$\Rightarrow -1.4I_2 + j0.2I_3 + (5 + j1.2)I_4 = -j9$$

— (4)

3) Given,  $R_1 = 1\Omega$   
 $\Rightarrow Z_{R1} = 1\Omega$

$$L_1 = 100\text{mH} \Rightarrow Z_{L1} = j2\Omega$$

$$R_2 = 2\Omega \Rightarrow Z_{R2} = 2\Omega$$

$$L_2 = 150\text{mH} \Rightarrow Z_{L2} = j3\Omega$$

$$V_s = 5 \sin(20t + 12^\circ) V = 5 \cos(20t + 12^\circ - 90^\circ)$$

$$= 5 \cos(20t - 78^\circ)$$

$$\boxed{V_s = 5 \angle -78^\circ V = (1.04 - j4.89) V}$$

$$I_s = 2 \sin(20t + 45^\circ) = 2 \cos(20t - 45^\circ)$$

$$\boxed{I_s = 2 \angle -45^\circ A = (1.41 - j1.41) A}$$


→ Apply KCL at node 'A' & voltage divider rule to find out  $V_a$ .

\* Let us apply voltage divider rule,

$$V_a = \frac{V_s Z_{L1}}{Z_{R1} + Z_{L1}} = \frac{(1.04 - j4.89)(j2)}{(1 + j2)} V$$

$$\Rightarrow V_a = \frac{9.78 + j2.08}{1 + j2} V = 2.79 - j3.49 V$$

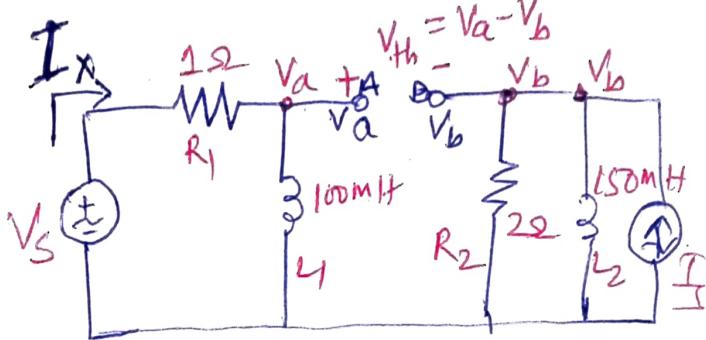
$$\Rightarrow \boxed{V_a = 2.79 - j3.49 V = 4.47 \angle -51.2^\circ V}$$



\* Let's find  $V_b$ :

→ By using current division rule,
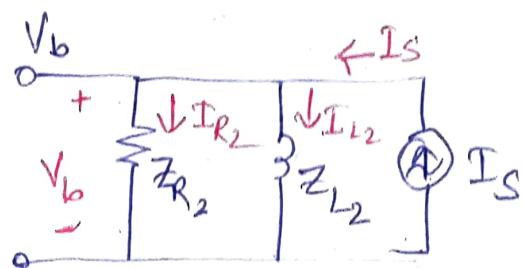
$$I_{R_2} = \frac{I_s Z_{L_2}}{Z_{R_2} + Z_{L_2}}$$



$$\Rightarrow I_{R_2} = \frac{(1.41 - j1.41)j3}{2 + j3}$$

$$\Rightarrow I_{R_2} = 1.63 - j0.33 \text{ A} \quad \text{---(4)}$$

$$\therefore V_b = I_{R_2} R_2 = (1.63 - j0.33) \times 2$$

$$\Rightarrow V_b = 3.26 - j0.66 \text{ V} \quad \text{---(5)}$$

(b)

Using (3) & (5),


$$V_{th} = V_a - V_b = (2.79 - j3.49) - (3.26 - j0.66)$$

$$\Rightarrow V_{th} = (-0.47 - j2.83) \text{ V} = 2.87 \angle -99.43^\circ$$

$$Z_{th} = \left( \frac{Z_{R_1} Z_{L_1}}{Z_1 + Z_{L_1}} \right) + \left( \frac{Z_{R_2} Z_{L_2}}{Z_2 + Z_{L_2}} \right)$$


$$\Rightarrow Z_{th} = \left( \frac{1 \times j2}{1 + j2} \right) + \left( \frac{2 \times j3}{2 + j3} \right)$$
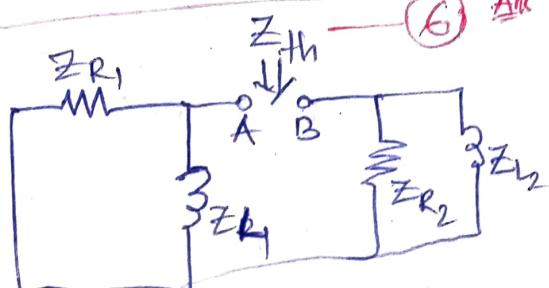
$$\Rightarrow Z_{th} = (2.19 + j1.32) \text{ } \Omega = 2.56 \angle 31.08^\circ \quad \text{---(7)}$$



Apply KVL,

$$-V_{Th} + IZ_{Th} + IZ_C = 0$$

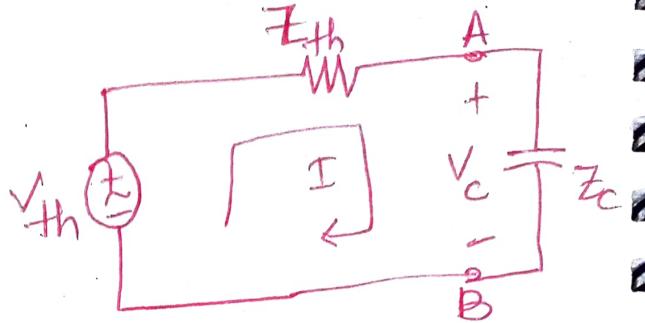

$$\Rightarrow I = \frac{V_{Th}}{Z_{Th} + Z_C}$$

$$\Rightarrow I = \frac{(-0.47 - j2.83)}{2.19 + j1.32 + (-j3.33)}$$

$$\left[ \begin{array}{l} C = 15 \text{ mF} \\ \therefore Z_C = -j3.33 \Omega \end{array} \right]$$

$$\Rightarrow I = \frac{-0.47 - j2.83}{2.19 - j2.01} A$$

$$\Rightarrow \boxed{I = (0.53 - j0.81) A = 0.97 \angle -56.8^\circ A} \quad (8)$$

$$\therefore V_C = IZ_C = (0.53 - j0.81)(-j3.33)$$

$$\Rightarrow \boxed{V_C = (-2.69 - j1.76) V = 3.21 \angle -146.8^\circ V} \quad (9)$$

$$(b) \quad \therefore \boxed{v_C(t) = 3.21 \sin(20t - 146.8^\circ) V} \quad (10)$$

(c) The current flowing out of the positive reference terminal of the source voltage is

$$I_X = \frac{V_S - V_A}{Z_R} = \frac{(1.04 - j4.89) - (2.79 - j3.49)}{1}$$

$$\Rightarrow \boxed{I_X = (-1.75 - j1.4) A} \quad \text{Ans}$$