

tr5frbj 12/08/24

## Circuit Theory and Devices

Lab: LT Spice (2nd week onwards)

book: Engineering Circuit Analysis (9th edition)

### Relative grading


Labs	20%
Quiz	20%
Midsem	30%

Scientific calc

Course: 9 modules chapter 10 onwards  
{continuation of BE3}

### Lecture 1

⇒ Linear Circuits

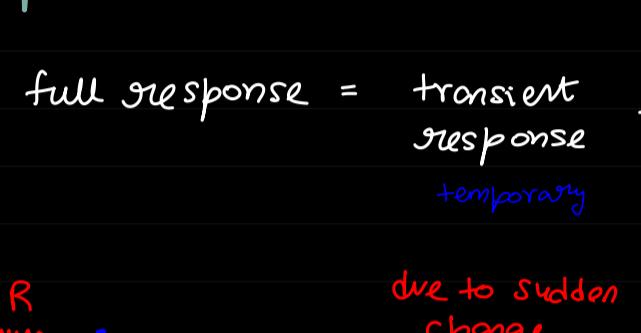

System is linear if

$$Kx \rightarrow [\text{sys}] \rightarrow Ky$$

where  $K$  is constant

"R" Resistor: linear element ✓  
 $V = iR$

"L" Inductor: linear element ✓  
 $V = L \frac{di}{dt}$


### \* Linear Electric Circuits:

consists of ⇒

①  $R, L, C \rightarrow$  linear elements

② Independent voltage & current sources



③ Linear dependent sources

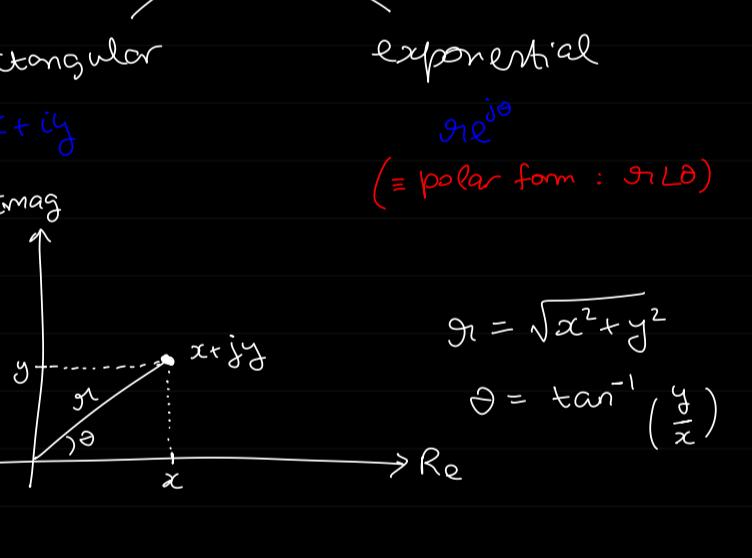

Note: diode and transistors are non-linear elements
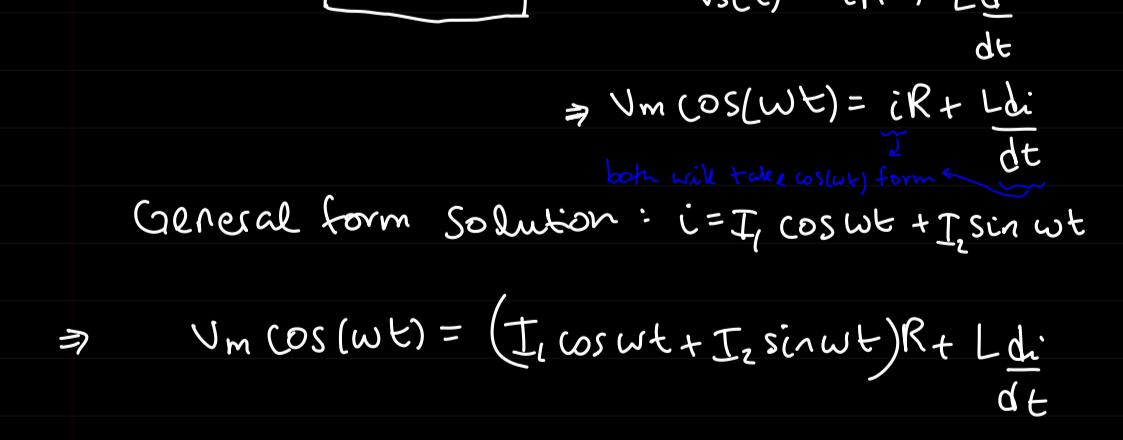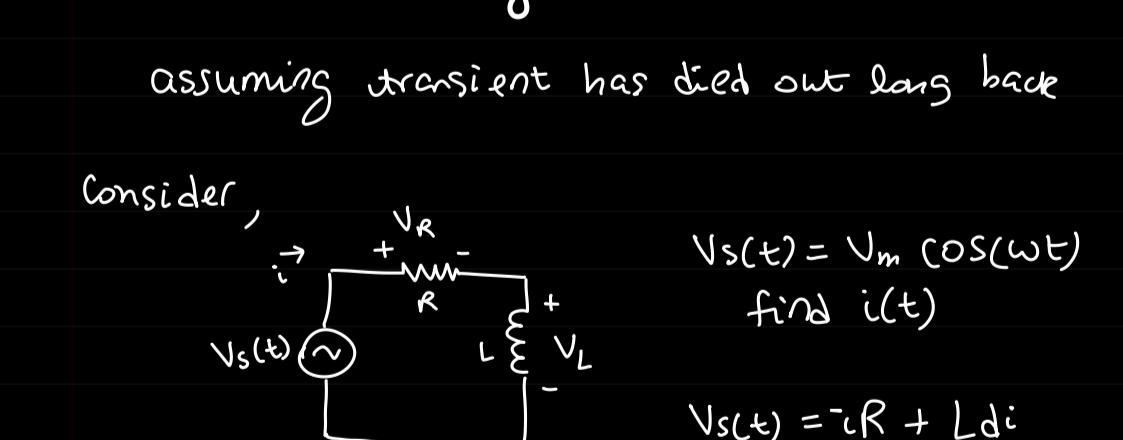
### \* Response of a linear circuit

① full response = transient response + steady state  
transient temporary persists  $t \rightarrow \infty$



$$i_{\text{final}} = i_{\text{transient}} + i_{\text{steady state}}$$

$$\text{as } t \rightarrow \infty, i_{\text{final}} = i_{\text{steady state}}$$

$$i_{\text{final}} = I_1 \cos(\omega t) + I_2 \sin(\omega t)$$

$$V_s(t) = V_m \cos(\omega t)$$

$$I_s(t) = I_1 \cos(\omega t) + I_2 \sin(\omega t)$$

$$V_s(t) = I_1 R + I_2 L \frac{dI}{dt}$$

$$V_m \cos(\omega t) = iR + L \frac{di}{dt}$$







## \* Section 10.1

(a)  $Q_1 \rightarrow 5\sin(5t - 9^\circ)$

$$t=0 \Rightarrow 5\sin(-9^\circ) = -5\sin(9^\circ) = -0.782$$

$$t=0.01 \Rightarrow 5\sin(0.05 - 9^\circ) = -5\sin(8.95^\circ) \quad X$$

$\Downarrow$   
radians

$$5\sin\left(\frac{0.05 \times 180}{\pi} - 9^\circ\right) = 5\sin(2.86^\circ - 9^\circ)$$

$$\Rightarrow -5\sin(6.14^\circ) = -0.534$$

$$t=0.1 \Rightarrow 5\sin(0.5 - 9^\circ) = 5\sin(28.64^\circ - 9^\circ) = 5\sin(19.64^\circ)$$

$$\Rightarrow 1.6805$$

(b)  $4\cos 2t$

$$t=0 \Rightarrow 4\cos(0) = 4$$

$$t=1 \Rightarrow 4\cos(2) = 3.997$$

$$t=1.5 \Rightarrow 4\cos(3) = 3.994$$

(c)  $3.2 \cos(6t + 15^\circ)$

$$t=0 \Rightarrow 3.2 \cos(15^\circ) = 3.09$$

$$t=0.01 \Rightarrow 3.2 \cos(0.06 + 15^\circ) = 3.2 \cos(3.43^\circ + 15^\circ)$$

$$\Rightarrow 3.2 \cos(18.43^\circ)$$

$$\Rightarrow 3.035$$

$$t=0.1 \Rightarrow 3.2 \cos(0.6 + 15^\circ) = 3.2 \cos(34.8^\circ + 15^\circ)$$

$$= 3.2 \cos(49.8^\circ)$$

$$= 2.086$$

Q2) (a)  $300\sin(628t) \rightarrow 300 \cdot \cos(628t - 90^\circ)$

$$4\sin(3\pi t + 30^\circ) \rightarrow 4\cos(3\pi t - 60^\circ)$$


$$14\sin(50t - 8^\circ) - 10\cos 50t \rightarrow$$

Q3)

$$V_L = 10\cos(10t - 45^\circ)$$


(a)  $i_L = 5\cos 10t$

$$-45^\circ$$

 



## ⇒ AC Power Analysis {Module: 3}

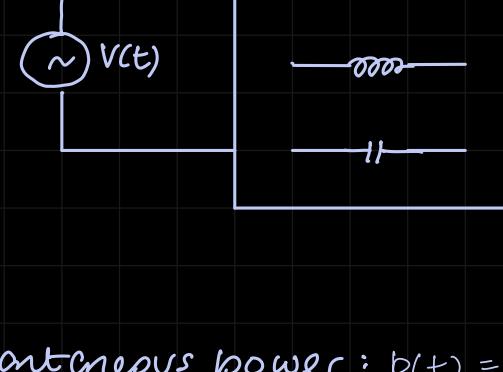

$$\cos(A) \cos(B) =$$

$$\frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

Instantaneous power:  $p(t) = v(t) \cdot i(t)$

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$p(t) = V_m \cos(\omega t + \theta) \cdot I_m \cos(\omega t + \phi)$$

$$p(t) = \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{constant}} + \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)}_{\text{twice frequency}}$$

(DC term)

(harmonic)

## • Average Power

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{real part}} dt + \underbrace{\frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) dt}_{\text{imaginary part}}$$


$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

## \* Avg. Power absorbed

## • by a purely resistive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

here, phase diff = 0°

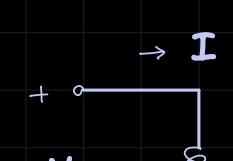


$$P_{avg} = \frac{V_m \cdot I_m}{2} = \frac{I_m^2 R}{2} = \frac{V_m^2}{2R}$$

## • by a purely inductive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

here, phase diff = 90°

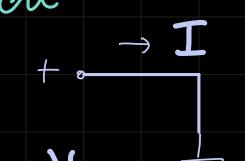

$$P_{avg} = 0 \text{ for inductor}$$

## • by a purely capacitive element

$$P_{avg} = \frac{V_m \cdot I_m}{2} \cos(-90^\circ)$$



## \* Lecture: 6

$$v(t) = V_m \cos(\omega t + \phi) \quad \leftarrow \text{Revision}$$

$$\downarrow$$


$$v(t) = R \Re \{ V_m e^{j\omega t} e^{j\phi} \}$$

$$\downarrow -e^{j\omega t}$$

$$V_m e^{j\phi} = V_m \angle \phi$$

exponential polar

• eq)

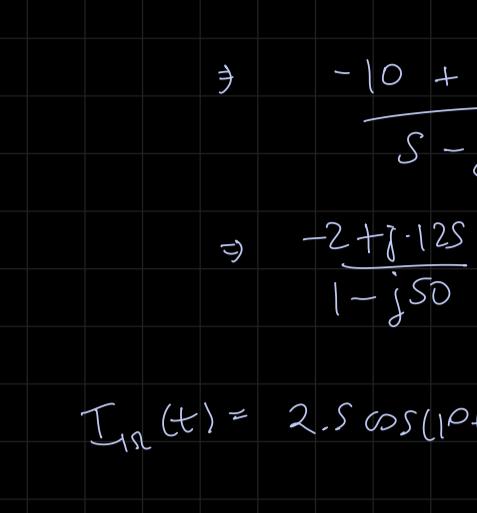


① find power delivered to each element at  $t = 0, 10, 20 \text{ ms}$

② find  $P_{avg}$  to each element

(ans) convert to freq. domain

$$V_{1\text{R}} = V_{u\text{R}} + V_c$$

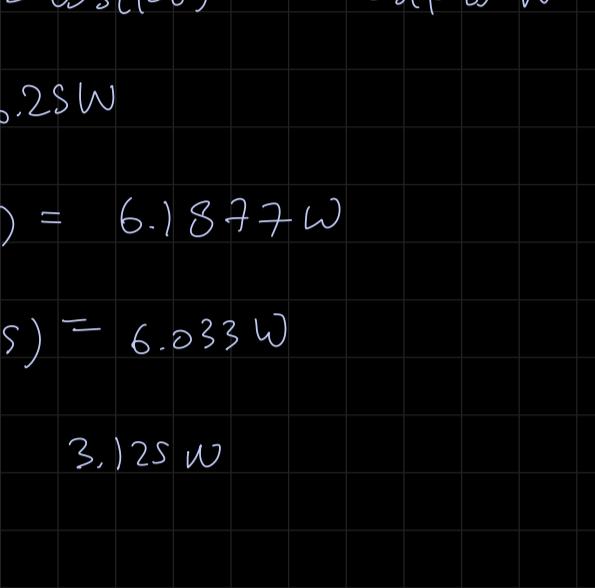

$$\textcircled{1} \quad P_{inst} = \frac{V_m I_m \cos(\theta - \phi)}{2} + \frac{V_m I_m}{2} \cos(2\omega t + \phi + \theta)$$

$$I_i = -2.5 \times \left( \frac{4 - j2.5 \times 10^4}{1 + j - j2.5 \times 10^4} \right) \approx -2.5 \text{ A}$$

$$\Rightarrow \frac{-10 + j62.5 \times 10^4}{5 - j2.5 \times 10^4} \Rightarrow \frac{-2 + j12.5}{1 - j50}$$

$$\Rightarrow \frac{-2 + j1.25}{1 - j50} \times \frac{1 + j50}{1 + j50} =$$

$$I_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$V_{1\text{R}} = (I_{1\text{R}})(2 \Omega) \Rightarrow V_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$\cos^2(\theta) = \frac{1 + \cos(2\theta)}{2}$$

$$P_{1\text{R}}(t) = 2.5 \cos(10t) \cdot 2.5 \cos(10t) \text{ W}$$

$$P_{1\text{R}}(t=0) = 6.25 \text{ W}$$

$$P_{1\text{R}}(t=20 \text{ ms}) = 6.033 \text{ W}$$

$$(P_{avg})_{1\text{R}} = 3.125 \text{ W}$$

$\Rightarrow$  P delivered to 4 ohm

$$P_{4\text{R}}(t) = V_{u\text{R}}(t) \times I_{u\text{R}}(t)$$

$$\Rightarrow I_{4\text{R}} = I_s \times \frac{1}{5 - j2.5 \times 10^4} = 10^{-4} \angle 90^\circ \text{ A}$$

$$V_{u\text{R}} = 4 \times I_{4\text{R}} = 4 \times 10^{-4} \angle 90^\circ \text{ V}$$

convert to time domain

$$P_{4\text{R}}(t) = 2 \times 10^{-8} + 2 \times 10^{-8} \cos(20t) \text{ W}$$

$$t=0^- \quad 4 \times 10^{-8} \text{ W}$$

$$t=10 \text{ ms} = 3.96 \times 10^{-8} \text{ W}$$

$$P_{4\text{R}}(t=20 \text{ ms}) = 3.87 \times 10^{-8} \text{ W}$$

$$\Rightarrow P_{avg} = 2 \times 10^{-8} \text{ W}$$

$\Rightarrow$  P delivered to capacitor

$$P_c(t) = V_c(t) \cdot I_c(t)$$

$$\left( P_{avg} \right)_c = 0 \quad \text{since phase diff} = 90^\circ$$

$$I_c = I_2 = 10^{-4} \angle 90^\circ \text{ A} \Rightarrow I_c(t) = 10^{-4} \cos(10t + 90^\circ)$$

$$V_c = (-j2.5 \times 10^4) \times 10^{-4} \angle 90^\circ$$

$$-j2.5 \times 10^4 \times (+j10^{-4}) = 2.5 \text{ V}$$

$$P_c(t) = 1.25 \times 10^{-4} \cos(20t + 90^\circ) \text{ W}$$

$$t=0 \Rightarrow P = 0 \text{ W}$$

$$t=10 \text{ ms} \Rightarrow P = 2.48 \times 10^{-8} \text{ W}$$

$$\Rightarrow P_{avg} = 2 \times 10^{-8} \text{ W}$$

$$\text{Note: we cannot multiply } I_c \text{ and } V_c \text{ in phasor form and then convert to time domain for getting } P_c \text{ (power) because power does not have a phasor part. It is a real value.}$$

\* Correct or not?

$$\text{depends on } \times \quad \textcircled{1} \quad P_{1\text{R}}(t) + P_{4\text{R}}(t) + P_c(t) = \text{constant 1}$$

$$\checkmark \quad \textcircled{2} \quad P_{avg} = P_{avg} + P_{avg} + P_{avg} = \text{constant 2} \quad \text{= Power source}$$

active sign convention



this instant power is given by the source some part = 2.5

passive sign convention



current voltage current unit: A rms

maximum power delivered to load when

$$Z_L = Z_S^*$$

complex conjugate of  $Z_S$



impedance matching circuit

$\Rightarrow$  Impedance Matching

$$100 \Omega$$

$$50 \Omega$$

$$100 \Omega$$

$$j50 \Omega$$

$$50 \Omega$$

$$Z_L = Z_S^*$$

• Sinusoidally varying voltage

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = I_m \sqrt{\frac{1}{2} \cos^2(\phi)}$$

$$V_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = V_m \sqrt{\frac{1}{2} \cos^2(\phi)}$$

$$P_{avg} = I_{eff} V_{eff}$$

$$I_{eff} = \frac{I_m}{\sqrt{2}}$$

$$V_{eff} = \frac{V_m}{\sqrt{2}}$$

$$P_{avg} = \frac{V_m \cdot I_m}{2} \cos(\phi)$$

$$P_{avg} = \frac{V_{eff} \cdot I_{eff}}{2}$$

$$P_{avg} = \frac{V_{eff}^2}{R}$$

$$P_{avg} = \frac{V_{eff}^2}{Z_L}$$

$$P_{avg} = \frac{V_{eff}^2}{Z_S}$$

$$P_{avg} = \frac{V_{eff}^2}{Z_S}$$

$$P_{avg} = \frac{V_{eff}^2}{Z_L}$$

$$P_{avg} = \frac{V$$

## \* Lecture: 7


- Instantaneous Power:  $p(t) = v(t)i(t)$
- Average Power:  $P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) = \frac{1}{2} R_{eff} \{VI^*\}$
- $P_{avg, sources} = \sum P_{avg, elements}$

\* Note:  $Z = R + jX$   
 $\downarrow$  resistive      reactive


$P_{avg, resistive} : P \neq 0$

$P_{avg, reactive} : P = 0$


## \* Max Power Transfer:

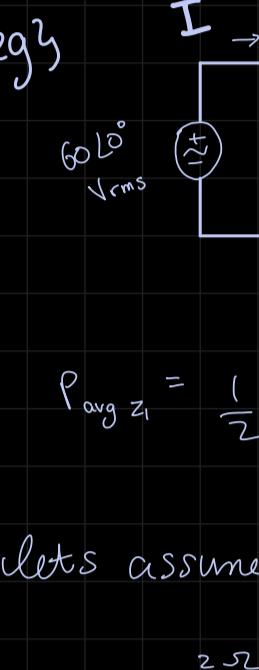

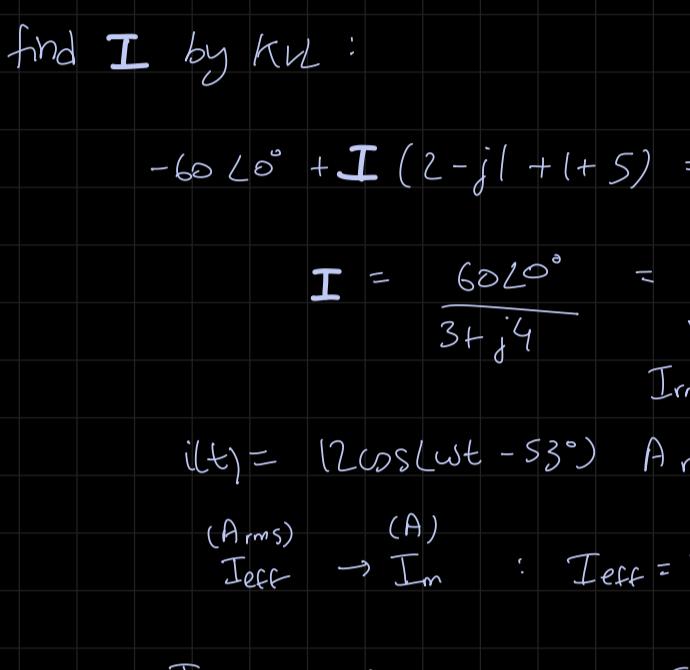Circuit has max. power when  $Z_S = Z_L^*$  complex conjugate



↓ apply Thevenin's theorem

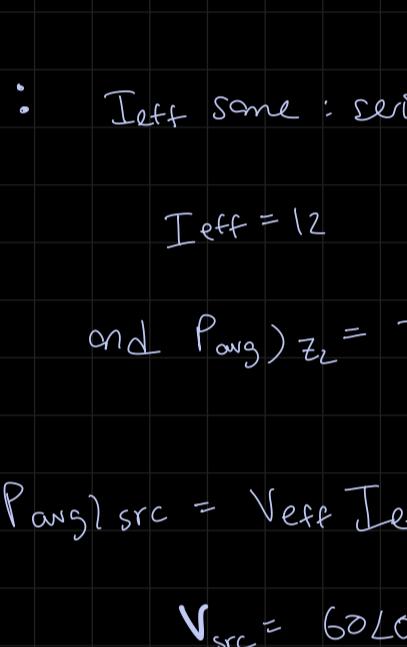

$$Z_L = Z_{th}$$

## \* Power Factor

$$PF = \cos(\theta - \phi) = \frac{\text{Power active}}{\text{Power apparent}}$$

for purely resistive load:  $PF = 1$  {Max}  $\theta - \phi = 0^\circ$   
 for purely reactive load:  $PF = 0$  {min}

Note  $\rightarrow PF = 0.5$  leading  $\rightarrow$  capacitive  $(\theta - \phi) < 0^\circ$   
 $PF = 0.5$  lagging  $\rightarrow$  inductive  $(\theta - \phi) > 0^\circ$

eg)  $I \rightarrow$   $z_1 = 2 - j1$   $z_2 = 1 + j5$   $\downarrow$  find  
 $V_{rms} = 60^\circ$   $\downarrow$   $\theta = 53.13^\circ$   $A_{rms}$   
 $I_{eff} = 12 A_{rms}$   $\downarrow$   $I_m = 12\sqrt{2} A$   
 $P_{avg, z_1} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} R_{eff} \{VI^*\}$   
 $\downarrow$  voltage across  $z_1$ , not the src

lets assume  $z_1$ :

$$\frac{2-j1}{2+j1} = \frac{-j2}{1+j4} \quad \text{so, } P_{avg, z_1} = \text{Power delivered to } 2\Omega \text{ resistor}$$

$$= I_{eff}^2 R$$

find  $I$  by KVL:

$$-60^\circ + I(2 - j1 + 1 + j5) = 0$$

$$I = \frac{60^\circ}{3 + j4} = 12L - 53.13^\circ A_{rms}$$

$$i(t) = 12 \cos(\omega t - 53.13^\circ) A_{rms}$$

$$\frac{(A_{rms})}{I_{eff}} \rightarrow \frac{(A)}{I_m} : I_{eff} = I_m = \frac{I_{eff} \sqrt{2}}{\sqrt{2}}$$

$$I_{eff} = 12 A_{rms} \Rightarrow I_m = 12\sqrt{2} A$$

$$i(t) = 12\sqrt{2} \cos(\omega t - 53^\circ) A$$

$$P_{avg}(z_1) = (12)^2 \times 2 = 288 W$$

$$\text{note: } P_{avg} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$Z_2 : I_{eff} \text{ same : series circuit}$$

$$I_{eff} = 12$$

$$\text{and } P_{avg, z_2} = I_{eff}^2 R = (144)(1) = 144 W$$

$$(2) P_{avg, src} = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$V_{src} = 60L^\circ V_{rms} \Rightarrow V_{eff} = 60 V_{rms}$$

$$I_{src} = 12L - 53.13^\circ V_{rms} \Rightarrow I_{eff} = 12 A_{rms}$$

$$\theta = 0^\circ, \phi = -53.13^\circ$$

$$P_{avg, src} = [60 \times 12] \cos(53.13^\circ) = 432 W$$

$$\text{we can observe that } 288 + 144 = 432$$

and hence,

$$P_{avg, sources} = \sum P_{avg, elements} \text{ holds}$$

$$(3) P_{apparent} = V_{eff} \cdot I_{eff} = (60)(12) = 720 W$$

$$(4) PF of combined loads = PF of source$$

$$PF = \cos(\theta - \phi) = \cos(0 + 53.13^\circ) = 0.6$$

$\theta - \phi > 0^\circ$  lagging

lagging  $\Rightarrow$

$$* P_{avg} = \frac{1}{2} R_{eff} \{VI^*\}$$

$$V_{eff} = V_{eff} L \theta$$

$$I_{eff} = I_{eff} L \phi$$

$$P_{avg} = Re \{ V_{eff} I_{eff}^* \}$$

$$Q_{reactive} = Im \{ V_{eff} I_{eff}^* \}$$

$$S = P + jQ$$

$$S = (V_{eff} L \theta)(I_{eff} L \phi)$$


$$= V_{eff} I_{eff} e^{j(\theta - \phi)}$$

$$S = P + jQ$$

## \* Lecture - 8

### • Polyphase Circuits (Chp 12)

⇒ Three Phase Source

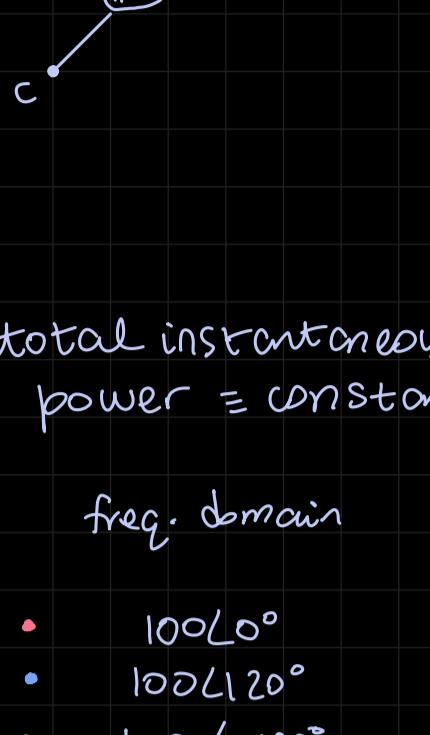

$$V_{an} = 100\angle 0^\circ \text{ V}$$

$$V_{bn} = 100\angle 120^\circ \text{ V}$$

$$V_{cn} = 100\angle -120^\circ \text{ V}$$

if  $|V_{an}| = |V_{bn}| = |V_{cn}|$   
 &  $V_{an} + V_{bn} + V_{cn} = 0$   
 then it is a

Balanced Source


total instantaneous power = constant

freq. domain

- $100\angle 0^\circ$
- $100\angle 120^\circ$
- $100\angle -120^\circ$

time domain

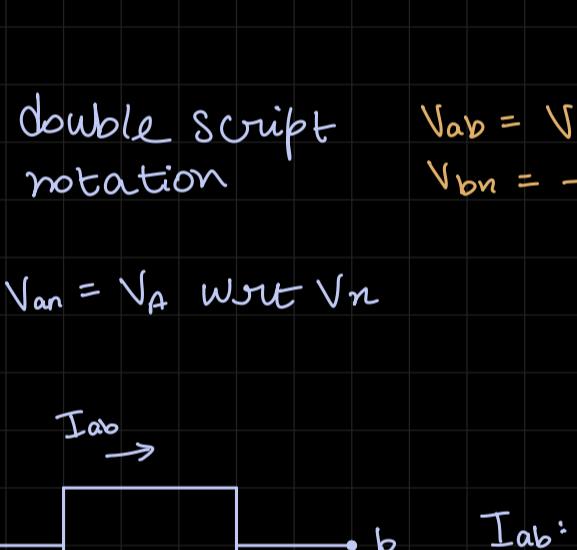
- $100 \cos(\omega t)$
- $100 \cos(\omega t + 120^\circ)$
- $100 \cos(\omega t - 120^\circ)$



total  $p(t) \rightarrow \text{constant}$

## \* Single Phase Three-wire Source

≡ Two phase source

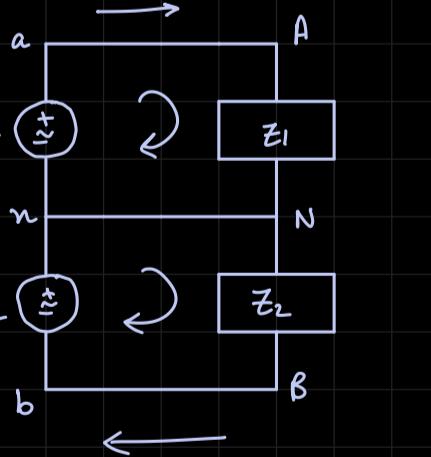

$$V_1 = V_m \angle 0^\circ$$

$$V_{an} = V_1 = V_m \angle 0^\circ$$

$$V_{bn} = -V_1 = V_m \angle 0^\circ - 180^\circ$$

$$V_{bn} \leftarrow \xrightarrow{180^\circ} V_{an}$$

double script notation

$$V_{ab} = V_{an} - V_{bn} = V_{an} + V_{nb}$$

$$V_{bn} = -V_{nb}$$

$$V_{an} = V_A \text{ wrt } V_n$$



$$I_{aa} = \frac{V_1}{Z_1}$$

$$I_{bb} = \frac{V_1}{Z_2}$$

$$I_{nn} = -I_{aa} + I_{bb}$$

$$\Rightarrow \frac{V_1}{Z_1} - \frac{V_1}{Z_2}$$

Assume  $Z_1 = Z_2$

$$I_{nn} = \frac{V_1}{Z_1} - \frac{V_1}{Z_1} = 0$$

when both srcs &  
and loads are equal

Balanced Load : current in neutral line is equal to zero.



all terms are phasors

even with resistance,  
 $I_{nn} = 0 = I_{bb} - I_{aa}$

due to

① Balanced Load  
 ≡ Symmetry



all terms are phasors

even with resistance,  
 $I_{nn} = 0 = I_{bb} - I_{aa}$

due to

① Balanced Load  
 ≡ Symmetry

## \* Lecture: 9

09/09/29

time domain freq. domain

$$\begin{array}{ll} \sqrt{V_p} \cos(\omega t + \theta^\circ) & \sqrt{V_p} L^{\theta^\circ} \\ \sqrt{V_p} \cos(\omega t + \theta^\circ - 180^\circ) & \sqrt{V_p} L^{\theta^\circ - 180^\circ} \end{array}$$

We cannot directly say,

$$P_{avg} = \sqrt{I} \times \quad \times$$

$$\text{but } P_{avg} = \frac{1}{2} \operatorname{Re}\{ \sqrt{I}^* \} \quad \checkmark$$

$$\begin{aligned} \textcircled{2} \quad a) \quad I_{AB} &= \frac{115 L^{\theta^\circ} + 115 L^{\theta^\circ}}{2(10 + j^2)} = \frac{230 L^{\theta^\circ}}{2(10 + j^2)} \\ &= 11.27 / (\theta^\circ - 11.3^\circ) A \end{aligned}$$

$$\phi = \theta - 11.3^\circ$$


$$PF = \cos(\theta - \phi + 11.3^\circ) = 0.98 \text{ lagging}$$

because PF angle is true

$$b) \quad PF = 1 \Rightarrow \cos(\theta - \phi) = 1 \Rightarrow \theta - \phi = 0$$

$$\Rightarrow \theta = \phi$$

$$f = 50 \text{ Hz}$$

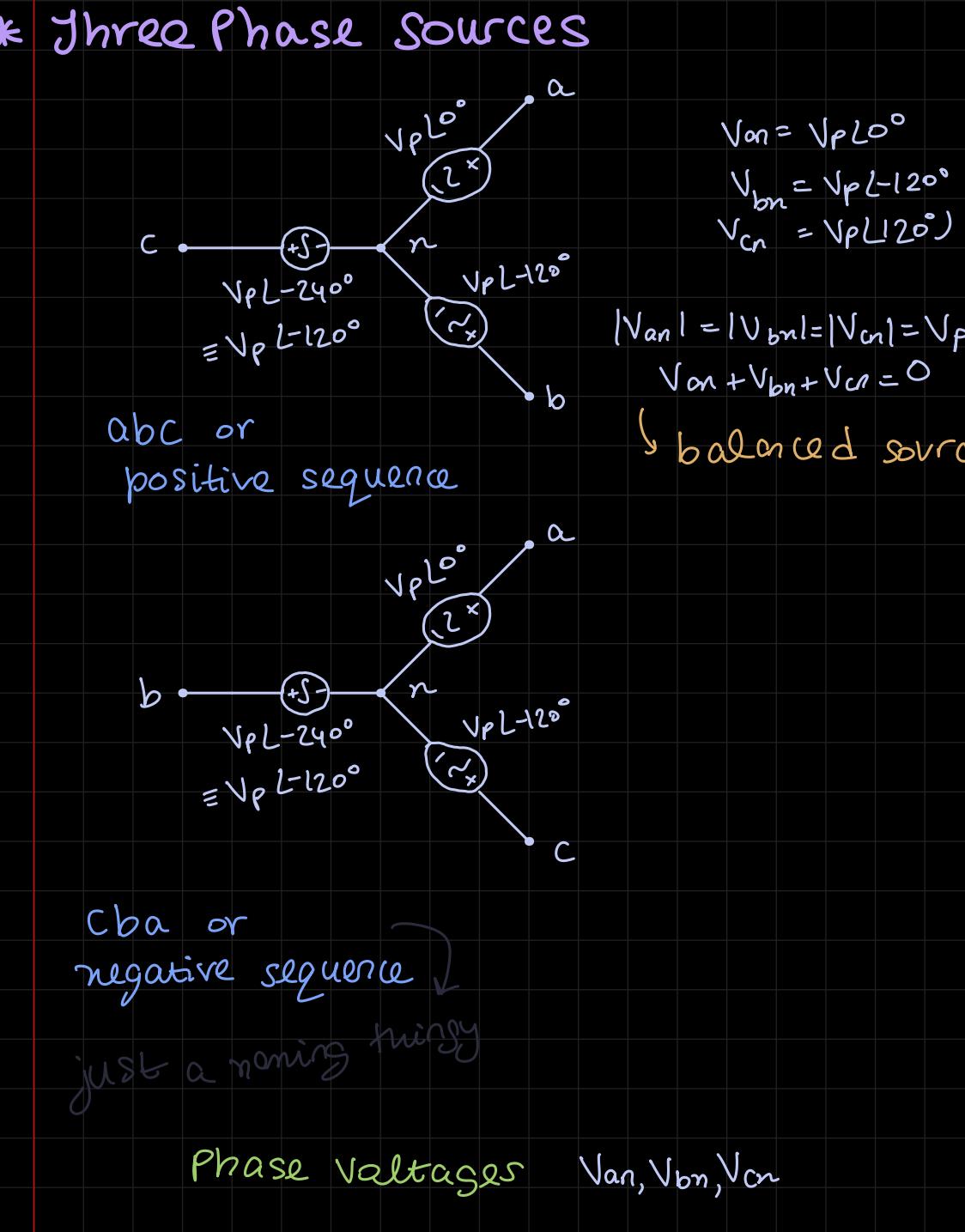

Note that this is still a balanced load, so we can remove MN since  $I_{MN} = 0$

using complex power

$S = \text{complex power of total load}$

$$S = \frac{1}{2} \sqrt{I}^*$$

$$PF = \frac{\operatorname{Re}\{ S \}}{|S|} = 1 \Rightarrow \operatorname{Re}\{ S \} = |S|$$

so,  $\operatorname{Im}\{ S \} = 0$  here

$$S = \frac{1}{2} V_{an} I_{An}^* + \frac{1}{2} V_{nb} I_{Nb}^* + \frac{1}{2} V_{ab} I_{Ab}^*$$

$$\Rightarrow \frac{1}{2} V_{an} \left( \frac{V_{an}}{Z_p} \right)^* + \frac{1}{2} V_{nb} \left( \frac{V_{nb}}{Z_p} \right)^* + \frac{1}{2} V_{ab} \left( \frac{V_{ab}}{Z_p} \right)^*$$

$$\Rightarrow \frac{1}{2} \frac{|V_{an}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{nb}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{ab}|^2}{|Z_p|^2} Z_p$$

$$\Rightarrow \frac{115^2}{10^4} (10 + j^2) + \frac{1}{2} \left( \frac{230^2}{(j\omega C)^2} \right) \left( \frac{-j}{\omega C} \right) = \frac{1}{j\omega C} = \frac{1}{j\omega} \times \frac{-1}{j\omega C}$$


$$\Rightarrow 115^2 \left( \frac{10 + j^2}{10^4} - \frac{1}{j\omega C} \right)$$

$$\Rightarrow 2 \times 115^2 \left( \frac{j}{10^4} - \frac{1}{j\omega C} \right)$$

$$\Rightarrow 2 \times 115^2 \left( \frac{1}{10^4} - \frac{1}{j\omega C} \right) = 0$$

$$\frac{1}{10^4} - \frac{1}{j\omega C} = 0 \Rightarrow C = \frac{1}{10400\pi} = 30.6 \mu F$$

\* Three Phase Sources

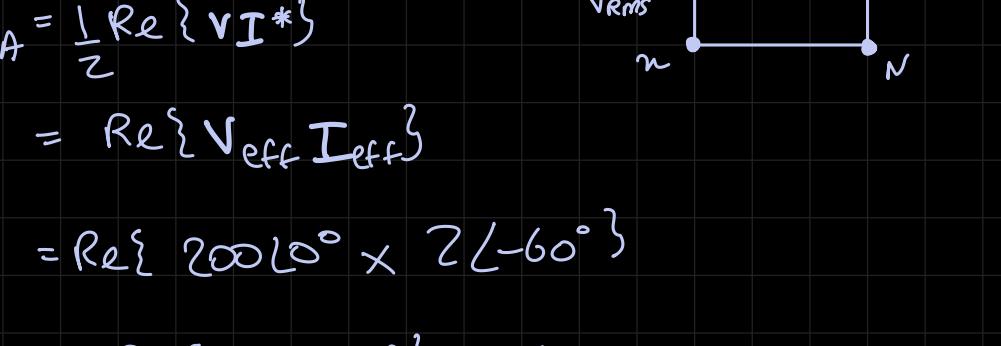

balanced source



just a naming thingy

Phase Voltages  $V_{an}, V_{bn}, V_{cn}$

Line-to-line Voltages  $V_{ab}, V_{bc}, V_{ca}$  OR line voltages

$$V_{ab} = V_{an} - V_{bn} = V_{an} + V_{nb}$$

$$V_{ab} = \sqrt{3} V_p L^{30^\circ}$$

$$V_{bc} = \sqrt{3} V_p L^{-90^\circ}$$

$$V_{ca} = \sqrt{3} V_p L^{-210^\circ}$$

\* Y-Y connection



used for easier analysis

e.g. to find total power by CRT, just add the three individual power obtained from above CRTs.

going back to the Y-Y connection =

$$I_{aa} = \frac{V_{an}}{Z_p}$$

$$I_{bb} = \frac{V_{bn}}{Z_p} = \frac{V_{an} L^{-120^\circ}}{Z_p} = I_{aa} L^{-120^\circ}$$

$$I_{cc} = \frac{V_{cn}}{Z_p} = \frac{V_{an} L^{-240^\circ}}{Z_p} = I_{aa} L^{-240^\circ}$$

$$I_{nn} = I_{aa} + I_{bb} + I_{cc} = 0$$

e.g. consider three phase balanced Y-Y connected system

$$V_{an} = 200 L^{\theta^\circ} \text{ Vrms}$$

$$V_{bn} = 200 L^{-120^\circ} \text{ Vrms}$$

$$V_{cn} = 200 L^{-240^\circ} \text{ Vrms}$$

line voltage:

$$V_{ab} = \sqrt{3} V_p L^{30^\circ} = 200 \sqrt{3} L^{30^\circ} \text{ Vrms}$$

$$V_{bc} = 200 \sqrt{3} L^{-90^\circ} \text{ Vrms}$$

$$V_{ca} = 200 \sqrt{3} L^{-210^\circ} = 200 \sqrt{3} L^{150^\circ} \text{ Vrms}$$

line currents:

$$I_{aa} = \frac{V_{an}}{Z_p} = \frac{200 L^{\theta^\circ}}{100 L^{60^\circ}} = 2 L^{-60^\circ} \text{ A rms}$$


$$I_{bb} = 2 L^{-180^\circ} \text{ A rms}$$

$$I_{cc} = 2 L^{-300^\circ} \text{ A rms} = 2 L^{60^\circ} \text{ A rms}$$

total avg. power:  $P_{avg} = \frac{1}{2} \operatorname{Re}\{ \sqrt{I}^* \}$



→ Y-Y connection

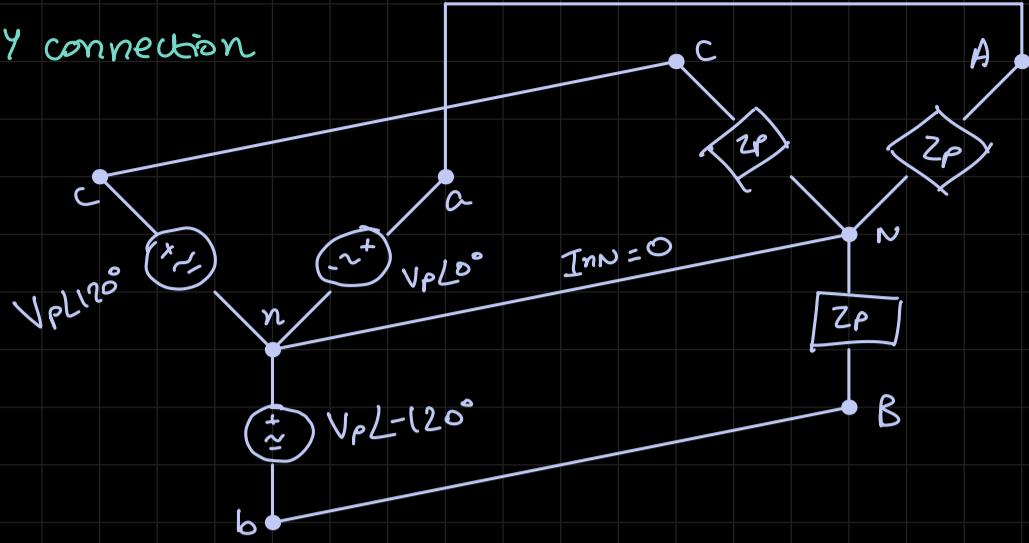

balanced load: all load are same

balanced src: all src magnitudes are equal

line: lines connecting load to src

aa cC

bb nn

Phase Voltages:  $V_{AN} = V_{an}$ ,  $V_{BN} = V_{bn}$ ,  $V_{CN} = V_{cn}$ line voltages:  $V_{ab}$ ,  $V_{ba}$ ,  $V_{ca}$ ,  $V_{ac}$ line currents:  $I_{aA}$ ,  $I_{bB}$ ,  $I_{cC}$ phase currents:  $I_{AN} = I_{aA}$ ,  $I_{BN} = I_{bB}$ ,  $I_{CN} = I_{cC}$ 

$$V_{an} = V_p L 0^\circ$$

$$V_{bn} = V_p L -120^\circ$$


$$V_{cn} = V_p L -240^\circ$$

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_p L 30^\circ$$

$$V_{bc} = \sqrt{3} V_p L -90^\circ$$

$$V_{ca} = \sqrt{3} V_p L -210^\circ$$

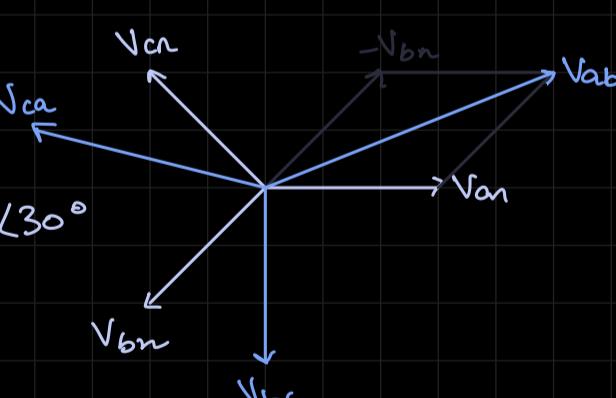

line voltages

$$V_{\text{line}} = \sqrt{3} V_{\text{phase}}$$

line currents = phase currents

\* Total Instantaneous Power

$$P_{\text{total}}(t) = P_A(t) + P_B(t) + P_C(t)$$

# Classes & Attribs

interface (entity)

~~ ~~~

Bird

↓

dmg  
(chits)

Pig

↓

health  
(units)

User

↓

save  
stage

Score

level-status

→ max-score

→ no. of pigs

(center point)

level mg

blocks

pigs

type

(wood  
glass  
steel)

Game

update score

Slingshot

angle

stretch

↙

b°



$$v = 10 \text{ m/s}$$

0°

180°

S, P

$$\sqrt{v \cos \theta, v \sin \theta}$$

per second


/ rate

-1 → 0


\* TODO: revise lecture 11 (missed due to SNS quiz)

## \* Lecture 12:

eg 3

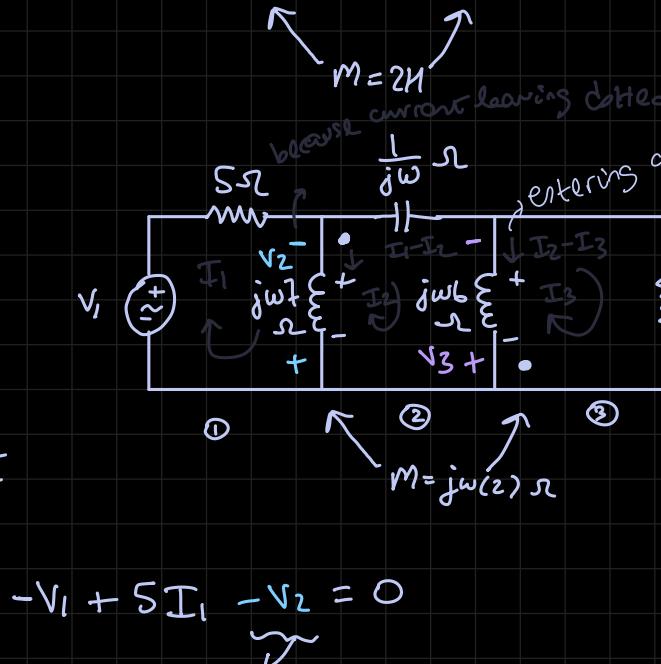

ans 3

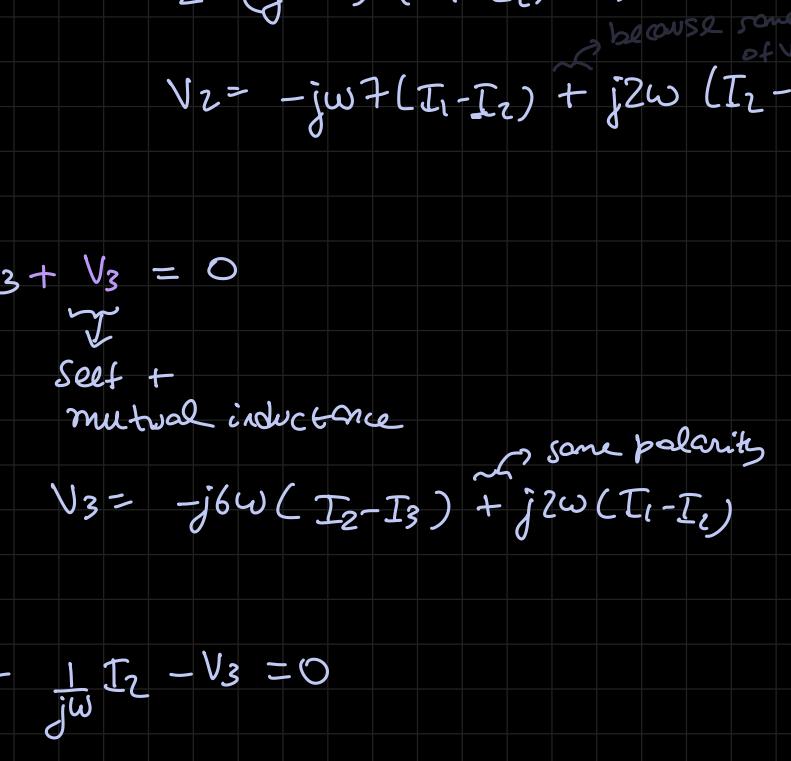

$$\textcircled{1} \quad -V_1 + 5I_1 - V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)(-1)$$

$$V_2 = -j\omega 7(I_1 - I_2) + j2\omega(I_2 - I_3)$$

$$\textcircled{3} \quad 3I_3 + V_3 = 0$$

$\downarrow$   
Self + mutual inductance


$$V_3 = -j6\omega(I_2 - I_3) + j2\omega(I_1 - I_2)$$

$$\textcircled{2} \quad V_2 + \frac{1}{j\omega} I_2 - V_3 = 0$$

$$-j\omega 7(I_1 - I_2) + j2\omega(I_2 - I_3) + j6\omega(I_2 - I_3) - j^2\omega(I_1 - I_2) + \frac{I_2}{j\omega} = 0$$

$$I_1(-j5\omega) + I_2(j17\omega) + I_3(-j8\omega) + \frac{I_2}{j\omega} = 0$$

eg 3

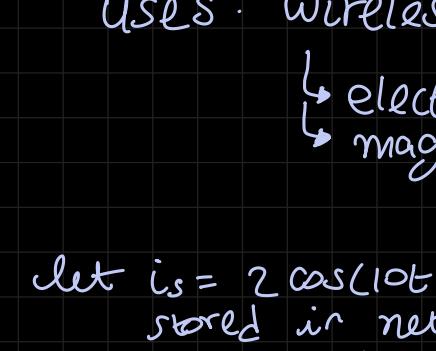

$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$\downarrow$   
we don't need to care about this sign if we use  $V_2, V_3$  method.

## \* ENERGY STORED

$$w(t) = \frac{1}{2} L(i(t))^2 \quad \text{for only one inductor}$$



$$w(t) = \frac{1}{2} L_1(i_1)^2 + \frac{1}{2} L_2(i_2)^2 \pm M_i_1(t)i_2(t)$$

$\boxed{+ve}$  sign with occur iff both  $i_1$  and  $i_2$  are entering either dotted or undotted

$\boxed{-ve}$  sign iff both enter different (dotted/undotted)

- Coupling coefficient ( $K$ )

$$M \leq \sqrt{L_1 L_2}$$

$$K = \frac{M}{\sqrt{L_1 L_2}} \Rightarrow 0 \leq K \leq 1$$

$\boxed{K \rightarrow 0}$

poor coupling or no coupling

$\boxed{K \rightarrow 1}$

Strong coupling (very close to each other)

$\Rightarrow K$  depends on: distance ; size ; ferrite b/w coils of coils core

$$y \propto \frac{1}{x}$$

$$y \propto x$$

$$y \propto x$$

uses: wireless power transfer  $\nwarrow$  inductively coupled

$\nwarrow$  electric vehicle charging

$\nwarrow$  magsafe charging

eg 3 let  $i_s = 2 \cos(10t)$  A. find total energy stored in network at  $t=0$  if  $K=0.6$  and

- (a) if  $x_y$  terminals are open circuited
- (b)  $x_y$  are short circuited



$$\text{Ans 3} \quad w(t) = \frac{1}{2} L_1(i_1)^2 + \frac{1}{2} L_2(i_2)^2 \pm M i_1(t) i_2(t)$$

$$j\omega L_1 = j4 \Rightarrow L_1 = \frac{4}{\omega} = 0.4 \text{ H}$$

- (a) if  $x_y$  are open:  $i_2 = 0$

$$\therefore w(t) = \frac{1}{2} \times 0.4 \times (2 \cos 10t)^2$$

$$w(t) = 0.8 \cos^2(10t)$$

$$\text{at } t=0 \Rightarrow w(t) = 0.8 \text{ J}$$

$$(b) \quad w(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$

$$i_1 = i_s = 2 \cos 10t$$



$$i_2 = \frac{v_x}{j2s} \quad \text{and} \quad v_x = -j\omega M i_1$$

$$i_2 = -0.6 \frac{(2 \cos 10t)}{2.5} = -0.48A$$


$$w(t=0) = \frac{1}{2} (0.4) (2^2) + \frac{1}{2} (-0.48)^2$$



$$i_2 = \frac{v_x}{j2s} \quad \text{and} \quad v_x = -j\omega M i_1$$

$$i_2 = -0.6 \frac{(2 \cos 10t)}{2.5} = -0.48A$$
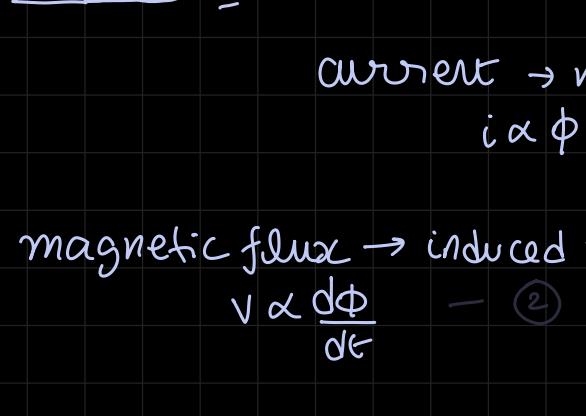
## • MODULE 5: magnetically coupled circuits



current  $\rightarrow$  magnetic flux  
 $i \propto \phi$  — ①

magnetic flux  $\rightarrow$  induced voltage


$$V \propto \frac{d\phi}{dt} \quad - \text{ ②}$$

① and ②  $\rightarrow V = L \frac{di}{dt}$

for DC source: current is constant


hence  $\frac{di}{dt} = 0$  and  $\therefore V = 0$   
 (induced)

### • Mutual Inductance

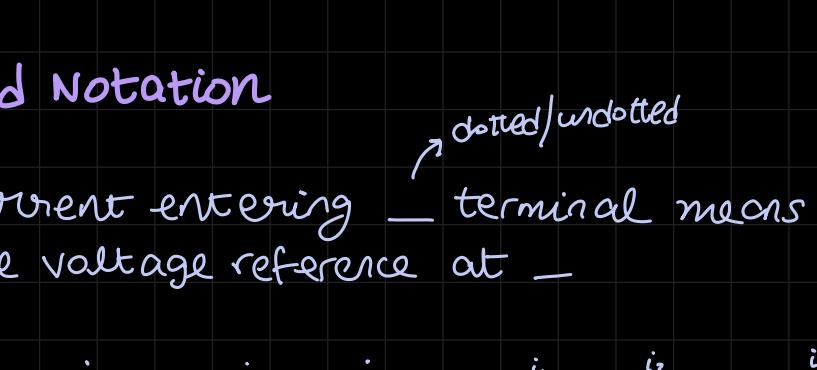

$L$ : self inductance

mutual inductance

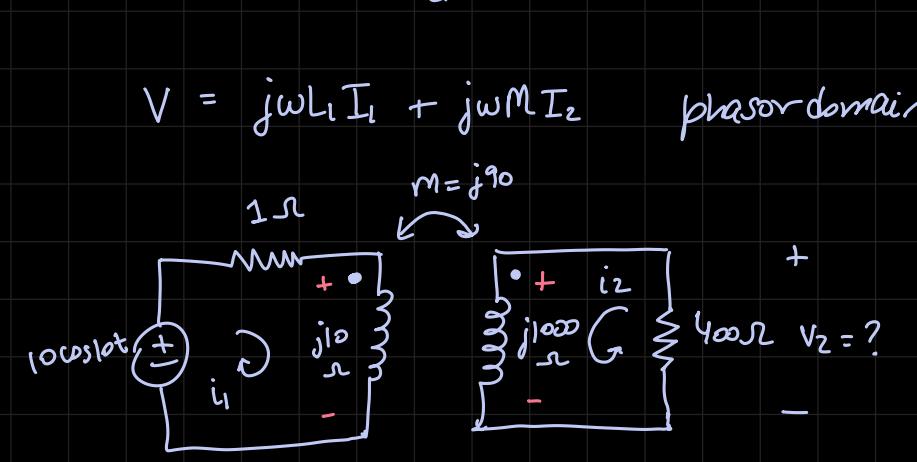

\* Additive / Subtractive Property {two different coils?}

$$i_1 \leftarrow \begin{array}{c} \circlearrowleft \\ i_1 \end{array} \quad v_2 = L \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$i_2 \leftarrow \begin{array}{c} \circlearrowright \\ i_2 \end{array} \quad v_2 = L \frac{di_2}{dt} - M \frac{di_1}{dt}$$

### • Dotted Notation

dotted/undotted

Current entering  $-$  terminal means  
 +ve voltage reference at  $-$

$$\begin{array}{cccccc} \rightarrow i_1 & \xleftarrow{i_2} & \rightarrow i_1 & \xleftarrow{i_2} & \rightarrow i_1 & \xleftarrow{i_2} \\ \bullet & \circlearrowleft & \bullet & \circlearrowleft & \bullet & \circlearrowleft \\ v & + & v & - & v & + \\ - & & + & & - & & + \\ \end{array}$$

$$v = L \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \text{time domain}$$

$$V = j\omega L_1 I_1 + j\omega M I_2 \quad \text{phasor domain}$$

$$\text{eg: } \begin{array}{c} 1\Omega \\ \text{1000} \angle 0^\circ \end{array} \quad \begin{array}{c} M \\ + \bullet \\ j10 \Omega \end{array} \quad \begin{array}{c} \bullet + \\ j1000 \Omega \\ G \end{array} \quad 400\Omega \quad v_2 = ?$$

$$(1) -10 \angle 0^\circ + I_1 + j10 I_1 + j90 I_2 = 0$$

$$I_1 (1 + j10) + I_2 (j90) = 10$$

$$(2) 400 I_2 + j1000 I_2 + j90 I_1 = 0$$

$$I_1 (j90) + I_2 (400 + j1000) = 0$$

CURRENTS :

$$\Delta = \begin{vmatrix} 1+j10 & j1000 \\ j90 & 400+j1000 \end{vmatrix}$$

$$= (1+j10)(400+j1000) + 90000$$

$$= 400 + j1000 + j4000 - 10.000 + 90.000$$

$$= j5000 + 80,400 = 80555 \angle 3.55^\circ$$

$$\Delta_1 = \begin{vmatrix} j1000 & 10 \\ 400+j1000 & 0 \end{vmatrix} = -400 - j10.000 = 10770 \angle -111.8^\circ$$

$$\Delta_2 = \begin{vmatrix} 10 & 1+j10 \\ 0 & j90 \end{vmatrix} = j900 = 900 \angle 90^\circ$$

$$I_1 = \frac{\Delta}{\Delta_1} = -3.2 + 6.75j$$

full current part

wrong because I took  $M = L_2 = j1000$  above

$$\Delta_0 = \begin{vmatrix} 1+j10 & j90 \\ j90 & 400+j1000 \end{vmatrix}$$

$$= 400 + j1000 + j4000 - 10.000 + 8100$$

$$= j5000 - 1500 = 5220 \angle 106.69^\circ$$

$$\Delta_1 =$$