

# ECE113: Basic Electronics

**WINTER 2024**

Dr. Sayan Basu Roy  
Email: sayan@iiitd.ac.in

**Office Hours:**  
Will be posted in the classroom!

# Teaching staffs

## Instructors:

Tammam Tillo	Section A
Sayan Basu Roy	Section B

## Teaching Fellow:

Awanish Kumar Singh  
Mrityunjay Kumar Ray

## Teaching Assistants

Details will be uploaded in the google classroom soon. .

# Early History of Semiconductor Devices

1940's: Vacuum-tube era

- Vacuum tubes were used for radios, television, telephone equipment, and computers
- ... but they were expensive, bulky, fragile, and energy-hungry


ENIAC-The first digital computer



→ Invention of the point-contact transistor

- **Walter Brattain, John Bardeen, and William Shockley, Bell Labs, 1947**  
**Nobel Prize in Physics 1956**

– reproducibility was an issue, however

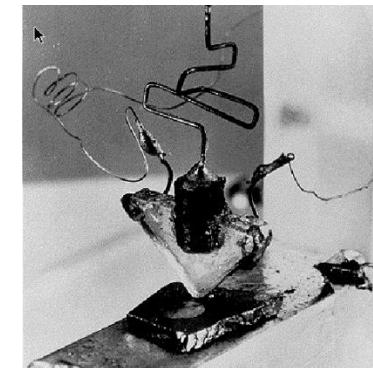

→ Invention of the bipolar junction transistor (BJT)

- **William Shockley, Bell Labs, 1950**
- more stable and reliable; easier and cheaper to make

# Discrete Electronic Circuits

- In 1954, Texas Instruments produced the first commercial silicon transistor.





~\$2.50 each

- Before the invention of the integrated circuit, electronic equipment was composed of discrete components such as transistors, resistors, and capacitors. These components, often simply called "discretes", were manufactured separately and were wired or soldered together onto circuit boards. Discretes took up a lot of room and were expensive and cumbersome to assemble, so engineers began, in the mid-1950s, to search for a simpler approach...
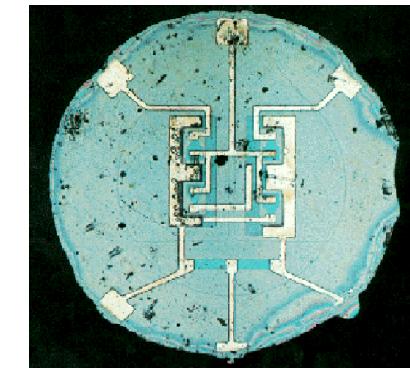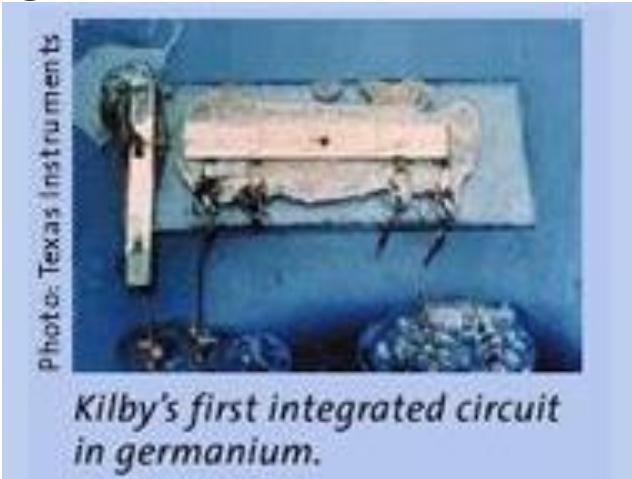
# The Integrated Circuit (IC)



- An IC consists of interconnected electronic components in a single piece ("chip") of semiconductor material.
  - In 1958, Jack S. Kilby (Texas Instruments) showed that it was possible to fabricate a simple IC in germanium.
  - In 1959, Robert Noyce (Fairchild Semiconductor) demonstrated an IC made in silicon using  $\text{SiO}_2$  as the insulator and Al for the metallic interconnects.



The first planar IC  
(actual size: ~1.5mm diameter)
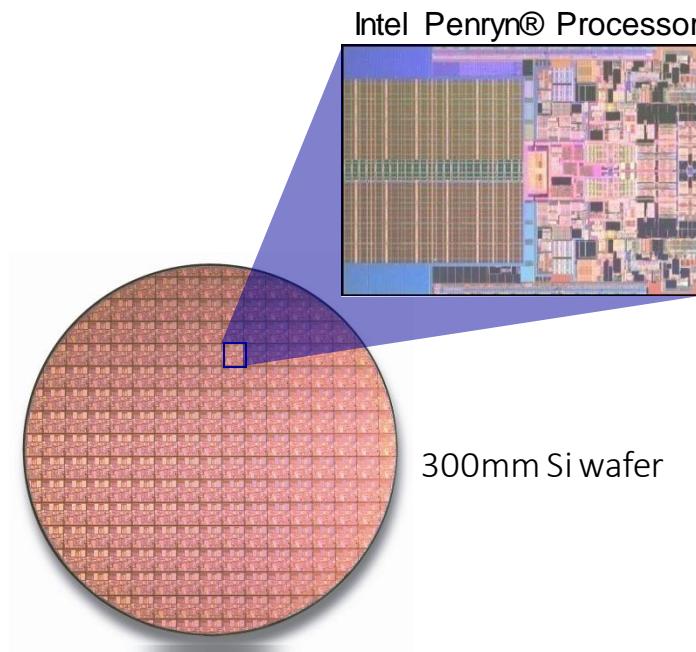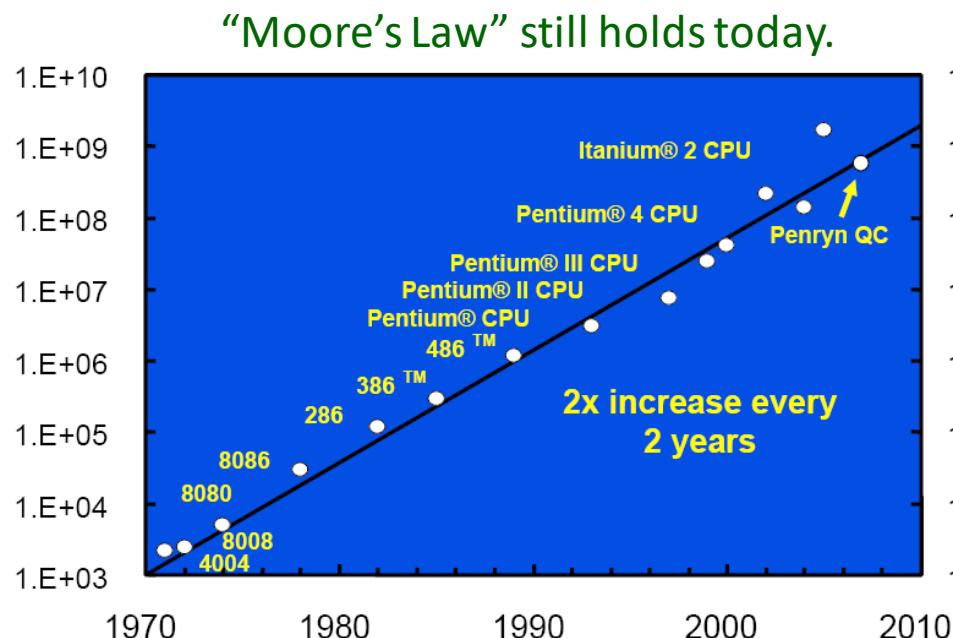
# From a Few, to Billions of Components

- By connecting a large number of components, each performing simple operations, an IC that performs complex tasks can be built.
- The degree of integration has increased at an exponential pace over the past ~40 years.
  - The number of devices on a chip doubles every ~2 years, for the same price.



# The Silicon Revolution

- Steady progress in integrated-circuit technology over 40+ years has had dramatic impact on the way people live, work, and play.
- The semiconductor industry is estimated to have more than \$600B/yr in sales in 2024. .



Military



Computers



Communications



Industrial




Transportation




Consumer Electronics

# Example electronic system: cell phone

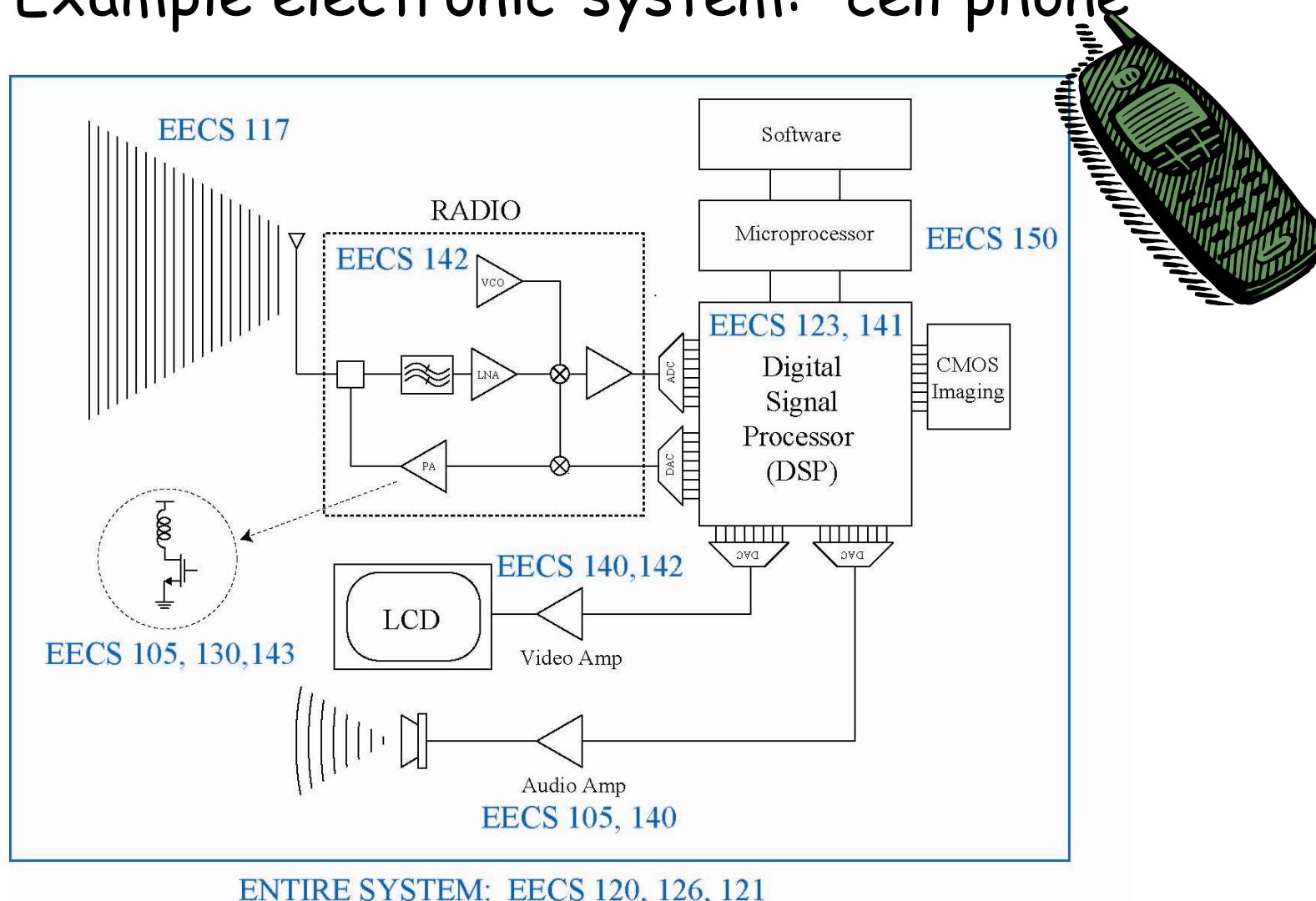

# Motivation

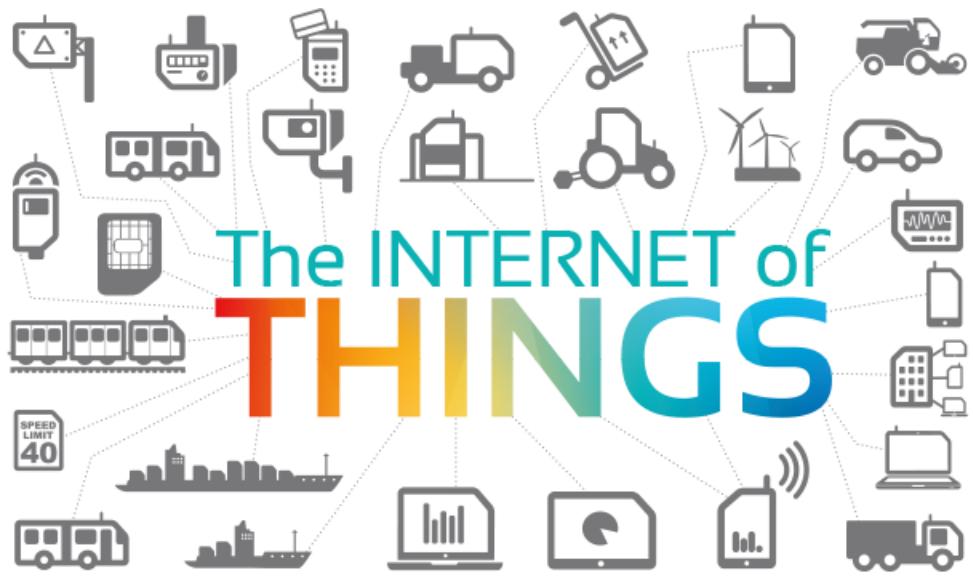

# Course Outline

- Basic components of Electrical Circuits: Fundamental Electrical variables - charge, current, voltage and power; independent and dependent voltage and current sources, Ideal circuit elements - Resistor, Capacitor and Inductor. Passive and Active Components, Constitutional relationship - Ohms Law;
- Basic concepts of Analysis of Resistive Networks: Nodes, Paths and Loops, Kirchoff's Voltage and Current Laws, Series and Parallel connection of Resistances and division voltage and current. Loop and Node Analysis.
- Network Theorems: Thevenin's Theorem, Norton's Theorem
- Superposition Theorem and Maximum Power Transfer Theorem.
- RC and RL circuits' response
- RLC circuits' response
- Concepts of impedance/admittance, Phasors and Representation
- RC, RL and RLC circuits' response to Alternating inputs (the response to alternating input will be handled only under steady state condition)

# Course Outline

- Operational Amplifier - Inverting configuration
- Operational Amplifier - Non-Inverting, Integrating and Differentiating configuration
- Diodes: Basic principle, Clipper, Clamper circuits and application
- LED, Zener Diode and Solar Cell
- Half Wave and Full Wave Rectifiers - Wave form and Ripple & its reduction.

- **Text books:**

William H. Hayt Jr., Jack E. Kemmerly and Steven M. Durbin, *Engineering Circuit analysis*. 8th Edition, Tata McGraw Hill

Smith, Ralph J and Dorf, R C, "Circuits Devices and Systems", 5<sup>th</sup> Edition, John Wiley and Sons

### Reference book

There are many text for Principles of Electrical Engineering

## Assessment

- Assignments 15% (two assignments)
- Quizzes 15% (two quizzes)
- Laboratory 20% (2% attendance, 8% lab report/file, 10% lab exam)
- Mid Semester 20%
- End Semester 30%

## Course communication

- All the announcements, assignments, lectures, lab materials will be shared through **google classroom**.
- No separate communications shall be done using email, unless necessary.
- Consult course site at **google classroom** regularly

# How to Join ECE113- Basic Electronics Section B in google classroom?

- Log on to google classroom using your IIITD credentials
- Click on the + sign at the top right corner
- Select join class
- Enter this class code: **nxgzhyt**

# Laboratory

- Location: We will have laboratory Session in ECE Labs
- Lab materials will be provided through google classroom
- From next week onward: **prepare for the lab beforehand**
- Lab Engineers with the help of TFs and TAs will manage laboratory

# Tutorial

- Location: We will have Tutorial Session once in every week
- Tutorial materials will be provided through google classroom
- TFs with the help of TAs will manage Tutorials

## Ground rules

- Be on time
- Ask questions and interact with me if some concepts are not clear!
- Post your questions in the google classroom! Use it as an interactive platform to discuss concepts!
- **IIIT Delhi plagiarism policy** will be strictly followed in this class
- Note that your first point of contacts are TAs; followed by TFs; followed by the Instructor.

# **ECE113: Basic Electronics**

**WINTER 2024**

Dr. Sayan Basu Roy  
A603, R&D Building  
Email: [sayan@iiitd.ac.in](mailto:sayan@iiitd.ac.in)

# Electrical quantities

- Charge: unit - Coulomb
- Current: unit - Ampere
- Voltage: unit - Volt
- Power: unit - Watt
- Resistance: unit - Ohm



SI units

# Charge

- A physical property of matter which interacts with electromagnetic field
  - Experiences a force due to a electromagnetic field
  - Responsible for creating electric field
- The force can be calculated using Coulomb's Law:
$$F = \frac{Kq_1q_2}{d^2}$$
- Two types of charges: +ve and -ve
- Same types of charges repel and unlike types attract
- Convention: charge of a proton is +ve and that of an electron is -ve
- The unit of charge is the coulomb (C),
- One coulomb is one ampere second (1 coulomb =  $6.24 \times 10^{18}$  electrons).
- The coulomb is defined as the quantity of electricity which flows past a given point in an electric circuit when a current of one ampere is maintained for one second




# Current

- Electric/ electronic circuits' function depends on flow of charge
- Current is defined as the instantaneous rate at which net positive charge move past a specific point/ cross-section at a specific direction:

$$i = \frac{dq}{dt}$$


- Unit: Ampere (A): 1 C/s
- Can vary with time (unless DC, in ideal case)
- A current of 5 A flows for 2 minutes in a circuit, find the quantity of electricity transferred.

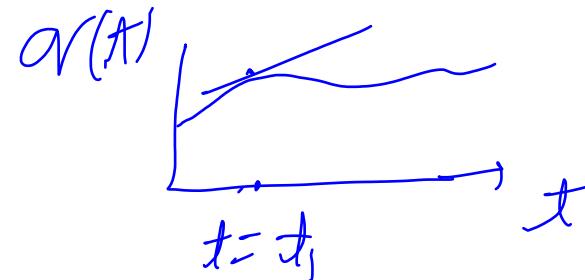- Quantity of electricity  $Q=It$  coulombs
- $I=5$  A,  $t=2\times 60=120$  s
- Hence  $Q=5\times 120=600$  C




# Current representation

- Direction is important

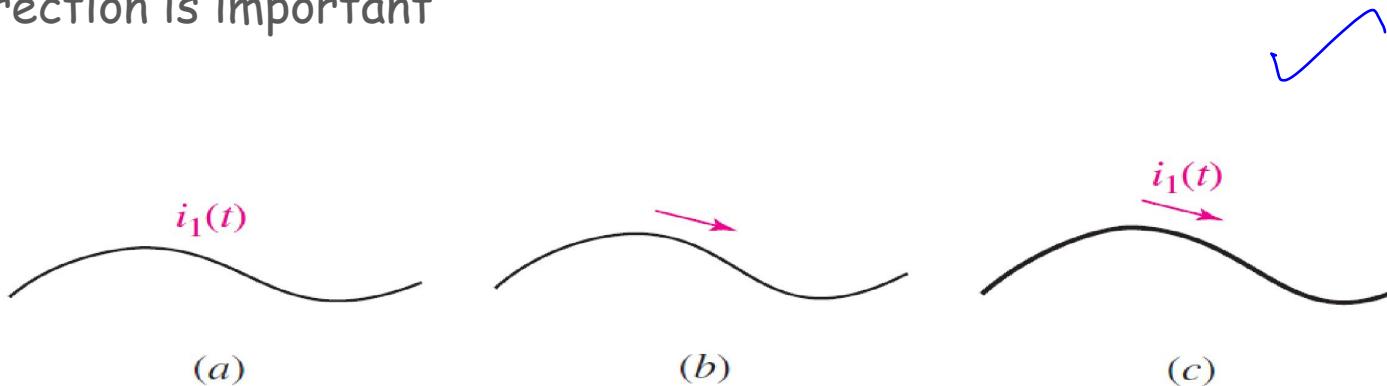


c) Is the correct  
representation

# Current representation

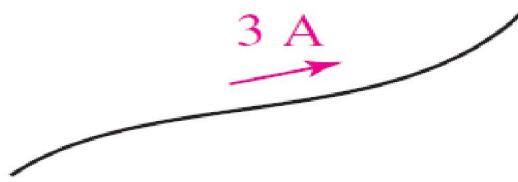


(a)

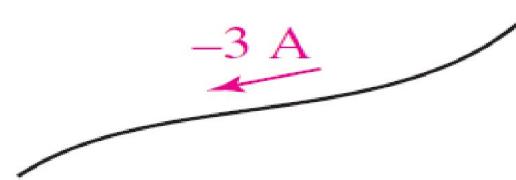


(b)

Both are  
same


# Types of current/voltage waveforms

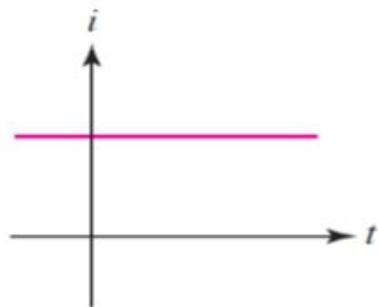


Direct Current (DC)

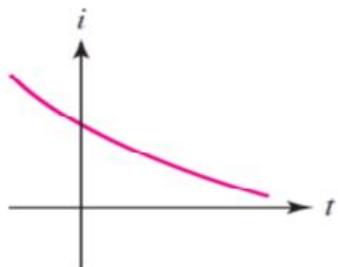

Exponential Current

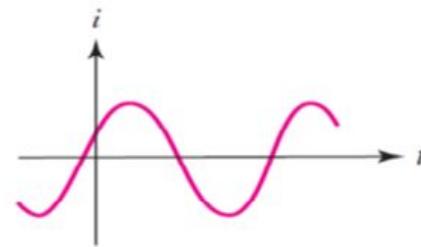

Sinusoidal Current

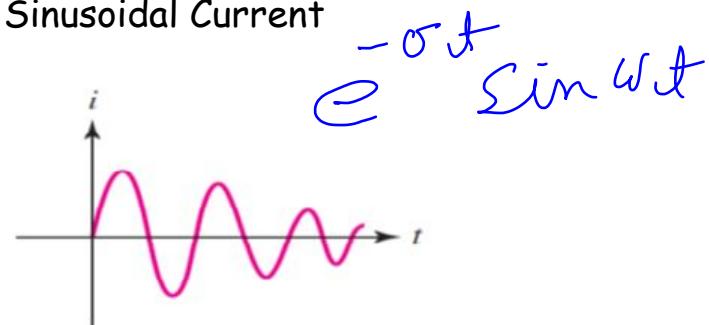

Damped Sinusoidal Current

# Voltage


The unit of electric potential is the volt (V), where one volt is one joule per coulomb. One volt is defined as the difference in potential between two points in a conductor which, when carrying a current of one ampere, dissipates a power of one watt, i.e.

$$\begin{aligned}\text{volts} &= \frac{\text{Watt}}{\text{ampères}} = \frac{\frac{\text{joules}}{\text{second}}}{\text{ampere}} \\ &= \frac{\text{joules}}{\text{ampères secounds}} = \frac{\text{joules}}{\text{coulombs}}\end{aligned}$$


A change in electric potential between two points in an electric circuit is called a potential difference and its unit is Volt.

The electromotive force (e.m.f.) provided by a source of energy such as a battery or a generator is measured in volts.


# Voltage representation

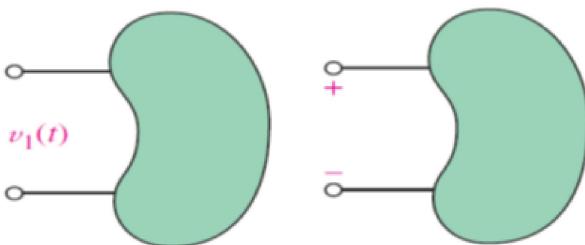


Incorrect  
representation

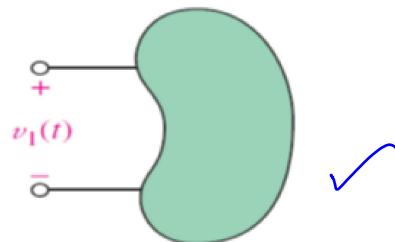


Correct  
representation

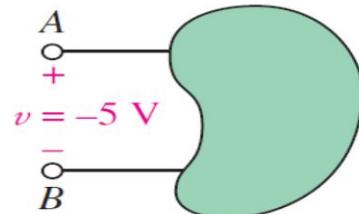


(a)

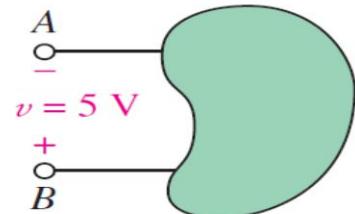

(b)

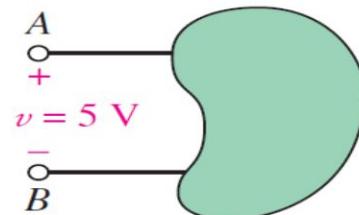

(c)

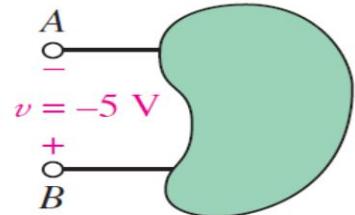

(d)

$$c = d$$

$$a \leq b$$

# Electric Power

- When a direct current of  $I$  amperes is flowing in an electric circuit and the voltage across the circuit is  $V$  volts, then

$$\text{power in watts } P = VI$$

Unit: Watt = 1

$$\begin{aligned}\text{Electrical energy} &= \text{Power} \times \text{time} \\ &= \underline{VI} \times t \text{ joules}\end{aligned}$$

$$E = P \cdot t$$

- Although the unit of energy is the joule, when dealing with large amounts of energy the unit used is the kilowatt hour (kWh)


where  $1\text{kWh} = 1000 \text{ watt hour}$

$$= 1000 \times 3600 \text{ watt seconds (joules)} = 3600 \ 000 \text{ J}$$

$$P = \frac{dE}{dt}$$
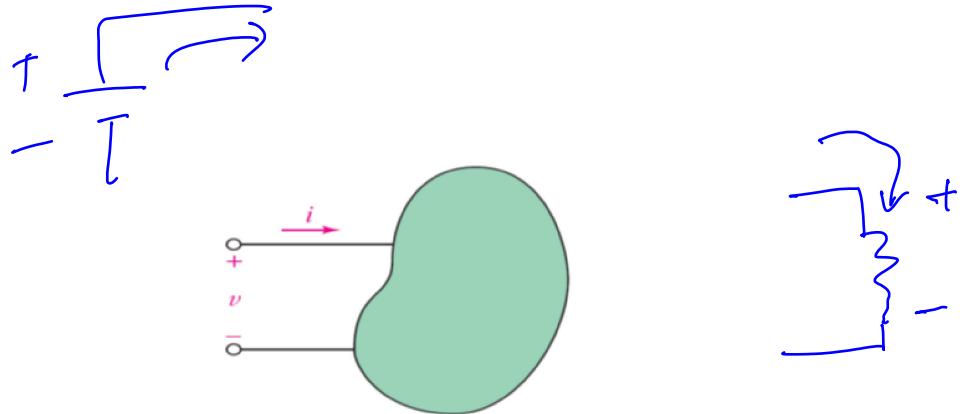
## Passive sign convention

Power absorbed by the element  $p = vi$   
We can also say that element generates or supplies a power of  $-vi$



- When the current arrow is directed into the element at the plus-marked terminal, we satisfy the passive sign convention.
- If the current arrow is directed into the "+" marked terminal of an element, then  $p = vi$  yields the *absorbed power*. A negative value indicates that power is actually being generated by the element.
- If the current arrow is directed out of the "+" terminal of an element, then  $p = vi$  yields the *supplied power*. A negative value in this case indicates that power is being absorbed.

- If a current of 5 A flows for 2 minutes, find the quantity of electricity transferred.

$$Q = I \times t = 5 \times 2 \times 60 = 600 \text{ C}$$


- An e.m.f. of 250 V is connected across a resistance and the current flowing through the resistance is 4 A. What is the power developed?
- 450 J of energy are converted into heat in 1 minute. What power is dissipated?
- A current of 10 A flows through a conductor and 10 W is dissipated. What p.d. exists across the ends of the conductor?
- A battery of e.m.f. 12 V supplies a current of 5 A for 2 minutes. How much energy is supplied in this time?
- A d.c. electric motor consumes 36 MJ when connected to a 250 V supply for 1 hour. Find the power rating of the motor and the current taken from the supply.

# Energy Sources

Although every generator supplies both voltage and current, it is desirable to distinguish between two general classes of devices.


If the voltage output is relatively independent of the circuit to which it is connected (as in the battery of Fig. 1), the device is called a "voltage source."

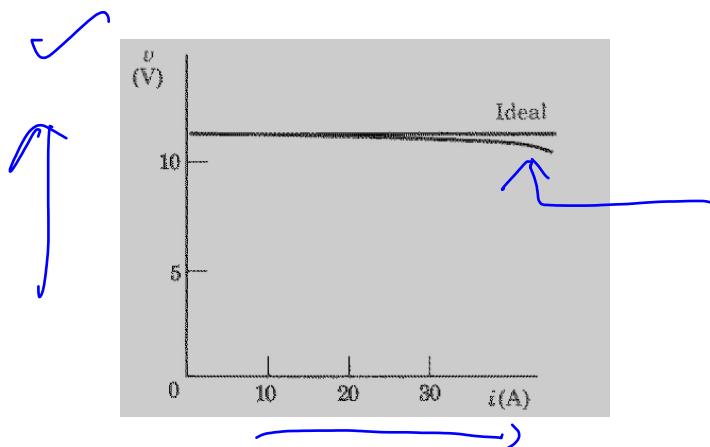If over wide ranges the output current tends to be independent of the connected circuit (as in the transistor of Fig. 2), it is treated as a "current source."



voltage  
source

Fig. 1

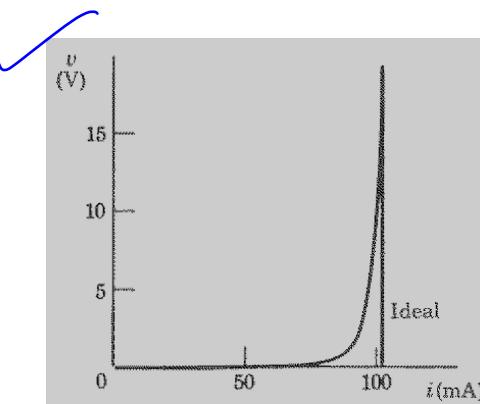

current  
source

Fig. 2

# Energy Sources

Ideal voltage source: the output voltage is completely independent of current.


An ideal constant-voltage generator is one with zero internal resistance so that it supplies the same voltage to all loads.

Output voltage is function of time and the voltage is unaffected by changes in circuit configuration. Examples : DC battery, DC power supply


Ideal current source: the output current is completely independent of voltage.

An ideal constant-current generator is one with Infinite internal resistance so that it supplies the same current to all loads.

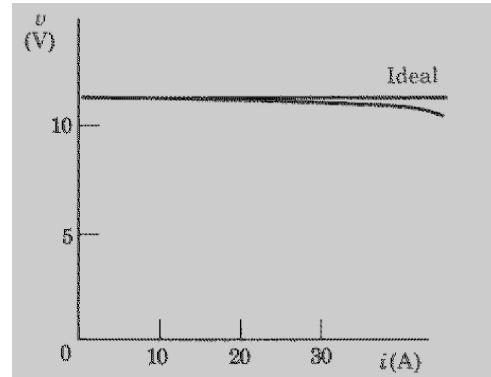Output current is also function of time and the current is unaffected by changes in circuit configuration.




voltage  
source  
Fig. 1

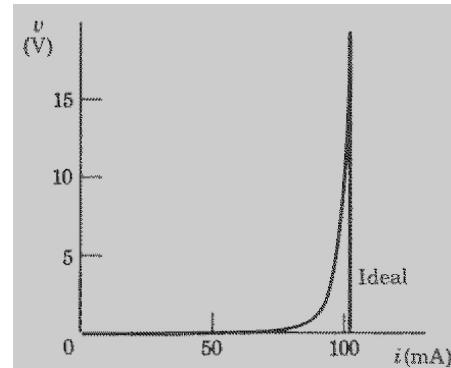

current  
source  
Fig. 2

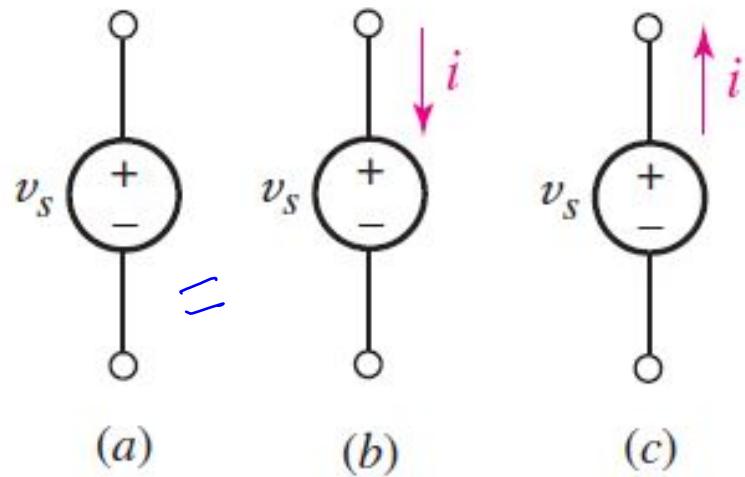
# Independent Voltage Source

- Terminal voltage is completely independent of the current
- + sign is a reference, does not necessarily mean that upper terminal is numerically +ve
- This is a theoretical notion, a mathematical model that can be used for further analysis



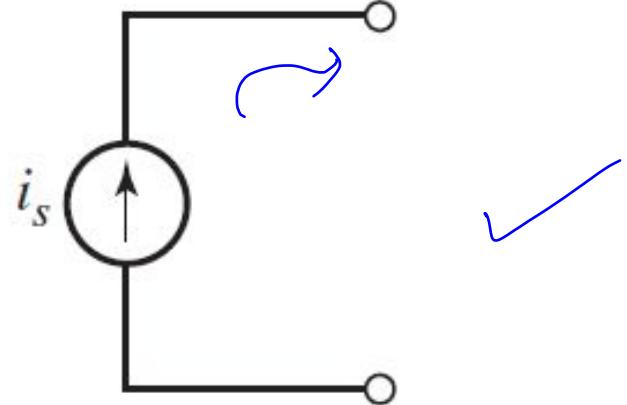
# Independent Current Source

- Current is completely independent of the terminal voltage
- Arrow denotes the direction
- Does not necessarily mean that terminal voltage difference will be 0
- Direction: +ve to -ve is +
- Direction: -ve to +ve is -




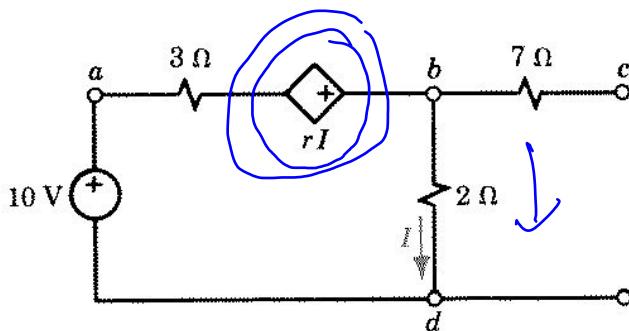
# Dependent Voltage or Current Sources

- These are also ideal sources
- Dependent on current or voltage at some other area of the circuit
- Again independent of terminal voltage/current




Dependent Voltage Source

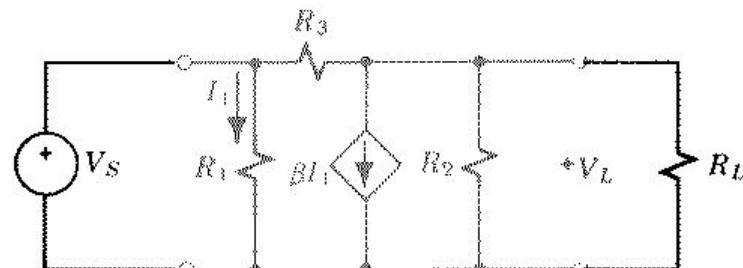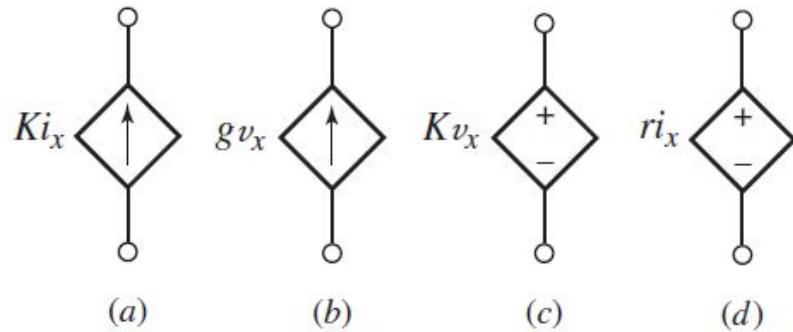


Dependent Current Sources
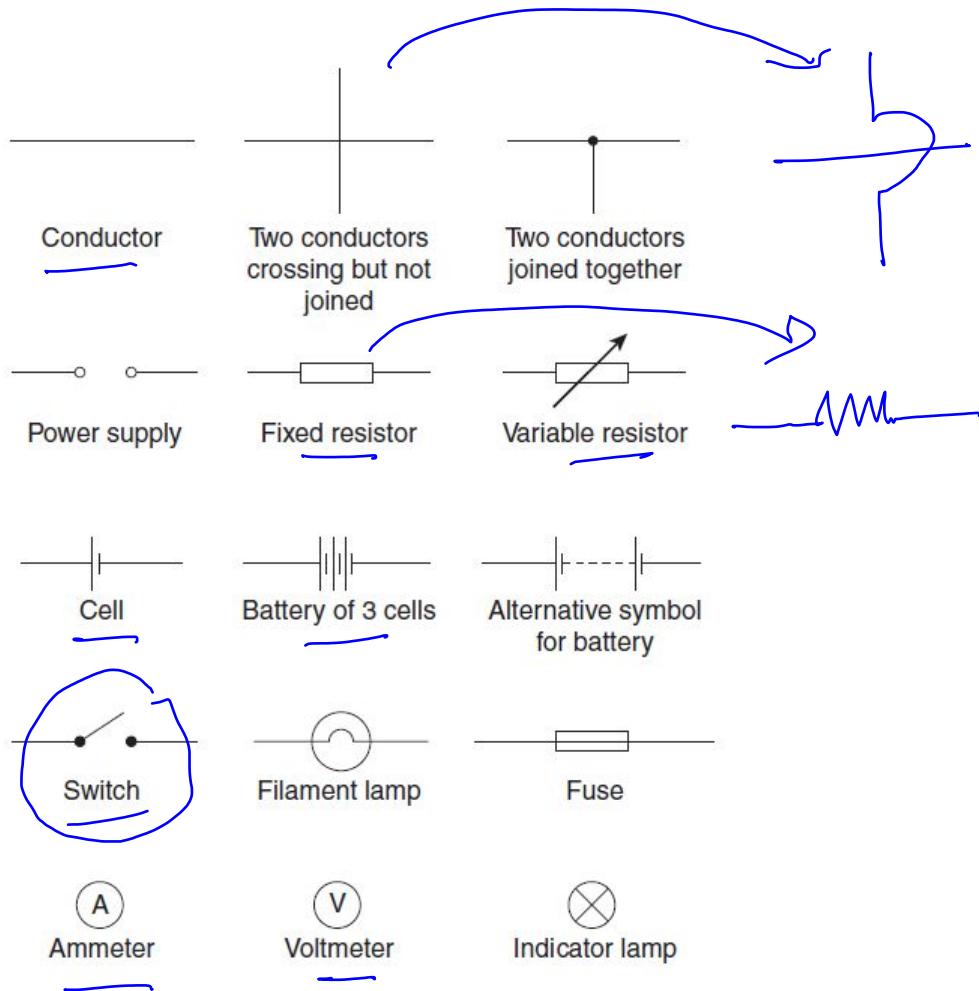
## Standard symbol for electrical components


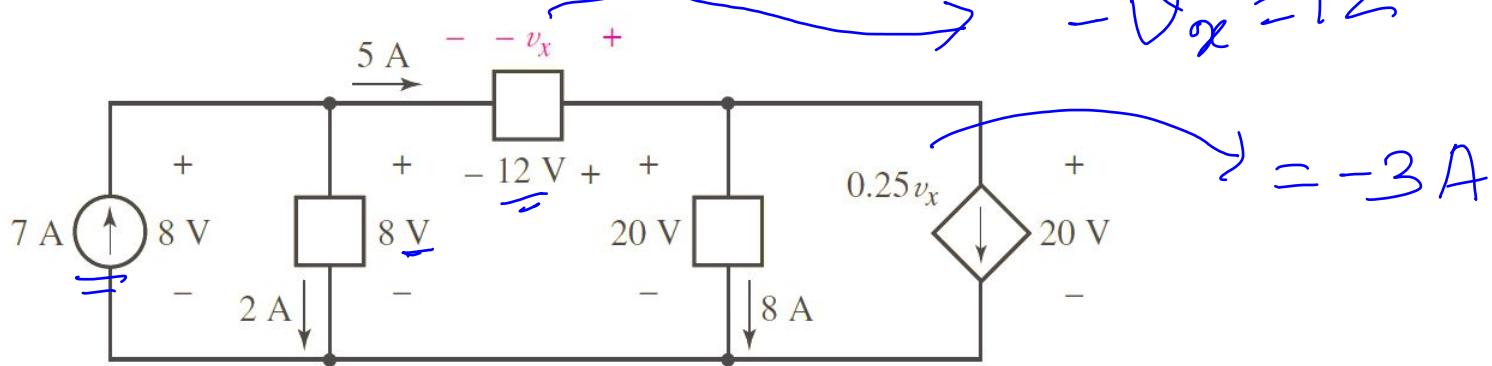
# Example problem

Find the power *absorbed* by each element in the circuit in Fig



Ans: (left to right) -56 W; 16 W; -60 W; 160 W; -60 W.

# Resistance


- The flow of electric current is subject to friction. This friction, or opposition, is called **resistance**,  $R$ , and is the property of a conductor that limits current.
- The unit of resistance is the **ohm**; 1 ohm is defined as the resistance which will have a current of 1 ampere flowing through it when 1 volt is connected across it.

$$\text{resistance } R = \frac{\text{potential difference}}{\text{current}}$$

- Ohm's law** states that the current  $I$  flowing in a circuit is directly proportional to the applied voltage  $V$  and inversely proportional to the resistance  $R$ , provided the temperature remains constant. Thus

$$i = \frac{v}{R} \quad \text{or} \quad v = I \cdot R \quad \text{or} \quad R = \frac{v}{i}$$

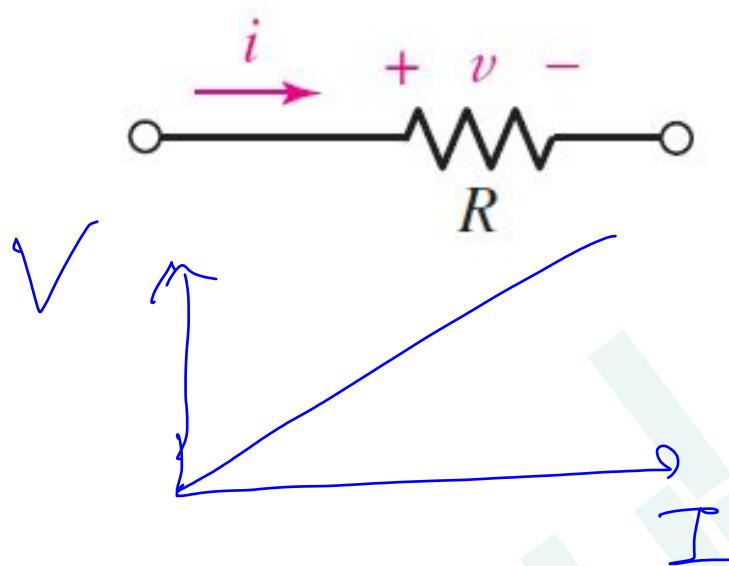- Symbol of resistance is shown in figure



# Resistance



## Electric Power

- **Power  $P$**  in an electrical circuit is given by the product of potential difference  $V$  and current  $I$
- The unit of power is the **watt, W**.

$$P = V \times I \text{ watts}$$

From Ohm's law  $V = I R$ , thus

$$\underline{P = I^2 R \text{ watts}}$$

This is also equivalent to  $\underline{P = \frac{V^2}{R} \text{ watts}}$

$$\begin{aligned} P &= VI = I^2 R \\ &= \frac{V^2}{R} \end{aligned}$$

- A 100 W electric light bulb is connected to a 250 V supply. Determine (a) the current flowing in the bulb, and (b) the resistance of the bulb

$$\text{Current } I = P / V = 100/250 = 0.4 \text{ amp}$$

$$\text{Resistance } R = V/I = 250/0.4 = 625 \Omega$$

$$R = \epsilon$$

$$\epsilon \rightarrow 0$$

# Resistance and resistivity

The resistance of an electrical conductor depends on

- the length of the conductor
- the cross-sectional area of the conductor
- the type of material and
- the temperature of the material.

Resistance,  $R$ ,

- directly proportional to length,  $l$ , of a conductor, i.e.  $R \propto l$ .
- inversely proportional to cross-sectional area,  $a$ , of a conductor, i.e.  $R \propto 1/a$ .

Thus resistance  $R \propto l/a$

By inserting a constant of proportionality into this relationship the type of material used may be taken into account.

The constant of proportionality is known as the **resistivity** of the material and is given the symbol  $\rho$  (Greek rho). Thus

$$\text{Resistance } R = \frac{\rho l}{A} \text{ ohms}$$

Unit of  $\rho$  is ohm meter.

$$R = \frac{\rho l}{A}$$


## Problems

- A piece of wire of cross-sectional area  $2 \text{ mm}^2$  has a resistance of  $300 \Omega$ . Find (a) the resistance of a wire of the same length and material if the cross-sectional area is  $5 \text{ mm}^2$ , (b) the cross-sectional area of a wire of the same length and material of resistance  $750 \Omega$ .
- Calculate the resistance of a 2 km length of aluminium overhead power cable if the cross-sectional area of the cable is  $100 \text{ mm}^2$ . Take the resistivity of aluminium to be  $0.03 \times 10^{-6} \Omega\text{m}$ .
- Some wire of cross-sectional area  $1 \text{ mm}^2$  has a resistance of  $20 \Omega$ . Determine (a) the resistance of a wire of the same length and material if the cross-sectional area is  $4 \text{ mm}^2$ , and (b) the cross-sectional area of a wire of the same length and material if the resistance is  $32 \Omega$ .

$$\frac{R_1}{R_2} = \left\{ \frac{A_2}{A_1} \right\} l$$

$$\frac{R_1}{R_2} = \left\{ \frac{l_1}{l_2} \right\} A$$

# Circuit Elements

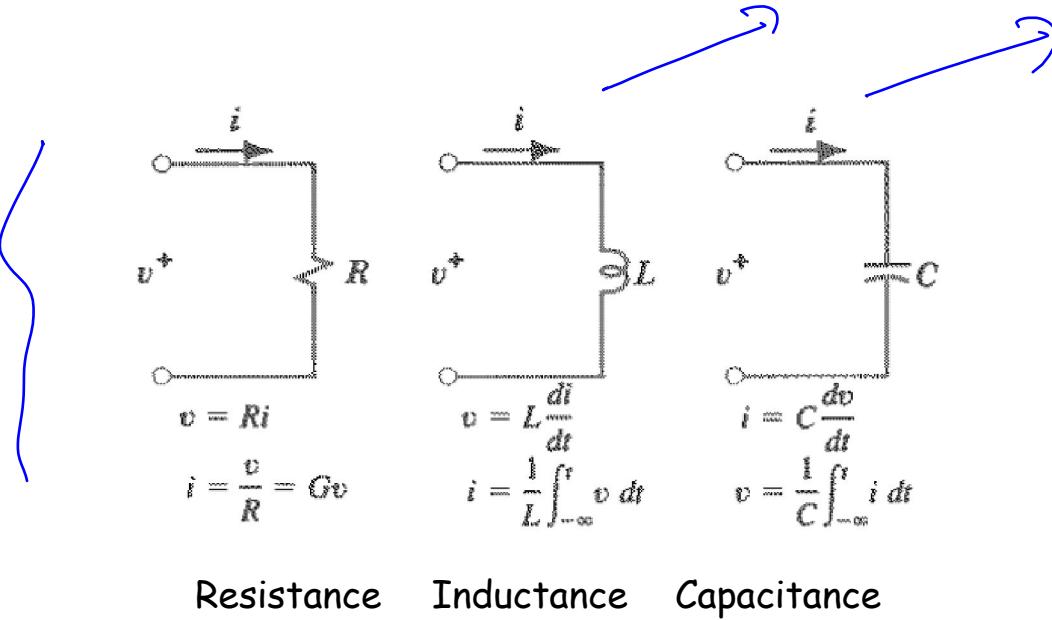

# Capacitor

A capacitor is an electrical device that is used to store electrical energy.

Next to the resistor, the capacitor is the most commonly encountered component in electrical circuits.

Capacitors are used extensively in electrical and electronic circuits.

For example, capacitors are used to smooth rectified a.c. outputs, they are used in telecommunication equipment - such as radio receivers - for tuning to the required frequency, they are used in time delay circuits, in electrical filters, in oscillator circuits and in magnetic resonance imaging (MRI) in medical body scanners, to name but a few practical applications.

Every system of electrical conductors possesses capacitance.

For example, there is capacitance between the conductors of overhead transmission lines and also between the wires of a telephone cable.

In these examples the capacitance is undesirable but has to be accepted, minimized or compensated for.

There are other situations where capacitance is a desirable property. Devices specially constructed to possess capacitance are called capacitors (or condensers, as they used to be called). In its simplest form a capacitor consists of two plates which are separated by an insulating material known as a dielectric. A capacitor has the ability to store a quantity of static electricity.

# Capacitor

Figure 1(a) shows two parallel conducting plates separated from each other by air. They are connected to opposite terminals of a battery of voltage  $V$  volts.

Static electric fields arise from electric charges, electric field lines beginning and ending on electric charges. Thus the presence of the field indicates the presence of equal positive and negative electric charges on the two plates of Figure 1. Let the charge be  $+Q$  coulombs on one plate and  $-Q$  coulombs on the other. If the voltage is disconnected, the charge persists on capacitor.

The property of this pair of plates which determines how much charge corresponds to a given p.d. between the plates is called their capacitance:

$$C = \frac{Q}{V} \text{ Farad or } Q = C V$$

$$Q = C V$$

Symbol of capacitor is shown in Figure 1(b)

If voltage  $V$  is constant, no current flows through capacitor. If  $V$  is changing with time, there is a current flow through the capacitor and it is given by

$$i \approx C \frac{dv}{dt}$$

$$C = \frac{\epsilon A}{d}$$

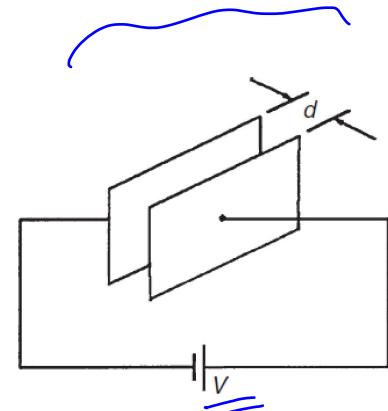


Figure 1(a)

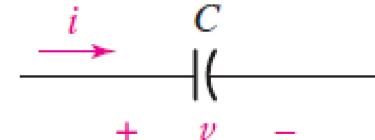


Figure 1(b)

# Capacitor

$$i = C \frac{dv}{dt}$$

Current-voltage relationship

We have  $C = Q/V$  or  $V = Q/C$

Thus for a current  $i(t)$ , the voltage  $v(t)$  across the capacitor is given as

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t') dt' + v(t_0)$$

where  $v(t_0)$  is initial charge

- Find the capacitor voltage that is associated with the current shown graphically in Figure 3. The value of capacitor is  $5 \mu F$ .

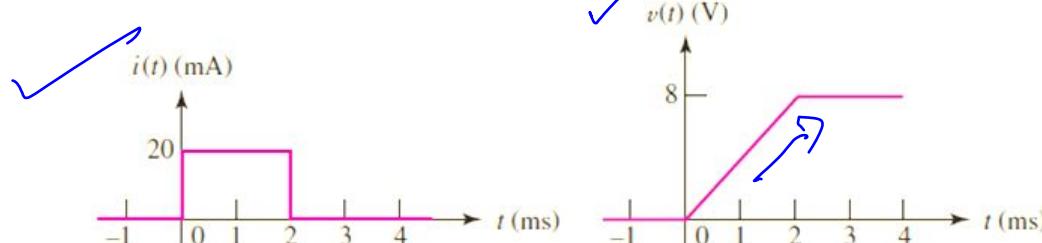


Figure  
3

# Capacitor

The power across the capacitor is given as

$$\text{Power: } p = vi = vC \frac{dv}{dt}$$

Stored energy can be calculated by integrating power considering zero initial voltage:

$$w_C(t) = \frac{1}{2} C v(t)^2$$

$$\begin{aligned} E &= \int P dt = \int V I dt \\ &= \int_0^t V \cdot C \frac{dv}{dt} \cdot dt \\ &= \int_0^{v(t)} V C dv = \frac{1}{2} C V(t)^2 \end{aligned}$$

# Inductor

If a conductor is wound as a coil as shown in Figure 5, the coil behaves as an inductance.

Voltage across the coils is approximately proportional to rate of change of current and it is given by following relation:

$$\text{Induced voltage } (v) = L \frac{di}{dt} \text{ volts.}$$

L is constant of proportionality and is measured in henrys.

This relationship can be derived from our knowledge of magnetic fields.

If a magnetic flux ( $\Phi$ ) is obtained by passing a current  $i$ , the Inductance (L) is

$$L = \frac{\Phi}{i}$$

(Faraday's Law of induction) and we get,

$$v = \frac{d\Phi}{dt} = L \frac{di}{dt}$$

Given the waveform of the current as shown in Figure 6(a). Plot the voltage waveform.

The voltage output is  $3 di/dt$  and voltage waveform is plotted in

$$\Phi = L \cdot I$$



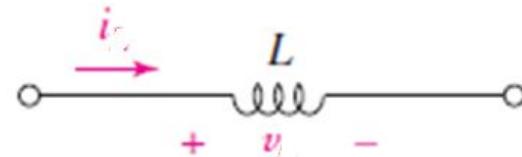


Figure 5

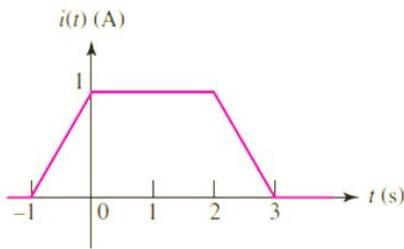

(a)


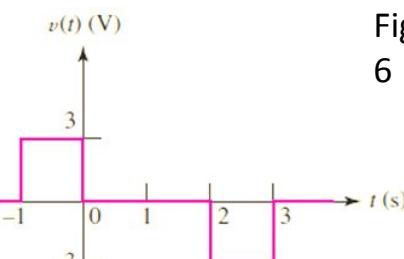


(b)

Figure 6

# Inductor

Inductor Symbols

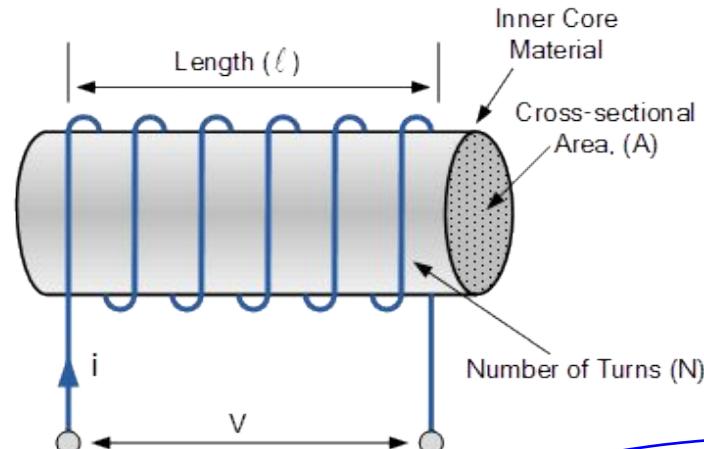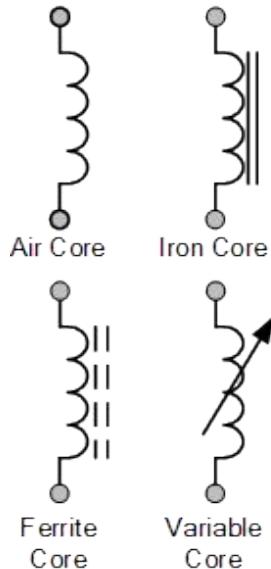

$$V(t)$$

$$V \neq \infty$$

$$I(t)$$

$$L = \frac{N^2 \mu A}{l}$$

$\mu$  is the permeability of the core

Capacitors

$$I(t)$$

$$I \neq \infty$$

$$= V(t)$$

# Inductor

The Voltage-current relationship is given as

$$i(t) = \frac{1}{L} \int_{t_0}^t v dt' + i(t_0)$$

$$\text{Power } p = vi = Li \frac{di}{dt}$$

$$\text{Energy with zero initial current: } \underline{w_L(t)} = \underline{\frac{1}{2}} L \underline{i(t)^2}$$

$$\begin{aligned} E &= \int P dt = \int V I dt \\ &= \int L I \cdot \frac{dI}{dt} \cdot dt \\ &= \frac{1}{2} L I^2 \end{aligned}$$

# Energy stored in linear elements

If the  $v-i$  characteristics of a device is known, energy =  $\int v i dt$

## Inductance

We know  $v = L di/dt$  volts and  $I = 0$  at  $t = 0$ ,

and

This equation tells  $w_L = \int_0^T L \frac{di}{dt} i dt = \int_0^T Li di = \underline{\underline{\frac{1}{2}LI^2}}$  and it is not dissipated like resistance.

## Capacitance

In capacitance, we know  $i = C dv/dt$  and  $v$  across the capacitor is zero at  $t = 0$ .

and

In capacitance also  $w_C = \int_0^T vC \frac{dv}{dt} dt = \int_0^V Cv dv = \underline{\underline{\frac{1}{2}CV^2}}$

## Resistance

In resistance, we have  $v = R i$  and  $I = 0$  at  $t = 0$  and

$$w_R = \int_0^T Ri i dt = \int_0^T Ri^2 dt = \underline{\underline{R i^2 T}}$$

## Capacitor and Inductor


- These elements store and deliver finite amount of energy
- Passive linear circuit elements
- The current-voltage relationships for these new elements are time dependent
- Ideal Capacitors and Inductors can neither generate nor dissipate energy

## Applicability of KCL and KVL


- L and C are linear elements
- Kirchhoff's laws can be applied (are not restricted to only  
resistance)

# ✓ Non-ideal Voltage Source

*trade-off*

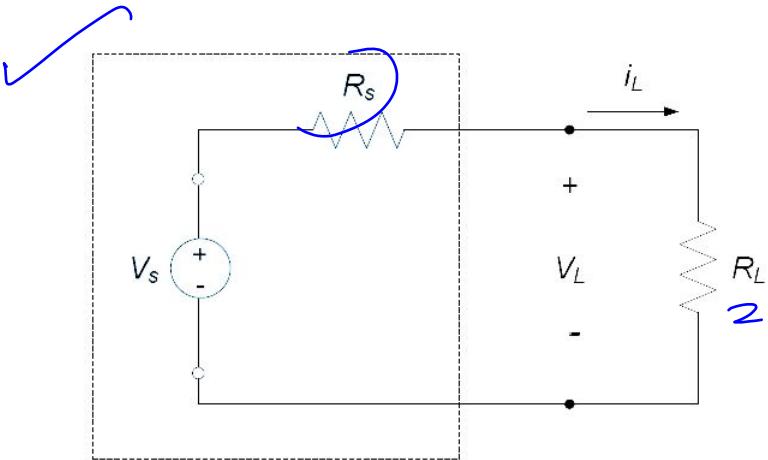

$$R_L \gg R_s$$

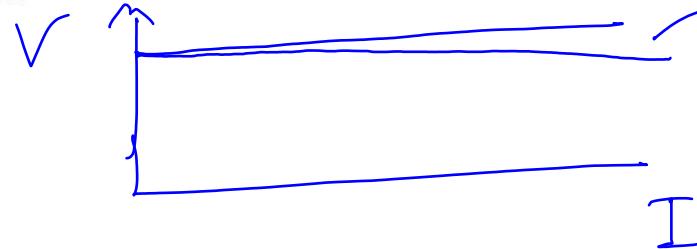

- Modelled as an ideal voltage source  $V_s$  and internal resistance  $R_s$
- When load resistance  $R_L$  draws large current, supply voltage  $V_s$  decreases and the converse
- It does not provide infinite power
- Ideal voltage source has zero internal resistance  $R_s$

Problem:


- The no load or open circuit voltage of voltage source is 16 Volts. When a load resistance of 10 ohm is applied, the output voltage  $V_L$  is 8 Volts. Find the source resistance  $R_s$ .
- Twelve cells, each with an internal resistance of 0.24 and an e.m.f. of 1.5 V are connected (a) in series, (b) in parallel. Determine the e.m.f. and internal resistance of the batteries so formed.

*non-ideal  
source*
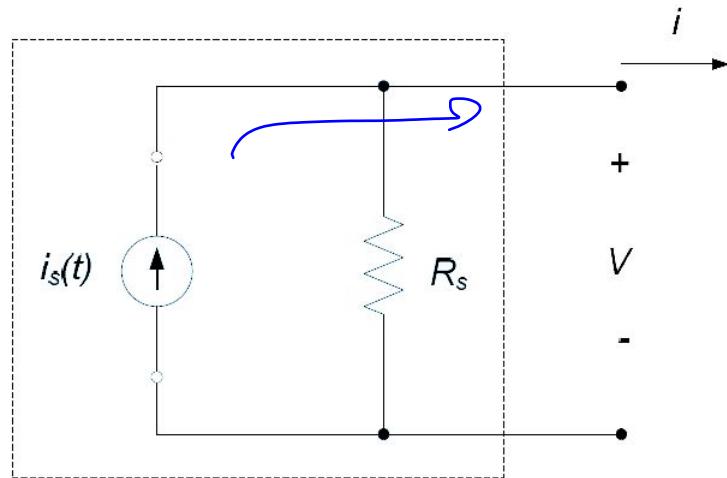
# Non-ideal current source



- Modelled as an ideal current source  $i_s$  and internal resistance  $R_s$  in parallel
- Higher terminal voltage results in lower supply current
- Ideal current source means a source with infinite internal resistance






Ideal  
case

$\leftarrow R_s \approx \infty$

# Nodes

- Node: A point at which two or more circuit elements have a common connection.




branches

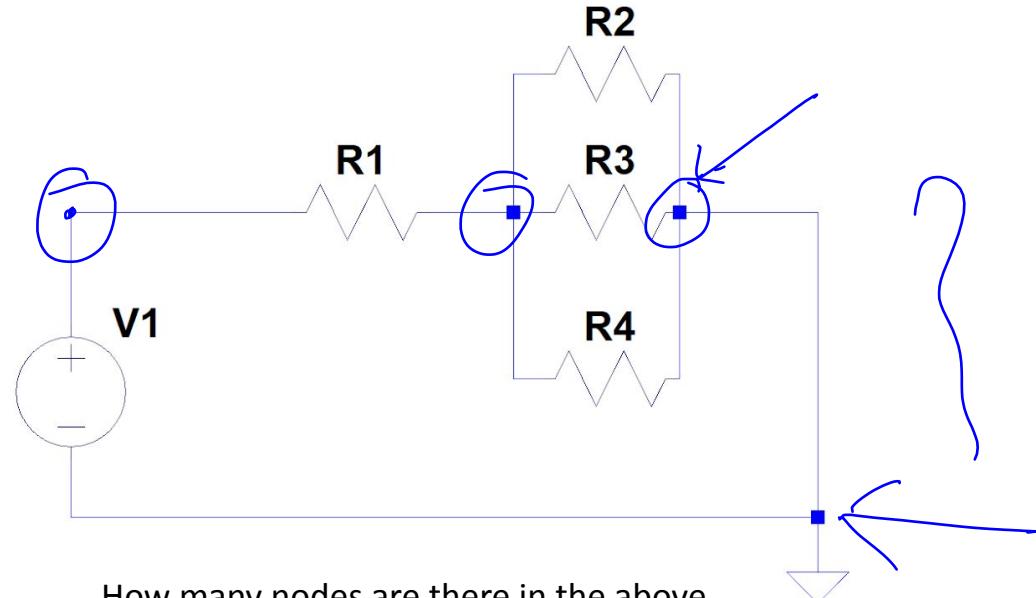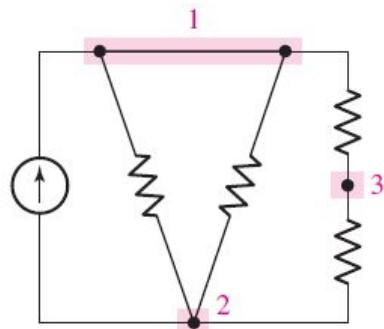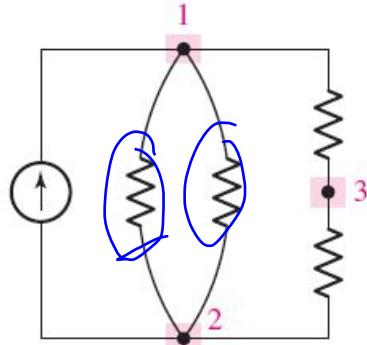

How many nodes are there in the above circuit?
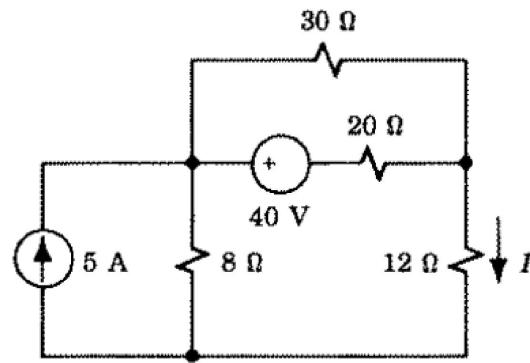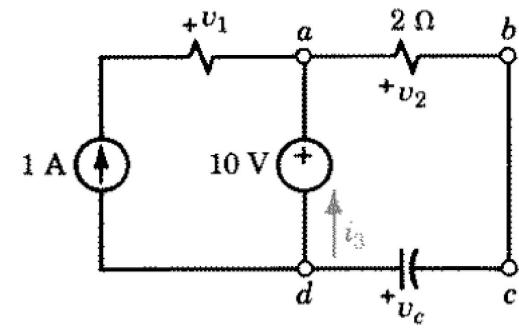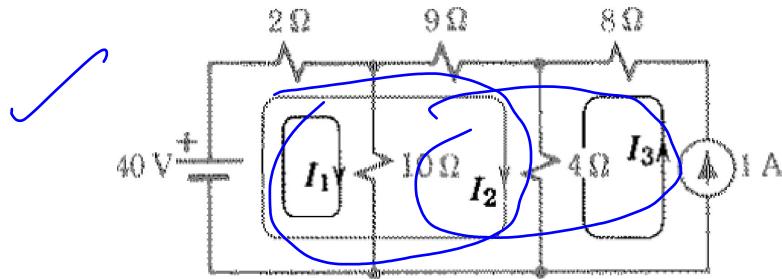
# Loops

- Loop: If a set of nodes and elements are traversed in such a way that no node is encountered more than once, then the set of nodes and elements are called a path. If the start and end point of a path is the same node, then it is called a loop.





# Kirchhoff's Laws

- Kirchhoff's Current Law (KCL):
- At any junction in an electric circuit the total current flowing towards that junction is equal to the total current flowing away from the junction, i.e.  $\sum I = 0$
- Thus current entering a node is equal to the current exiting the node
- For the given example

$$I_1 + I_2 = I_3 + I_4 + I_5 \text{ or}$$

$$I_1 + I_2 - I_3 - I_4 - I_5 = 0$$

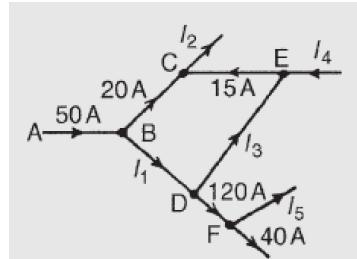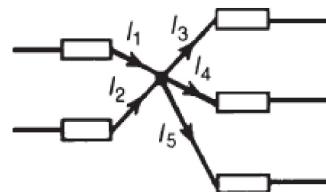

# Kirchhoff's Laws - Examples

Use Kirchhoff's laws to determine the currents flowing in each branch of the network shown in Figure 1.

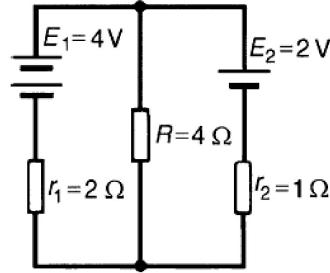


Fig. 1

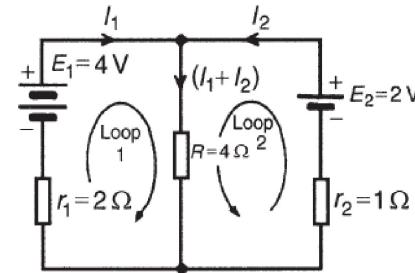


Fig. 2

**Procedure** Use Kirchhoff's current law and label current directions on the original circuit diagram. The directions chosen are arbitrary, but it is usual, as a starting point, to assume that current flows from the positive terminals of the batteries. This is shown in Figure 2, where the three branch currents are expressed in terms of  $I_1$  and  $I_2$  only, since the current through  $R$  is  $I_1 + I_2$ .

# Kirchhoff's Laws - Examples

- Divide the circuit into two loops and apply Kirchhoff's voltage law to each. From loop 1 of Figure 2, and moving in a clockwise direction as indicated (the direction chosen does not matter), gives

$$E_1 = I_1 r_1 + (I_1 + I_2)R, \text{ i.e. } 4 = 2I_1 + 4(I_1 + I_2)$$

$$\text{i.e. } 6I_1 + 4I_2 = 4 \quad (1)$$

- From loop 2 of Figure 2, and moving in an anticlockwise direction as indicated (once again, the choice of direction does not matter; it does not have to be in the same direction as that chosen for the first loop), gives:


$$E_2 = I_2 r_2 + (I_1 + I_2)R, \text{ i.e. } 2 = I_2 + 4(I_1 + I_2)$$

$$\text{i.e. } 4I_1 + 5I_2 = 2 \quad (2)$$

- From equ. 1 and 2, we get

$$I_1 = 0.867 \text{ A and } I_2 = -0.286 \text{ A and } I_1 + I_2 = 0.571 \text{ A}$$

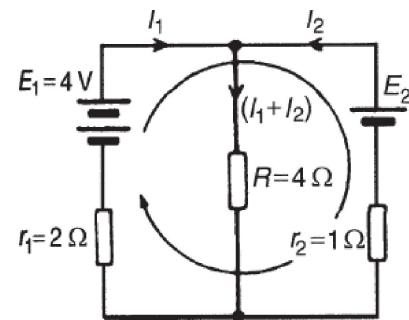- Note that a third loop is possible, as shown in Figure 3, giving a third equation which can be used as a check. How?



# Kirchhoff's Laws - Examples

For the bridge network shown in Figure 4 determine the currents in each of the resistors.

Let the current in the 2 resistor be  $i_1$ , then by Kirchhoff's current law, the current in the 14 resistor is  $(i - i_1)$ . Let the current in the 32 resistor be  $i_2$  as shown in Figure 5. Then the current in the 11 resistor is  $(i_1 - i_2)$  and that in the 3 resistor is  $(i - i_1 + i_2)$ . Applying Kirchhoff's voltage law to loop 1 and moving in a clockwise direction as shown in Figure 5 gives:

$$13 i_1 - 11 i_2 = 54 \quad (1)$$

Applying Kirchhoff's voltage law to loop 2 and moving in an anticlockwise direction as shown in Figure 5 gives:

$$16 i_1 + 32 i_2 = 112 \quad (2)$$

Using equ. (1) and (2), find all currents.


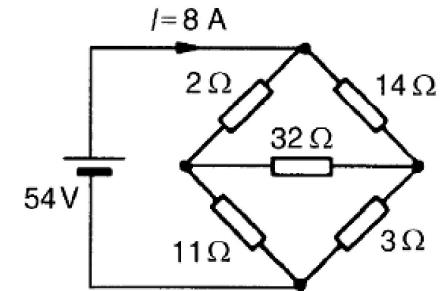


Fig.  
4

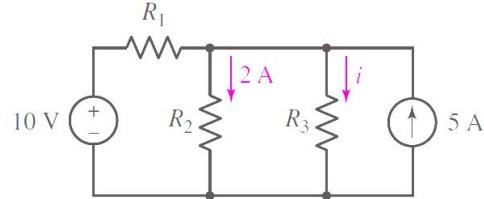
# Problems

---

For the circuit in the Fig, compute the current through resistor  $R_3$  if it is known that the voltage source supplies a current of 3 A.



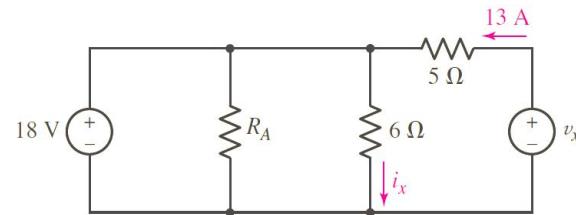
If  $i_x = 3$  A and the 18 V source delivers 8 A of current, what is the value of  $R_A$ ?


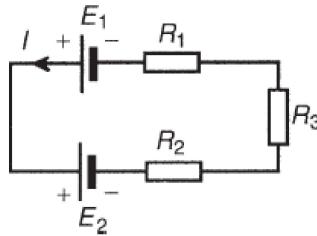
# Kirchhoff's Laws


Kirchhoff's Voltage Law (KVL):

In any closed loop in a network, the algebraic sum of the voltage drops (i.e. products of current and resistance) taken around the loop is equal to the resultant e.m.f. acting in that loop.



$$\text{Thus } E_1 - E_2 = IR_1 + IR_2 + IR_3$$

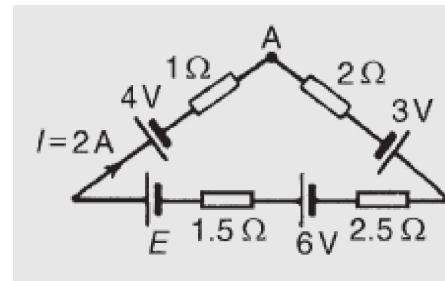
Determine the value of e.m.f.  $E$  in Figure



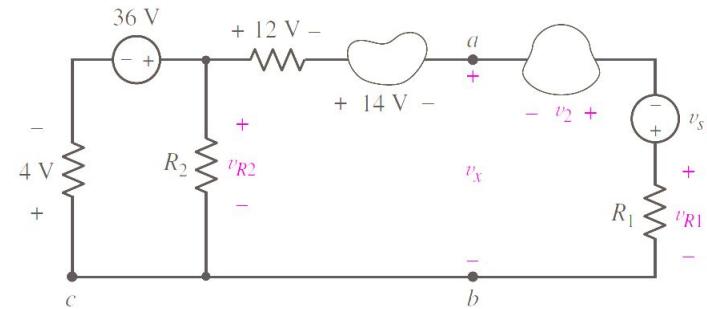
# Problems



Find  $v_{R2}$  (the voltage across R2) and the voltage labeled  $v_x$ .



Determine  $v_x$

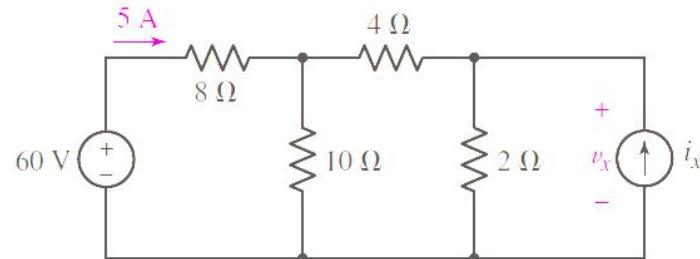

## Quick Recap

Resistance ( $R$ )      }  
Inductance ( $L$ )      }  
Capacitance ( $C$ )      }  
Passive Elements


Voltage source      }  
Current source      }  
Active Elements  
Independent source  
Dependent source  
Current-controlled  
Voltage controlled

$$R = \frac{Pd}{A}$$


Algebraic Sum ✓

KCL → }

KVL → }

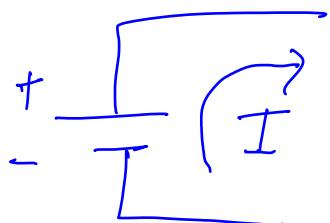


Power generated

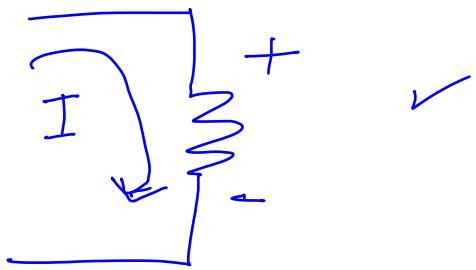

Power absorbed

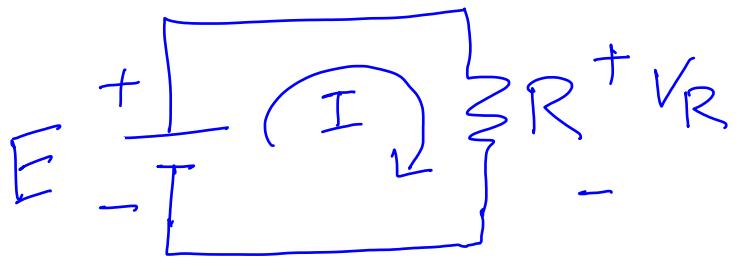KCL and KVL are also applicable to circuits having C and L.




$$E - V_R = 0 \Rightarrow E = V_R = IR$$

A circuit diagram consisting of a battery with EMF  $E$  and an open terminal pair with voltage  $V_R$  connected in series. A current  $I'$  flows counter-clockwise through the loop.

$$E + V_R = 0 \Rightarrow I' = -\frac{E}{R}$$

Initial choice of current direction  
can be arbitrary ...

$I = -I'$  (in the above example)

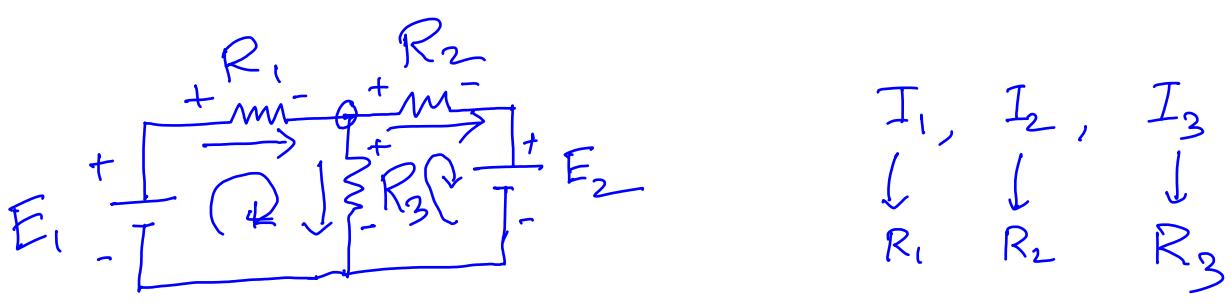

$$I_1 = I_2 + I_3 \quad \text{--- } ① \quad (\text{KCL})$$

$$E_1 = I_1 R_1 + I_3 R_3 \quad \text{--- } ② \quad (\text{KVL})$$

$$I_3 R_3 = I_2 R_2 + E_2 \quad \text{--- } ③ \quad (\text{KVL})$$

System of Linear Equations . . .

$$\underbrace{A \mathcal{X}}_{3 \times 3} = \underbrace{b}_{3 \times 1} \quad \checkmark \quad \mathcal{X} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}_{3 \times 1}$$

$$A = \begin{bmatrix} 1 & -1 & -1 \\ R_1 & 0 & R_3 \\ 0 & -R_2 & R_3 \end{bmatrix} \quad b = \begin{bmatrix} 0 \\ E_1 \\ E_2 \end{bmatrix}$$

check for  $\det(A) \neq 0$   
for unique sol.

$$\mathcal{X} = A^{-1} b$$

$$\left\{ \begin{array}{l} a_{11}x_1 + a_{12}x_2 = b_1 \\ a_{21}x_1 + a_{22}x_2 = b_2 \end{array} \right.$$

$\begin{bmatrix} C_1 & C_2 \end{bmatrix}$        $\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \end{bmatrix}$   
 $A$                    $x$                    $b$


infinitely many solutions

$$\frac{a_{11}}{a_{21}} = \frac{a_{12}}{a_{22}} \rightarrow \text{no solution (parallel lines)}$$

$$x_1 C_1 + x_2 C_2 = 0 \Rightarrow x_1 = 0 \text{ and } x_2 = 0$$

$C_1, C_2$  are linearly independent.

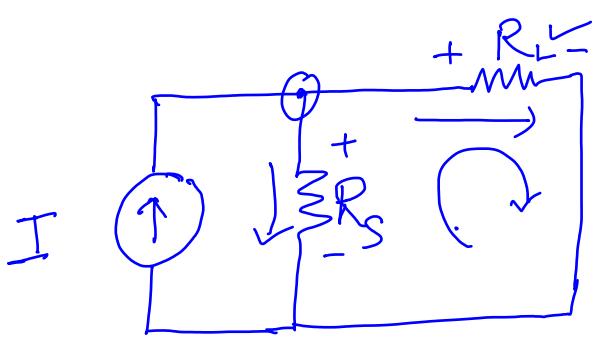Same concept can be extended  
to "n" equations. - .



$$I_S, I_L$$

$$I = I_S + I_L \quad (\text{KCL})$$

$$I_S R_S = I_L R_L \quad (\text{KVL})$$


$$I_L = \frac{R_S}{R_L} I_S$$

$$\check{A} = \begin{bmatrix} 1 & 1 \\ R_S & -R_L \end{bmatrix}$$

$$\check{b} = \begin{bmatrix} I \\ 0 \end{bmatrix}$$

$$\check{x} = \check{A}^{-1} \check{b}$$
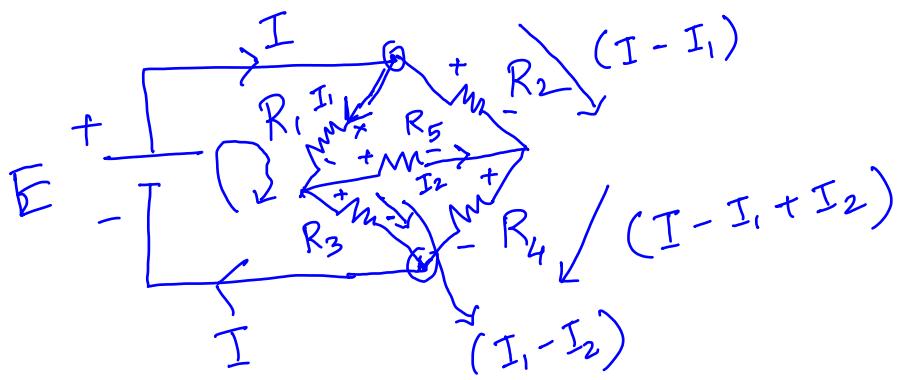
$$\check{x} = \begin{bmatrix} I_S \\ I_L \end{bmatrix}$$



$$A\chi = b$$

$$E = I_1 R_1 + (I_1 - I_2) R_3$$

$$I_1 R_1 + I_2 R_5 = (I - I_1) R_2 \quad \checkmark$$

$$I_2 R_5 + (I - I_1 + I_2) R_4 = (I_1 - I_2) R_3$$

$$\chi = \begin{bmatrix} I \\ I_1 \\ I_2 \end{bmatrix} \quad A \rightarrow 3 \times 3$$

$$b \rightarrow 3 \times 1$$

A circuit having "b" no. of branches

How many minimum no. variables you need to compute "b" branch voltages and "b" branch currents?


b no. of unknowns!

Let's use the following notations throughout - .

$b$  = no. of branches / elements

$n$  = no. of nodes

(in a circuit)

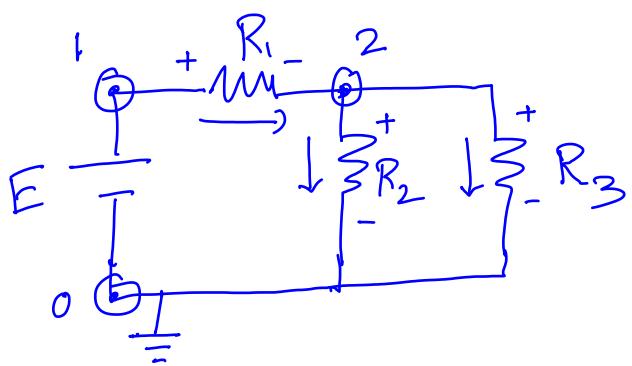


$$n = 3$$

$$b = 4$$

$$V_1 \text{ and } V_2 =$$

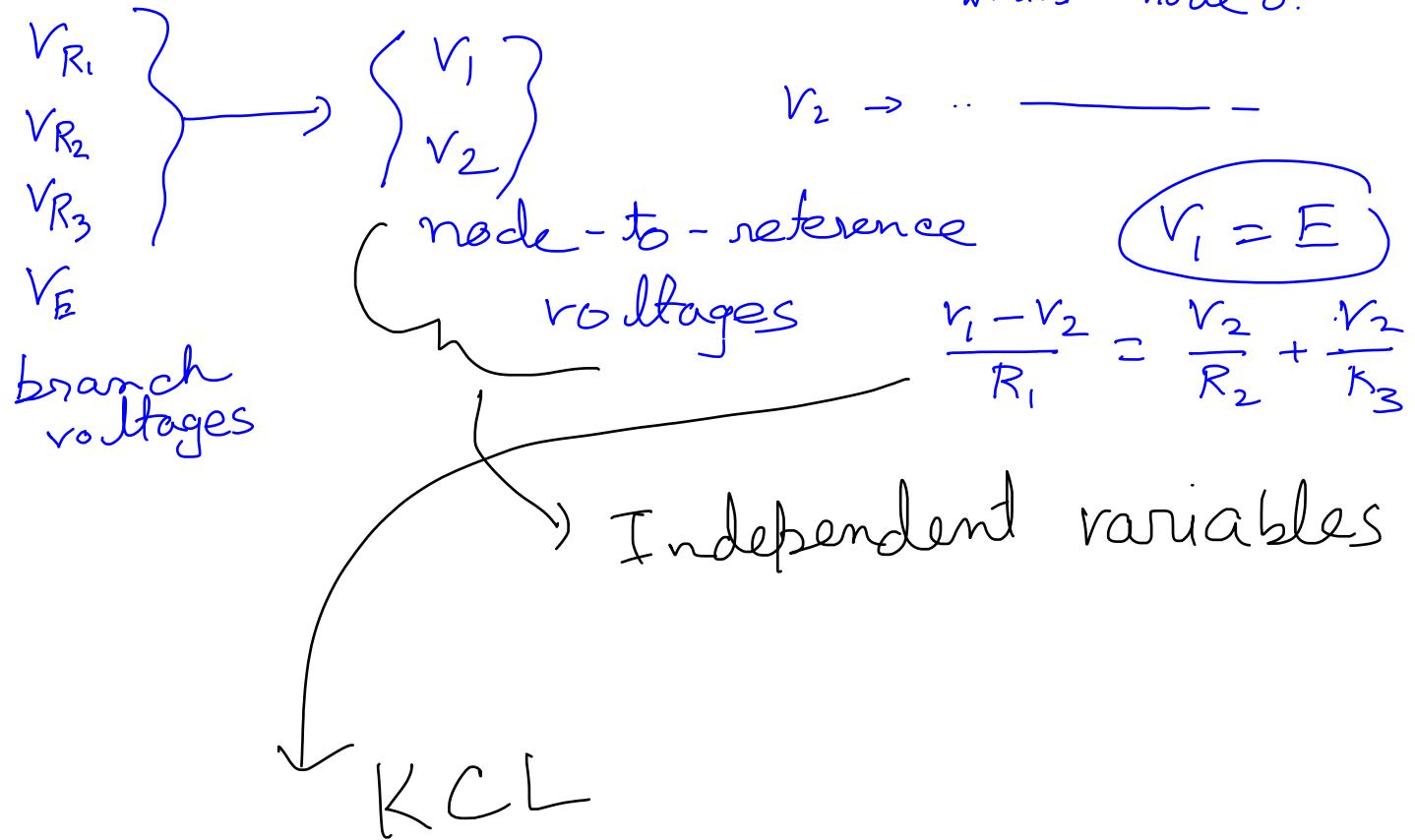$V_1 \rightarrow$  voltage of node 1  
w.r.t node 0.



Here, node "0" is considered as reference node.

(n - 1) voltage variables to solve for  
a linear circuit problem -

(node-to-reference voltages)  
(datum)










## Node Variable Analysis

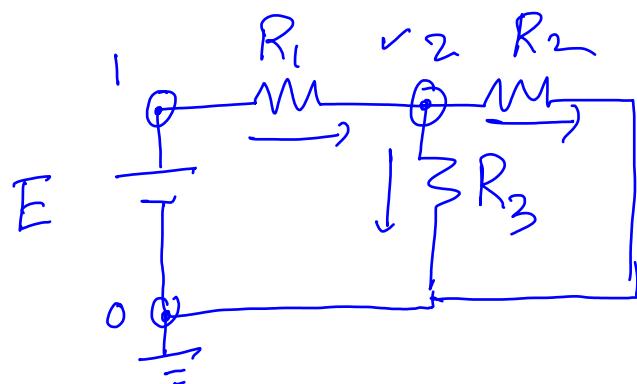


$$\begin{aligned} b &= 4 \\ n &= 3 \\ \underline{(n-1)} &= \end{aligned} \quad \left. \right\}$$

$V_1, V_2$

$$\frac{V_1 - V_2}{R_1} = \frac{V_2}{R_3} + \frac{V_2}{R_2}$$

$$V_1 = E$$

Solve for  $V_2$

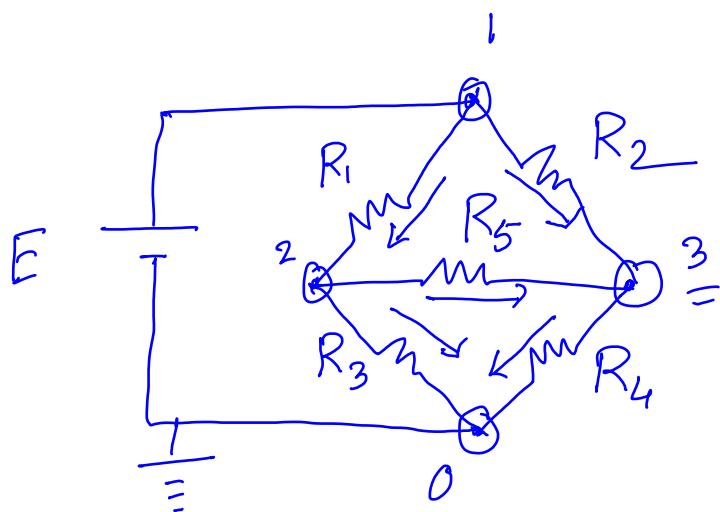

$$b = 6$$

$$n =$$

$V_1, V_2, V_3$

$$V_1 = E$$


KCL at node 2,

$$\frac{V_1 - V_2}{R_1} = \frac{V_2 - V_3}{R_5} + \frac{V_2}{R_3}$$

KCL at node 3,

$$\frac{V_1 - V_3}{R_2} + \frac{V_2 - V_3}{R_5} = \frac{V_3}{R_4}$$


} Solve  
for  $V_2$   
and  $V_3$

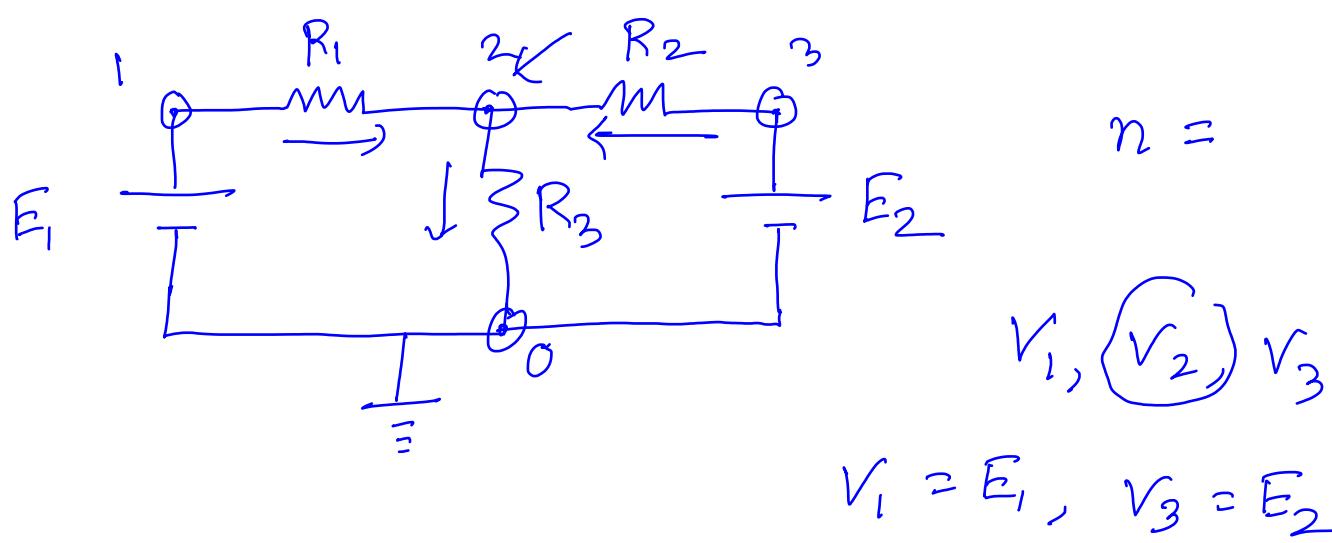

$$\frac{V_1 - V_2}{R_1} + \frac{V_3 - V_2}{R_2} = \frac{V_2}{R_3}$$

## Loop Variable Analysis

To topological description of a circuit

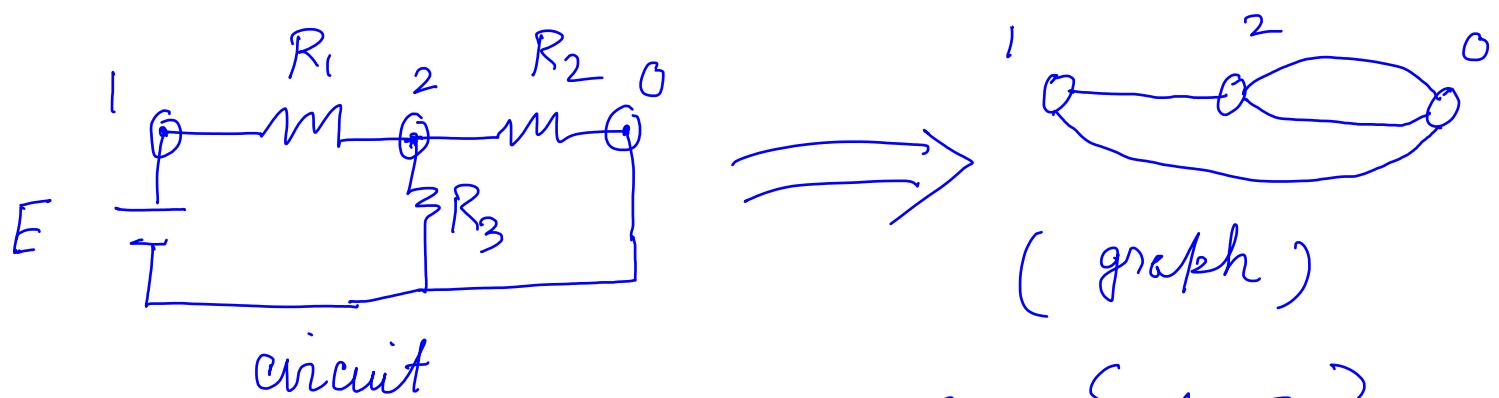

$$V = \{0, 1, 2\}$$


$$E = \{\{1, 2\}, \dots\}$$

$G_2 = \{V, E\}$   
 set of nodes (vertices)  
 set of edges (links/branches)

From a graph, if we remove few edges, we can create a sub-graph.

Tree is a special type of Graph, which has the following properties.

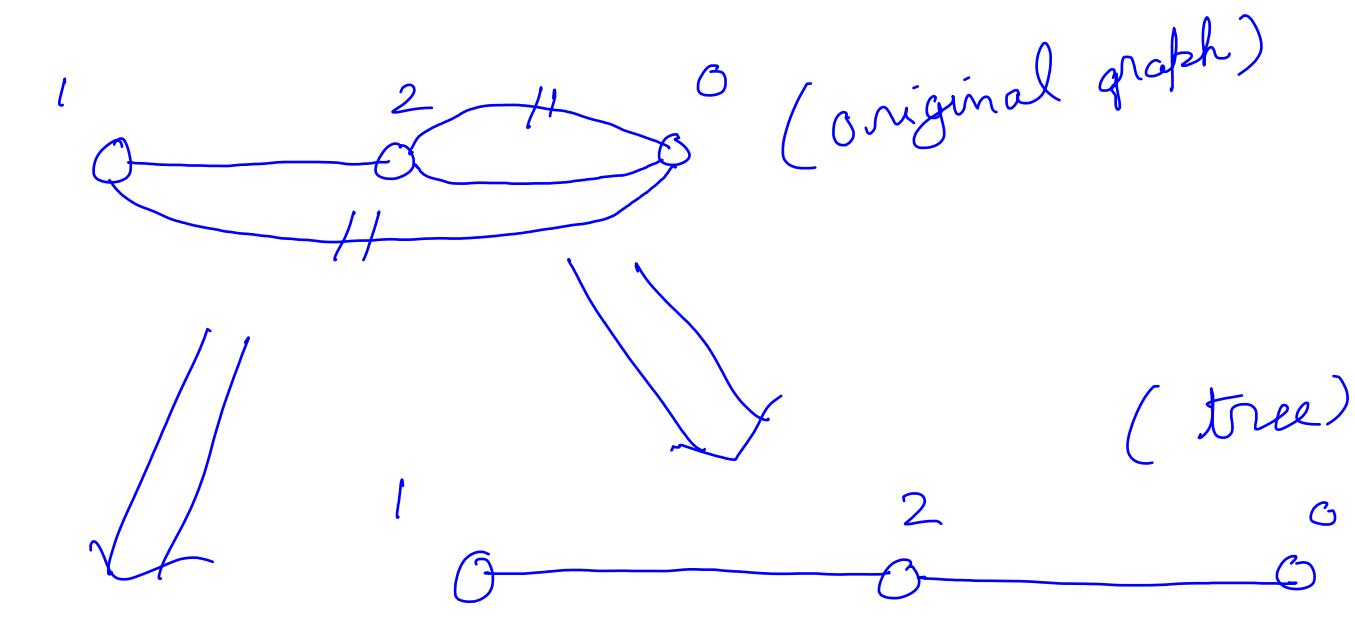- 1> There are no closed-paths (loops)
- 2> It has exactly  $(n-1)$  links/edges
- 3> No node is kept isolated.




Chords = branches that you remove from the graph to construct a tree.


no. of chords = no. of branches in the original graph - no. of branches in the tree

$$= b - (n - 1)$$

$$= b - n + 1 \quad \checkmark$$

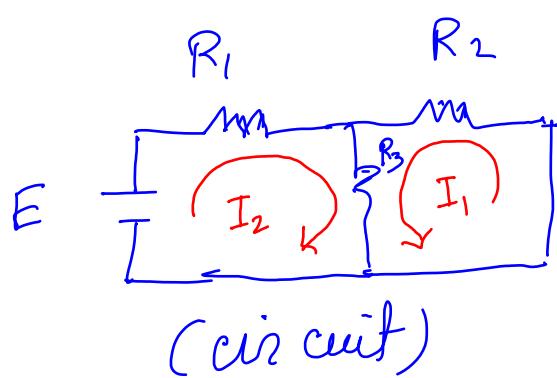


(circuit)

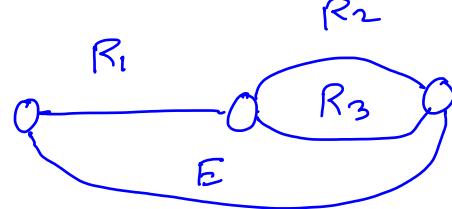



(graph)

$(E, R_2) \rightarrow$  chords

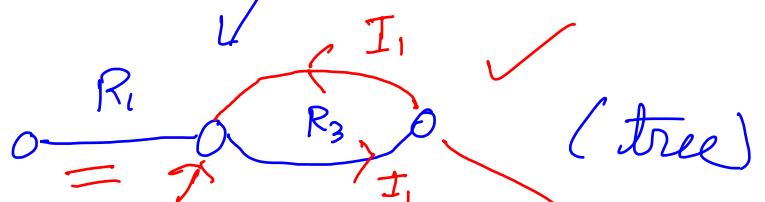

(tree)

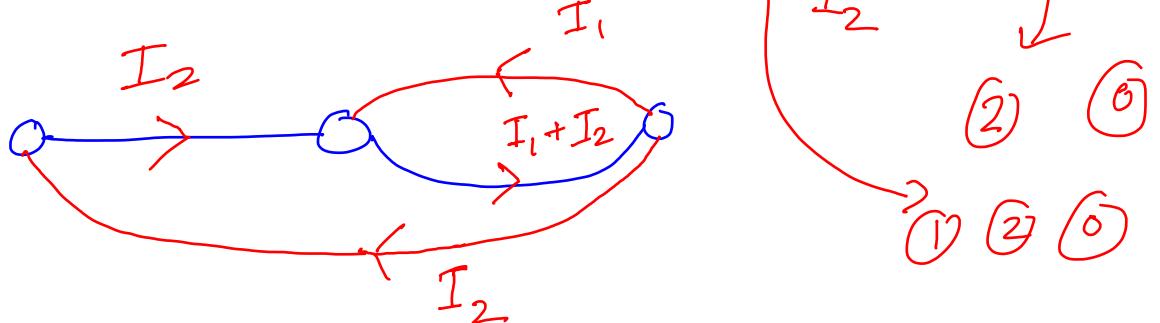

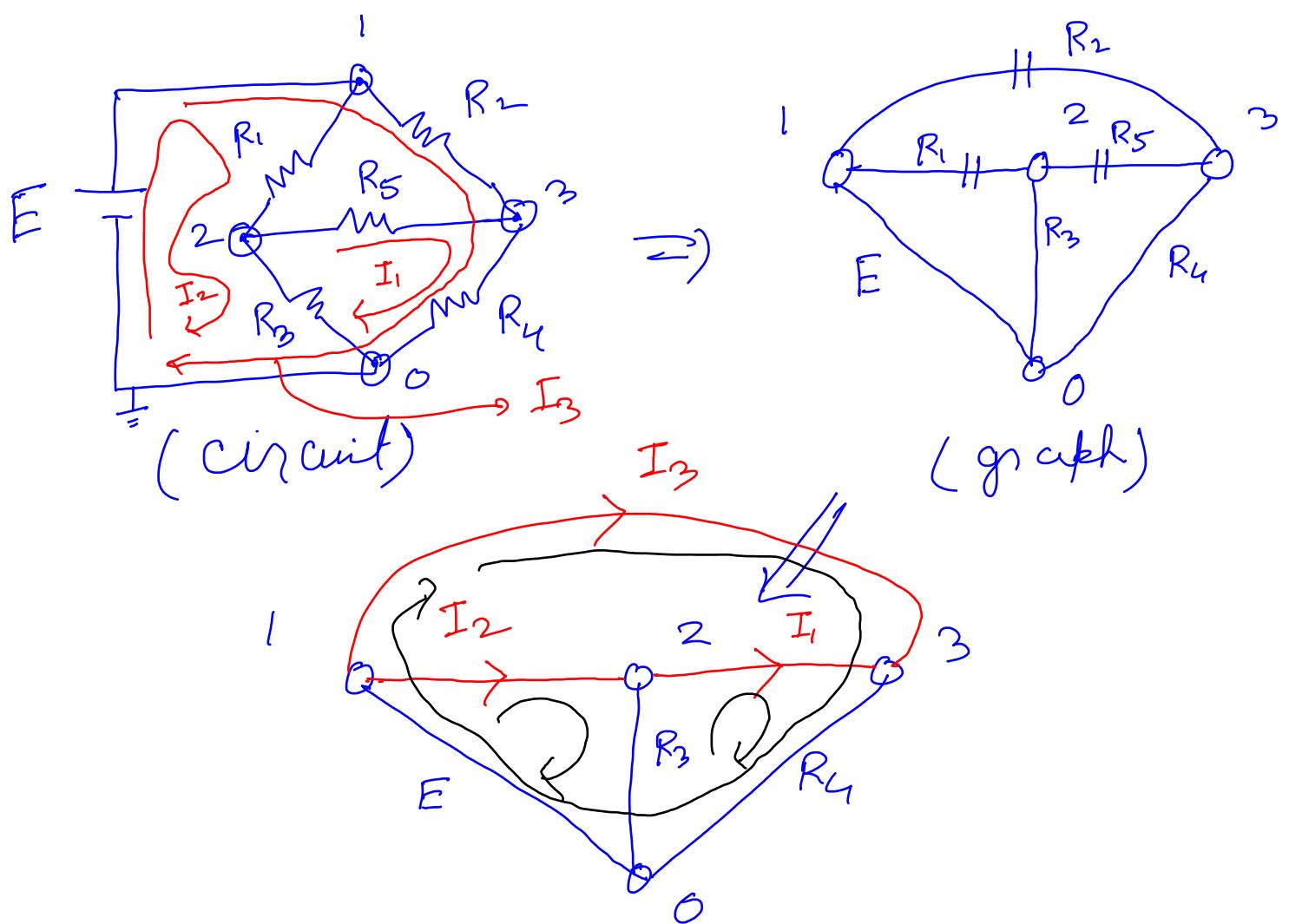

$$I_1 R_5 + (I_1 + I_3) R_4 + (I_1 - I_2) R_3 = 0$$

$$I_2 R_1 + (I_2 - I_1) R_3 = E$$

$$I_3 R_2 + (I_1 + I_3) R_4 = E$$






















### Quick Recap

" $b$ " → no. of branches }  
 "n" → no. of nodes }


$(n-1)$  variables to do node analysis }

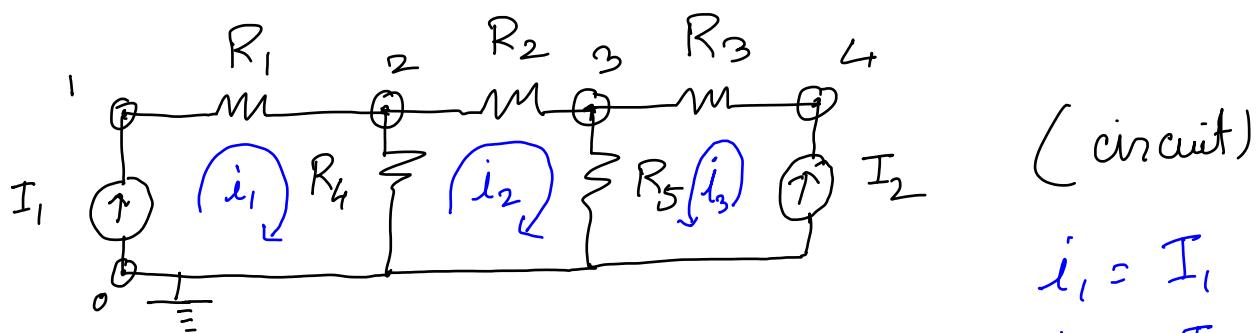$(b-n+1)$  variables to do loop analysis }  
 =





$$i_1 = I_1$$

$$i_2 = I_2$$

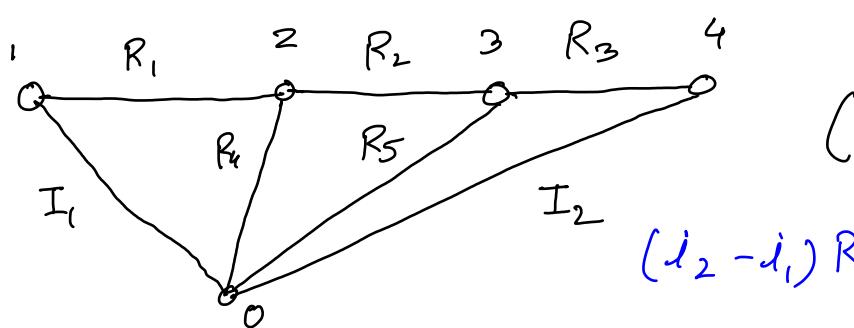
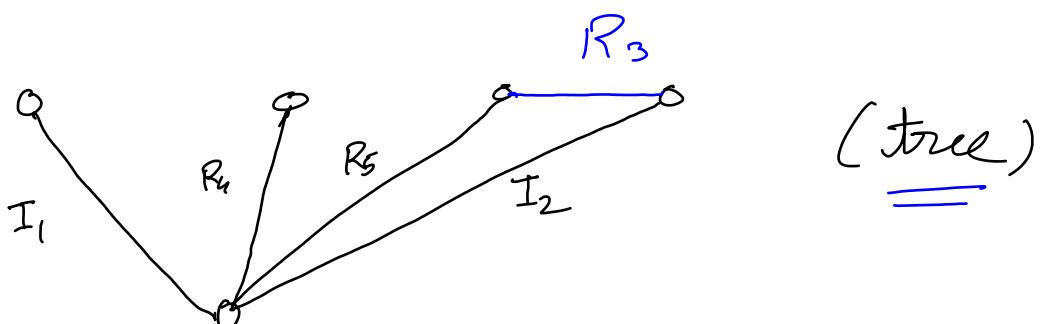
$$(i_2 - i_1)R_4 + i_2 R_2 + (i_2 + i_3)R_5 = 0$$




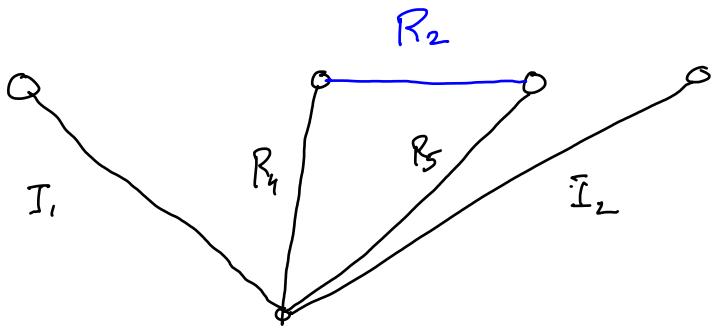


Mesh  $\rightarrow$  a loop which does not contain any other loops.

Loops  $\rightarrow$  6

Meshes  $\rightarrow$  3

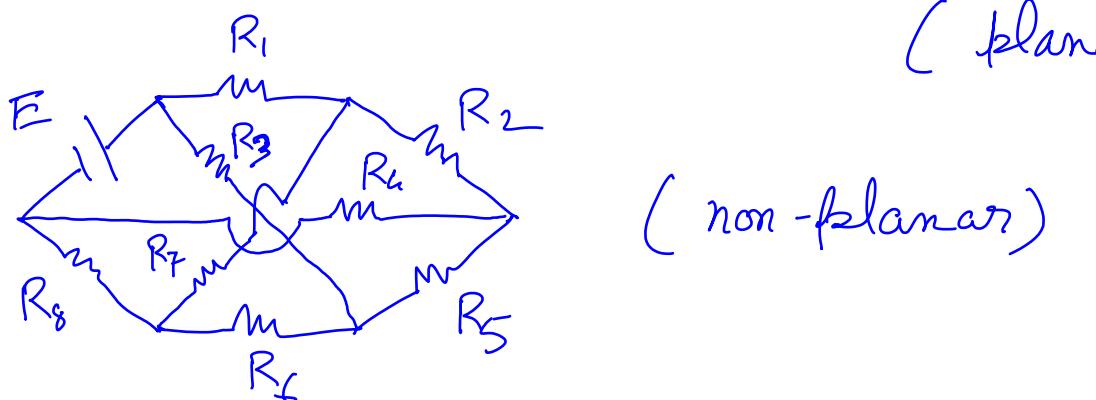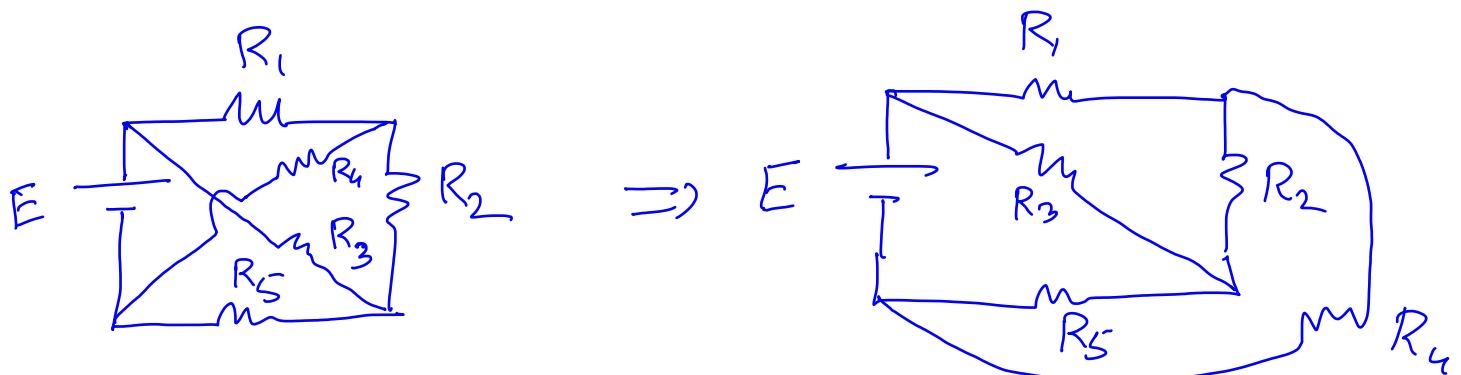
For planar circuits, use Mesh currents as independent variables - -



(planar)

(non-planar)

## Node Analysis

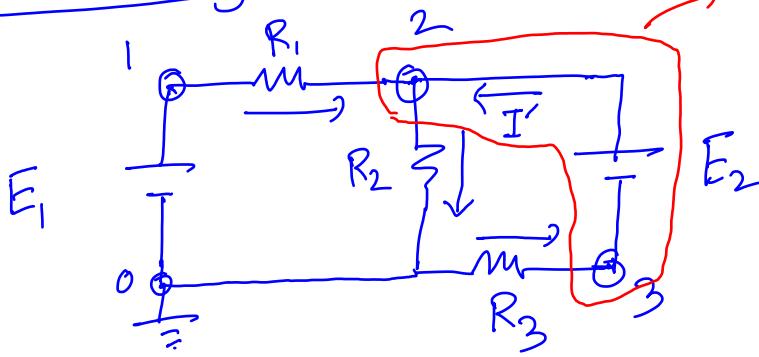

Super node

$$V_1, V_2, V_3$$

$$V_1 = E_1$$

$$V_2 - V_3 = E_2$$

$$\frac{V_1 - V_2}{R_1} + I' = \frac{V_2}{R_2}$$


Combine

$$-\frac{V_3}{R_3} = I'$$

$$\frac{V_1 - V_2}{R_1} - \frac{V_3}{R_3} = \frac{V_2}{R_2}$$

{ sol. using  
super-node }

## Mesh Analysis

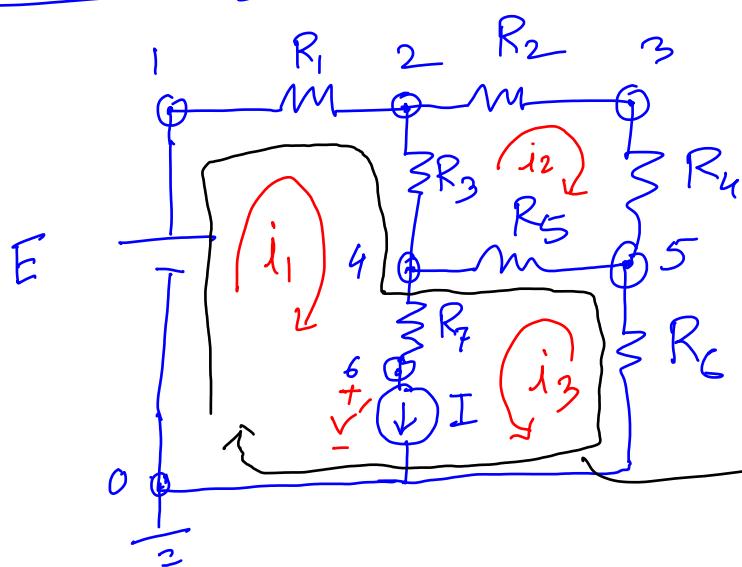

$$b = 9$$

$$n = 7$$

$$b - n + 1 = 3$$

(Super Mesh)

KVL will lead to eq. (5).

KVL at Mesh 1,

$$E = i_1 R_1 + (i_1 - i_2) R_3 + (i_1 + i_2) R_7 + V' \quad \text{--- (1)}$$

$$(i_2 - i_1) R_3 + i_2 R_2 + i_2 R_4 + (i_2 + i_3) R_5 = 0 \quad \text{--- (2)}$$

$$(i_3 + i_1) R_7 + V' + i_3 R_6 + (i_3 + i_2) R_5 = 0 \quad \longrightarrow \textcircled{3}$$

Adding  $\textcircled{1}$  and  $\textcircled{3}$ ,

$$E + i_3 R_6 + (i_3 + i_2) R_5 = i_1 R_1 + (i_1 - i_2) R_3 \quad \longrightarrow \textcircled{5}$$

$$i_1 + i_3 = I \quad \longrightarrow \textcircled{4}$$

Use  $\textcircled{2}$ ,  $\textcircled{4}$  and  $\textcircled{5}$  to solve for  $i_1$ ,  $i_2$  and  $i_3$ .

















## Quick Recap

R, L, C (v-I characteristics)


source  $\begin{cases} \text{voltage source} \\ \text{current source} \end{cases}$

KCL (conservation of charge) ✓

KVL (conservation of energy) ✓

Node variable analysis }  
Loop " " } mesh  
(planar circuit)

## Circuits with dependent sources

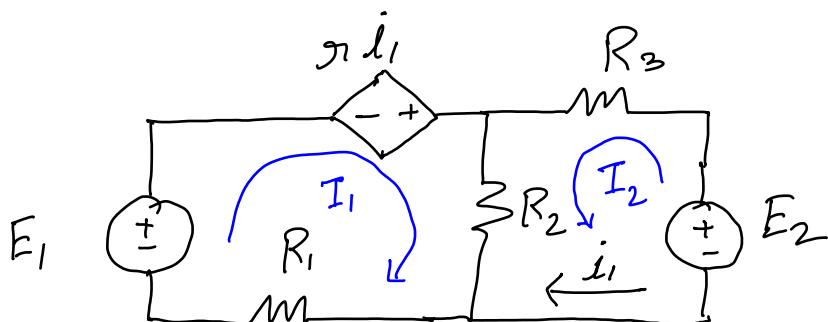

Mesh Analysis

$$\text{KVL for Mesh 1, } i_1 = -I_2$$

$$E_1 + g_1 i_1 - (I_1 + I_2) R_2 - I_1 R_1 = 0$$


$$\text{KVL for Mesh 2,}$$

$$E_2 - I_2 R_3 - (I_1 + I_2) R_2 = 0$$

$$A \mathbf{x} = \mathbf{b}$$

$$\mathbf{x} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$
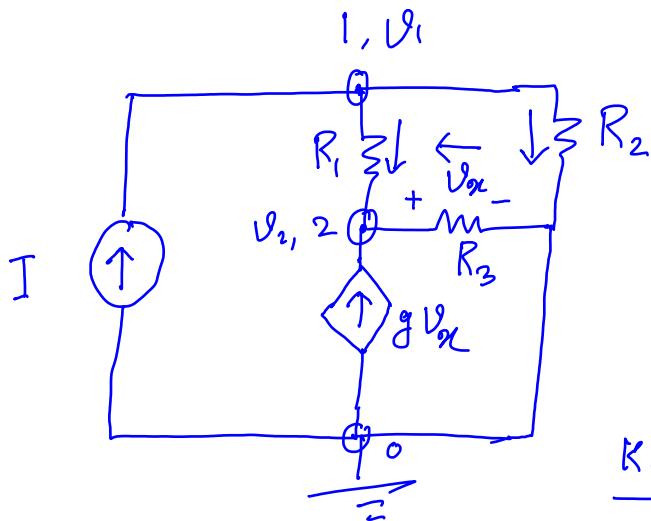
$$A = \begin{bmatrix} -R_1 - R_2 & -R_1 - R_2 \\ -R_2 & -R_2 - R_3 \end{bmatrix} \quad b = \begin{bmatrix} -E_1 \\ -E_2 \end{bmatrix}$$



(Node Analysis)

KCL at node 1,


$$I = \frac{V_1 - V_2}{R_1} + \frac{V_1}{R_2}$$

KCL at node 2,

$$\frac{V_1 - V_2}{R_1} - \frac{V_2}{R_3} + gV_x = 0$$

$$V_x = V_2$$

Non-planar Circuit

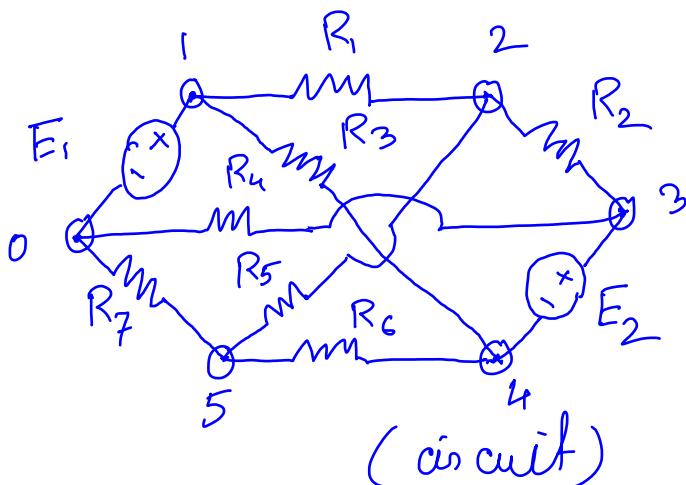


$$n = 6$$






$$b = 9$$

$$\text{no. of chords} = b - n + 1$$

$$= 9 - 6 + 1$$

$$= 4$$

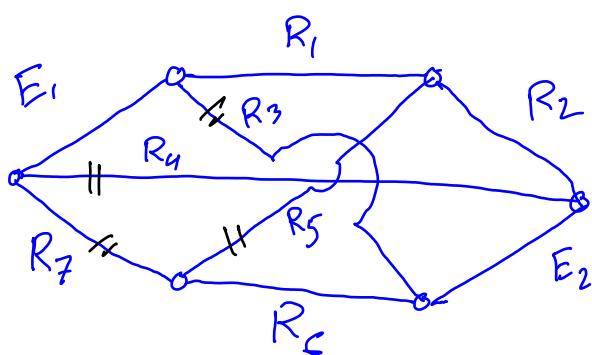

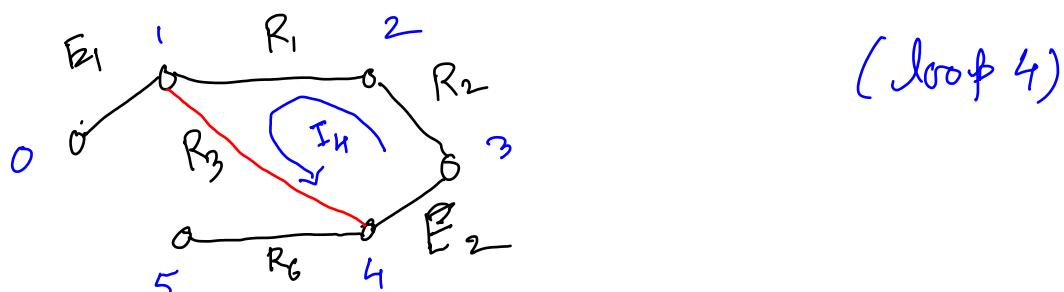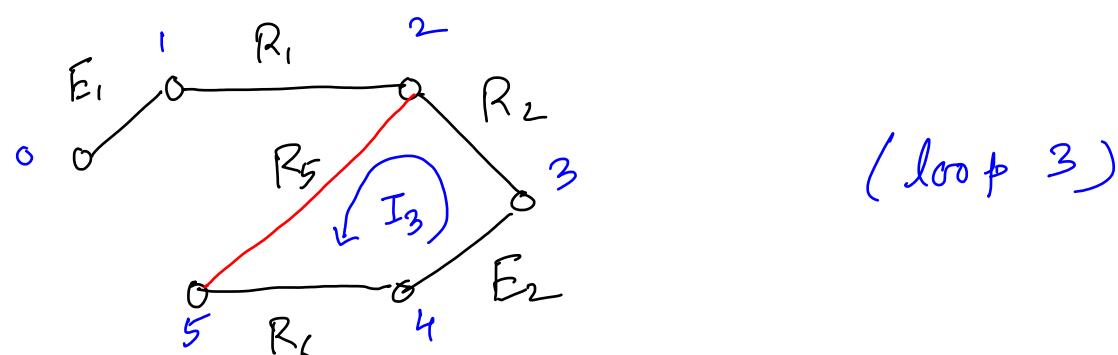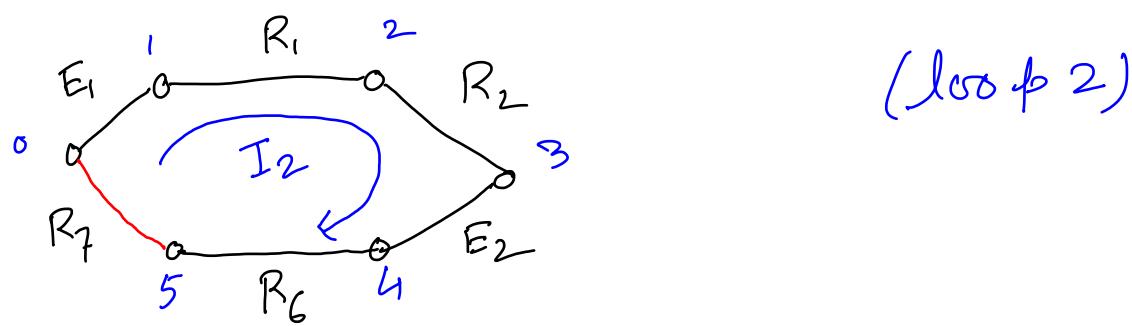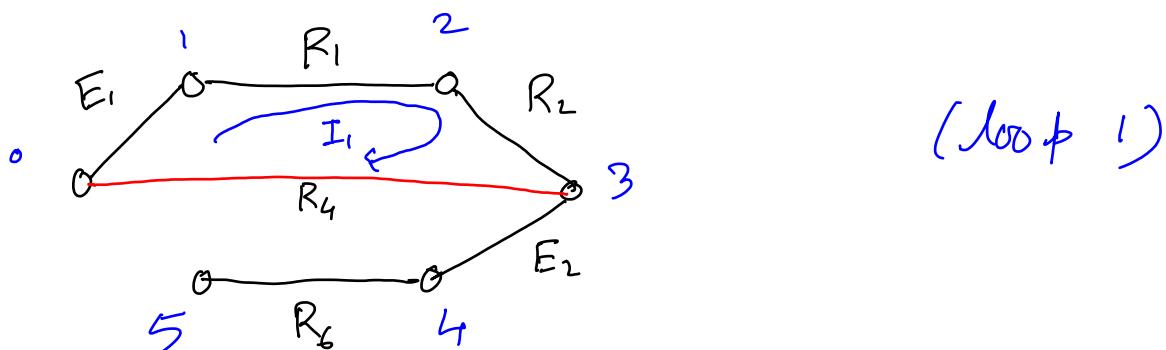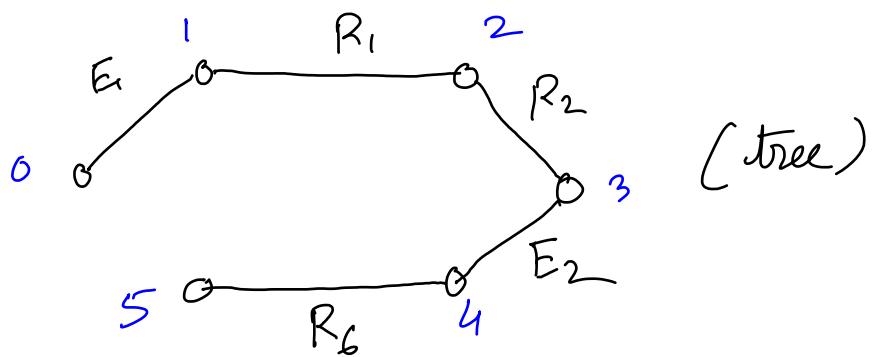

branch

Magnitude

Direction

$R_1$

$(I_1 + I_2 - I_4)$

① → ②

$R_2$ 

$$(I_1 + I_2 - I_3 - I_4)$$

$$\textcircled{2} \rightarrow \textcircled{3}$$

 $E_2$ 

$$(I_3 + I_4 - I_2)$$

$$\textcircled{4} \rightarrow \textcircled{3}$$

 $R_6$ 

$$(I_2 - I_3)$$

$$\textcircled{4} \rightarrow \textcircled{5}$$

 $E_1$ 

$$(I_1 + I_2)$$


$$\textcircled{0} \rightarrow \textcircled{1}$$

KVL for loop 1,

$$E_1 = (I_1 + I_2 - I_4) R_1 + (I_1 + I_2 - I_3 - I_4) R_2 \\ + I_1 R_4$$

KVL for loop 2,
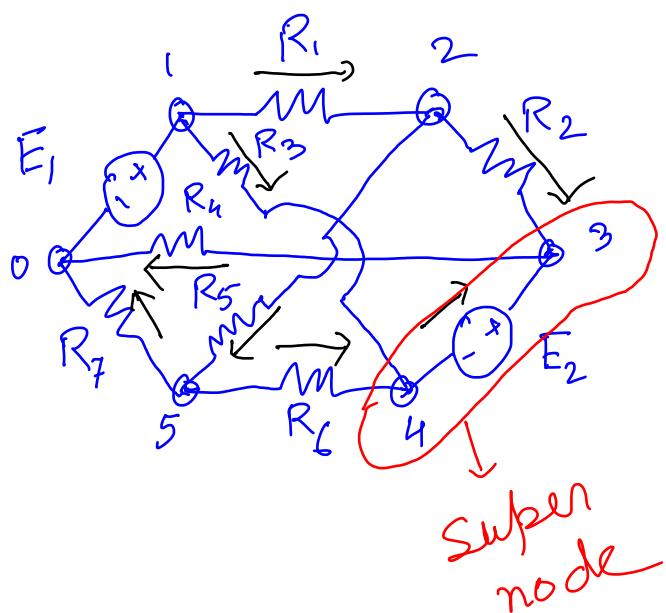
$$E_1 = (I_1 + I_2 - I_4) R_1 + (I_1 + I_2 - I_3 - I_4) R_2 + E_2 \\ + (I_2 - I_3) R_6 + I_2 R_7$$



(Node Analysis)

$$V_1 = E_1$$

KCL at node 2,

$$\frac{V_1 - V_2}{R_1} = \frac{V_2 - V_3}{R_2} + \frac{V_2 - V_5}{R_5}$$

KCL at node 5,

$$\frac{V_2 - V_5}{R_S} = \frac{V_5}{R_7} + \frac{V_5 - V_4}{R_L}$$

KCL at super node,

$$\frac{V_5 - V_4}{R_6} + \frac{V_1 - V_4}{R_3} + \frac{V_2 - V_3}{R_2} = \frac{V_3}{R_4}$$

$$V_3 - V_4 = E_2$$











### Quick Recap


Node Analysis (using node-to-reference voltages)

Mesh Analysis (Mesh currents)

$(n-1)$

$(b-n+1)$

Super node

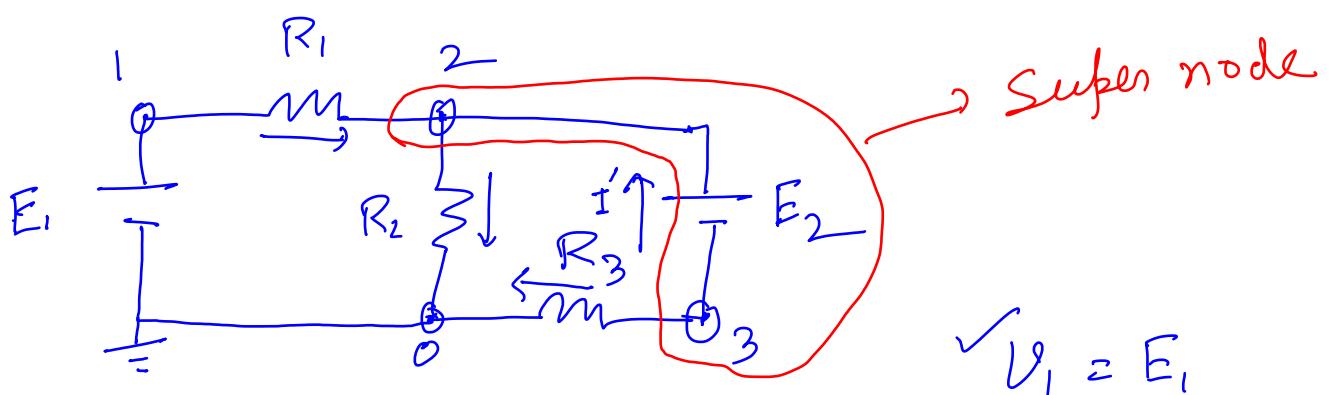


$$\frac{V_1 - V_2}{R_1} + I' = \frac{V_2}{R_2} \quad (\text{KCL at node 2})$$

$$0 = \frac{V_3}{R_3} + I' \quad (\text{KCL at node 3})$$

$$\checkmark V_2 - V_3 = E_2$$

$$\Rightarrow \checkmark \frac{V_1 - V_2}{R_1} - \frac{V_3}{R_3} = \frac{V_2}{R_2} \quad (\text{KCL at Super node})$$

## Super Mesh

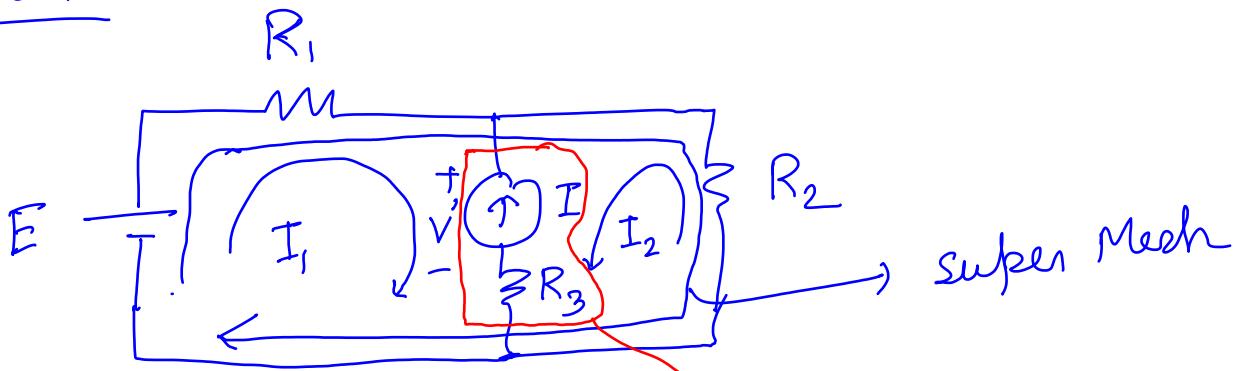

KVL for loop 1,

$$E = I_1 R_1 + V' + (I_1 + I_2) R_3$$


KVL for loop 2,

$$0 = I_2 R_2 + V' + (I_1 + I_2) R_3$$


$$E = I_1 R_1 - I_2 R_2 \rightarrow (\text{KVL for Super Mesh})$$

$$I = -I_1 - I_2$$



## Series Resistances

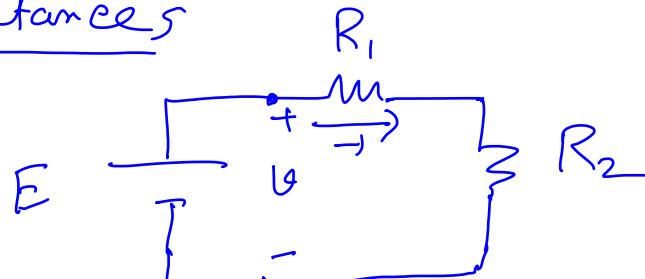








$$R_{\text{eq}} = R_1 + R_2$$

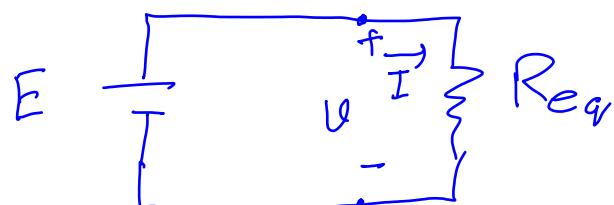


## Parallel Resistances

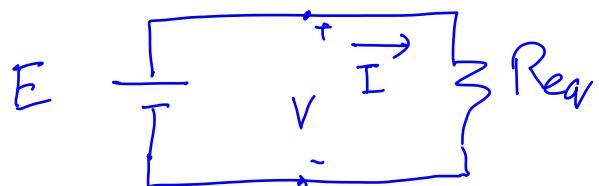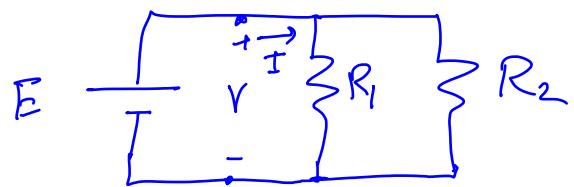
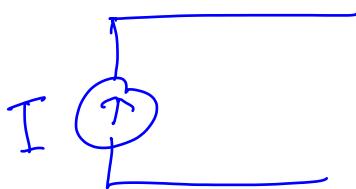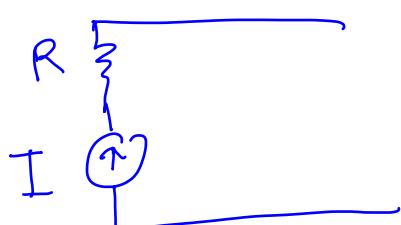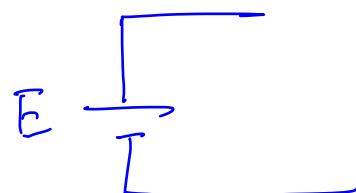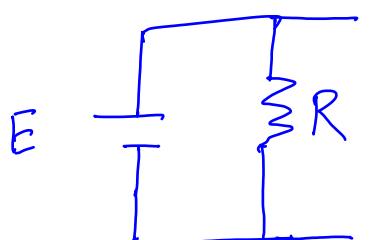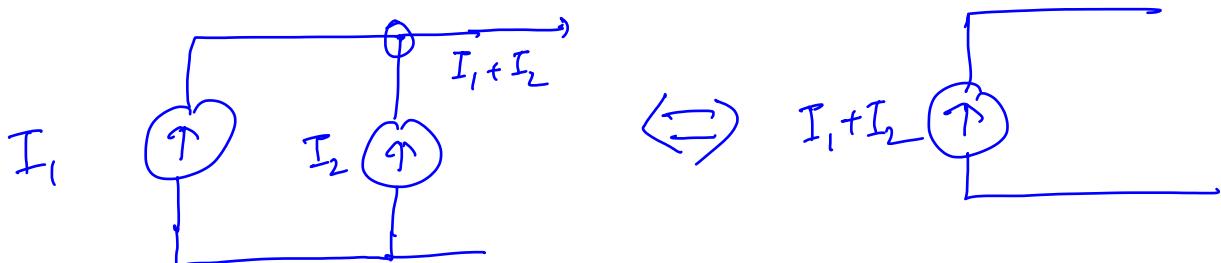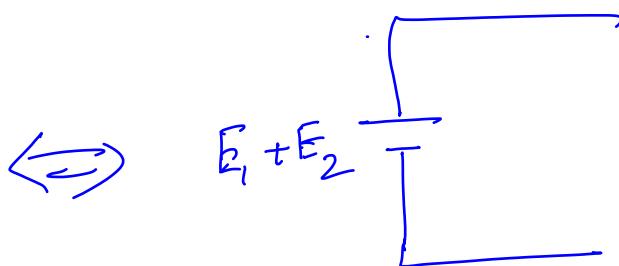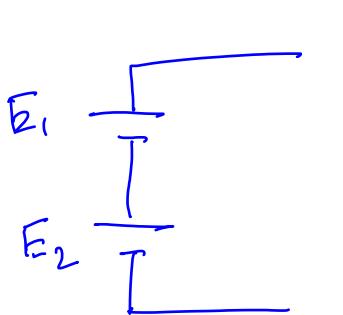
$$\frac{1}{Reav} = \frac{1}{R_1} + \frac{1}{R_2}$$




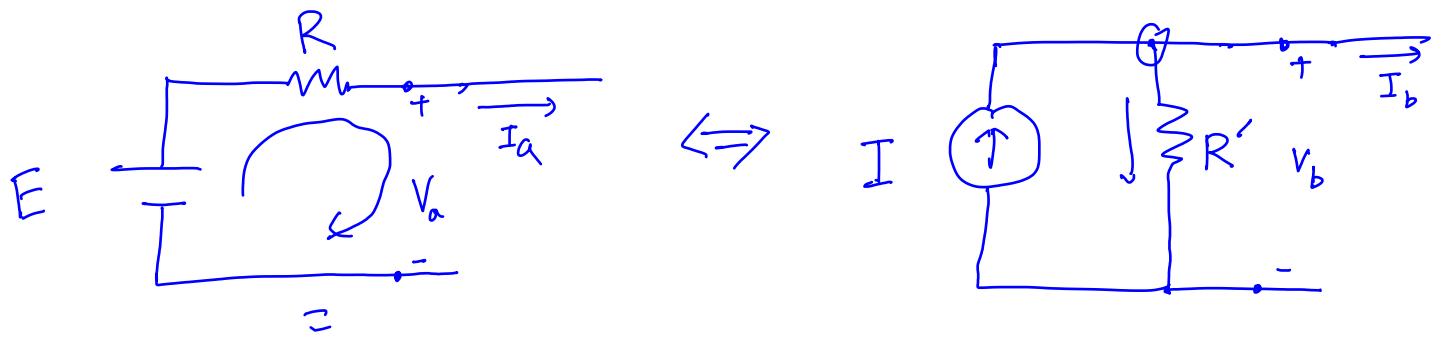


$$E = I_a R + V_a$$

$$I = \frac{V_b}{R'} + I_b$$

For equivalence  $I_a = I_b$  and  $V_a = V_b$

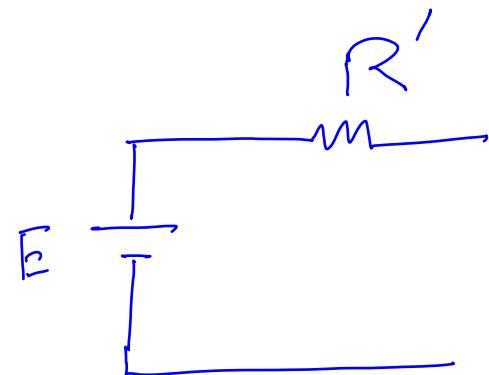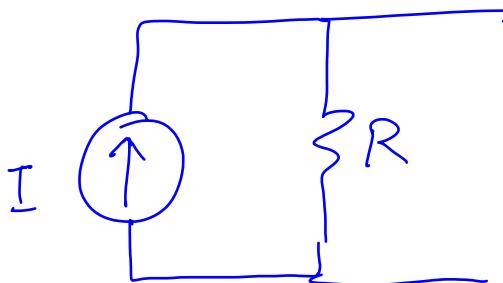
$$\left. \begin{array}{l} I = \frac{E}{R} \\ R' = R \end{array} \right\}$$



$$R' = R$$


Super Position Principle

$$E = IR$$

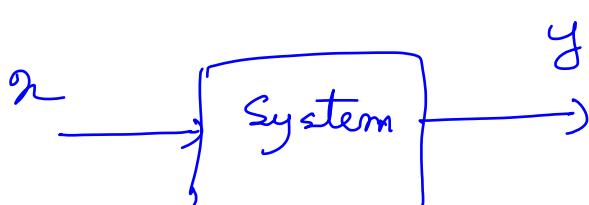

$$\left. \begin{array}{l} x_1 \rightarrow y_1 \\ x_2 \rightarrow y_2 \end{array} \right\} \Rightarrow \alpha_1 x_1 + \alpha_2 x_2 \rightarrow \alpha_1 y_1 + \alpha_2 y_2$$

The system is linear

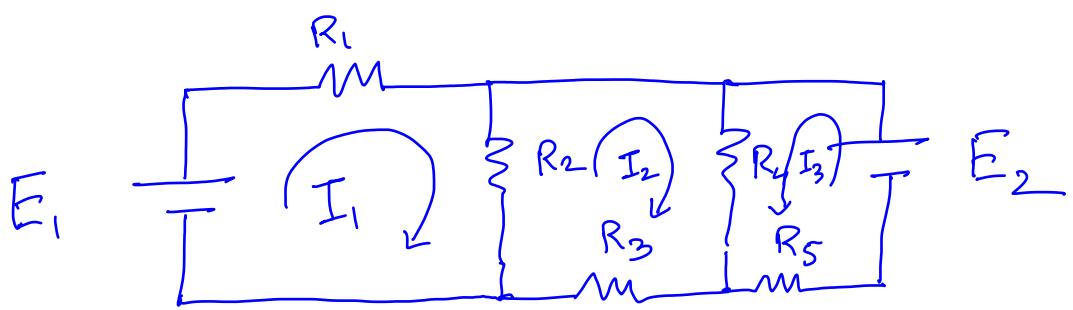

$$E_1 = I_1 R_1 + (I_1 - I_2) R_2$$

$$0 = -(I_1 - I_2) R_2 + (I_2 + I_3) R_4 + I_2 R_3$$

$$E_2 = (I_2 + I_3) R_4 + I_3 R_5$$

$$A \chi = b, \quad A \in \mathbb{R}^{3 \times 3}$$

$$\chi = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}, \quad b \in \mathbb{R}^{3 \times 1}$$

$$A = \begin{bmatrix} R_1 + R_2 & -R_2 & 0 \\ -R_2 & R_2 + R_3 + R_4 & R_4 \\ 0 & R_4 & R_4 + R_5 \end{bmatrix}, \quad b = \begin{bmatrix} E_1 \\ 0 \\ E_2 \end{bmatrix}$$

$$b = \begin{bmatrix} E_1 \\ 0 \\ E_2 \end{bmatrix} = \underbrace{\begin{bmatrix} E_1 \\ 0 \\ 0 \end{bmatrix}}_{b_1} + \underbrace{\begin{bmatrix} 0 \\ 0 \\ E_2 \end{bmatrix}}_{b_2}$$

$$A \chi = b = b_1 + b_2$$

$$x \in A^T b_1 + A^T b_2$$

$\underbrace{x_1}_{\text{contribution from } E_1}$        $\underbrace{x_2}_{\text{contribution from } E_2}$

} superposition holds

$$A x = b$$

there are "p" no. of independent sources.

$$b = \sum_{i=1}^p b_p$$

Example

$$b = \begin{bmatrix} E_1 - E_2 \\ 0 \\ E_3 \end{bmatrix} = \underbrace{\begin{bmatrix} E_1 \\ 0 \\ 0 \end{bmatrix}}_{b_1} - \underbrace{\begin{bmatrix} E_2 \\ 0 \\ 0 \end{bmatrix}}_{b_2} + \underbrace{\begin{bmatrix} 0 \\ 0 \\ E_3 \end{bmatrix}}_{b_3}$$

Superposition Theorem


Each branch current or voltage can be decomposed into contributions from individual independent current or voltage sources.





### Quick Recap

Superposition Theorem  $\rightarrow$

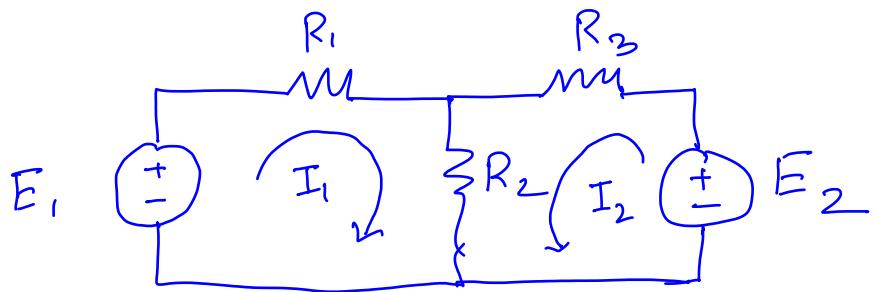

$$E_1 = I_1 R_1 + (I_1 + I_2) R_2$$

$$E_2 = I_2 R_3 + (I_1 + I_2) R_2$$

$$A \mathbf{x} = \mathbf{b}$$

$$A = \begin{bmatrix} R_1 + R_2 & R_2 \\ R_2 & R_2 + R_3 \end{bmatrix}$$


$$\mathbf{x} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\mathbf{b} = \begin{bmatrix} E_1 \\ E_2 \end{bmatrix}$$


$$\mathbf{b} = \begin{bmatrix} E_1 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ E_2 \end{bmatrix}$$

$$A \mathbf{x} = \mathbf{b} = \mathbf{b}_1 + \mathbf{b}_2$$
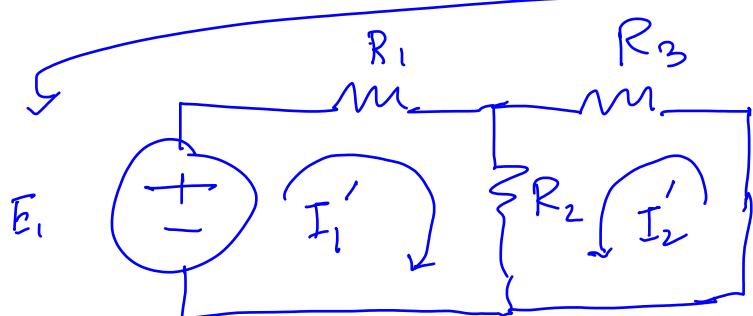
$$\mathbf{x} = \underbrace{\mathbf{A}^{-1} \mathbf{b}_1}_{\mathbf{x}_1} + \underbrace{\mathbf{A}^{-1} \mathbf{b}_2}_{\mathbf{x}_2}$$



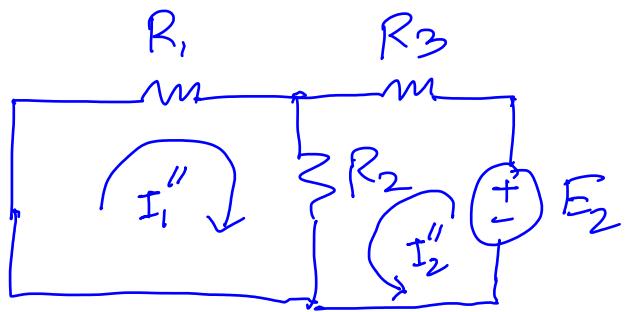
$$\mathbf{x}_1 = \begin{bmatrix} I_1' \\ I_2' \end{bmatrix}$$




$$x_2 = \begin{bmatrix} I_1'' \\ I_2'' \end{bmatrix}$$

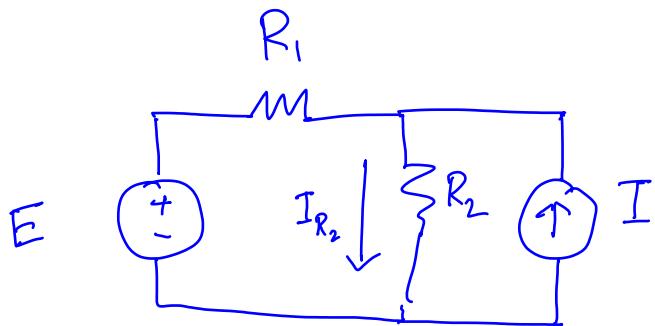
$$\left. \begin{array}{l} I_1 = I_1' + I_1'' \\ I_2 = I_2' + I_2'' \end{array} \right\}$$



$$I_{R_2} = ?$$

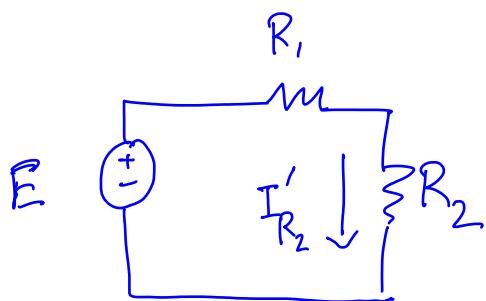

$$I_{R_2}' = \frac{E}{R_1 + R_2}$$

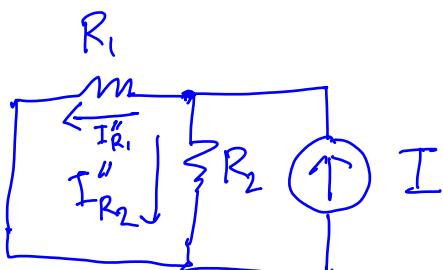

$$\left. \begin{array}{l} I = I_{R_1}'' + I_{R_2}'' \\ I_{R_1}'' \cdot R_1 = I_{R_2}'' \cdot R_2 \end{array} \right\}$$




*Total current*  $\rightarrow$  *Current due to E*  $\rightarrow$  *Current due to I*

$$I_{R_2} = I_{R_2}' + I_{R_2}''$$

$$= \frac{E}{R_1 + R_2} + \frac{R_1 I}{R_1 + R_2}$$

$$I_{R_2}'' + \frac{R_2}{R_1} I_{R_2}'' = I$$
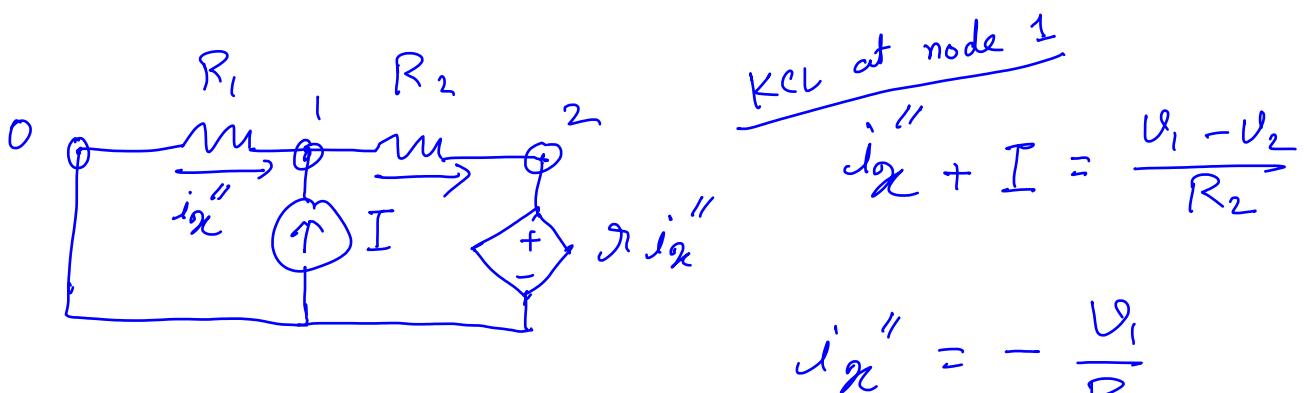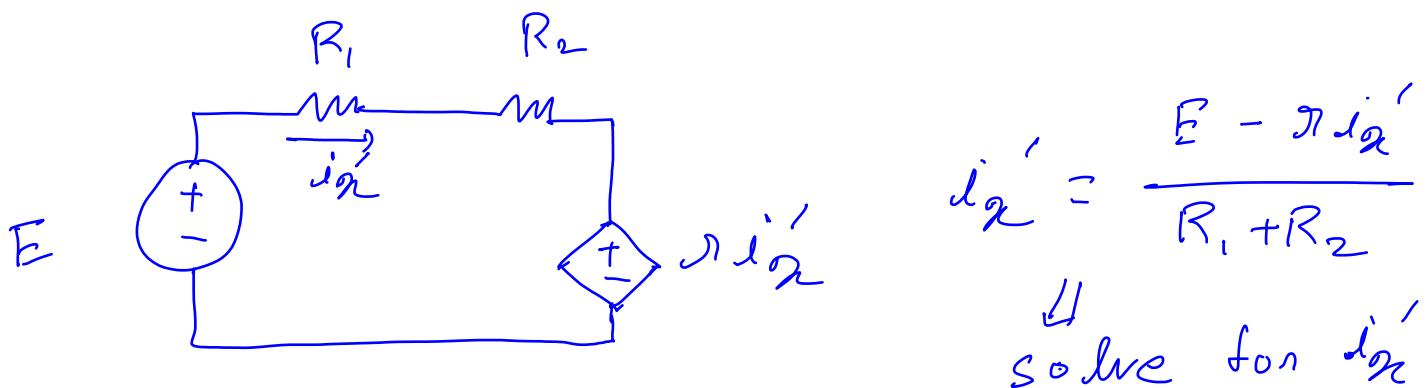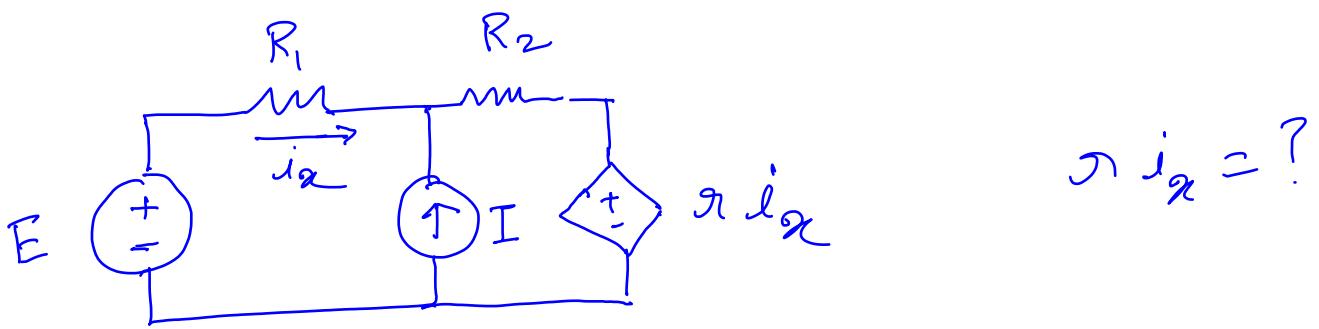
$$\Rightarrow I_{R_2}'' = \frac{R_1 I}{R_1 + R_2}$$



$$i_x'' = -\frac{V_1}{R_1}$$


To total current      Current due to  $E$       Current due to  $I$

$i_x = i_x' + i_x''$


$$V_2 = g_r i_x''$$

Solve for  $i_x''$


## Thevenin's Theorem / Norton's Theorem

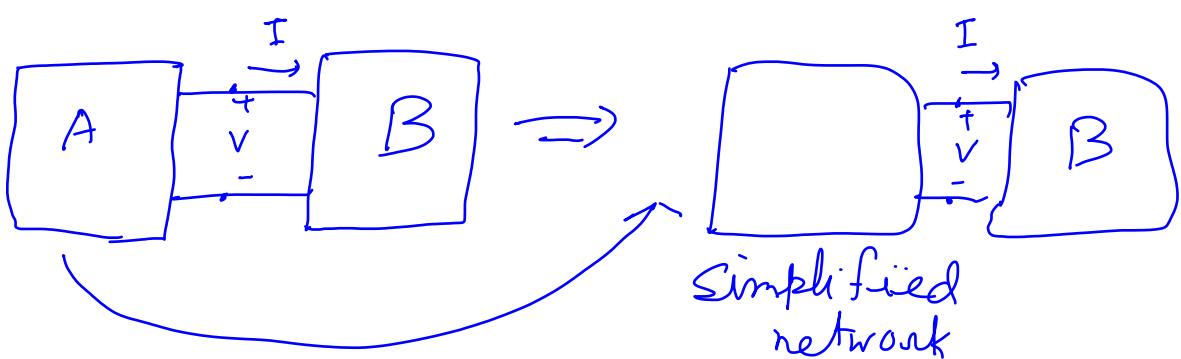

Thevenin Equivalent of Network A

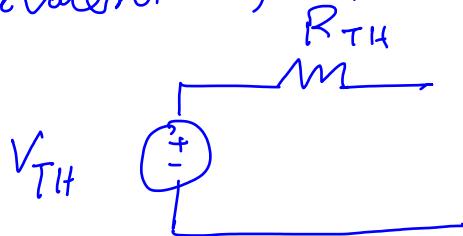

Norton Equivalent of Network A

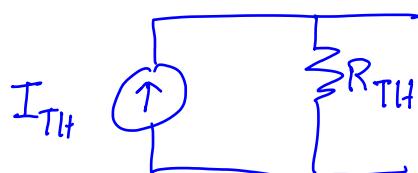

$$V_{TH} = I_{TH} \cdot R_{TH}$$


### Properties of Network A

- 1) It should be a linear network.
- 2) Voltage sources or current sources can be present.
- 3) There should be no controlled-source coupling with network B.

### Properties of Network B

- 1) It can be linear or non-linear.
- 2) There should not be any coupling via controlled sources with network A.


### How to Compute $V_{TH}$

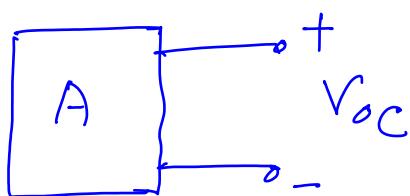

Remove network B and compute  $V_{OC}$

$$V_{TH} = V_{OC}$$


## How to Compute $I_{TH}$

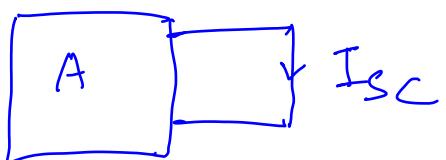


Remove network B, short-circuit the terminal and compute  $I_{sc}$

$$I_{TH} = I_{sc}$$


## How to compute $R_{TH}$

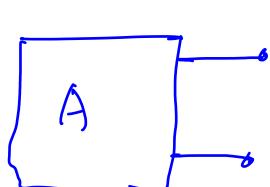

Remove all the independent sources

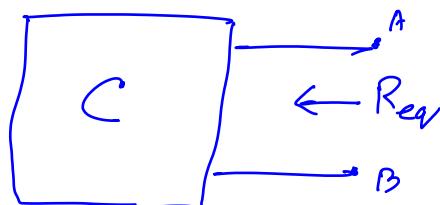

$$R_{TH} = R_{eq}$$

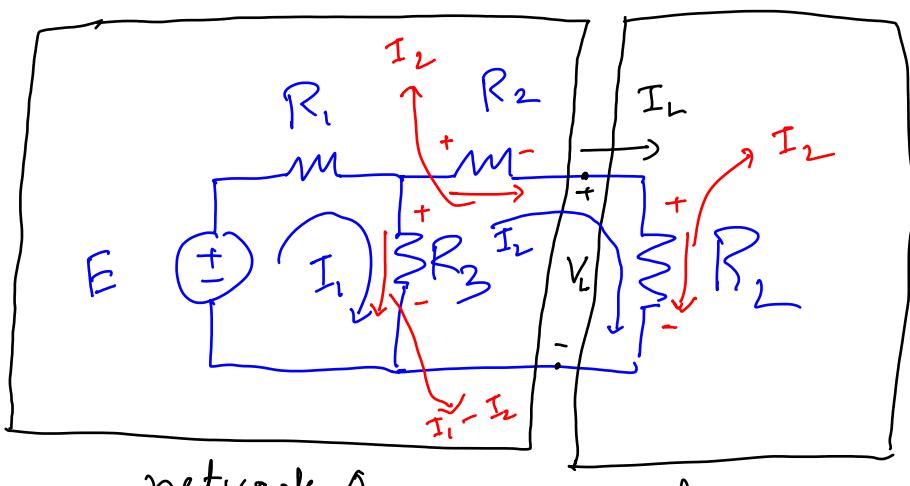


network A

$$E = I_1 R_1 + (I_1 - I_2) R_3$$

$$(I_1 - I_2) R_3 = I_2 (R_2 + R_L)$$

$$I_L = I_2$$

$$I_1 R_3 = I_2 (R_3 + R_2 + R_L)$$

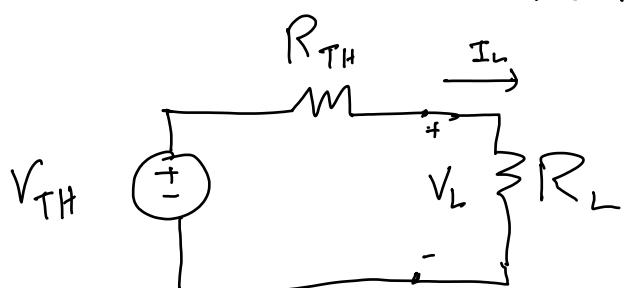

$$E = I_1 (R_1 + R_3) - I_2 R_3$$


$$= \frac{R_1 + R_3}{R_3} \cdot (R_3 + R_2 + R_1) \cdot I_2$$

$$- I_2 R_3$$


$$I_2 \left( \frac{(R_1 + R_3)(R_3 + R_2 + R_L)}{R_3} - R_3 \right) = E$$

$$I_L = I_2 = \frac{E \cdot R_3}{R_1 R_3 + R_1 R_2 + R_1 R_L + R_3 R_2 + R_3 R_L}$$

Thevenin Equivalent Circuit,

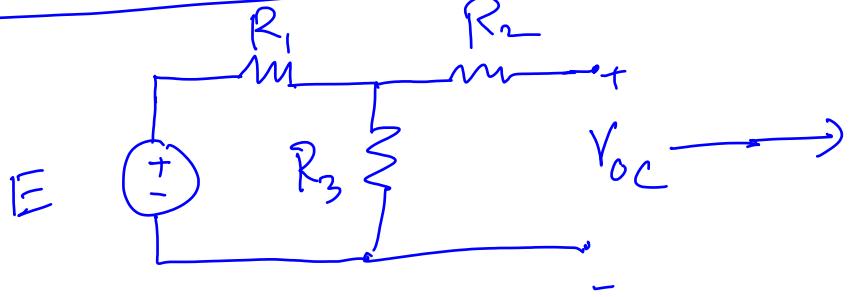


= net work A

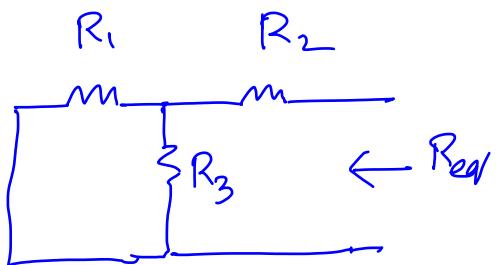

$$R_{TH} = R_2 + \frac{R_1 R_3}{R_1 + R_3}$$
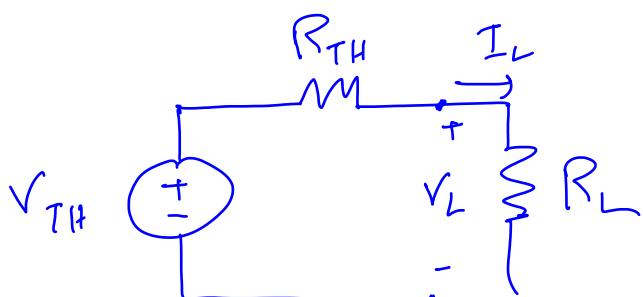
$$V_{TH} = V_{oc} = \frac{R_3 E}{R_1 + R_3} \quad \checkmark$$



$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$\frac{E R_3}{R_1 + R_3}$$



$$= \frac{\frac{E R_3}{R_1 + R_3}}{R_2 + \frac{R_1 R_3}{R_1 + R_3} + R_L}$$

$$= \frac{E R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3 + R_1 R_L + R_3 R_L}$$






## Norton Equivalence

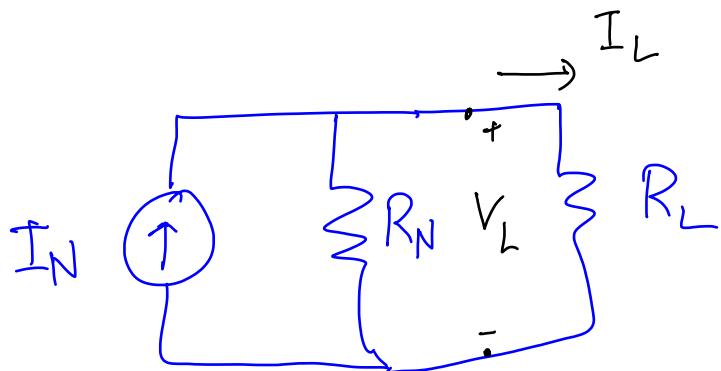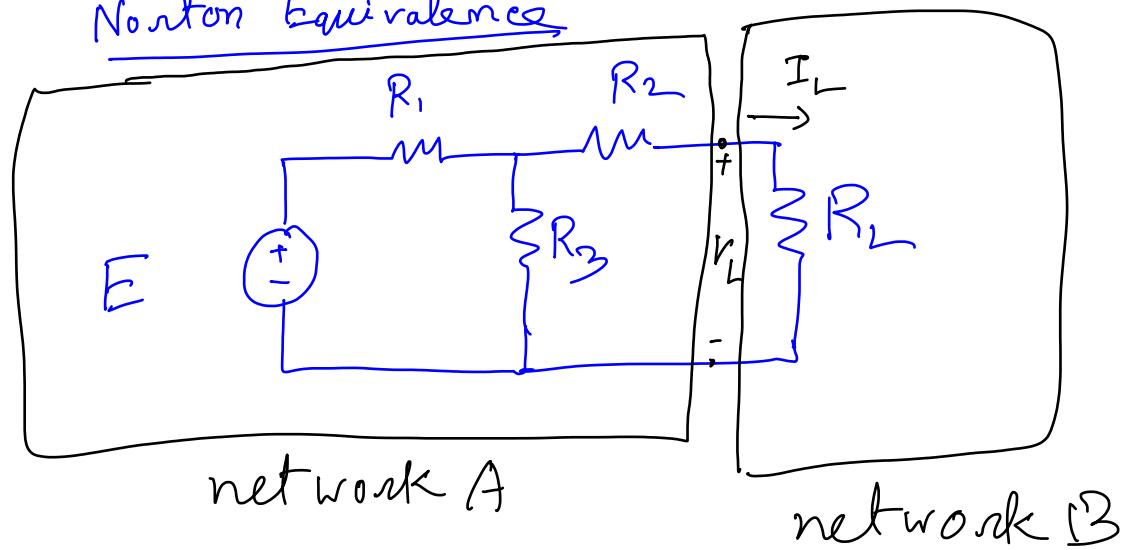

Calculating  $\frac{I_N}{R_1}$ ,

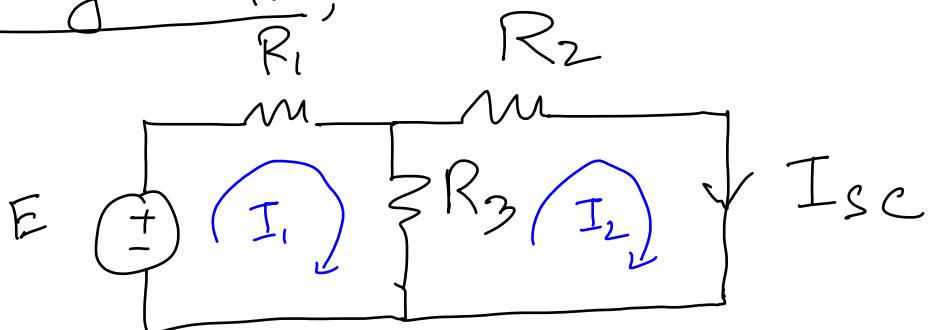

$$E = I_1 R_1 + (I_1 - I_2) R_3$$

$$I_{sc} = I_2$$

$$(I_1 - I_2) R_3 = I_2 R_2$$

$$\Rightarrow I_1 R_3 = (R_2 + R_3) I_2$$

$$\Rightarrow I_1 = \frac{R_2 + R_3}{R_3} I_2$$

$$E = I_1 (R_1 + R_3) - I_2 R_3$$

$$E = \frac{(R_1 + R_3)(R_2 + R_3)}{R_3} I_2 - I_2 R_3$$




$$= I_2 \left[ \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3} \right]$$

$$I_N = I_{SC} = I_2 = \frac{R_3 E}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$





$$V_{TH} = I_N \cdot R_{TH}, \quad R_N = R_{TH}$$

$$V_{TH} = \frac{R_3 E}{R_1 + R_3} \quad R_{TH} = R_2 + \frac{R_1 R_3}{R_1 + R_3}$$

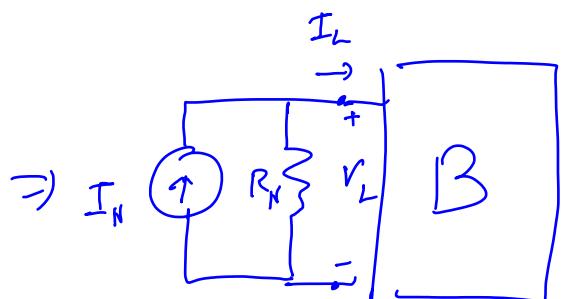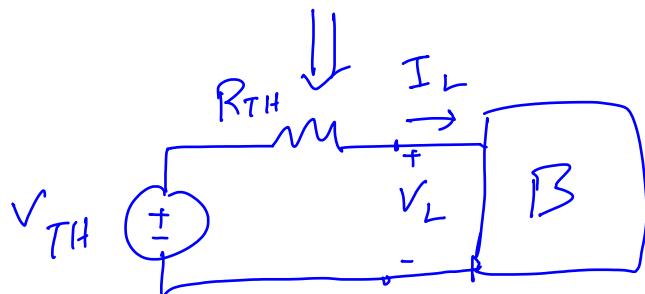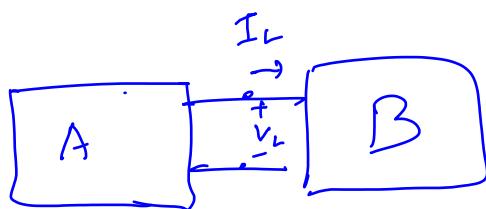
$$\frac{V_{TH}}{R_{TH}} = \frac{R_3 E / (R_1 + R_3)}{R_2 + \frac{R_1 R_3}{R_1 + R_3}} = \frac{R_3 E}{R_1 R_2 + R_2 R_3 + R_1 R_3} = I_N$$





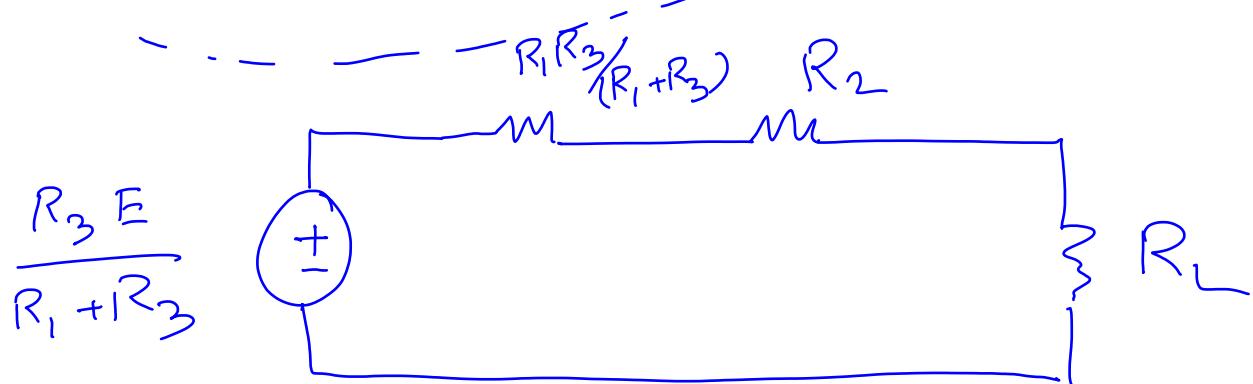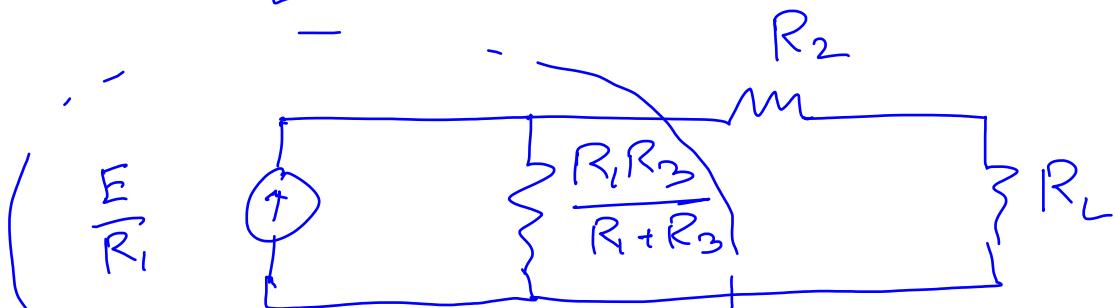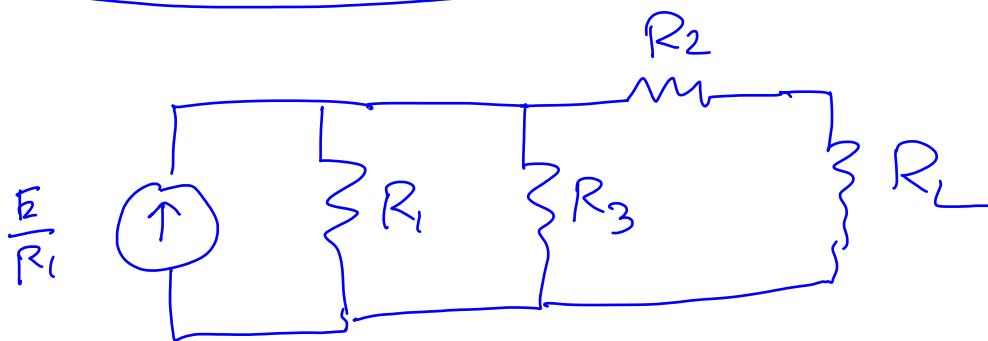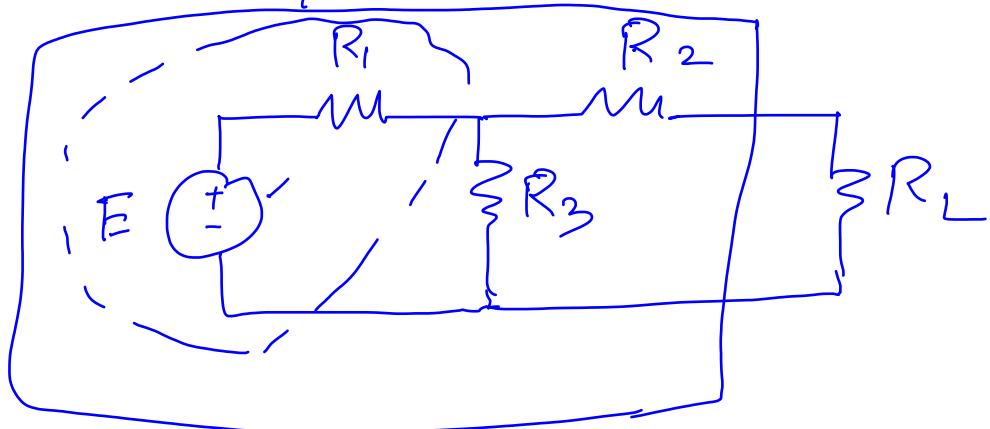Alternative Approach to figure out  
Thermis / Norton Equivalent network




$$\frac{R_3 E}{R_1 + R_3} = V_{TH}$$


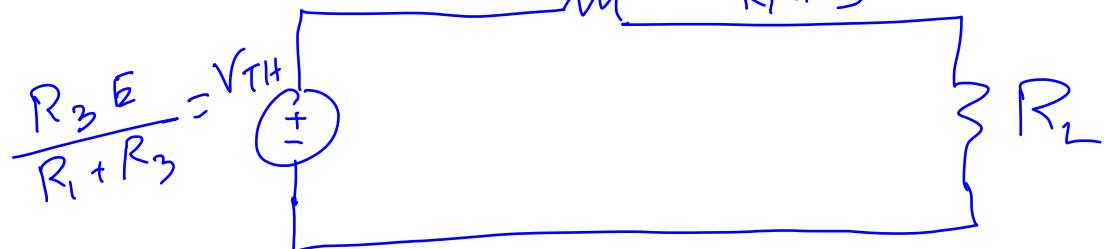


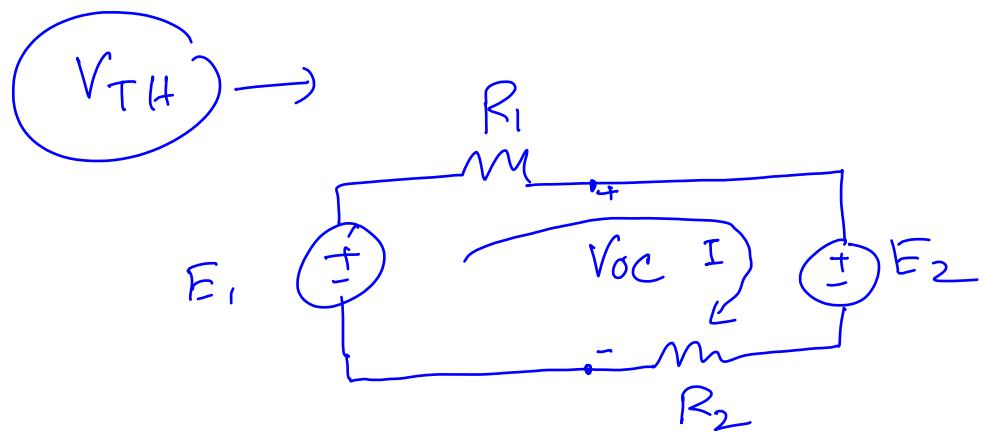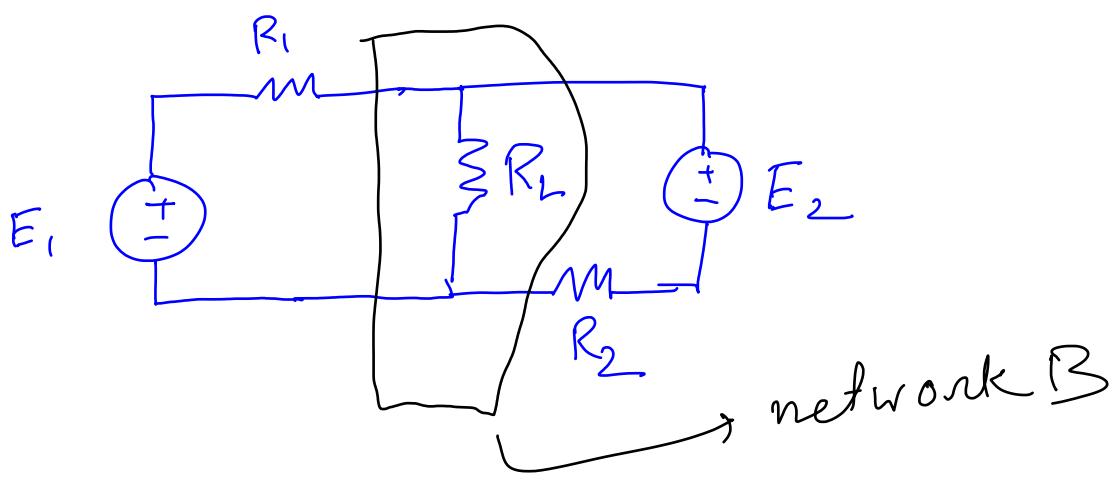

$$E_1 - E_2 = I (R_1 + R_2)$$
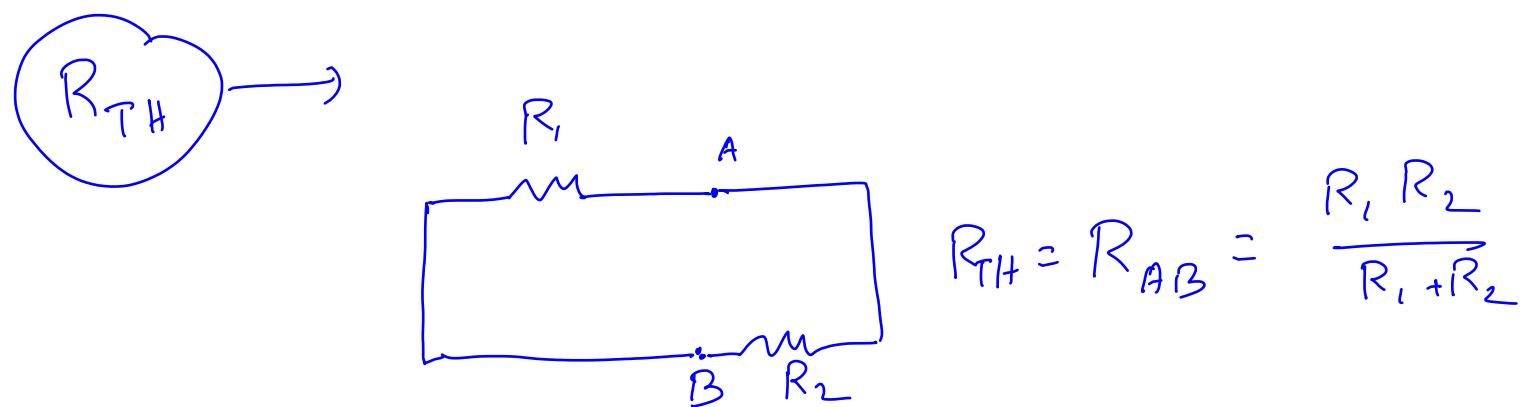
$$\begin{aligned} V_{TH} &= V_{oc} = E_1 - IR_1 \\ &= E_1 - \frac{E_1 - E_2}{R_1 + R_2} \cdot R_1 \quad \checkmark \end{aligned}$$



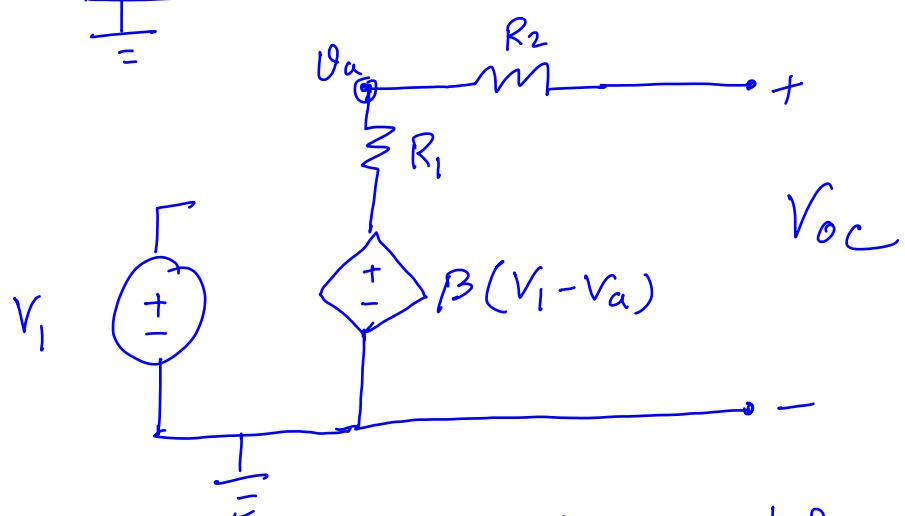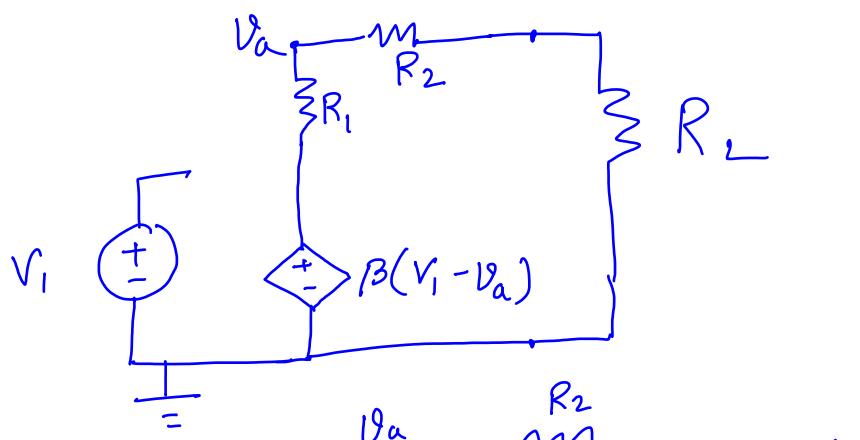


$$V_{oc} = V_a = \beta (V_i - V_a)$$

$$V_a = \beta (V_i - V_a)$$

$$(1 + \beta) V_a = \beta V_i$$

$$V_a = \frac{\beta}{1 + \beta} V_i$$
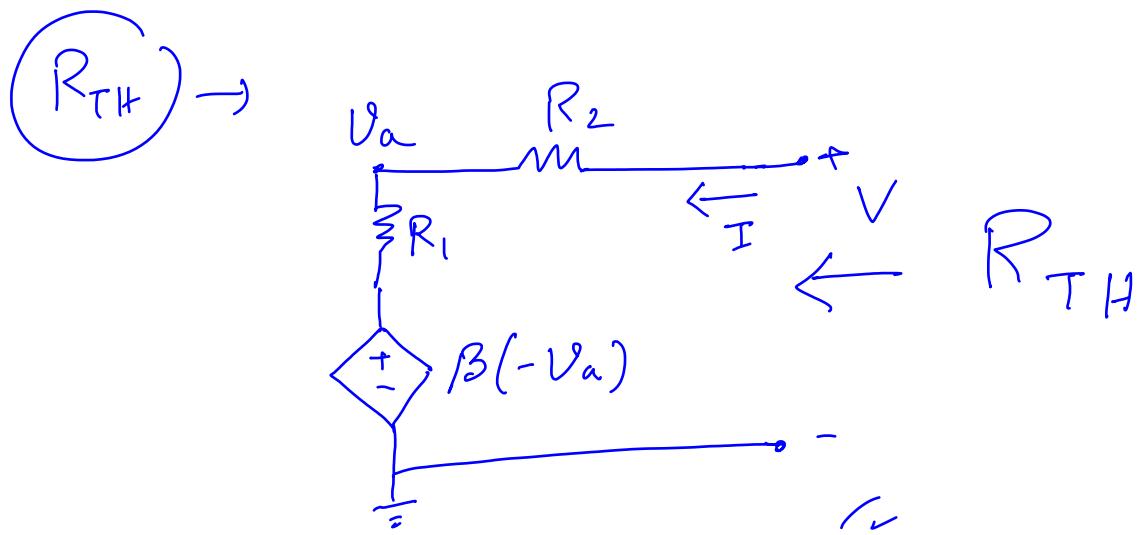
$$V_{TH} = V_{oc} = \frac{\beta}{1 + \beta} V_i$$



$$V = IR_2 + IR_1 - \beta V_a$$

$$V_a = IR_1 - \beta V_a$$



$$(1 + \beta)V_a = IR_1$$

$$V = I(R_1 + R_2) - \frac{\beta}{1 + \beta} IR_1$$

$$= I \left[ R_1 + R_2 - \frac{\beta}{1 + \beta} R_1 \right]$$

$$= I \left[ R_2 + \frac{1}{1 + \beta} R_1 \right]$$
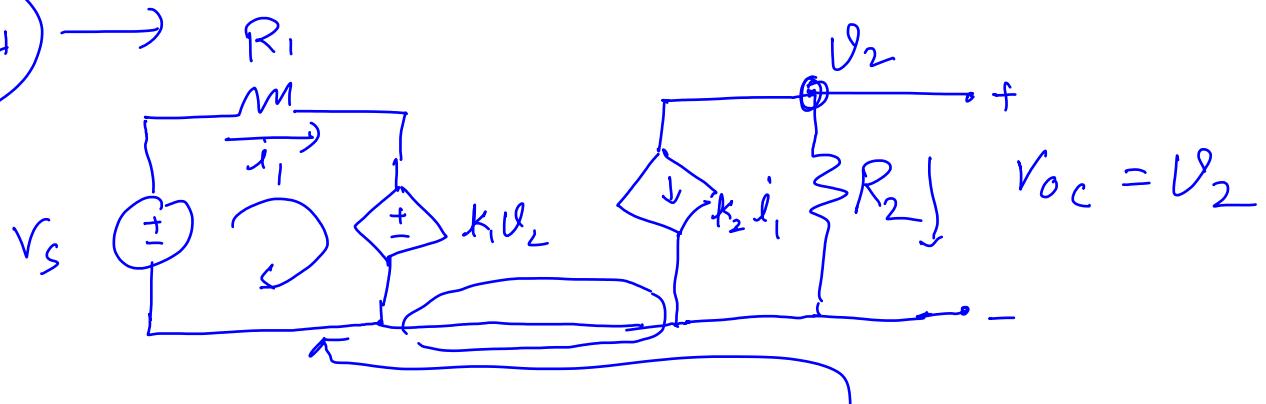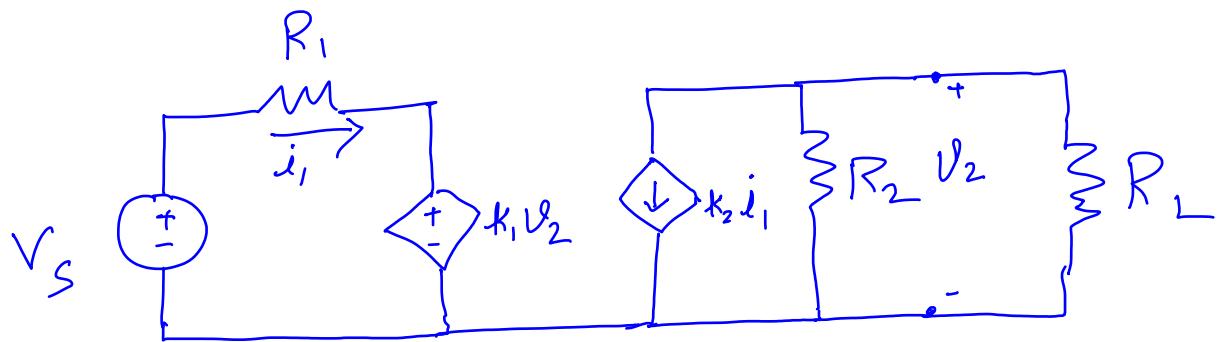
$$\Rightarrow R_{TH} = \frac{V}{I} = \left( R_2 + \frac{1}{1 + \beta} R_1 \right)$$



$$V_s = i_1 R_1 + k_1 V_2 \quad (\text{KVL})$$

$$k_2 i_1 + \frac{V_2}{R_2} = 0 \quad (\text{KCL at node 2})$$

$$i_1 = -\frac{1}{k_2 R_2} V_2$$

$$V_s = -\frac{R_1}{k_2 R_2} V_2 + k_1 V_2$$



$$\Rightarrow V_2 = \frac{V_s}{k_1 - \frac{R_1}{k_2 R_2}}$$

$$V_{TH} = V_{oc} = V_2$$




## Quick Recap


### Thevenin's Theorem

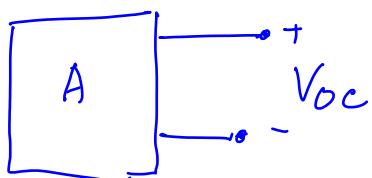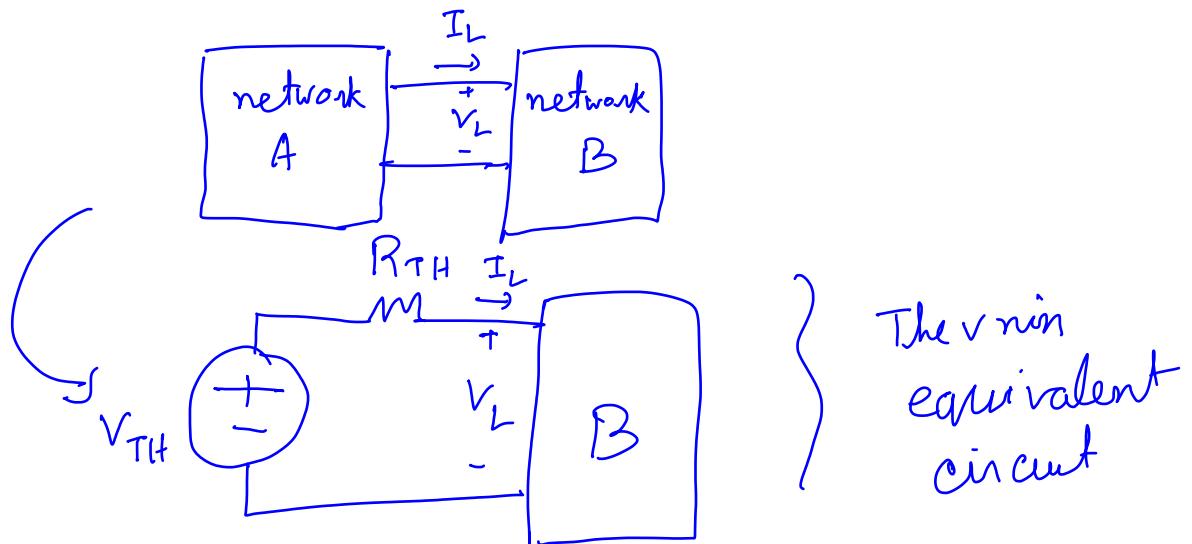




$$V_{TH} = V_{oc}$$

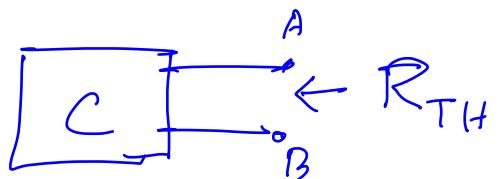

(switch off all the independent sources)

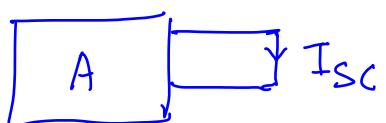

$$I_N = I_{sc}$$

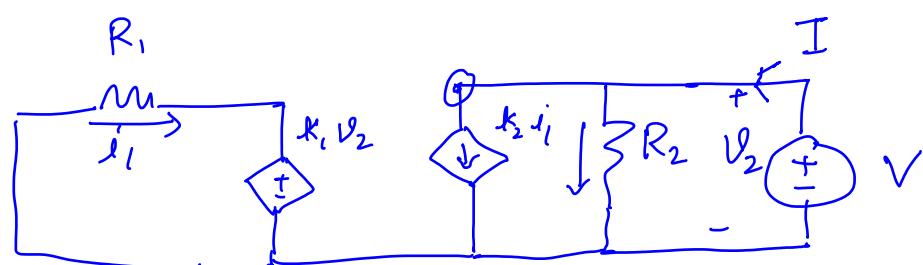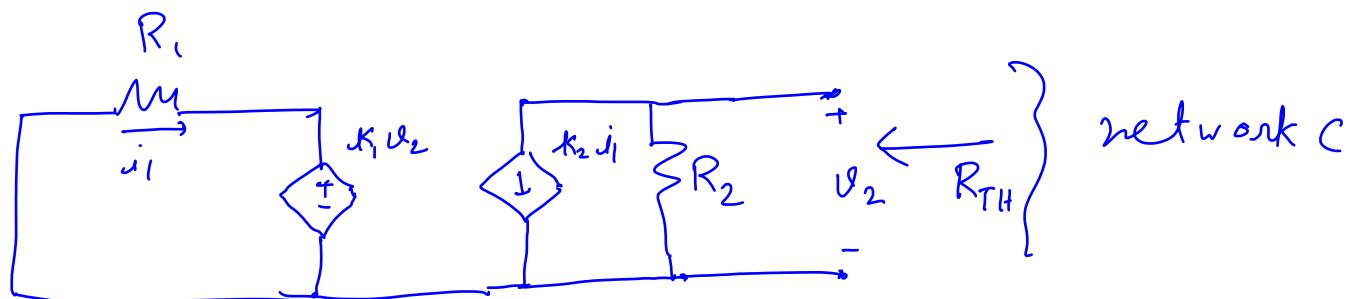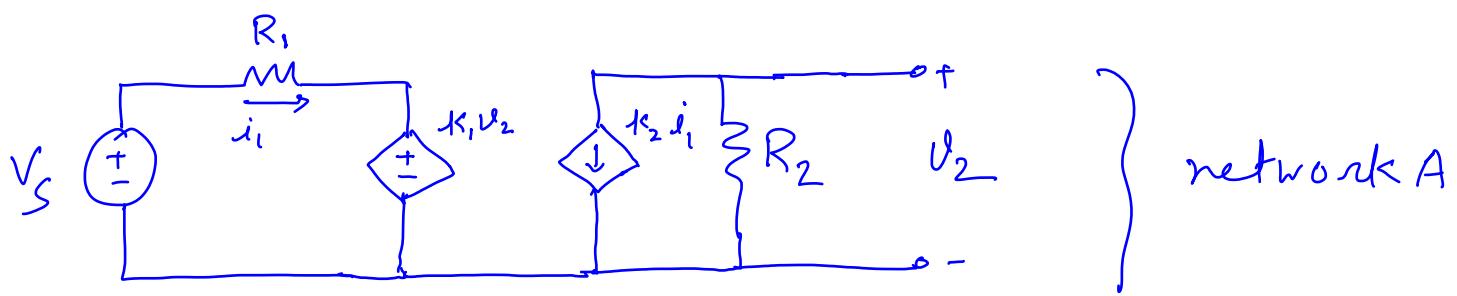

$$i_1 R_1 + k_1 V_2 = 0 \quad (\text{KVL})$$


$$I = k_2 i_1 + \frac{V_2}{R_2} \quad (\text{RCL}) \quad V_2 = V$$

$$i_1 = -\frac{k_1 V_2}{R_1}$$


$$I = -\frac{k_1 k_2}{R_1} V_2 + \frac{V_2}{R_2}$$

$$= V \left( -\frac{k_1 k_2}{R_1} + \frac{1}{R_2} \right)$$
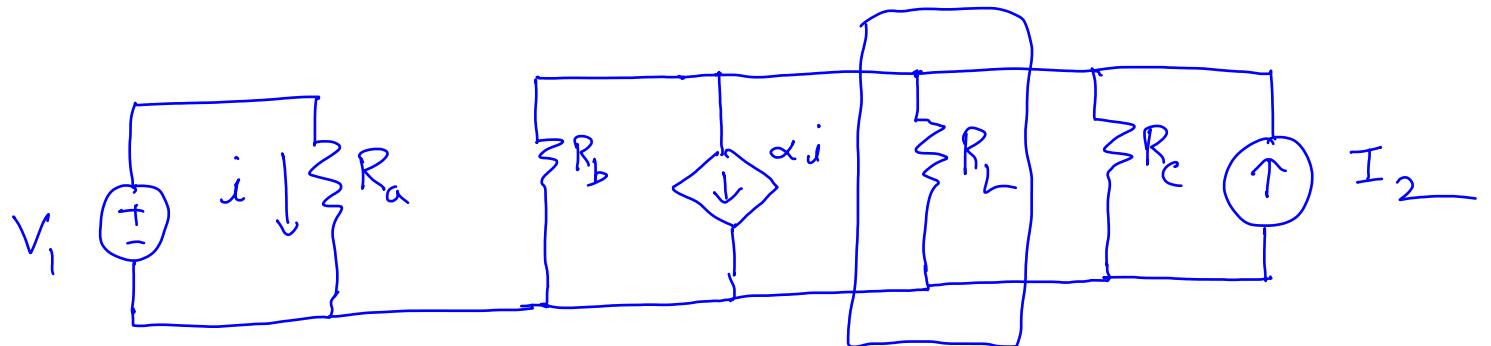
$$R_{TH} = \frac{V}{I} = \frac{1}{\left( -\frac{k_1 k_2}{R_1} + \frac{1}{R_2} \right)}$$



network B

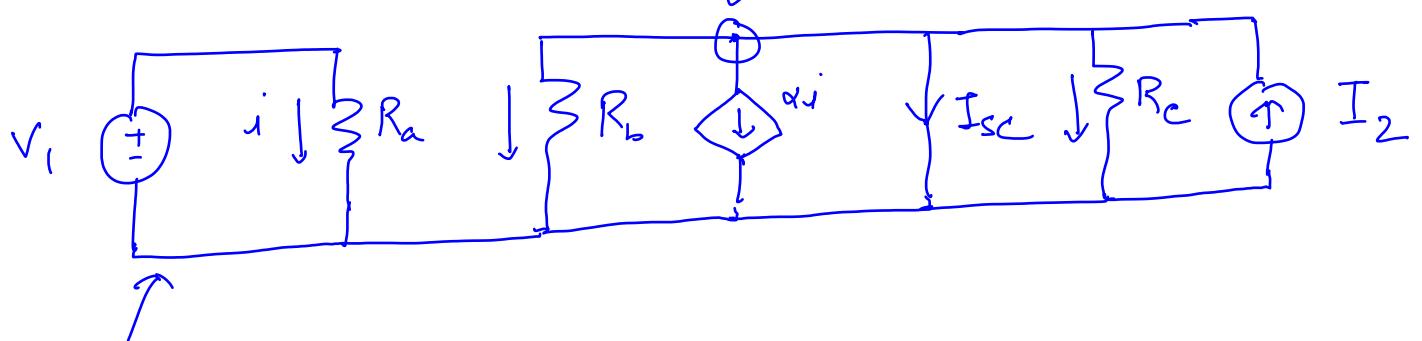


$$V_1 = i R_a \quad (\text{KVL})$$

$$I_2 = \frac{v}{R_b} + \frac{v}{R_c} + I_{SC} + \alpha i \quad (\text{KCL})$$

$$I_{SC} = I_2 - \alpha i$$
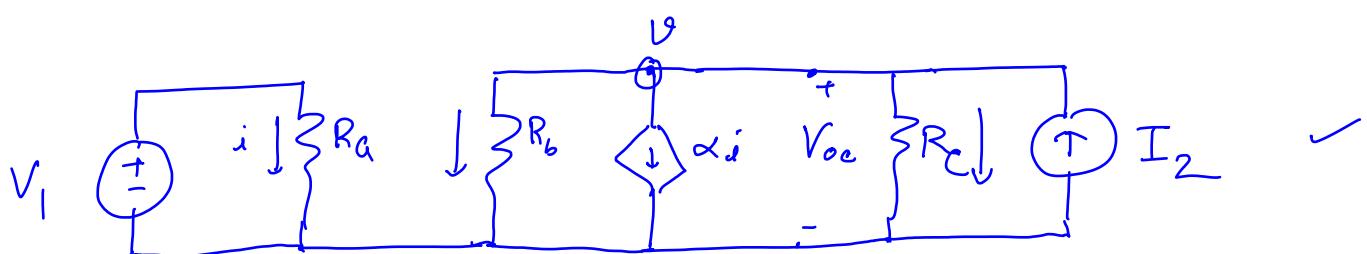
$$I_N = I_{SC} = I_2 - \alpha \frac{V_1}{R_a}$$



$$V_1 = i R_a \quad (\text{KVL})$$

$$v = V_{OC}$$


$$I_2 = \frac{v}{R_b} + \frac{v}{R_c} + \alpha i \quad (\text{KCL})$$

$$I_2 = \frac{U}{R_b} + \frac{U}{R_c} + \alpha \frac{V_t}{R_a}$$

$$I_2 - \frac{\alpha V_t}{R_a} = U \left( \frac{1}{R_b} + \frac{1}{R_c} \right)$$

$$V_{TH} = V_{OC} = U = \frac{I_2 - \frac{\alpha V_t}{R_a}}{\left( \frac{1}{R_b} + \frac{1}{R_c} \right)}$$
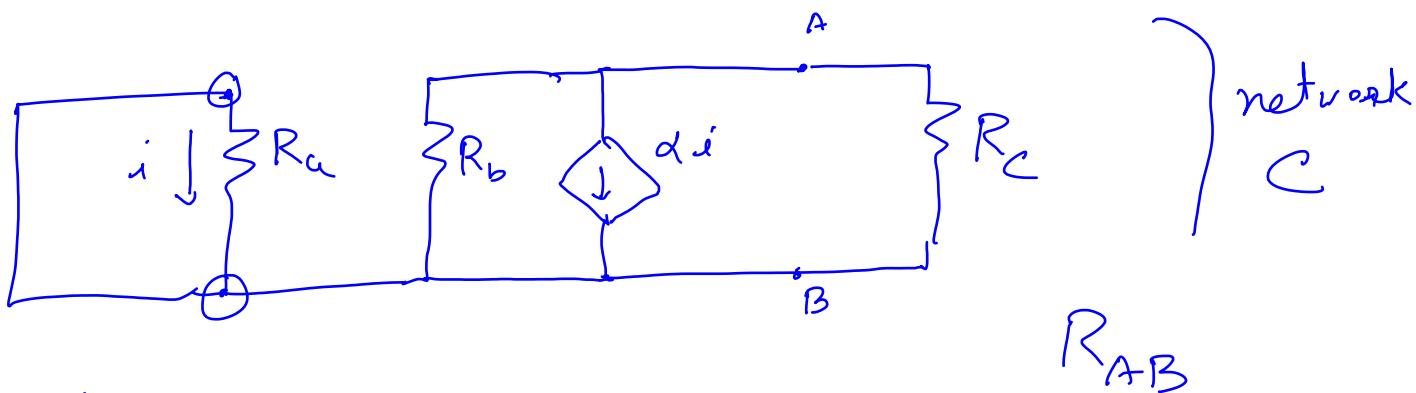
$$\Rightarrow \frac{V_{TH}}{I_N} = \frac{1}{\left( \frac{1}{R_b} + \frac{1}{R_c} \right)} = R_{TH}$$




$$i = 0$$

$$R_{AB}^{-1} = R_b^{-1} + R_c^{-1}$$

$$R_{TH} = R_{AB} = \frac{1}{\frac{1}{R_b} + \frac{1}{R_c}}$$

## Maximum Power Transfer Theorem

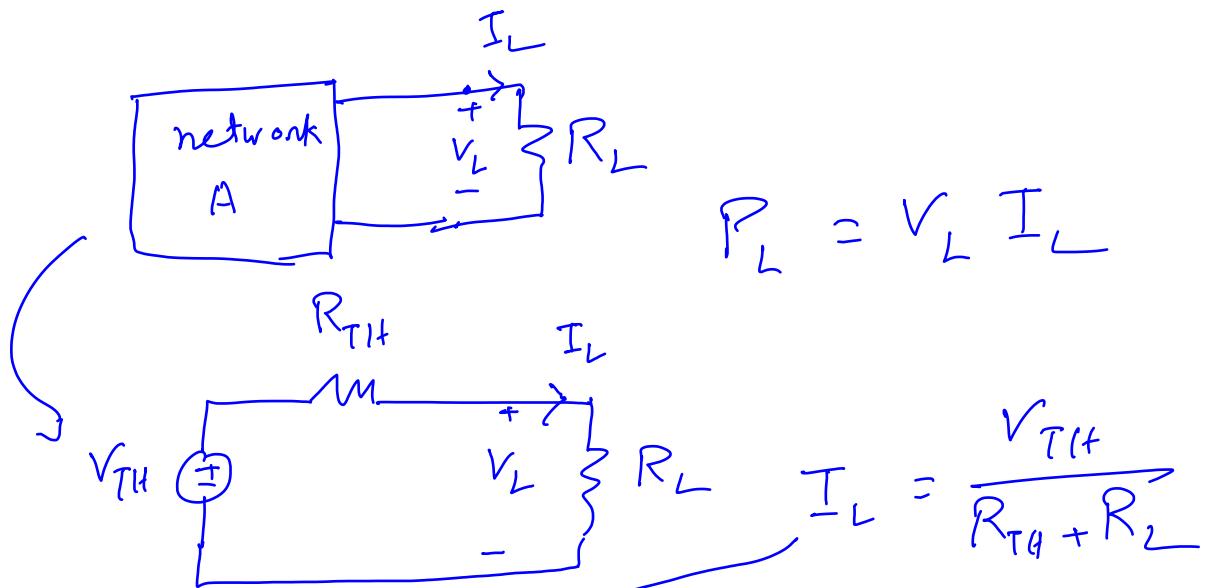

$$P_L = V_L I_L$$

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$P_L = I_L^2 R_L$$

$$P_L = \frac{V_{TH}^2}{(R_{TH} + R_L)^2} R_L$$

$$\frac{dP_L}{dR_L} = V_{TH}^2 \left[ \frac{-2R_L}{(R_{TH} + R_L)^3} + \frac{1}{(R_{TH} + R_L)^2} \right]$$


$$= V_{TH}^2 \left[ \frac{R_{TH} - R_L}{(R_{TH} + R_L)^3} \right]$$

$$\frac{dP_L}{dR_L} = 0 \Rightarrow R_L = R_{TH}$$

$$\frac{d^2 P_L}{d R_L^2} = V_{TH}^2 \left[ \frac{-3(R_{TH} - R_L)}{(R_{TH} + R_L)^4} - \frac{1}{(R_{TH} + R_L)^3} \right]$$




$$= V_{TH}^2 \left[ \frac{2R_L - 4R_{TH}}{(R_{TH} + R_L)^4} \right]$$

$$\left. \frac{d^2 P_L}{d R_L^2} \right|_{R_L = R_{TH}} < 0 \Rightarrow R_L = R_{TH} \text{ is a maxima.}$$

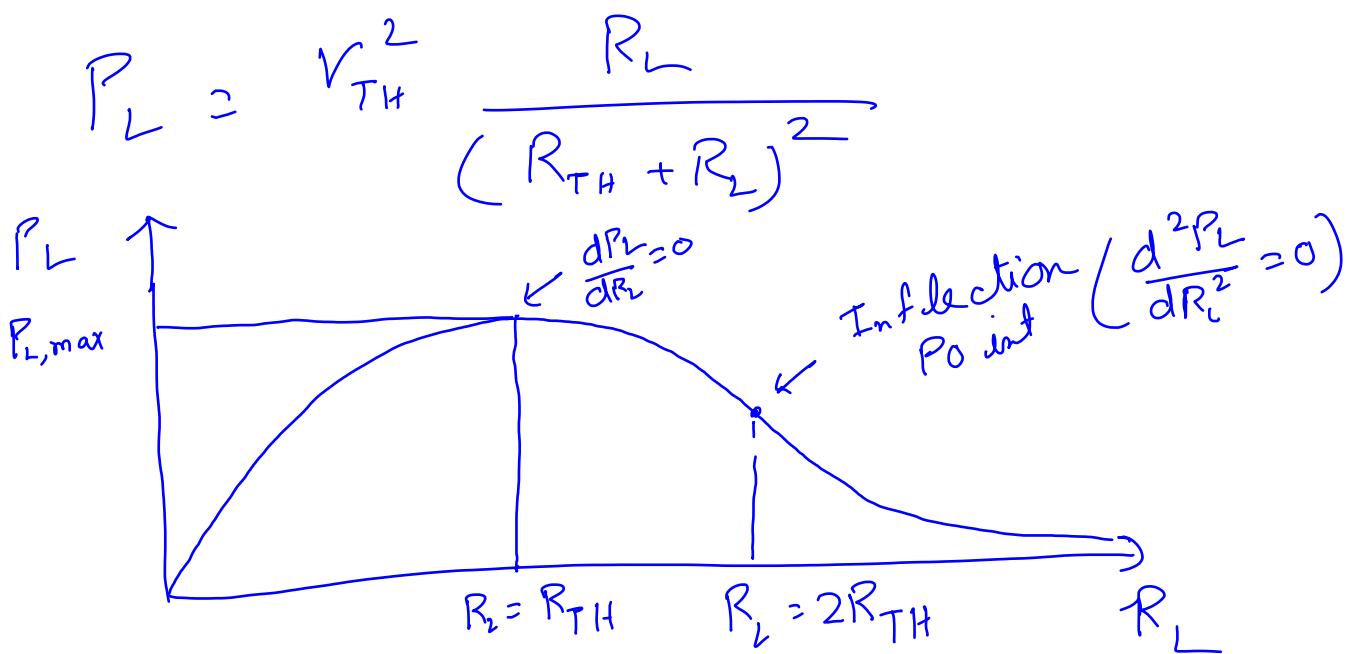


$$P_{L,\max} = V_{TH}^2 \frac{R_{TH}}{(R_{TH} + R_{TH})^2} = \frac{V_{TH}^2}{4R_{TH}}$$





### Quick Recap

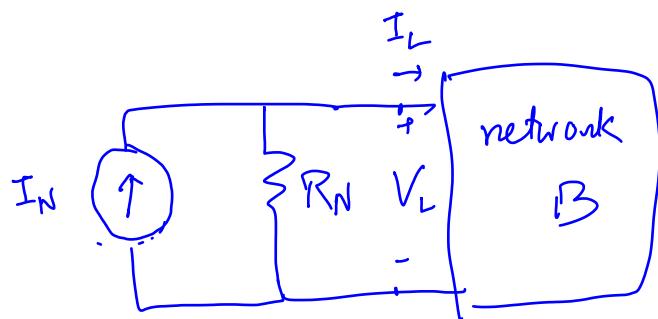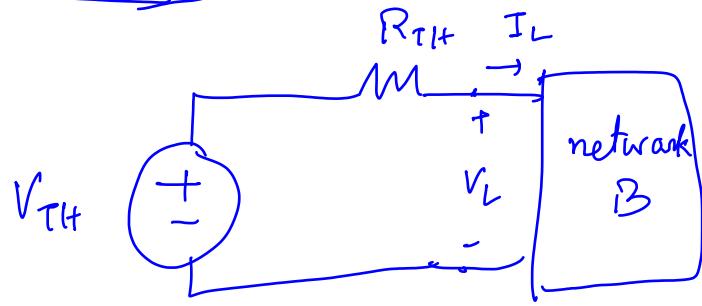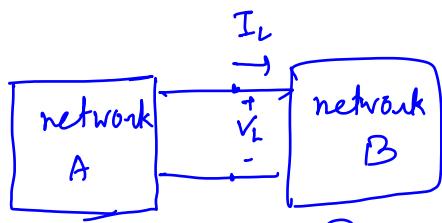


$$V_{TH} = I_N R_{TH}$$



$$R_{nr} = R_{TH}$$

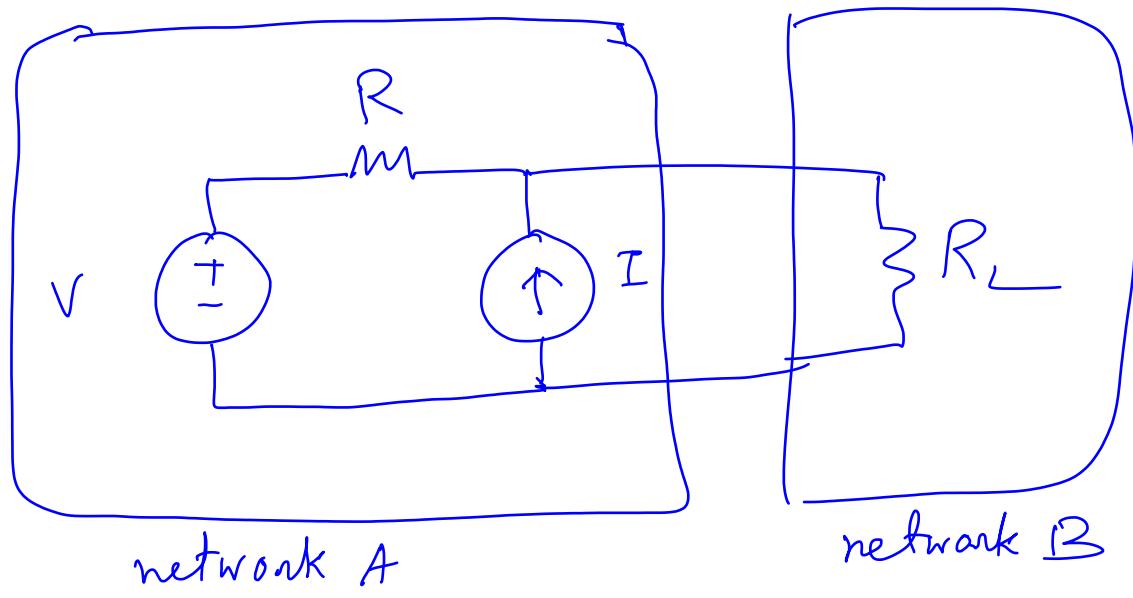

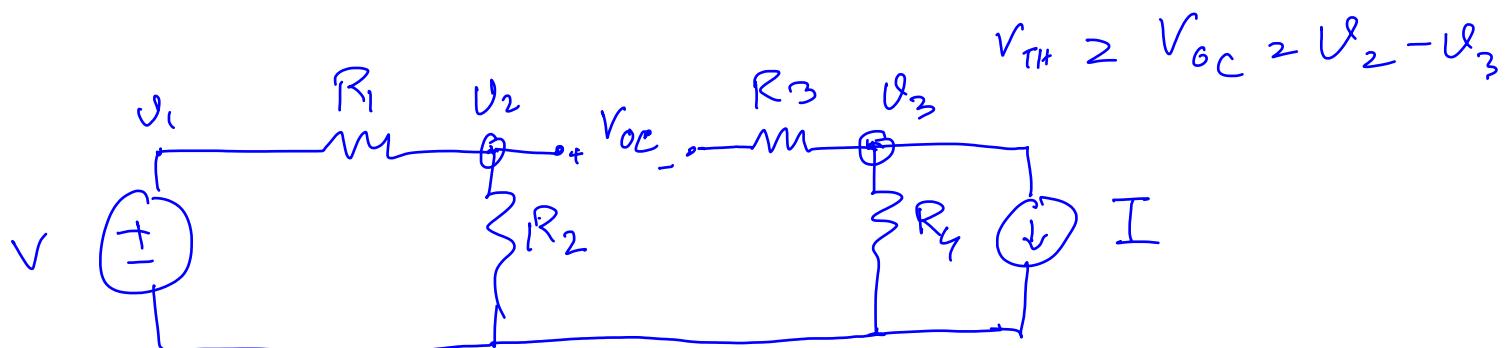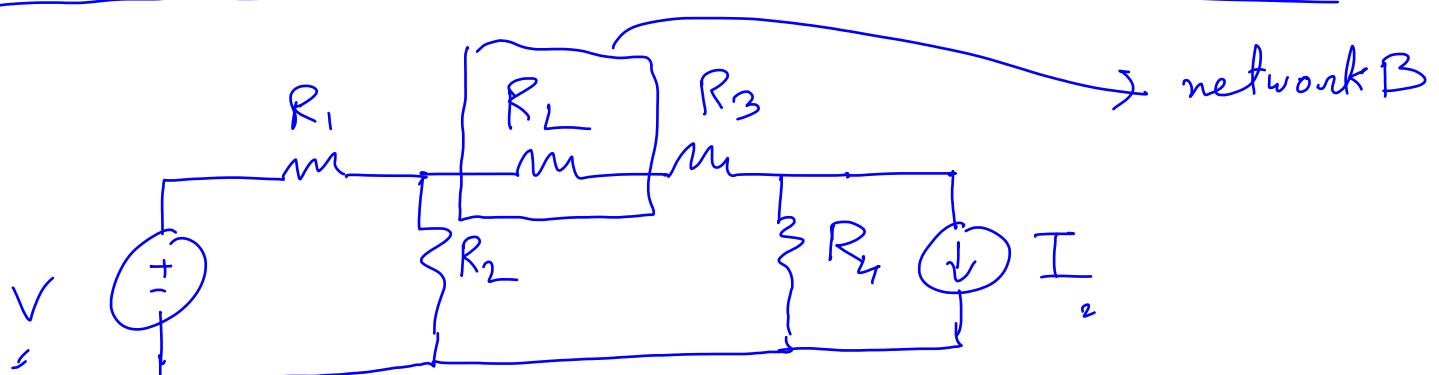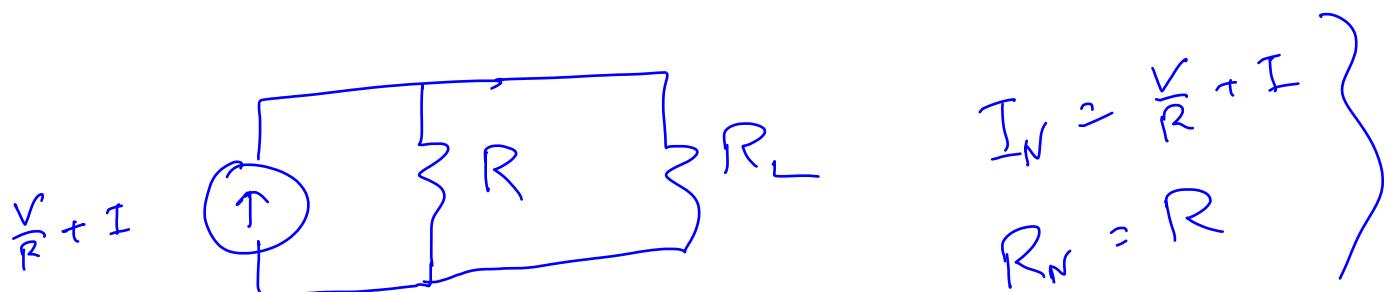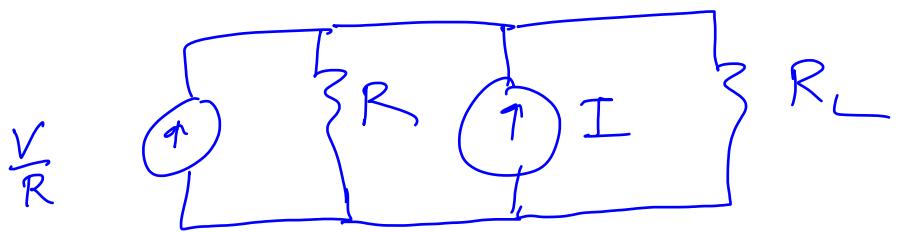
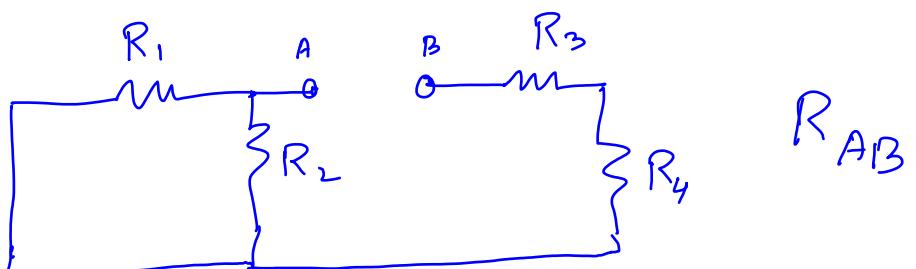
$$R_{TH} = (R_1 \parallel R_2) + R_3 + R_4$$



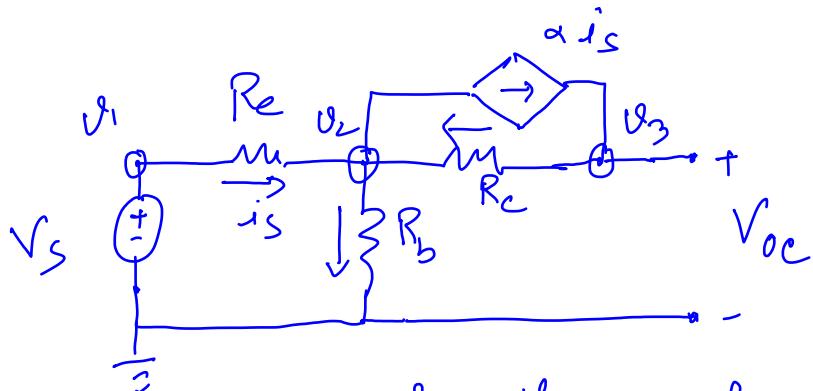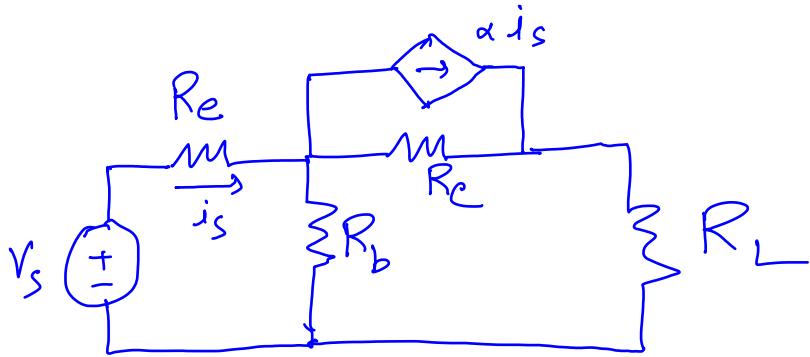


$$V_1 = V_s$$


$$\frac{V_1 - V_2}{R_e} + \frac{V_3 - V_2}{R_c} = \frac{V_2}{R_b} + \alpha \left( \frac{V_1 - V_2}{R_c} \right)$$

$$\frac{V_3 - V_2}{R_c} = \alpha \left( \frac{V_1 - V_2}{R_e} \right)$$

$$V_{TH} = V_{oc} = V_3$$


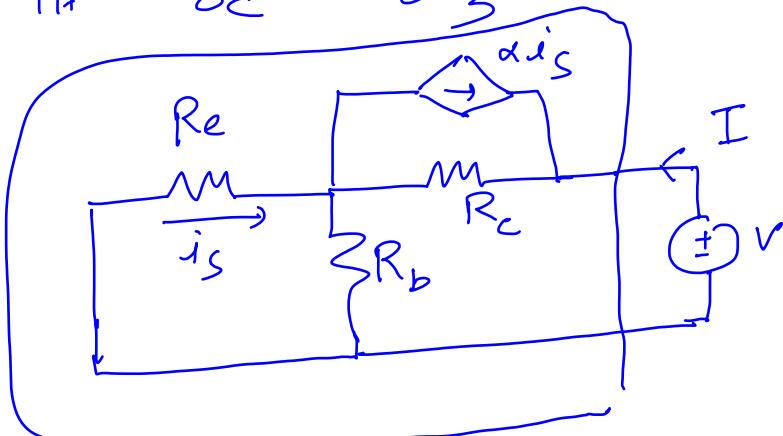


$$R_{TH} = \frac{V}{I}$$

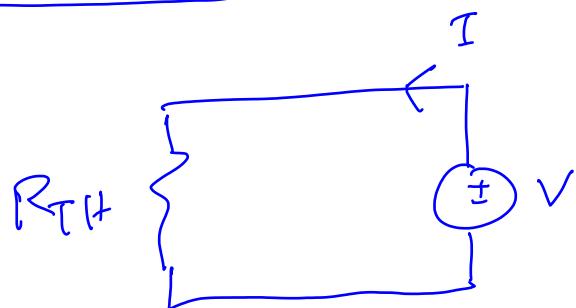






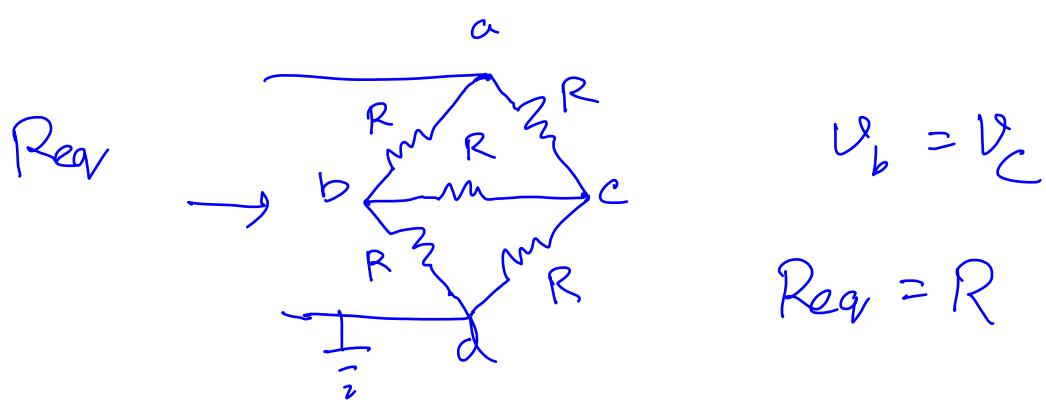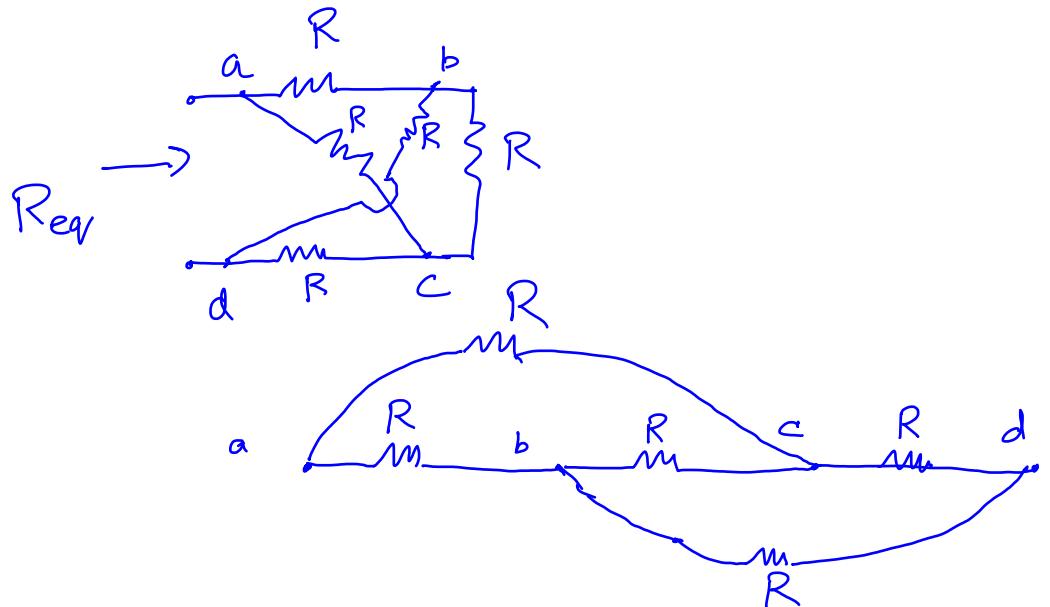

### Wheatstone Bridge

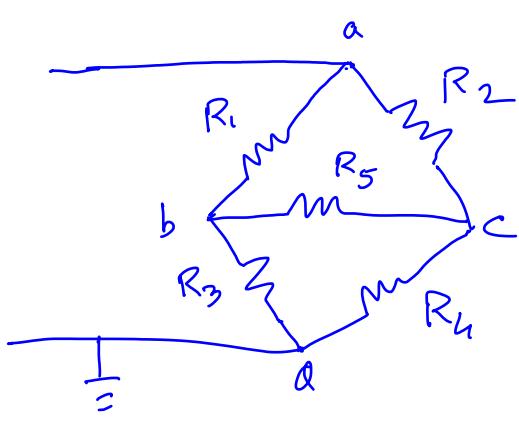

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$i_{R_5} = 0$$

Condition X,

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Condition Y,

$$i_{R_S} = 0 \quad \checkmark$$

$$Y \Rightarrow X$$


and

$$X \Rightarrow Y$$

X is a necessary and sufficient condition for Y.

Y is true if and only if X is true.  
iff

Proving  $Y \Rightarrow X$ ,

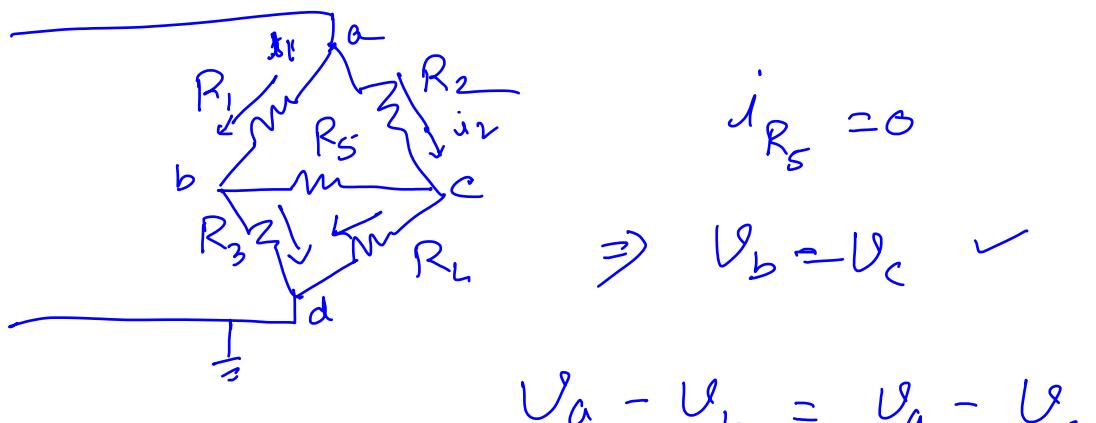

$$i_1 R_1 = i_2 R_2$$


$$\frac{i_1}{i_2} = \frac{R_2}{R_1}$$

$$V_b = i_1 R_3 = i_2 R_4 = V_c$$

$$\frac{i_1}{i_2} = \frac{R_4}{R_3} \Rightarrow \frac{R_2}{R_1} = \frac{R_4}{R_3}$$

$$\Rightarrow \boxed{Y \Rightarrow X}$$

Proving  $X \Rightarrow Y$ ,

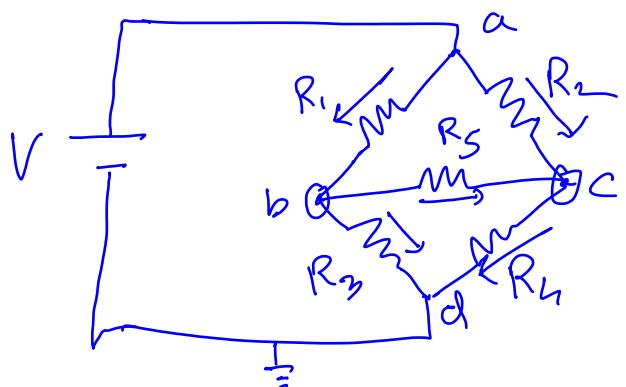

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\underline{V_a = V}$$

KCL at node b,

$$\frac{V_a - V_b}{R_1} = \frac{V_b - V_c}{R_S} + \frac{V_b}{R_3}$$

KCL at node c,

$$\frac{V_a - V_c}{R_2} + \frac{V_b - V_c}{R_S} = \frac{V_c}{R_4}$$

$$V_b \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_S} \right) - \frac{V_c}{R_S} = \frac{V}{R_1} \quad \text{--- (1)}$$

$$\frac{V_b}{R_S} - V_c \left( \frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_S} \right) = -\frac{V}{R_2} \quad \text{--- (2)}$$

Multiply ① by  $R_1$  and ⑪ by  $R_2$

$$R_1 \left( V_b \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_S} \right) - \frac{V_C}{R_S} \right) =$$

$$- R_2 \left( \frac{V_b}{R_S} - V_C \left( \frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_S} \right) \right)$$

$$\Rightarrow V_b \left( 1 + \left( \frac{R_1}{R_3} \right) + \frac{R_1}{R_S} + \frac{R_2}{R_S} \right) = V_C \left( 1 + \left( \frac{R_2}{R_4} \right) + \frac{R_2}{R_S} + \frac{R_1}{R_S} \right)$$

$$\Rightarrow V_b = V_C$$


$$\Rightarrow i_{R_S} = 0 \Rightarrow Y \text{ is true.}$$

So


$$\boxed{X \Rightarrow Y}$$

$\Rightarrow$



$$\boxed{X \Leftrightarrow Y}$$

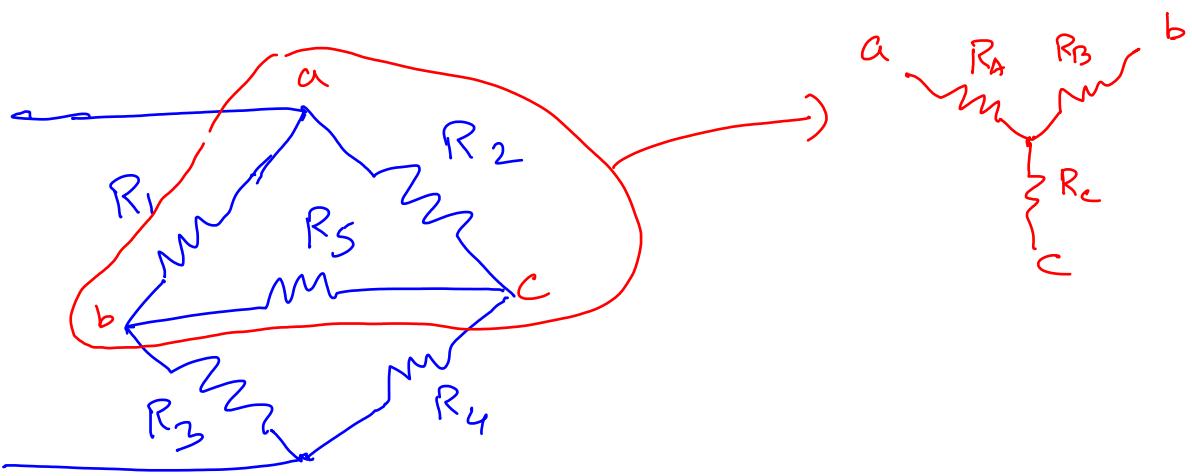


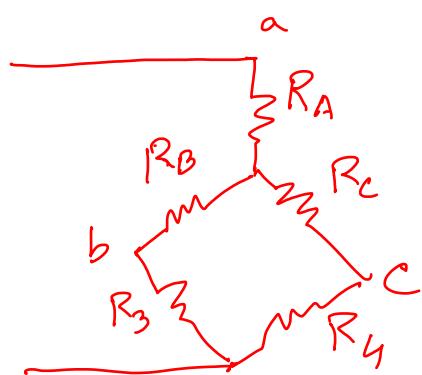What if  $\frac{R_1}{R_2} \neq \frac{R_3}{R_4}$




Star - delta Conversion,

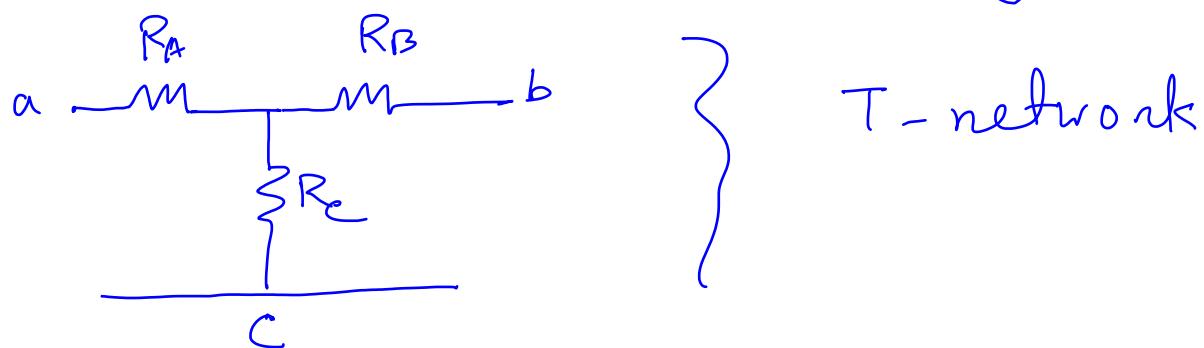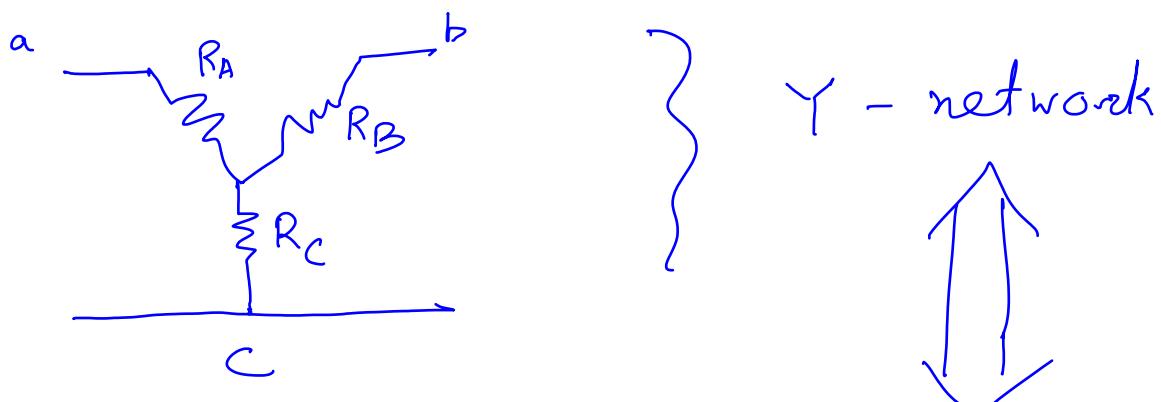


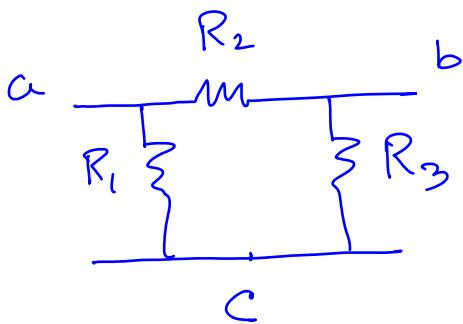


$\Pi$ -network

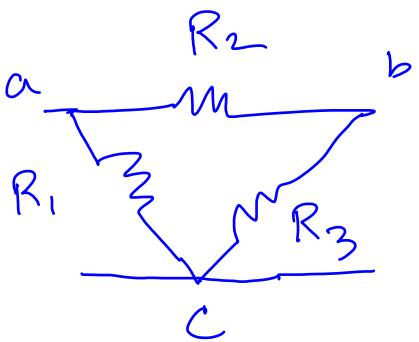

Delta-network

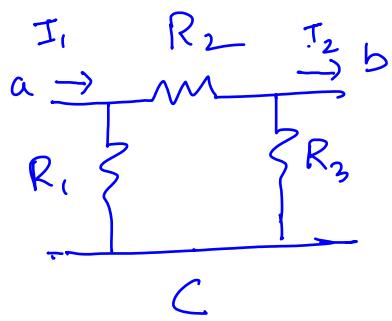

$V_{ac}$ ,  $V_{bc}$

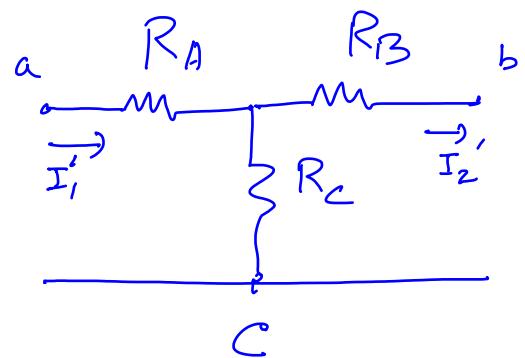


$V'_{ac}$ ,  $V'_{bc}$

$$I_1 = I_1', \quad I_2 = I_2'$$

$$\text{and} \quad V_{ac} = V'_{ac}, \quad V_{bc} = V'_{bc}$$

For equivalence, what should be the relation among the resistances?

} equivalent

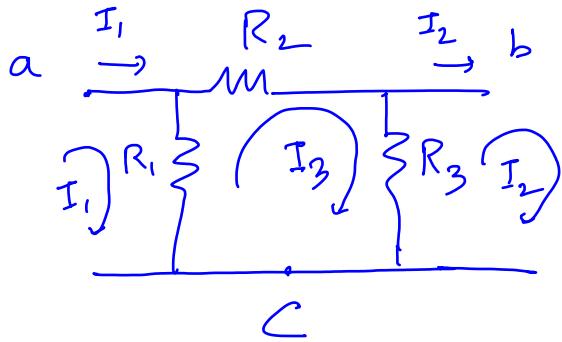

$$V_{ac} = I_1 R_1 - I_3 R_1$$

$$-(I_1 - I_3)R_1 + I_3 R_2 + (I_3 - I_2)R_3 = 0$$

$$V_{bc} = -(I_2 - I_3)R_3 \quad \checkmark$$

$$I_3(R_1 + R_2 + R_3) = I_1 R_1 + I_2 R_3$$

$$I_3 = \frac{I_1 R_1 + I_2 R_3}{(R_1 + R_2 + R_3)}$$

$$V_{ac} = I_1 R_1 - \frac{R_1^2}{R_1 + R_2 + R_3} I_1 - \frac{R_3 R_1}{R_1 + R_2 + R_3} I_2$$


$$V_{ac} = \underbrace{\left( R_1 - \frac{R_1^2}{R_1 + R_2 + R_3} \right) I_1}_{\text{1}} - \underbrace{\frac{R_3 R_1}{R_1 + R_2 + R_3} I_2}_{\text{2}}$$

$$V_{bc} = -I_2 R_3 + I_3 R_3$$

$$= -I_2 R_3 + R_3 \left( \frac{I_1 R_1 + I_2 R_3}{R_1 + R_2 + R_3} \right)$$

$$V_{bc} = \frac{R_3 R_1}{R_1 + R_2 + R_3} I_1 - I_2 \left( R_3 - \frac{R_3^2}{R_1 + R_2 + R_3} \right)$$

(I)

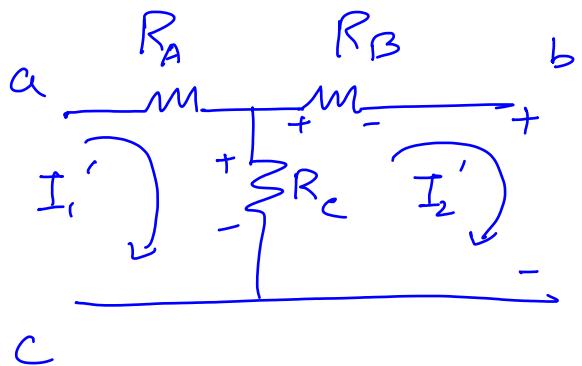

$$V_{R_C} = (I_1' - I_2') R_C$$

$$V_{R_B} = I_2' R_B$$

$$V'_{ac} = I_1' R_A + I_1' R_C - I_2' R_C \quad \}$$

$$V'_{bc} = + (I_1' - I_2') R_C - I_2' R_B \quad \}$$

$$V_{R_C} - V_{R_B} - V'_{bc} = 0$$

$$V'_{ac} = I_1' (R_A + R_C) - R_C I_2' \quad \text{III}$$

$$V'_{bc} = R_C I_1' - (R_C + R_B) I_2' \quad \text{IV}$$

(IV)

Comparing equations (I) and (III),

$$R_A + R_C = R_1 - \frac{R_1^2}{R_1 + R_2 + R_3}$$

$$\sqrt{R_C} = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

similarly derive the other expressions.



$$R_C = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

$$R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$



### Quick Recap

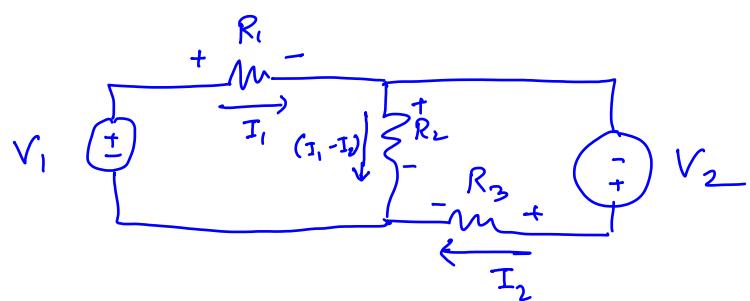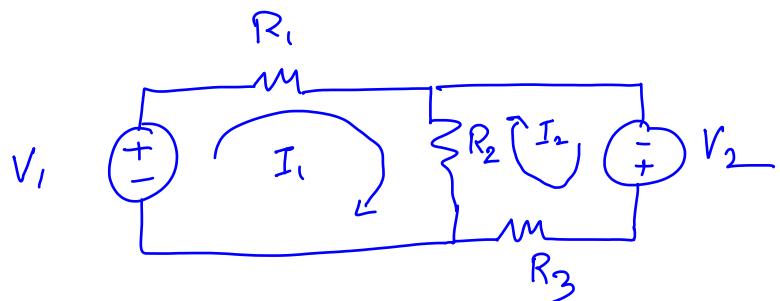

$$V_1 - V_{R_1} - V_{R_2} = 0$$

$$V_{R_1} = I_1 R_1$$

$$V_{R_2} = (I_1 - I_2) R_2$$


$$V_{R_3} = I_2 R_3$$

$$V_2 - V_{R_3} + V_{R_2} = 0$$

### Capacitors

$$Q = C V$$

Capacitance

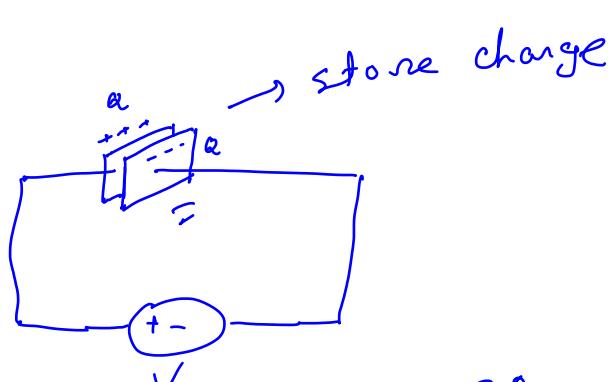

$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$C = \frac{\epsilon A}{d}$$


$\epsilon$  → permittivity

$A$  → area of the plate

$d$  → distance between the plates

unit of capacitance Farad =  $\frac{\text{Coulomb}}{\text{Volt}}$  }

### Capacitor Charging →

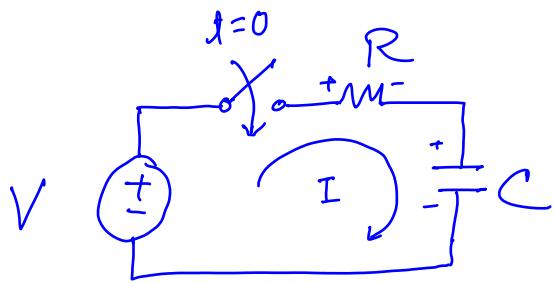

$$V_R = IR$$

$$V = V_R + V_C$$

$$I = C \frac{dV_C}{dt}$$

$$V = IR + V_C$$

$$= CR \frac{dV_C}{dt} + V_C$$

$$V = RC \frac{dV_C}{dt} + V_C$$

$$\Rightarrow \int_{0}^{V_C} \frac{dV_C}{V - V_C} = \int_{0}^t \frac{1}{RC} dt$$

$$\Rightarrow -\ln \left( \frac{V - V_C}{V} \right) = \frac{t}{RC}$$


$$\Rightarrow \frac{V - V_C}{V} = e^{-t/RC}$$

$$\Rightarrow V_C = V - V e^{-t/RC}$$

$$V_C = V(1 - e^{-t/RC}) \quad \forall t \geq 0$$

$$\text{at } t=0 \quad V_C = 0$$
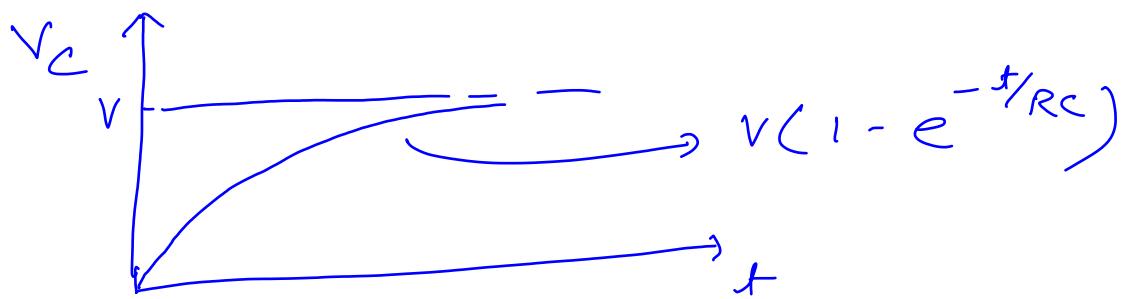
$$\text{at } t \rightarrow \infty \quad V_C \rightarrow V \quad \text{at } t \rightarrow \infty \quad \text{the capacitor is fully charged.}$$




$$I = C \frac{dV_C}{dt} = \frac{CV}{RC} e^{-t/RC} = \frac{V}{R} e^{-t/RC}$$


at  $t = 0$  the capacitor acts as a short circuit

at  $t \rightarrow \infty$  the capacitor acts as an open circuit.

### Capacitor discharging

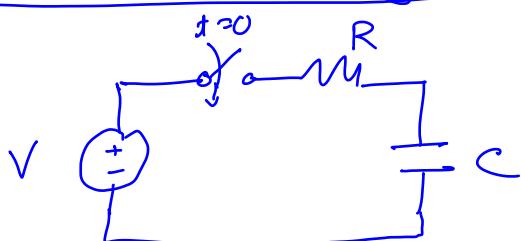

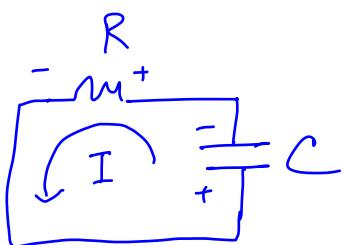After a very long time remove the voltage source and connect the  $R$  and  $C$  together.



$$V_R + V_C = 0$$

$$V_R = IR, \quad I = C \frac{dV_C}{dt}$$

$$IR + V_C = 0$$


$$RC \frac{dV_C}{dt} + V_C = 0$$

$$\int \frac{dV_C}{V_C} = \int_{0}^t -\frac{1}{RC} dt$$

$V_C(0) = V$

$$\ln \frac{V_C}{V} = -\frac{t}{RC}$$
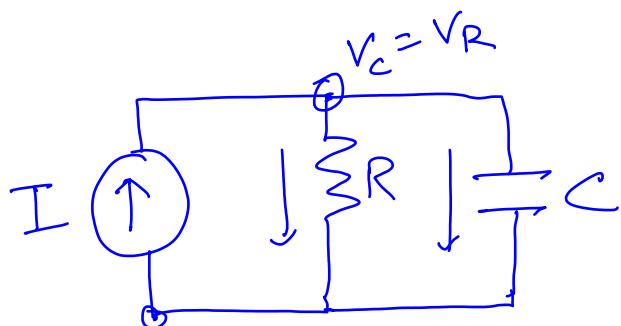
$$\Rightarrow V_C = V e^{-t/RC} \quad (\text{discharging})$$



$$I = \frac{V_C}{R} + C \frac{dV_C}{dt}$$

$$\Rightarrow \int_0^t \frac{dV_C}{IR - V_C} = \int_0^t \frac{1}{RC} dt$$

$$\Rightarrow -\ln \frac{IR - V_C}{IR} = \frac{t}{RC}$$

$$\Rightarrow IR - V_C = IR e^{-t/RC}$$

$$\Rightarrow V_C = IR (1 - e^{-t/RC})$$

$$I_C = C \frac{dV_C}{dt} = \frac{IRC}{RC} e^{-t/RC} = I e^{-t/RC}$$





## Quick Recap

Capacitors ( $C$ )

$$E = \int_0^t P dt$$

Energy      Power


$$C = \frac{\epsilon A}{d}$$

$$= \int_0^t VI dt = \int_0^t V \cdot C \frac{dv}{dt} dt$$

$$= \int_{V(0)}^{V(t)} CV dr$$

$$= \frac{1}{2} CV^2(t) - \frac{1}{2} CV^2(0)$$


## Charging of a capacitor

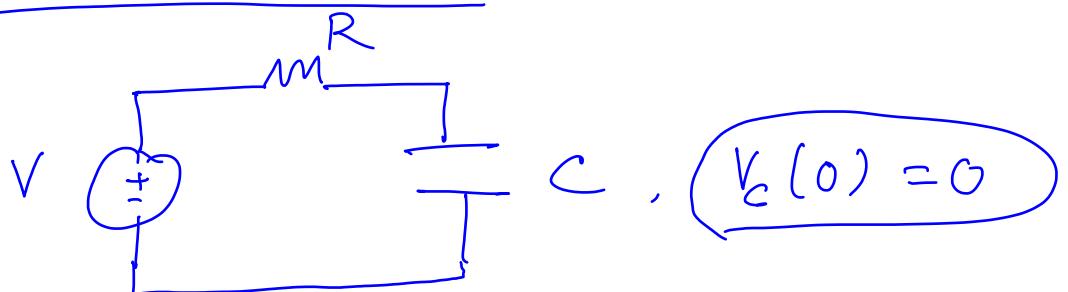


$$V_C(t) = V \left(1 - e^{-\frac{t}{RC}}\right) \quad \forall t \geq 0$$

$V_C(\infty) = V$

## Capacitor discharging

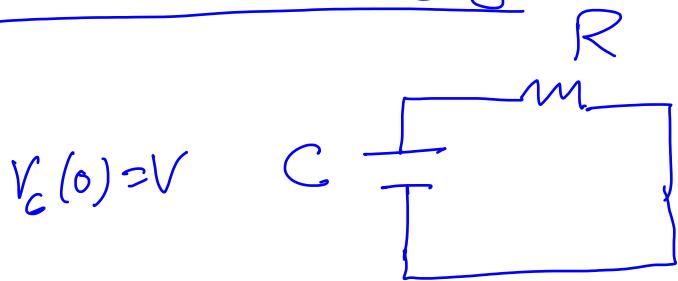
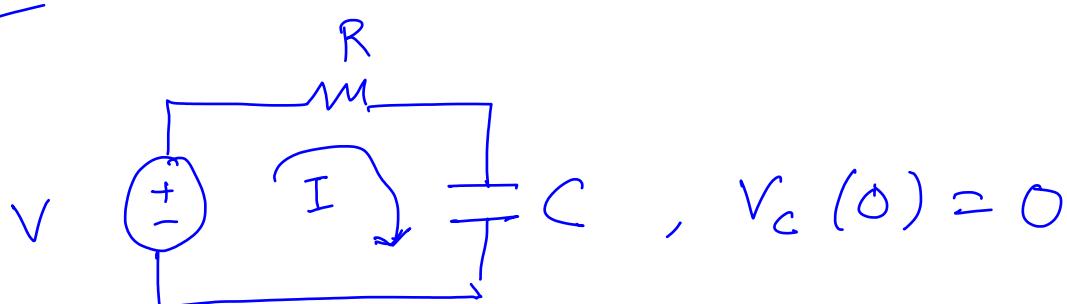
$$V_C(t) = V e^{-\frac{t}{RC}} \quad \forall t \geq 0$$



$$V = IR + \frac{1}{C} \int I dt$$

$$0 = \frac{dI}{dt} \cdot R + \frac{1}{C} I$$

$$\left\{ \begin{array}{l} \frac{dI}{I} = -\frac{1}{RC} dt \\ I(0) \end{array} \right.$$

$$\ln \frac{I(t)}{I(0)} = -\frac{1}{RC} t$$

$$\Rightarrow I(t) = I(0) e^{-\frac{t}{RC}}$$

$$V = V_R(t) + V_C(t) \quad \forall t \geq 0$$

$$V = V_R(0) + V_C(0) \Rightarrow V_R(0) = V$$


$$I(t) = \frac{V_R(t)}{R} \quad \forall t \geq 0$$

$$I(0) = \frac{V_R(0)}{R} = \frac{V}{R}$$

$$I(t) = I(0) e^{-t/RC}$$

$$= \frac{V}{R} e^{-t/RC}$$

$\equiv$

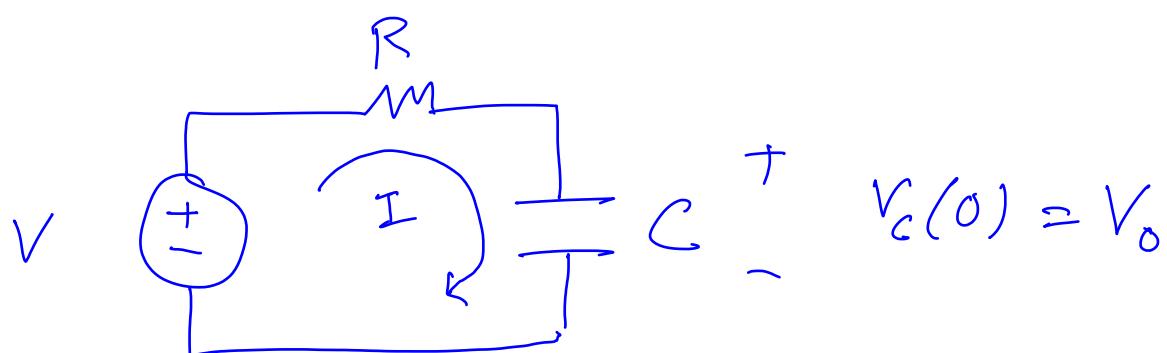

$$V = IR + V_C$$

$$= C \frac{dV_C}{dt} \cdot R + V_C$$

$$V - V_C = RC \frac{dV_C}{dt}$$


$$\Rightarrow \int_{V_0}^{V_C(t)} \frac{dV_C}{V - V_C} = \int_0^t \frac{dt}{RC}$$

$$-\ln \frac{V - V_C(t)}{V - V_0} = \frac{t}{RC}$$


$$\frac{V - V_c(t)}{V - V_0} = e^{-t/RC}$$

$$V - V_c(t) = V e^{-t/RC} - V_0 e^{-t/RC}$$

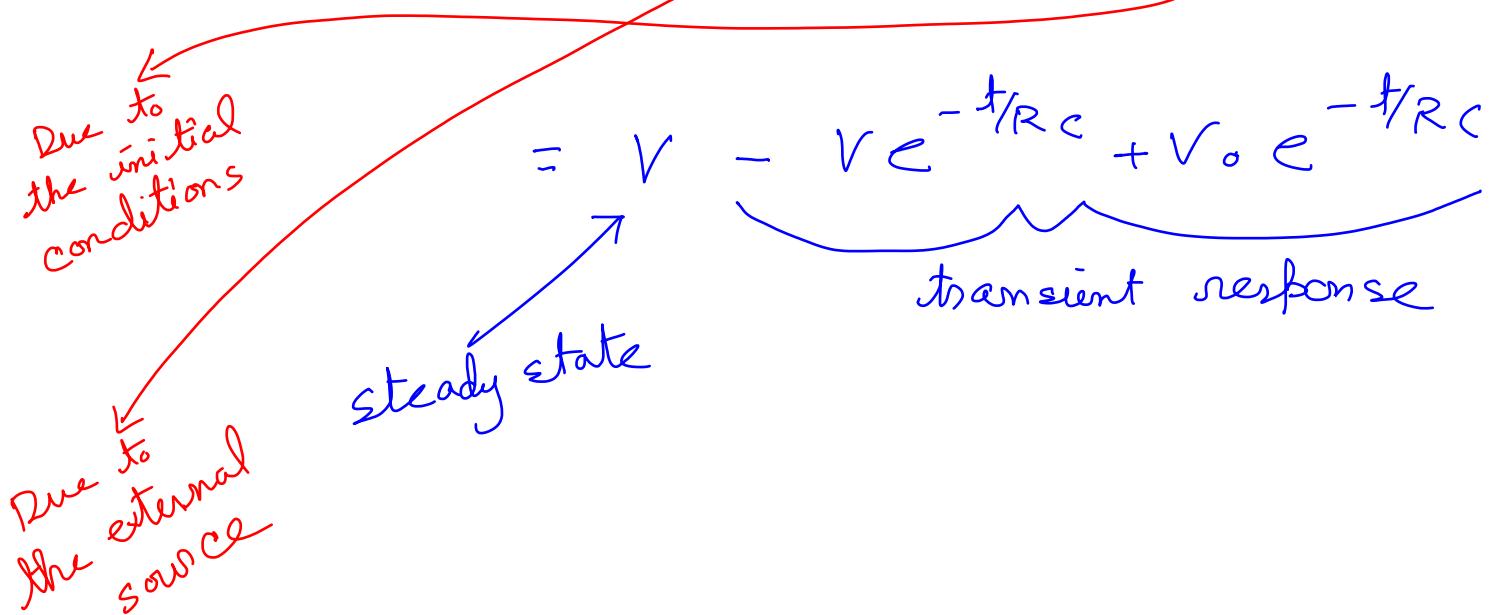
$$V_c(t) = \underbrace{V(1 - e^{-t/RC})}_{\text{Forced Response}} + \underbrace{V_0 e^{-t/RC}}_{\text{Natural Response}}$$



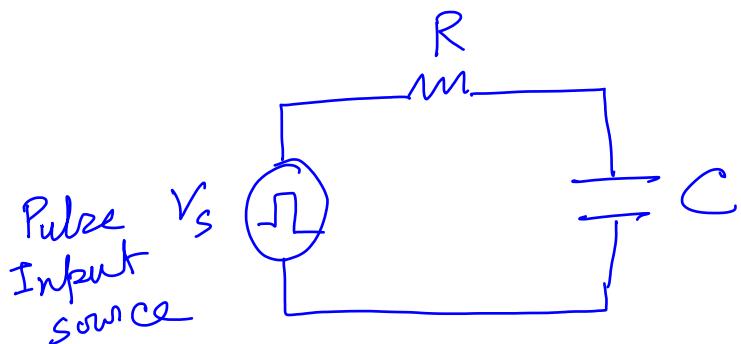\* Superposition principle can also be applied to derive the above.


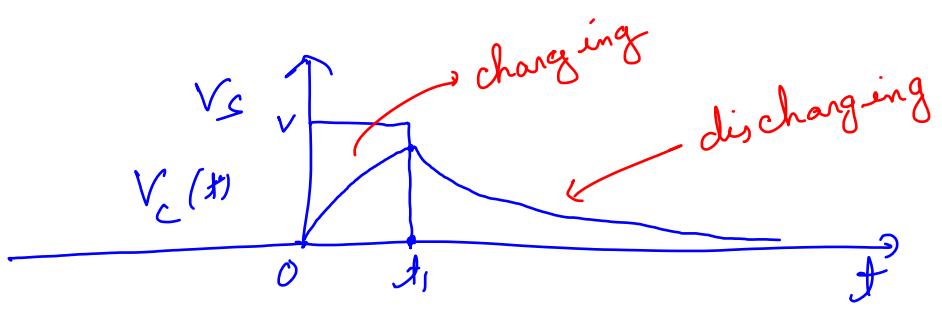
$$\begin{aligned} \rightarrow V_s &= V & 0 \leq t \leq t_1 \\ &= 0 & t > t_1 \end{aligned} \quad \left. \right\}$$




$$V_C(t) = V \left( 1 - e^{-t/RC} \right) \quad 0 \leq t \leq t_1$$

$$= \underbrace{V \left( 1 - e^{-t_1/RC} \right)}_{V_C(t_1)} e^{-\frac{(t-t_1)}{RC}} \quad t \geq t_1$$

Unit Step Function
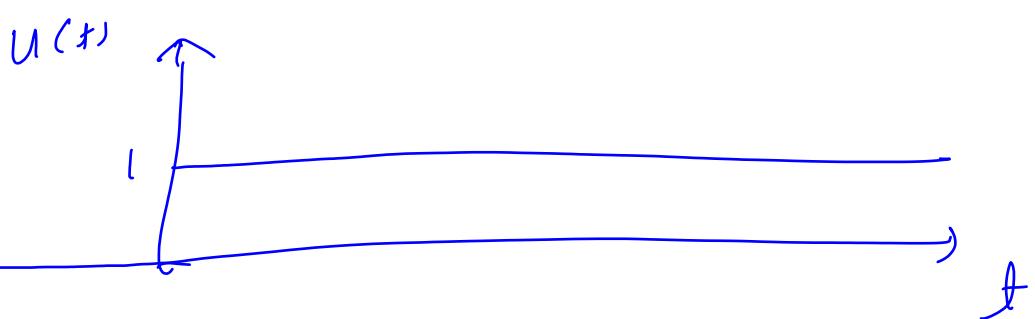
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$



$$V_S(t) = \underbrace{Vu(t)}_{\downarrow} - \underbrace{Vu(t-t_1)}_{\downarrow}$$

$$V_C(t) = V \left( 1 - e^{-t/RC} \right) u(t) - V \left( 1 - e^{-\frac{(t-t_1)}{RC}} \right) u(t-t_1)$$


$$f_{0n} \quad 0 \leq t \leq t_1$$

$$V_C(t) = V(1 - e^{-t/RC})$$


$$\underline{t \geq t_1}$$

$$\begin{aligned} V_C(t) &= V(1 - e^{-t/RC}) - V(1 - e^{-(t-t_1)/RC}) \\ &= V(e^{-(t-t_1)/RC} - e^{-t/RC}) \\ &= V e^{-(t-t_1)/RC} (1 - e^{-t_1/RC}) \end{aligned}$$

Q.1 (Midsem)

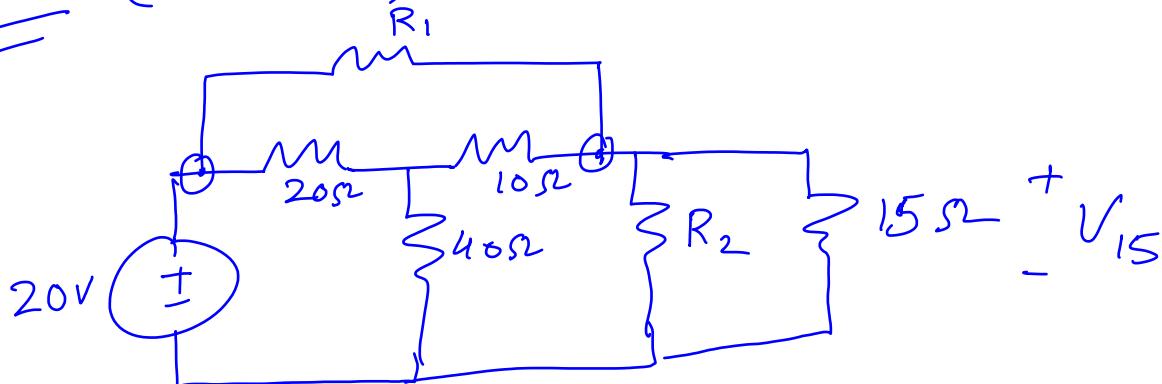

$$R_1 = 0 \Rightarrow V_{15} = 20$$

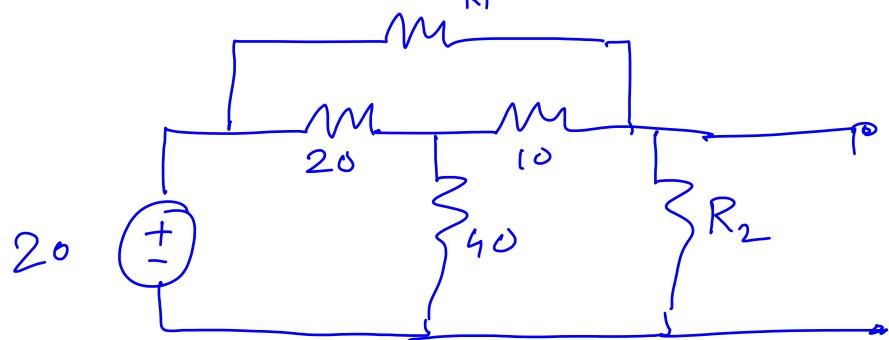

( $R_2$  can be any value, since  $V_{15}$  is independent of  $R_2$  when  $R_1 = 0$ )




$$P_{15} = \frac{V_{TH}^2}{(R_{TH} + 15)^2} \times 15$$

### Quick Recap

RC circuit       $\rightarrow$  charging      }  
                          $\rightarrow$  discharging }

Unit step function
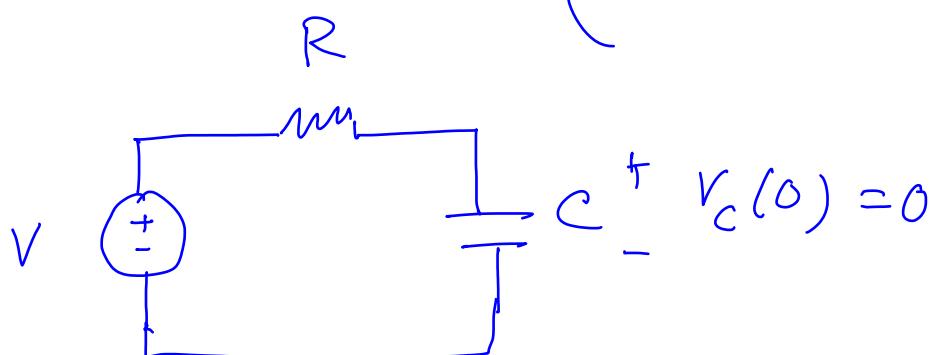
$$u(t) = \begin{cases} 0 & \forall t < 0 \\ 1 & \forall t \geq 0 \end{cases}$$



$$V_C(t) = V \left(1 - e^{-\frac{t}{RC}}\right)$$

time constant ( $T$ )


at  $t = T$ ,

$$V_C(t) \approx 63\% V$$

$$T = RC$$


$$\left. \frac{dV_C}{dt} \right|_{t=0} = \frac{V}{RC} e^{-\frac{t}{RC}} \Big|_{t=0} = \frac{V}{RC} = \frac{v}{T}$$

If the rate of change of  $V_C$  would have remained same as  $\left. \frac{dV_C}{dt} \right|_{t=0}$  for  $t > 0$ , the capacitor voltage would have reached  $V$  at  $t = T$ .

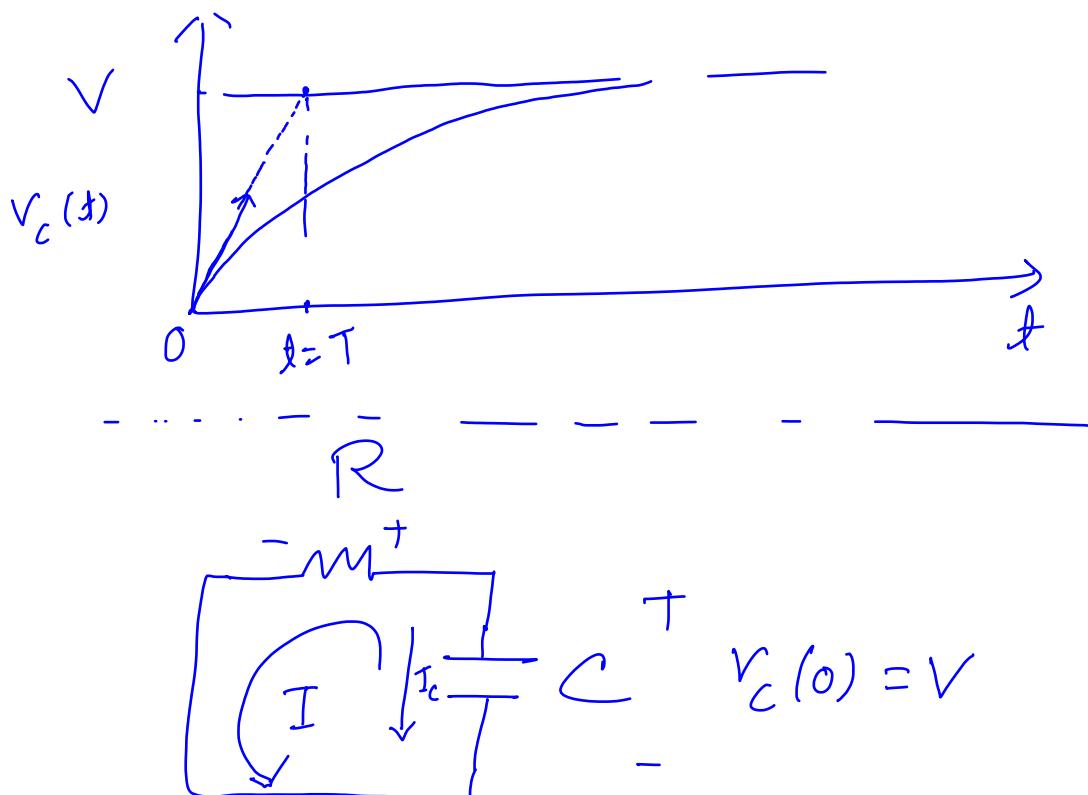


$$V_C(t) = V e^{-\frac{t}{RC}}$$

$$I_C = C \frac{dV_C}{dt} = -I$$

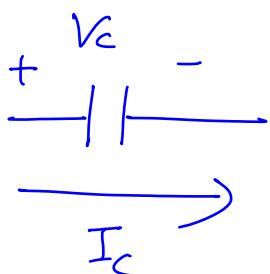


$$I_C = C \frac{dV_C}{dt}$$

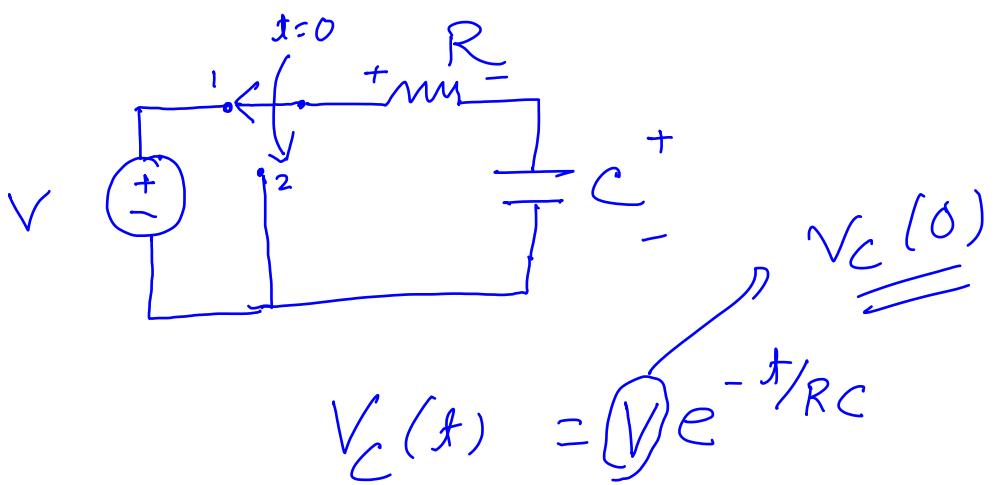


$$\underline{V_C(0-) = V \Rightarrow V_C(0+) = V \quad \text{if } I_C \neq \infty}$$

$\underset{\varepsilon \rightarrow 0}{\text{Let}} \quad V_C(0-\varepsilon) = \underset{\varepsilon \rightarrow 0}{V} \quad V_C(0+\varepsilon) \quad (\text{continuity property})$
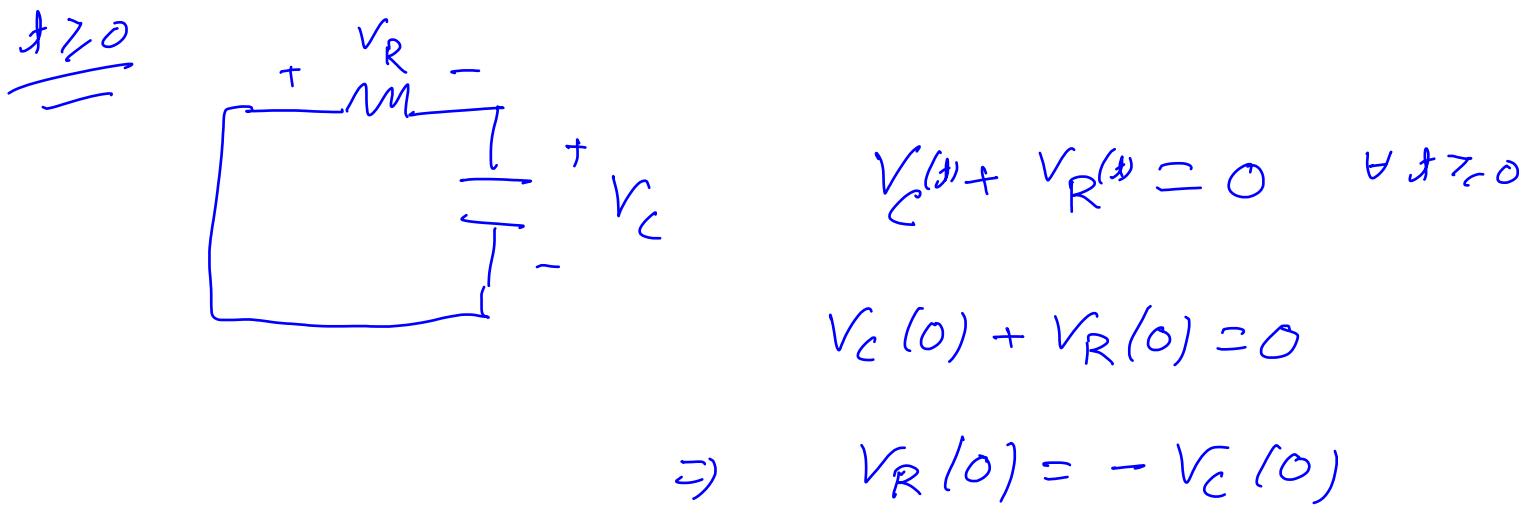
$$V_R(0-) = 0 \quad V_R(0+) = -V \quad (\text{discontinuous})$$





Let's consider the following circuit,

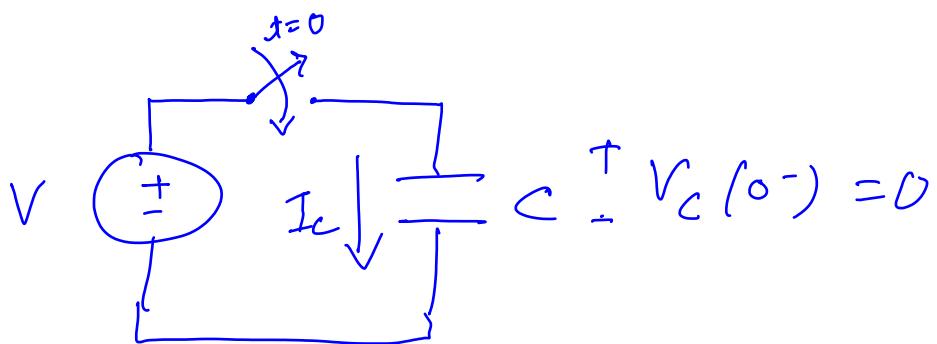

$$V_C(0^+) = V \quad (\text{using KVL})$$

$$I_C = C \frac{dV_C}{dt}$$

$$V_C(t) = V u(t)$$

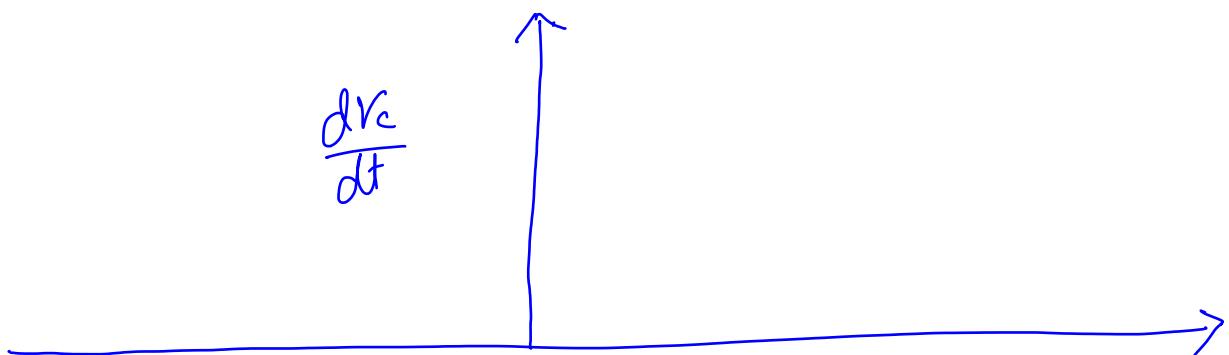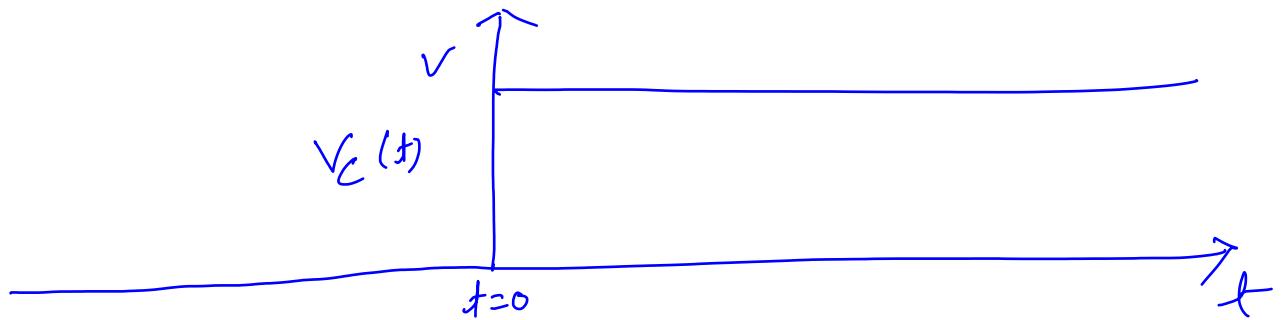


$$\text{1)} \quad \frac{dV_C}{dt} = 0 \quad \forall t \neq 0$$

2)  $\frac{dV_C}{dt}$  is not defined at  $t=0$

$$\int_{-\infty}^{\infty} \frac{dV_C}{dt} dt = V$$

## Dirac - delta function

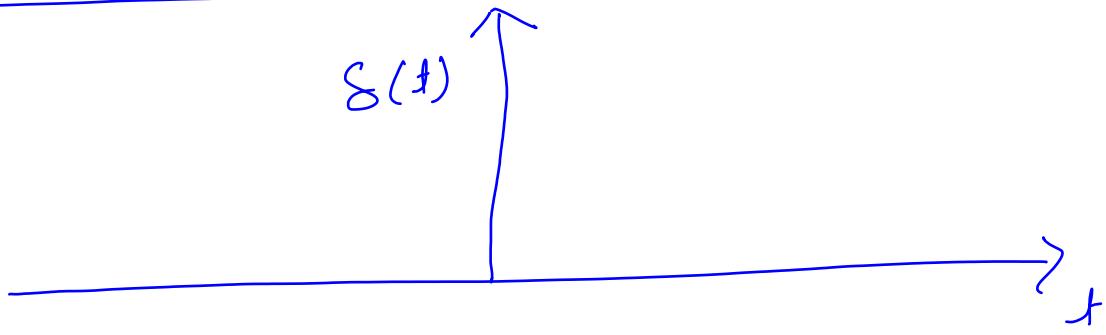

1)  $S(t) = 0 \quad \forall t \neq 0$

2)  $S(t)$  is not defined at  $t=0$

3)  $\int_{-\infty}^{\infty} S(t) dt = 1$

$$\Rightarrow \frac{d u(t)}{dt} = S(t)$$

$$u(t) = \int_{-\infty}^t S(t) dt$$

if  $t < 0$ ,


$$u(t) = \int_{-\infty}^t S(t) dt = 0$$

if  $t \geq 0$ ,

$$u(t) = \int_{-\infty}^t S(t) dt = \int_{-\infty}^{\infty} S(t) dt - \int_t^{\infty} S(t) dt$$

$$= 1 - 0 = 1$$

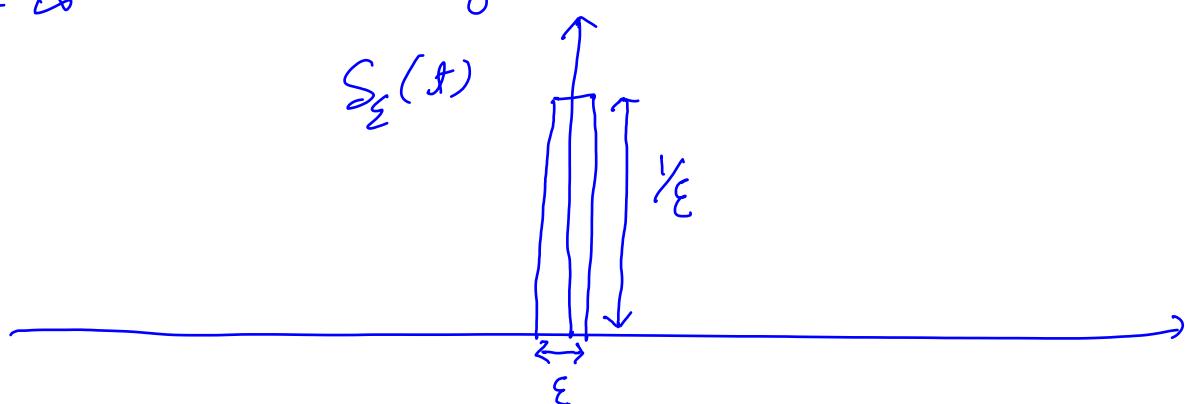
$$\int_{-\infty}^{+\infty} S(t) dt = \int_{0^-}^{0^+} S(t) dt = 1$$



$$S_\epsilon(t) = 0 \quad \forall t > \frac{\epsilon}{2} \text{ and } \forall t < -\frac{\epsilon}{2}$$


$$= \frac{1}{\epsilon} \quad -\frac{\epsilon}{2} \leq t \leq \frac{\epsilon}{2}$$
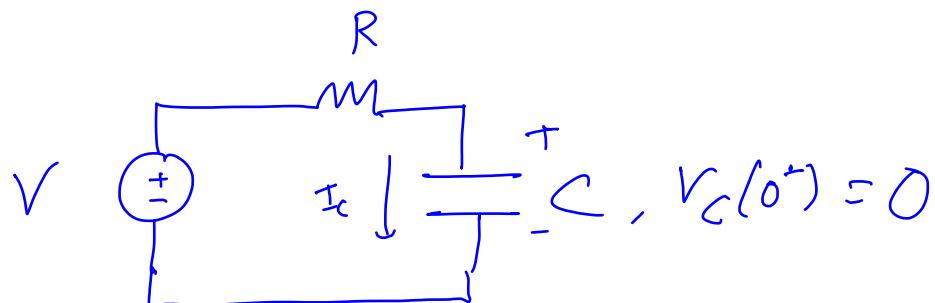
$$S(t) = \lim_{\epsilon \rightarrow 0} S_\epsilon(t)$$



$$V_C(t) = V \left( 1 - e^{-t/RC} \right) \quad \forall t \geq 0$$
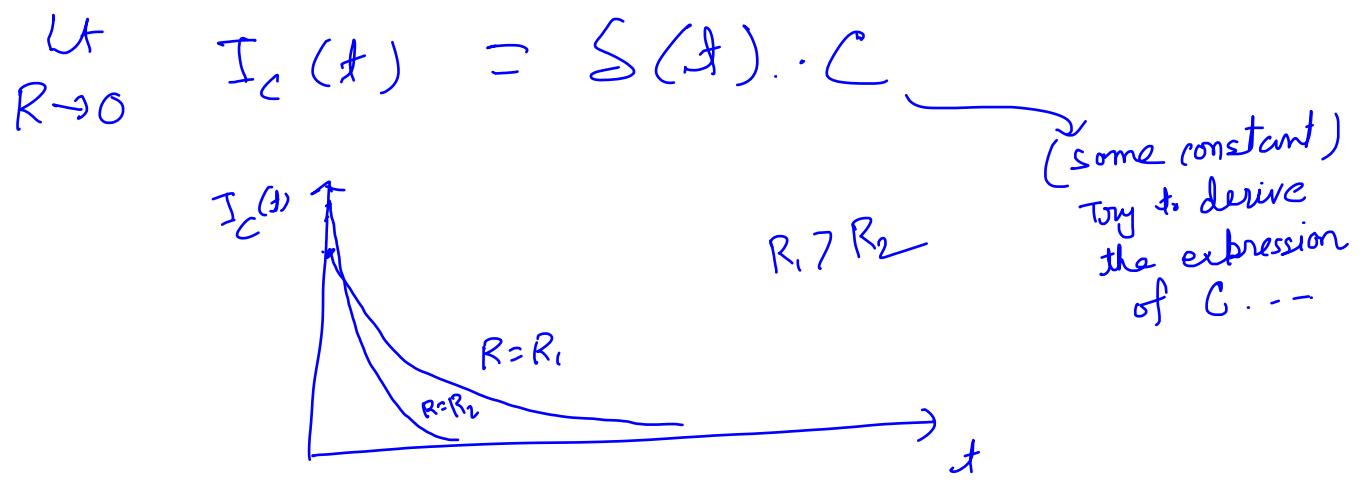
$$I_C(t) = C \frac{dV_C}{dt} = \frac{V}{R} e^{-t/RC}$$





## Quick Recap

Capacitors

$$C = \frac{\epsilon A}{d}$$

$\epsilon \rightarrow$  permittivity


$\epsilon_0 \rightarrow$  permittivity of free space  
( $8.854 \text{ pF/m}$ )

$$\epsilon = \epsilon_r \epsilon_0$$


↳ Relative permittivity

RC circuits ↳ charging  
↳ discharging

unit step function

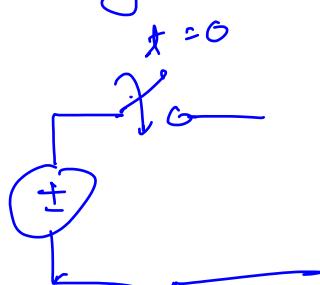

Dirac-delta (Impulse function)

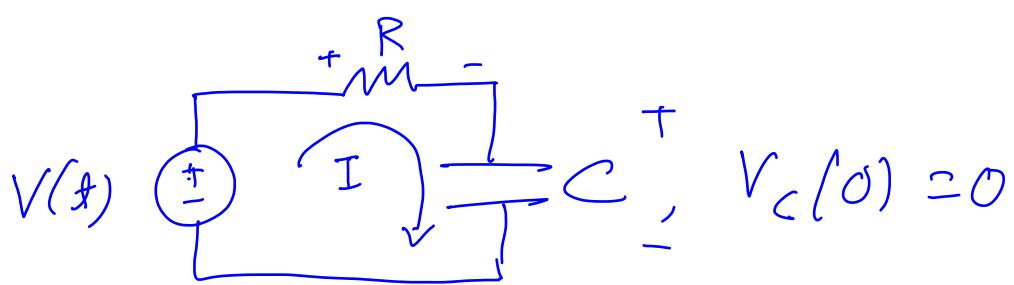

$$\begin{aligned} V(t) &= V_R(t) + \underline{V_C(t)} \\ &= \underline{\underline{I(t)R}} + \frac{1}{C} \int_0^t I(t) dt \end{aligned}$$

$$V(t) = R C \frac{dV_C}{dt} + V_C(t)$$

general structure of the problem,

$$\frac{dx}{dt} + P x = Q(t) \quad \left. \begin{array}{l} \forall t \geq 0 \\ x(0) = x_0 \end{array} \right\}$$

$$e^{Pt} \frac{dx}{dt} + P e^{Pt} x = e^{Pt} Q(t)$$

$$x_d(t) = e^{-Pt} \cdot x(t)$$

$$\begin{aligned} \frac{dx_d(t)}{dt} &= e^{Pt} \frac{dx}{dt} + P e^{Pt} x_d(t) \\ &= e^{Pt} Q(t) \end{aligned}$$

$$\frac{d\chi}{dt} = e^{Pt} Q(t)$$

$$\chi_d(t) = \chi_d(0) + \int_0^t e^{P\tau} Q(\tau) d\tau$$

$$\chi(t) = \underbrace{\chi_d(0) e^{-Pt}}_{\text{natural response}} + \underbrace{e^{-Pt} \int_0^t e^{P\tau} Q(\tau) d\tau}_{\text{forced response}}$$

$$\chi_d(t) = e^{Pt} \chi(t)$$

$$\chi_d(0) = \chi(0)$$

natural  
response

forced  
response


$$\checkmark \quad \frac{d\chi}{dt} + P\chi(t) = Q(t) \quad \chi(0) = \chi_0$$

$$\chi(t) = \chi_n(t) + \chi_f(t)$$

natural response      forced response

$$\frac{d\chi_n}{dt} + P\chi_n(t) = 0 \quad \chi_n(0) = \chi_0$$
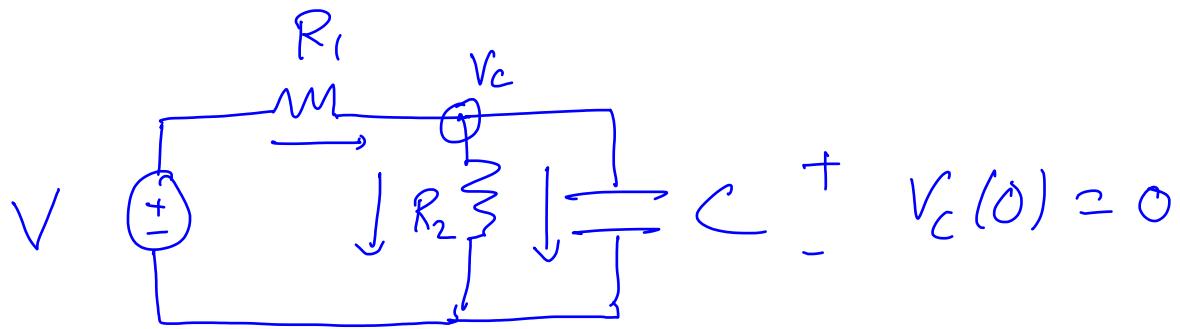
$$\frac{d\chi_f}{dt} + P\chi_f(t) = Q(t) \quad \chi_f(0) = 0$$



$$\frac{V - V_c}{R_1} = \frac{V_c}{R_2} + C \frac{dV_c}{dt}$$

$$\frac{V}{R_1} = V_c \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + C \frac{dV_c}{dt}$$

$$\frac{V}{R_1} = V_c \cdot \frac{1}{R_{eq}} + C \frac{dV_c}{dt}$$

$$\underbrace{\frac{R_{eq} V}{R_1}}_{= V_c} = V_c + R_{eq} C \frac{dV_c}{dt}$$



$$V_c(t) = \frac{R_{eq} V}{R_1} \left( 1 - e^{-\frac{t}{R_{eq} C}} \right)$$

$$= \frac{V}{R_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)} \left( 1 - e^{-\frac{t}{R_{eq} C}} \right)$$

$$= \frac{R_2 V}{R_1 + R_2} \left( 1 - e^{-\frac{t}{R_{eq} C}} \right)$$

$\downarrow$
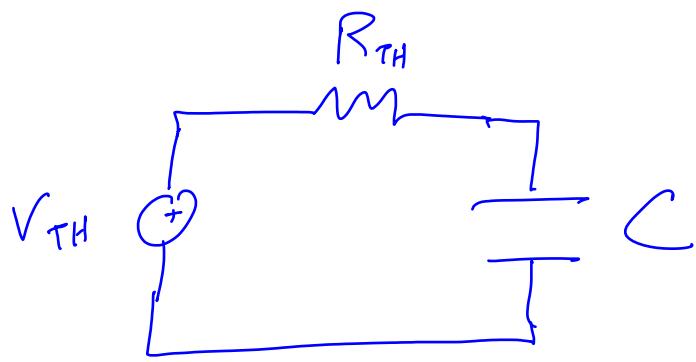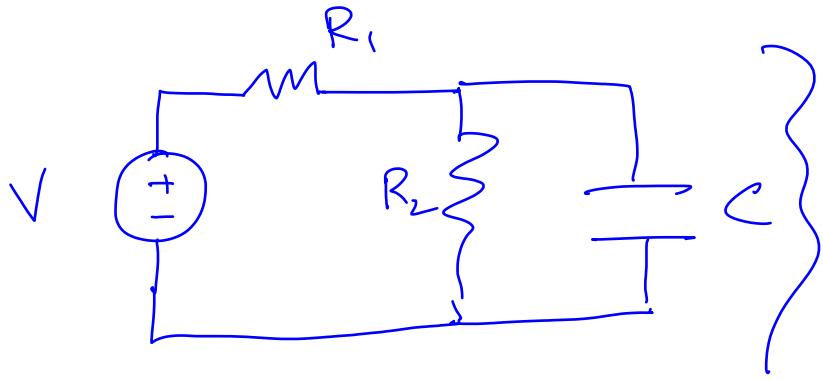
$$V_{Tf} = \frac{R_2 V}{R_1 + R_2} e^{-\frac{t}{R_{eq} C}}$$




$$V_{TH} = \frac{R_2 V}{R_1 + R_2}$$

$$R_{TH} = (R_1 \parallel R_2)$$

$$= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

Induction (L)

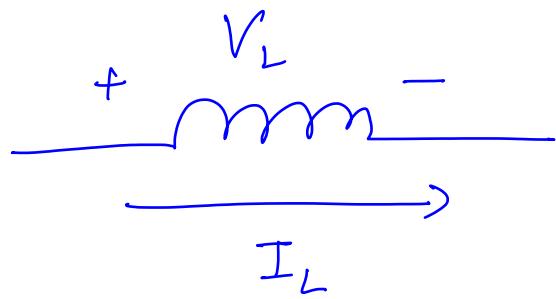

$$V_L = L \frac{dI_L}{dt}$$

Inductance (Henry)

Faraday's Law

$$V \propto \frac{d\psi}{dt}$$

$\psi \rightarrow$  magnetic flux linkage

$$\mathcal{V} = N\phi \quad \begin{array}{l} \xrightarrow{\hspace{1cm}} \text{magnetic flux} \\ \xrightarrow{\hspace{1cm}} \text{no. of turns} \end{array}$$

$$\mathcal{V} = L i$$


$$L = \frac{N^2 \mu A}{l} \quad \left. \begin{array}{l} \text{Solenoid} \\ (\text{thin and very long coil}) \end{array} \right\}$$

$$\begin{array}{l} \mu \rightarrow \text{permeability} \\ A \rightarrow \text{area of the core} \\ l \rightarrow \text{length} \end{array} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\}$$

$$\mu = \mu_r \mu_0 \quad \mu_0 \rightarrow 4\pi \times 10^{-7} \text{ H/m}$$

(free space)

Natural Response of a RL circuit

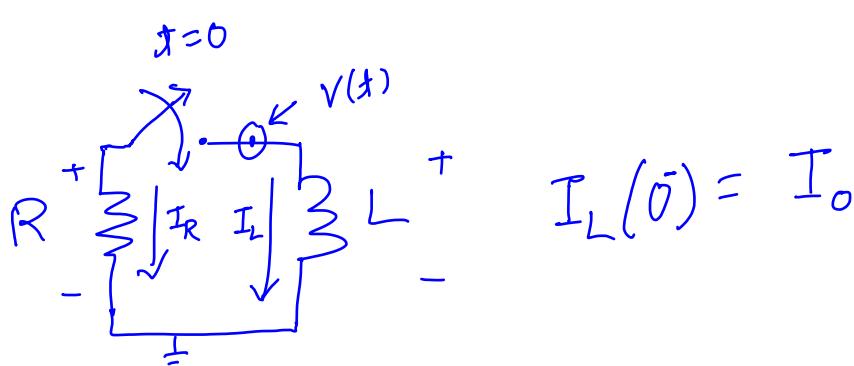

$$V_C(t^-) = V_C(t^+) \quad \text{if} \quad I_C(t) \neq 0$$

$$I_L(t^-) = I_L(t^+) \quad \text{if} \quad V_L(t) \neq 0$$

(continuity of Inductor current)


Applying KVL,

$$I_L(t) + I_R(t) = 0 \quad \forall t \geq 0$$

$$I_L(t) + \frac{V(t)}{R} = 0$$

$$I_L(t) + \frac{L}{R} \frac{dI_L(t)}{dt} = 0$$
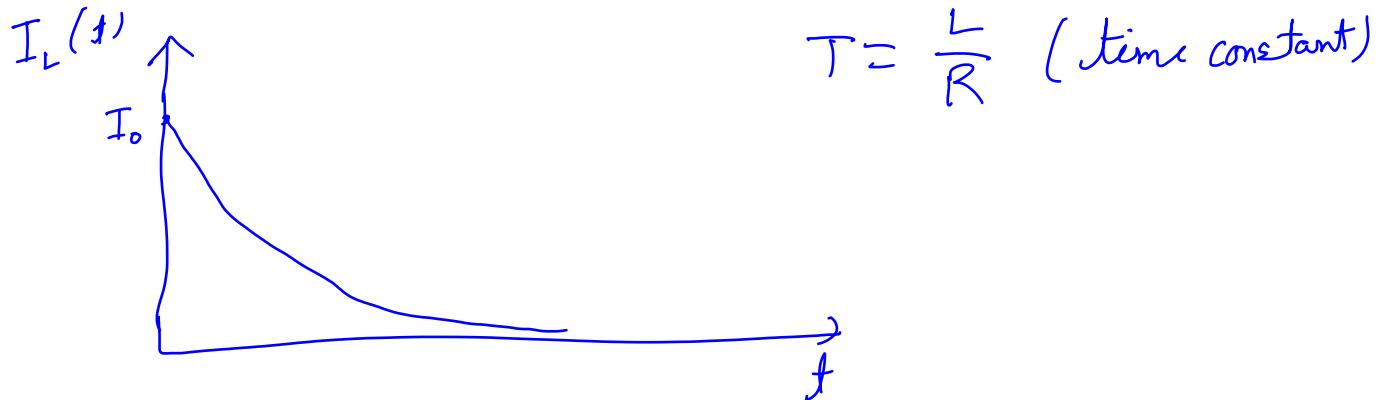
$$\begin{aligned} I_L(t) &= I_L(0) e^{-\frac{R}{L}t} \\ &= I_0 e^{-\frac{R}{L}t} \\ &= I_0 e^{-t/T} \end{aligned}$$



$$V_L(t) = L \frac{di_L(t)}{dt} = -\frac{L}{T} I_0 e^{-t/T}$$

$$V_L(t) = -(RI_0) e^{-t/T}$$

$$I_L(0^-) = I_0 \quad \text{or} \quad I_L(0) = I_0$$

$$I_L(t) + I_R(t) = 0 \quad \forall t \geq 0$$

$$\Rightarrow I_R(0) = -I_L(0)$$

$$= -I_0$$


$$V_R(0) = R I_R(0) = -I_0 R$$

$$V_L(t) = V_R(t) \quad \forall t \geq 0$$

$$V_L(0) = -I_0 R$$
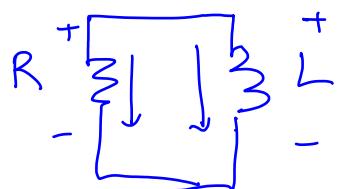
## Quick Recap

- Capacitors
- RC circuit
- Inductor
- RL circuit (natural response)



$$I_L(0) = I_0$$

$$I_L(t) = I_0 e^{-\frac{R}{L}t}, \quad \forall t \geq 0$$

$$E_R = \int_0^\infty V_R I_R dt$$

$$V_R = V_L$$

$$I_L + I_R = 0$$

$$= - \int_0^\infty V_L I_L dt$$

$$V_L = L \frac{dI_L}{dt}$$

$$= I_0 L e^{-\frac{R}{L}t} \times (-R/L)$$

$$= - \int_0^\infty -(I_0 R) e^{-\frac{R}{L}t} \times I_0 e^{-\frac{R}{L}t} dt$$


$$= -I_0 R e^{-\frac{R}{L}t}$$

$$= I_0^2 R \int_0^\infty e^{-\frac{2R}{L}t} dt$$

$$= \frac{1}{2} L I_0^2$$

$$E_L = \int_0^\infty V_L I_L dt = -\frac{1}{2} L I_0^2$$

Forced Response of RL circuit,

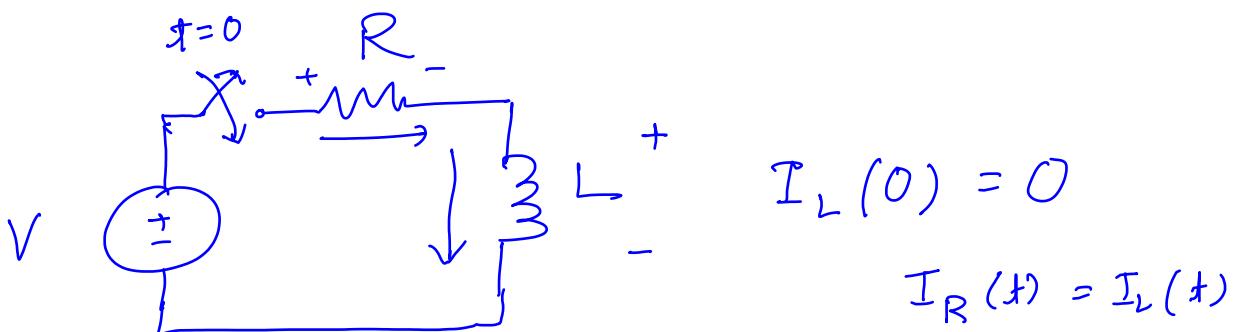

$$V = V_R(t) + V_L(t), \quad \forall t \geq 0$$

$$V = I_L(t) R + L \frac{d I_L(t)}{dt}, \quad \forall t \geq 0$$

$$I_L(t) = I_{L,ss} + I_{L,Tr}(t)$$

$$I_{L,ss} = A_1 \quad (\text{constant})$$

$$I_{L,Tr}(t) = A_2 e^{st}$$

$$I_L(t) = A_1 + A_2 e^{st}$$

$$V = (A_1 + A_2 e^{st}) R + L A_2 s e^{st}. \quad \forall t \geq 0$$

$$V = A_1 R + A_2 e^{st} R + L A_2 s e^{st} \quad \forall t \geq 0$$

2)

$$\text{and } V = A_1 R$$

$$A_2 e^{st} R + L A_2 s e^{st} = 0 \quad \forall t \geq 0$$

$$A_1 = \frac{V}{R}$$

$$A_2 e^{st} (R + Ls) = 0 \quad \forall t \geq 0$$

$$R + LS = 0$$

$$\Rightarrow S = -\frac{R}{L}$$

$$i_L(0) = A_1 + A_2 e^{so} = 0$$

$$\Rightarrow A_1 + A_2 = 0$$

$$\Rightarrow A_2 = -A_1 = -\frac{V}{R}$$


$$i_L(t) = A_1 + A_2 e^{st}$$

$$= \frac{V}{R} - \frac{V}{R} e^{-\frac{R}{L}t}$$

$$= \frac{V}{R} (1 - e^{-\frac{R}{L}t}) \quad \forall t \geq 0$$

$$i_L(\infty) = \frac{V}{R}$$

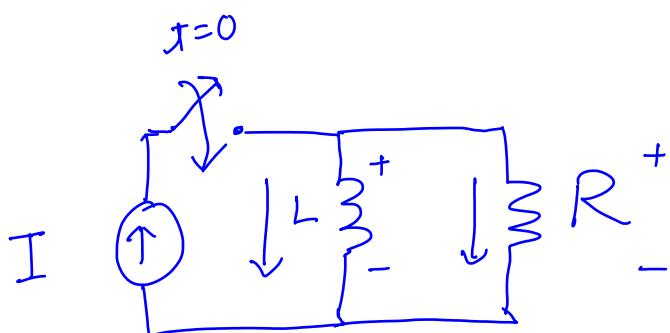$\Rightarrow$  At steady state, inductor acts as short circuit  
 $(V_L(\infty) = 0)$



$$I_L(0) = I_0$$

$$I_R(\infty) = 0 ?$$

$$V_L(0) =$$

$$\checkmark V_L(t) = V_R(t) \quad \forall t \geq 0$$

$$I = I_L(t) + I_R(t) \quad \forall t \geq 0$$


$$\begin{aligned} \Rightarrow I &= I_L(0) + I_R(0) \\ &= I_0 + I_R(0) \end{aligned}$$

$$\Rightarrow I_R(0) = I - I_0$$

$$V_R(0) = R I_R(0) = R(I - I_0)$$

$$\Rightarrow V_L(0) = R(I - I_0)$$

# RLC circuits

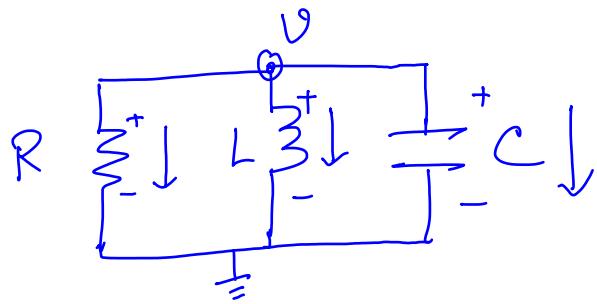

natural response

$$I_L(0) = I_0$$

$$V_C(0) = V_0$$

$$\xrightarrow{KCL} I_R(t) + I_L(t) + I_C(t) = 0 \quad \forall t \geq 0$$

$$V_R(t) = V_L(t) = V_C(t) = V(t)$$

$$\frac{V(t)}{R} + \underbrace{\frac{1}{L} \int_0^t V_L(s) ds + I_L(0)}_{I_L(t)} + C \frac{dV}{dt} = 0 \quad \forall t \geq 0$$

$$\left( \begin{array}{c} \text{+} \\ \text{---} \\ \text{-} \end{array} \right)$$

$$V_L = L \frac{di_L}{dt}$$

$$i_L(t) = \frac{1}{L} \int_0^t V_L(s) ds + i_L(0)$$

Integro-differential equation,

$$\frac{V(t)}{R} + \frac{1}{L} \int_0^t V(s) ds + i_L(0) + C \frac{dV}{dt} = 0$$

Differentiate both sides — — —

$$\frac{1}{R} \frac{dU}{dt} + \frac{U(t)}{L} + C \frac{d^2U}{dt^2} = 0 \quad (\text{second-order differential equation})$$

$$U(t) = A e^{st} \quad (\text{Assumption})$$

$$\frac{1}{R} A s e^{st} + \frac{A e^{st}}{L} + C s^2 A e^{st} = 0, \quad \forall t \geq 0$$

$$A e^{st} \left( \frac{1}{R} \cdot s + \frac{1}{L} + C s^2 \right) = 0, \quad \forall t \geq 0$$

$$\Rightarrow C s^2 + \frac{1}{R} s + \frac{1}{L} = 0 \rightarrow (\text{characteristic equation})$$

$$\Rightarrow C \left( s^2 + \frac{1}{RC} s + \frac{1}{LC} \right) = 0$$

$$\Rightarrow s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$\Rightarrow s^2 + 2s \cdot \frac{1}{2RC} + \left( \frac{1}{2RC} \right)^2 + \frac{1}{LC} - \left( \frac{1}{2RC} \right)^2 = 0$$

$$\Rightarrow \left( s + \frac{1}{2RC} \right)^2 = \left( \frac{1}{2RC} \right)^2 - \frac{1}{LC}$$

$$\Rightarrow s + \frac{1}{2RC} = \pm \sqrt{\left( \frac{1}{2RC} \right)^2 - \frac{1}{LC}}$$

$$\Rightarrow s = -\frac{1}{2RC} \pm \sqrt{\left( \frac{1}{2RC} \right)^2 - \frac{1}{LC}}$$

$$S_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$S_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

two roots


So, general structure of the natural response,

$$v(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$


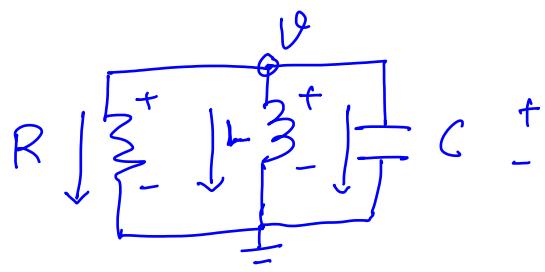
### Quick Recap

- natural response of a parallel RLC circuit



$$V_R = V_C = V_L = V, \forall t \geq 0$$

$$I_R + I_L + I_C = 0 \quad \forall t \geq 0$$

$$V_C(0) = V_0, \quad I_L(0) = I_0$$

$$C \frac{d^2 V}{dt^2} + \frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V = 0$$

↗

$$V(t) = A e^{st} \quad (\text{Assumption})$$

$$Cs^2 + \frac{1}{R}s + \frac{1}{L} = 0 \quad (\text{characteristic eq.})$$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$\alpha \rightarrow$  decay rate ,  $\omega_0 \rightarrow$  resonant frequency

$$\alpha = \frac{1}{2RC}, \quad \omega_0^2 = \frac{1}{LC}$$

$$V(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t} \quad (\text{general structure})$$

$A_1, A_2, S_1, S_2 \rightarrow (\text{complex numbers})$

$(\alpha > \omega_0) \rightarrow \text{Overshadowed System}$

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\Rightarrow \text{real roots} \quad S_1 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} < 0$$

$$\alpha > \sqrt{\alpha^2 - \omega_0^2} \Rightarrow S_2 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} < 0$$

negative real roots

$$V(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t} \quad \checkmark$$

$\Rightarrow A_1$  and  $A_2$  are real numbers.

$$V(0) = V_C(0) = V_0$$

$t=0$

$$V_0 = A_1 + A_2 \quad \text{---} \quad (1)$$

$$\frac{dV}{dt} = A_1 S_1 e^{S_1 t} + A_2 S_2 e^{S_2 t}$$

$$I_R(t) + I_L(t) + I_C(t) = 0 \quad \forall t \geq 0$$

$$I_R(0) + I_L(0) + I_C(0) = 0$$

$$I_R(0) = \frac{V_R(0)}{R} = \frac{V(0)}{R} = \frac{V_0}{R}$$


$$\begin{aligned} I_C(0) &= -I_R(0) - I_L(0) \\ &= -\frac{V_0}{R} - I_0 \end{aligned}$$

$$\frac{dV(0)}{dt} = \frac{dV_C(0)}{dt} = \frac{1}{C} I_C(0) = -\frac{1}{C} \left( I_0 + \frac{V_0}{R} \right)$$

$$\begin{aligned} \frac{dV}{dt} &= A_1 S_1 e^{S_1 t} + A_2 S_2 e^{S_2 t} \\ \downarrow t=0 & \\ -\frac{1}{C} \left( I_0 + \frac{V_0}{R} \right) &= A_1 S_1 + A_2 S_2 \quad \text{--- (ii)} \end{aligned}$$

Solve for  $A_1$  and  $A_2$  from (i) and (ii).
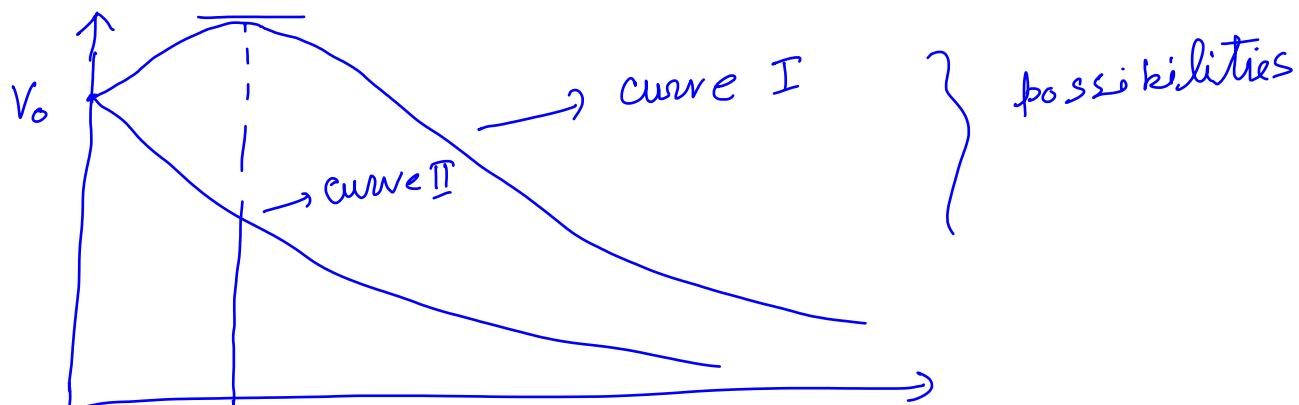
$$V(\infty) = 0 \quad \text{because} \quad S_1, S_2 < 0$$




$(\alpha < \omega_0) \rightarrow$  Underdamped System

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -\alpha \pm \sqrt{(-1)(\omega_0^2 - \alpha^2)}$$
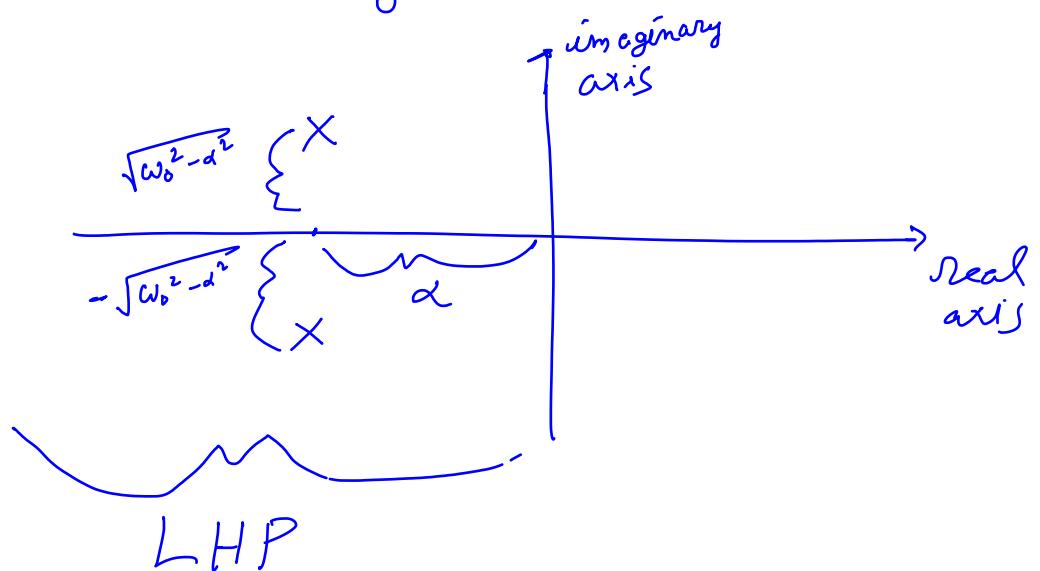
$$= -\alpha \pm j\sqrt{(\omega_0^2 - \alpha^2)}, \quad (j = \sqrt{-1})$$



$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\therefore S_{1,2} = -\alpha \pm j\omega_d$$

$$\Rightarrow v(t) = e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t})$$

$$A_1 = \gamma_1 + j\delta_1$$

$$A_2 = \gamma_2 + j\delta_2$$

$$V(t) = e^{-\alpha t} \left( (\gamma_1 + j\delta_1) e^{j\omega_d t} + (\gamma_2 + j\delta_2) e^{-j\omega_d t} \right)$$

$$= e^{-\alpha t} \left( (\gamma_1 + j\delta_1) (\cos \omega_d t + j \sin \omega_d t) + (\gamma_2 + j\delta_2) (\cos \omega_d t - j \sin \omega_d t) \right)$$

$$V(0) = (\gamma_1 + j\delta_1) + (\gamma_2 + j\delta_2)$$

$$= (\gamma_1 + \gamma_2) + j(\delta_1 + \delta_2)$$

$$\Rightarrow \delta_1 + \delta_2 = 0 \quad \checkmark$$

$$\delta_1 = \delta \quad \therefore \quad \delta_2 = -\delta$$

$$V(t) = e^{-\alpha t} \left( A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t} \right)$$

$$\begin{aligned} \frac{dV(t)}{dt} &= -\alpha e^{-\alpha t} \left( A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t} \right) \\ &\quad + e^{-\alpha t} \left( A_1 j\omega_d e^{j\omega_d t} - A_2 j\omega_d e^{-j\omega_d t} \right) \end{aligned}$$

$$\frac{dV(0)}{dt} = -\alpha (A_1 + A_2) + A_1 j\omega_d - A_2 j\omega_d$$

$$= -\alpha(\gamma_1 + j\beta + \gamma_2 - j\beta) + (\gamma_1 + j\beta) \cdot j\omega_d \\ - (\gamma_2 - j\beta) j\omega_d$$

$$= -\alpha(\gamma_1 + \gamma_2) + j\omega_d(\gamma_1 - \gamma_2) \\ - s\omega_d - s\omega_d$$

$$= -\alpha(\gamma_1 + \gamma_2) - 2s\omega_d + j\omega_d(\gamma_1 - \gamma_2)$$

$$\Rightarrow \gamma_1 - \gamma_2 = 0$$

$$\Rightarrow \gamma_1 = \gamma_2 = \gamma$$

$$\begin{aligned} A_1 &= \gamma + j\beta \\ A_2 &= \gamma - j\beta \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} \begin{array}{l} \text{Complex} \\ \text{conjugates} \end{array}$$

$$\begin{aligned} v(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ &= e^{-\alpha t} \left( A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t} \right) \\ &= e^{-\alpha t} \left( A_1 \cos \omega_d t + j A_1 \sin \omega_d t \right. \\ &\quad \left. + A_2 \cos \omega_d t - j A_2 \sin \omega_d t \right) \end{aligned}$$


$$= e^{-\alpha t} \left( \underbrace{(A_1 + A_2)}_{2\gamma} \cos \omega_d t + \underbrace{j(A_1 - A_2)}_{-2s} \sin \omega_d t \right)$$

$$v(t) = e^{-\alpha t} \left( A_d \cos \omega_d t + B_d \sin \omega_d t \right)$$

$A_d, B_d$  are real numbers

$$(A_d = 2Y, B_d = -2S)$$

$$v(\infty) = 0$$

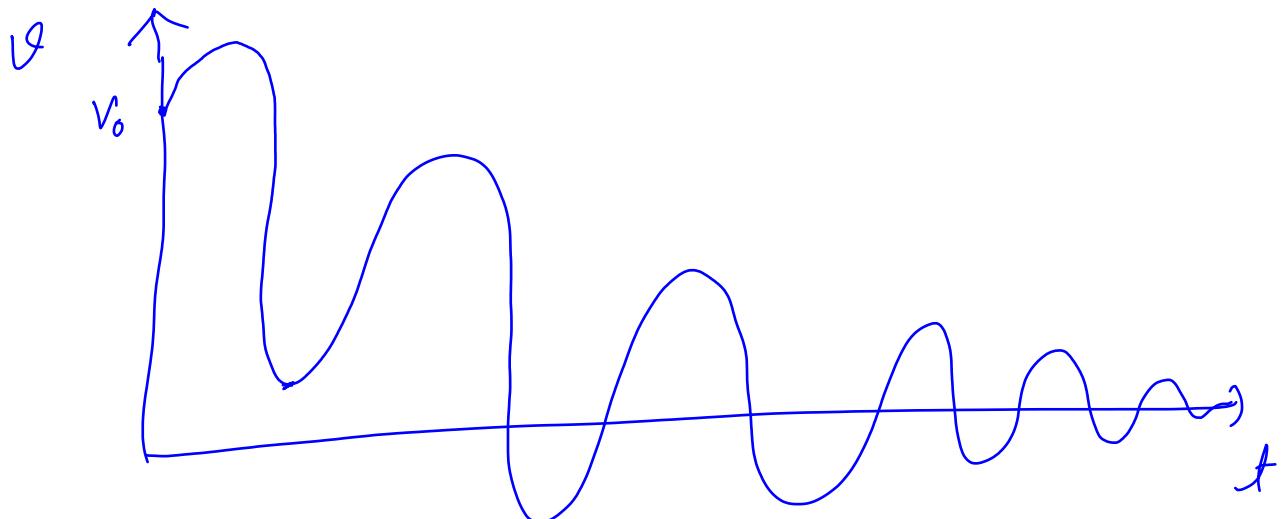


$\alpha = \omega_0$   $\rightarrow$  (critically damped)

$$C \frac{d^2v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$\alpha = \frac{1}{2RC}, \quad \omega_0^2 = \frac{1}{LC}$$
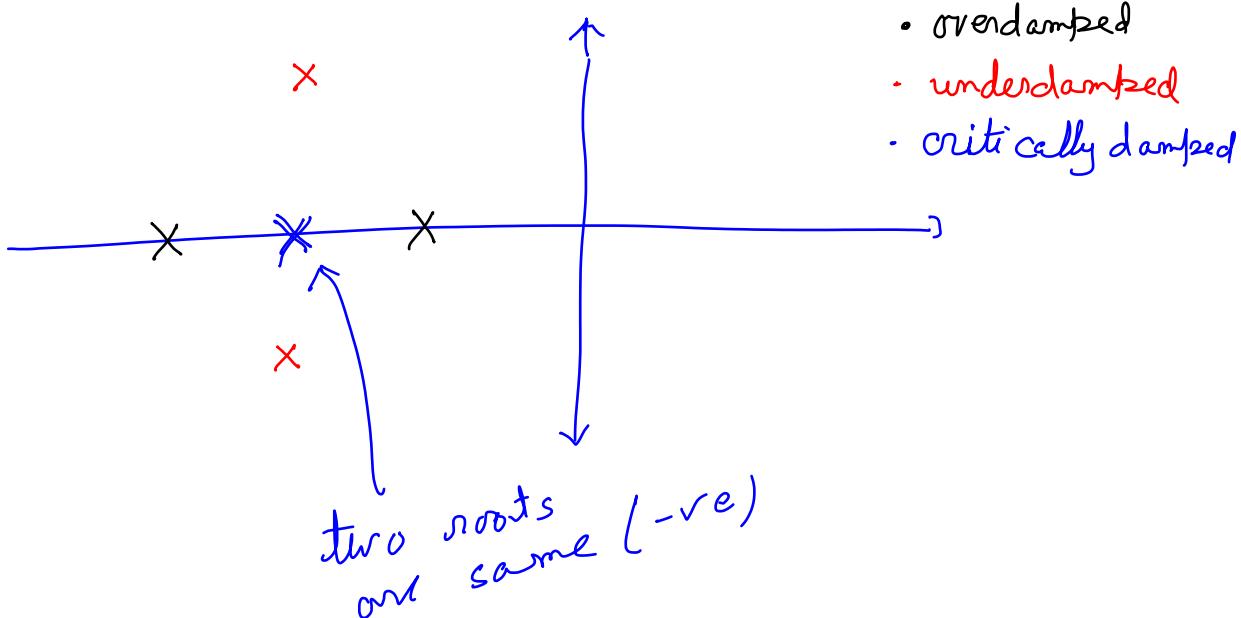
$$\frac{d^2v}{dt^2} + 2\alpha \frac{dv}{dt} + \alpha^2 v = 0$$



$$\zeta_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -\alpha \quad (\text{since } \alpha = \omega_0)$$

Let's assume,

$$V(t) = A_2 e^{st} \quad \begin{matrix} \leftarrow \\ \text{It's a valid solution} \end{matrix}$$

but, only unknown  $A_2$ , however, we have  
two initial conditions.

$$V(t) = A_1 t e^{st} \quad \begin{matrix} \leftarrow \\ (\text{Assumption}) \end{matrix}$$

This is also  
a valid  
solution

$$\frac{dV(t)}{dt} = A_1 t s e^{st} + A_1 e^{st}$$

$$\frac{d^2V}{dt^2} = A_1 t s^2 e^{st} + A_1 s e^{st} + A_1 s e^{st}$$

$$\frac{d^2v}{dt^2} + 2\alpha \frac{dv}{dt} + \alpha^2 v$$

$$\begin{aligned}
 &= A_1 t s^2 e^{st} + A_1 s e^{st} + A_1 s e^{st} \\
 &\quad + 2\alpha (A_1 t s e^{st} + A_1 e^{st}) + \alpha^2 A_1 t e^{st} \\
 &= A_1 t \cancel{\alpha^2} e^{-\alpha t} - A_1 \alpha \cancel{e^{-\alpha t}} - A_1 \alpha \cancel{e^{-\alpha t}} \\
 &\quad + 2\alpha (-A_1 t \cancel{\alpha} e^{-\alpha t} + A_1 \cancel{e^{-\alpha t}}) + \alpha^2 A_1 t \cancel{e^{-\alpha t}} \\
 &= 0
 \end{aligned}$$

general solution

$$v(t) = A_1 t e^{st} + A_2 e^{st}$$



$$\begin{aligned}
 &= e^{st} (A_1 t + A_2) \\
 &= e^{-\alpha t} (A_1 t + A_2)
 \end{aligned}$$


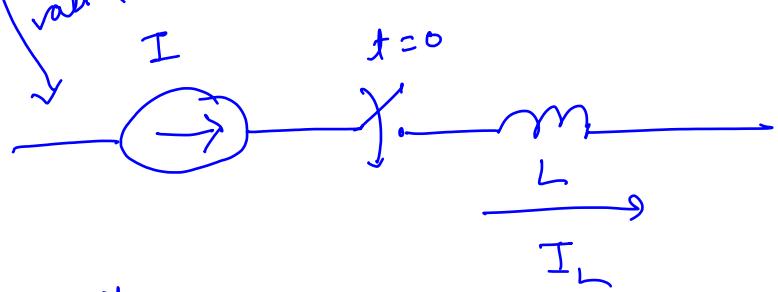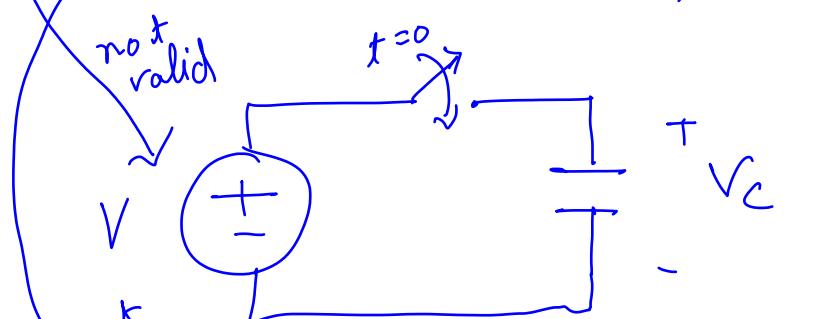
### Quick Recap

$$V_C(t^-) = V_C(t^+), \text{ provided } I_C(t) \neq \infty$$

$$I_L(t^-) = I_L(t^+), \text{ provided } V_L(t) \neq \infty$$



circuits involving dc sources

$$I_C(\infty) = 0 \quad \left( \begin{array}{l} \text{at } t \rightarrow \infty \\ I_C(t) = 0 \end{array} \right)$$

$$V_L(\infty) = 0$$


# RLC circuit (parallel)

→ natural response {

overdamped

underdamped

critically damped

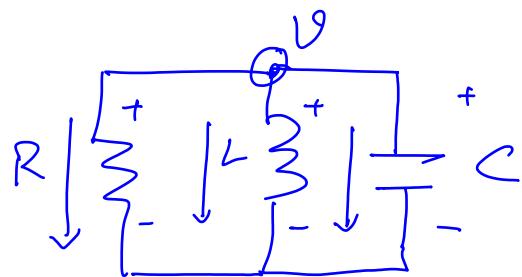

$$V_C(0) = V_0$$

$$I_L(0) = I_0$$


natural response,

$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{overdamped})$$

$$V(t) = e^{-\alpha t} (A_d \sin \omega_d t + B_d \cos \omega_d t) \quad (\text{underdamped})$$

$$V(t) = A_1 e^{s_+ t} + A_2 e^{s_- t} = e^{st} (A_1 t + A_2) \quad (\text{critically damped system})$$

Forced Response of RLC circuit,

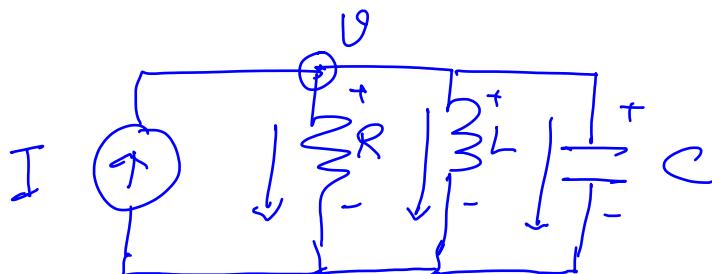

$$\left. \begin{aligned} V_C(0) &= V_0 \\ I_L(0) &= I_0 \end{aligned} \right\}$$

$$V(t) = V_f(t) + V_n(t)$$

$$\frac{d^2V}{dt^2} + 2\alpha \frac{dV}{dt} + \omega_0^2 V = \bar{V}$$

$$\left. \begin{aligned} V(0) &= V_0 \\ \frac{dV(0)}{dt} &= \dot{V}_0 \end{aligned} \right\}$$

$$\frac{d^2V_f}{dt^2} + 2\alpha \frac{dV_f}{dt} + \omega_0^2 V_f = \bar{V}$$

$$V_f(0) = 0$$

$$\frac{dV_f(0)}{dt} = 0$$

$$\checkmark \quad \frac{d^2V_n}{dt^2} + 2\alpha \frac{dV_n}{dt} + \omega_0^2 V_n = 0$$

$$V_n(0) = V_0$$

$$\frac{dV_n(0)}{dt} = \dot{V}_0$$


$$V(t) = V_f(t) + V_n(t)$$

$$= V_{ss} + V_T(t)$$

$$\left. \begin{aligned} & A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ & A_1 t e^{s_1 t} + A_2 t e^{s_2 t} \\ & \vdots \end{aligned} \right\}$$

$$V(t) = V_{SS} + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{overdamped case})$$

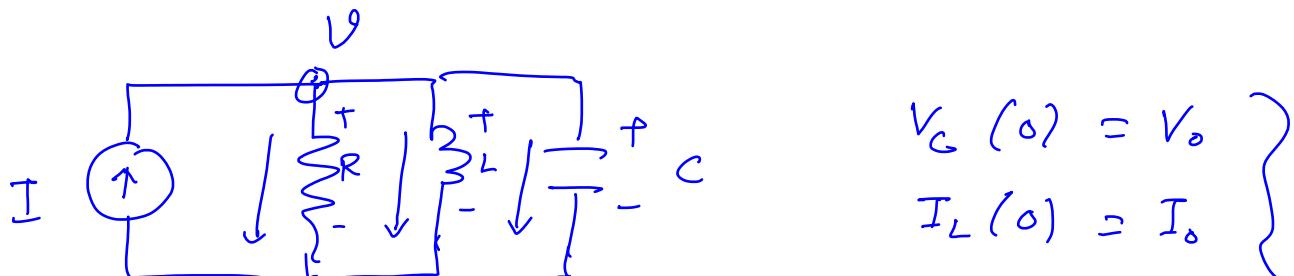✓  $V_{SS} = 0$  since ( $V(\infty) = 0$ )



$$I = I_R(t) + I_L(t) + I_c(t) \quad \forall t \geq 0$$

$$= \frac{V(t)}{R} + \frac{1}{L} \int_0^t V(\tau) d\tau + I_L(0) + C \frac{dV}{dt}$$

$$0 = \frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V + C \frac{d^2V}{dt^2}$$

$$\Rightarrow V_{SS} = 0$$


Total response, (general structure)

$$V(t) = V_{SS} + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{overdamped})$$

$$= V_{SS} + e^{-\alpha t} (A_1 \sin \omega t + B_1 \cos \omega t) \quad (\text{underdamped})$$

$$= V_{SS} + e^{-\alpha t} (A_1 t + A_2) \quad (\text{critically damped})$$

## Series RLC circuit,

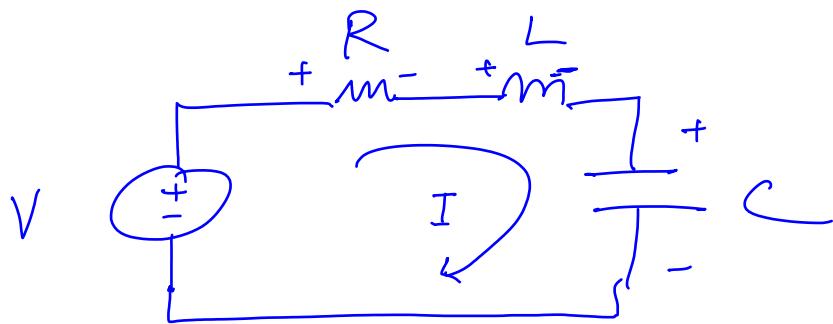

$$V_C(0) = V_0$$

$$I_L(0) = I_0$$

$$V = V_R(t) + V_L(t) + V_C(t) \quad \forall t \geq 0$$


$$I_C(t) = I_L(t) = I_R(t) \\ = I(t)$$

$$V = I(t)R + L \frac{dI(t)}{dt} + \frac{1}{C} \int_0^t I(\tau) d\tau + V_C(0)$$

$$0 = \frac{dI}{dt}R + L \frac{d^2I}{dt^2} + \frac{1}{C}I$$

## Operational Amplifiers (Active element)

(OpAmp)

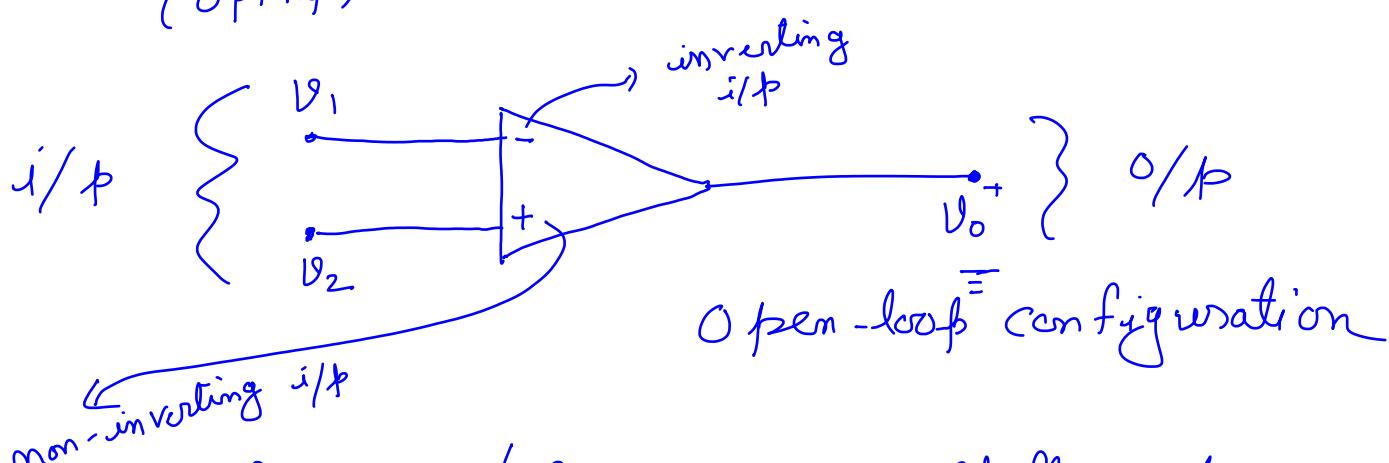


$$V_o = A(V_2 - V_1) \quad (\text{differential amplifiers})$$

(linear property, only valid in a certain range of operating condition)

For an ideal OpAmp ( $A \xrightarrow{\text{def}} \infty$ )

$$(V_2 - V_1) \approx 0$$

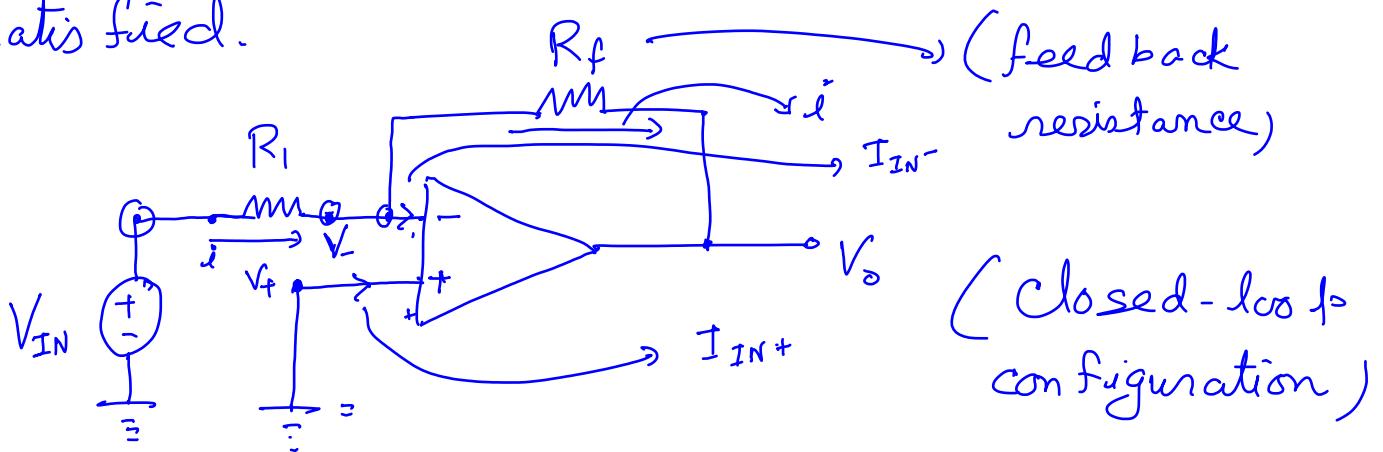In closed-loop, this property is automatically satisfied.



In closed-loop, an ideal OpAmp follows the subsequently defined properties.

$$1) V_+ = V_- \quad (\text{virtual short circuit})$$

$$2) I_{IN-} = I_{IN+} = 0$$

$$V_+ = 0 = V_-$$

(Inverting amplifiers)

$$i = \frac{V_{IN}}{R_I} = \frac{-V_O}{R_f} \Rightarrow V_O = -\frac{R_f}{R_I} V_{IN}$$





## Quick Recap


RLC  $\rightarrow$  total response

$$V(t) = V_f(t) + V_n(t)$$

$$= V_{ss} + \underbrace{V_T(t)}_{\begin{array}{l} \xrightarrow{} A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ \xrightarrow{} A_1 t e^{s_1 t} + A_2 e^{s_1 t} \\ \xrightarrow{} e^{-\alpha t} (A_d \sin \omega_d t + B_d \cos \omega_d t) \end{array}}$$

$$I_L(t) = I_L(t^+) \quad (V_L(t) \neq \infty)$$

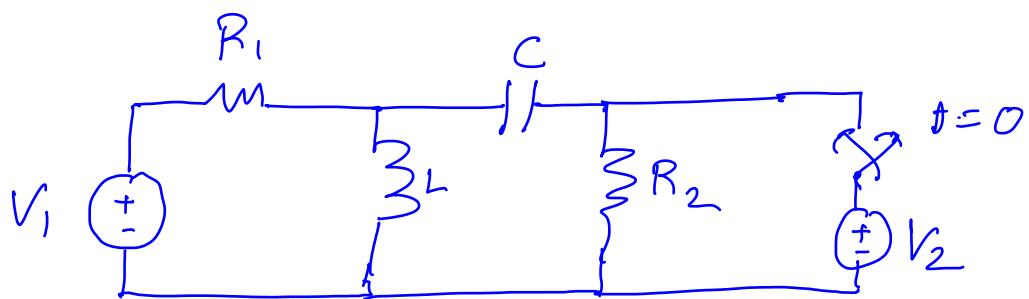
$$V_C(t^-) = V_C(t^+) \quad (I_C(t) \neq \infty)$$



$$I_L(0^-) = ?$$

$$V_C(0^-) = ?$$

at  $t = 0^-$

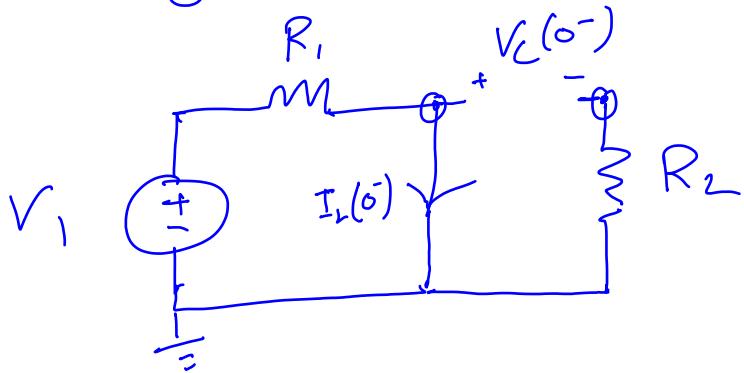


$$I_L(0^-) = \frac{V_1}{R_1}$$


$$V_c(0^-) = 0$$

Open-loop OpAmp

open-loop gain

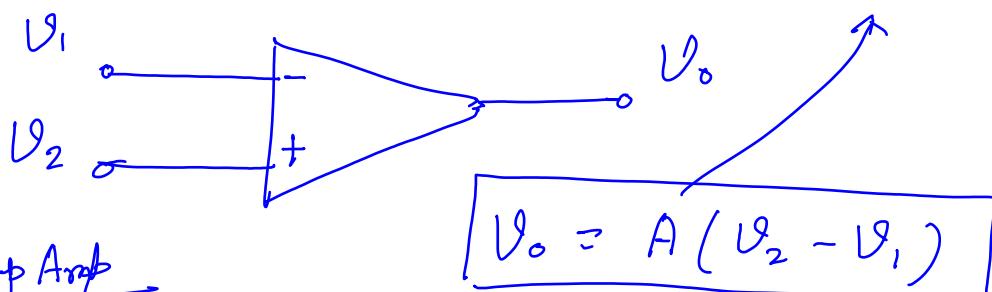

Closed-loop OpAmp

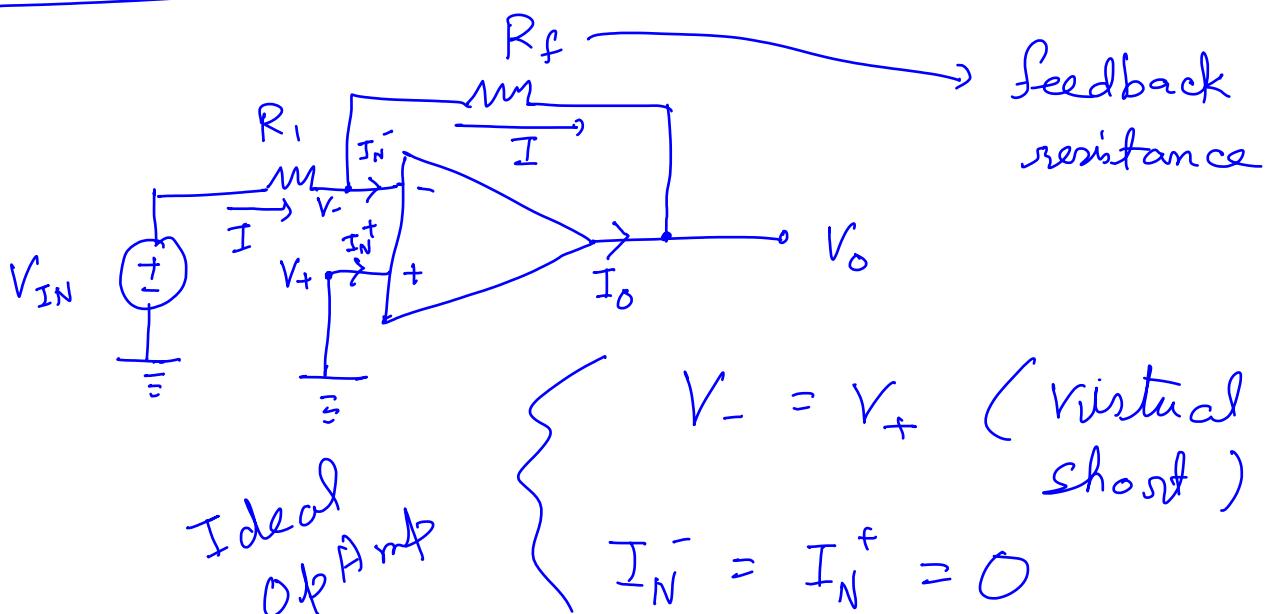

$$\frac{V_{IN}}{R_1} = -\frac{V_o}{R_f} \Rightarrow V_o = -\frac{R_f}{R_1} V_{IN}$$

$$I + I_o = 0 \Rightarrow I_o = -I = -\frac{V_{IN}}{R_1}$$

$I_{IN} = 0$ , however,  $I_o \neq 0$ . This is possible because of the power supplies ( $+V_{CC}, -V_{CC}$ ). OpAmp is an active element.

# Equivalent circuit of OpAmp ✓

## Fundamental questions

$$\frac{O}{O} = ?$$

$$\infty \times 0 = ?$$


$$\frac{O}{O} = m \Rightarrow O = m \times O$$

Let  $t \rightarrow \infty$

$$\frac{e^{-pt}}{e^{-qt}} \left\{ \begin{array}{ll} = 0 & \text{if } p > q \\ = \infty & \text{if } p < q \\ = 1 & \text{if } p = q \end{array} \right.$$

any real number

## Getting back to OpAmp

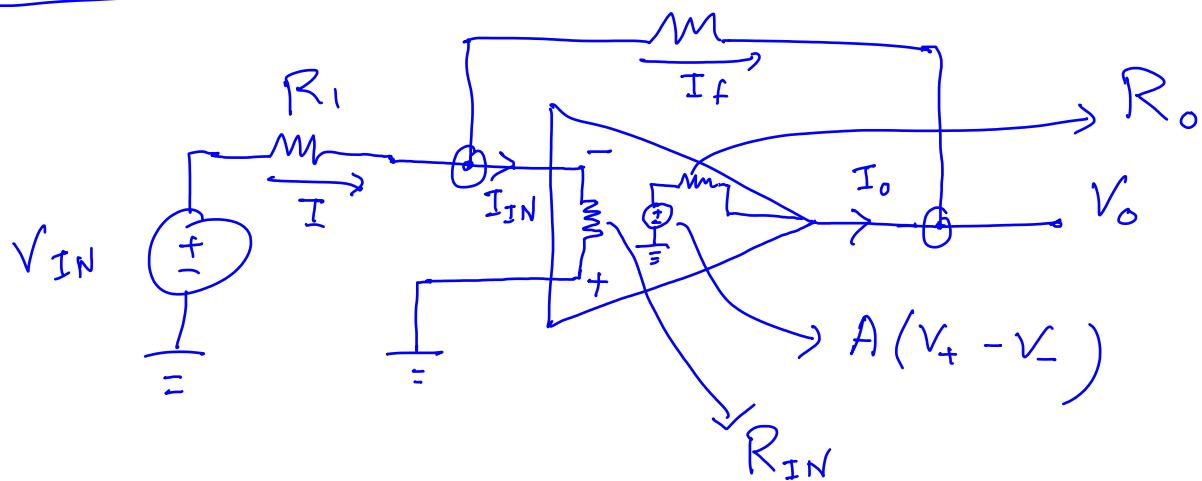

## Ideal OpAmp

$$A = \infty$$

$$R_{IN} = \infty$$

$$R_O = 0$$

$$I = I_f + I_{IN} \quad (1)$$

$$I_f + I_o = 0 \quad (2)$$

$$\frac{V_{IN} - V^-}{R_i} = \frac{V^- - V_o}{R_f} + \frac{V^-}{R_{IN}} \quad \text{--- (1)}$$

$$\frac{V^- - V_o}{R_f} + \frac{A(V^+ - V^-) - V_o}{R_o} = 0 \quad \text{--- (2)}$$

$$V^+ = 0$$

$$\text{since } R_{IN} = \infty$$

$$\Rightarrow \frac{V_{IN} - V^-}{R_i} = \frac{V^- - V_o}{R_f}$$

$$\text{since } R_o = 0 \Rightarrow A(V^+ - V^-) = V_o$$


$$A(V^+ - V^-) = V_o$$

$$A(0 - V^-) = V_o$$

since  $A = \infty \Rightarrow V^- = 0$  and  $V_o$  is finite.

$$\Rightarrow V^+ = V \quad \left. \begin{array}{l} \{ \\ \} \end{array} \right\} -$$

$$I_{IN} = 0$$

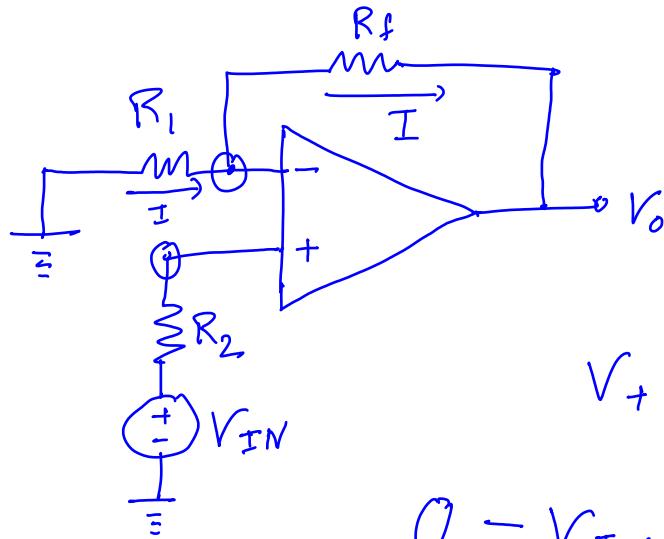


$$V_+ = V_- = V_{IN}$$

$$\frac{0 - V_{IN}}{R_1} = \frac{V_{IN} - V_O}{R_f}$$

$$\Rightarrow \frac{V_O}{R_f} = \left( \frac{1}{R_1} + \frac{1}{R_f} \right) V_{IN}$$


$$\Rightarrow V_O = \left( 1 + \frac{R_f}{R_1} \right) V_{IN}$$

(non-inverting amplifiers)

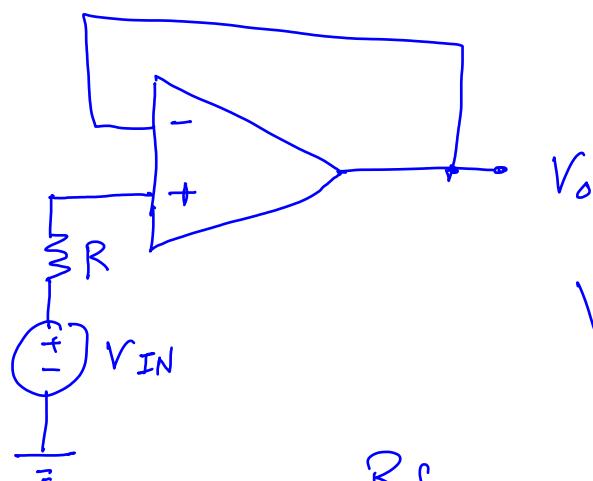

$$V_O = V_{IN}$$

(Buffer)

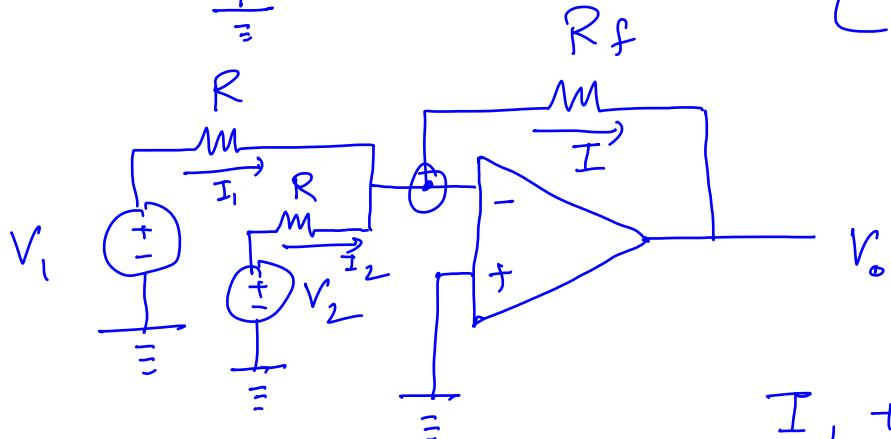


$$I_1 + I_2 = I$$

$$(V^+ = V^- = 0)$$

$$\frac{V_1}{R} + \frac{V_2}{R} = -\frac{V_o}{R_f}$$

$$V_o = -\frac{R_f}{R} (V_1 + V_2)$$

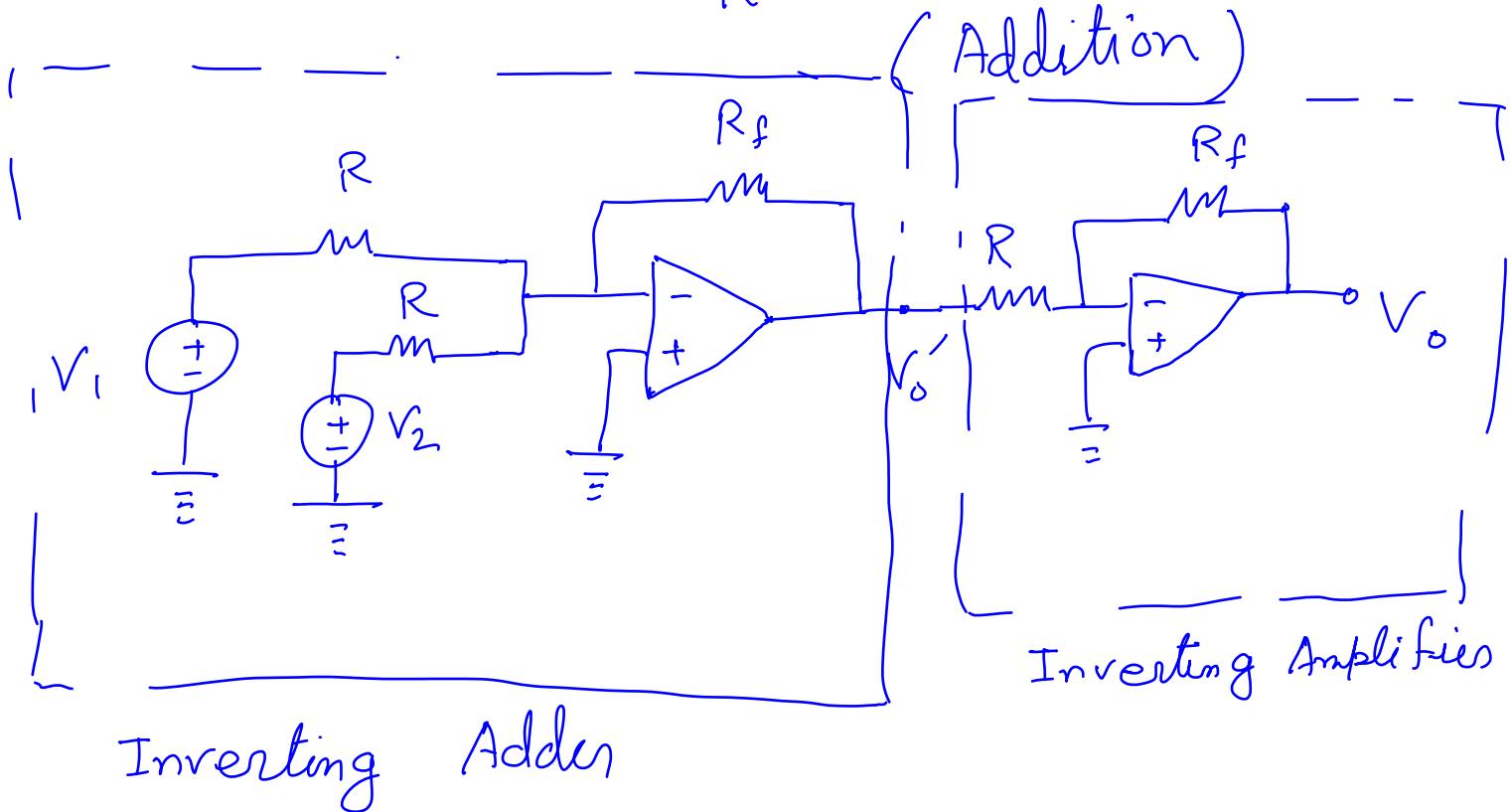

$$V'_o = -\frac{R_f}{R} (V_1 + V_2)$$


$$V_o = -\frac{R_f}{R} \quad V'_o = +\frac{R_f^2}{R^2} (V_1 + V_2)$$





### Quick Recap

## Operational Amplifiers (Op Amp)

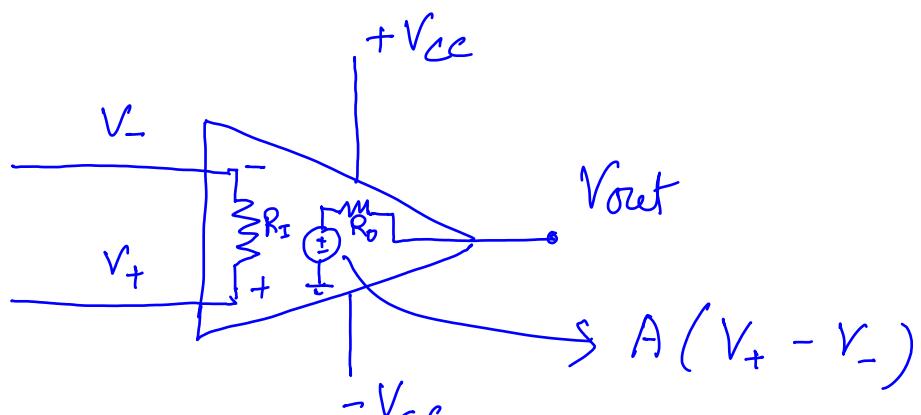


### Ideal OpAmp

$$A \rightarrow \infty, R_I \rightarrow \infty, R_o \approx 0 \quad \checkmark$$

$$V_- = V_+ \quad (\text{In closed-loop})$$

$( -V_{CC} \leq V_{out} \leq V_{CC} )$

linear operating zone

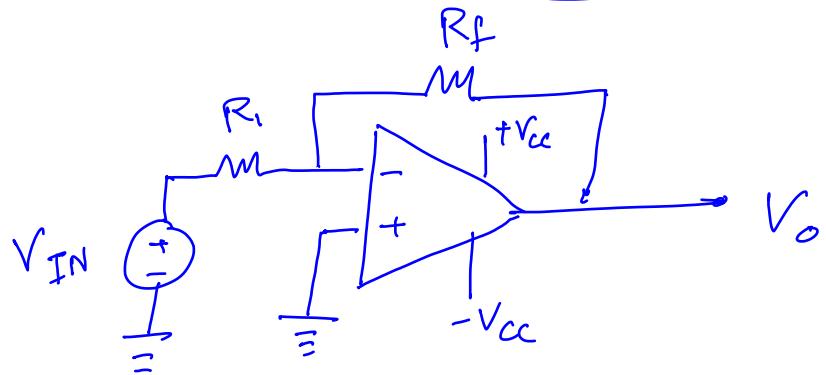

$$V_o = - \frac{R_f}{R_i} V_{IN} \quad (-V_{CC} \leq V_o \leq V_{CC})$$

EQU


$$R_f = 10 \Omega, \quad R_i = 1 \Omega$$

$$V_{IN} = 1 \text{ V}$$

$$V_{CC} = 5 \text{ V}$$

$$V_o = -5 \text{ V}$$

(Saturation property)

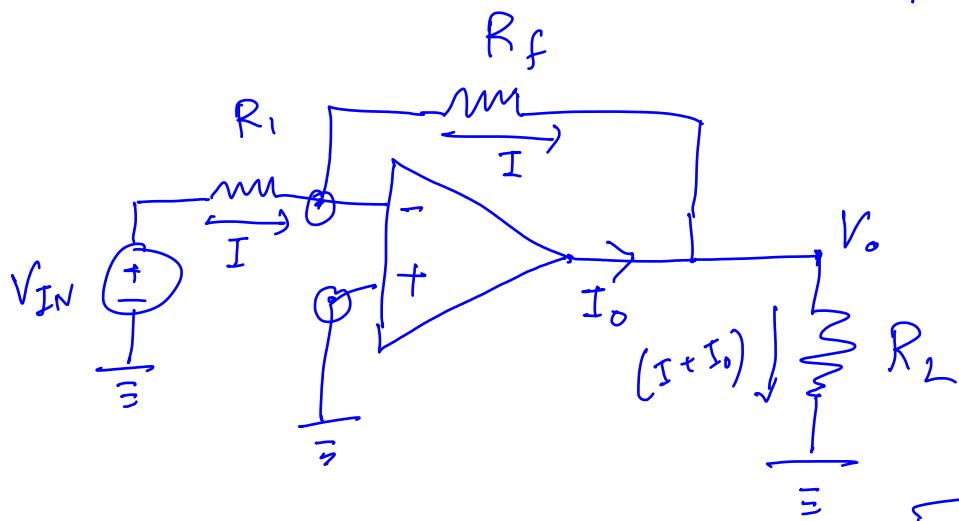

$$\checkmark \quad \frac{V_{IN}}{R_i} = - \frac{V_o}{R_f} = I$$

$$\boxed{V_- = V_+ = 0}$$

$$V_o = - \frac{R_f}{R_i} V_{IN}$$


$$I + I_o = \frac{V_o}{R_L} \Rightarrow I_o = \frac{V_o}{R_L} - I$$

$$= \frac{V_o}{R_L} + \frac{V_o}{R_f}$$

$$= V_o \left( \frac{1}{R_L} + \frac{1}{R_f} \right)$$

$$= - \frac{R_f}{R_i} V_{IN} \left( \frac{1}{R_L} + \frac{1}{R_f} \right)$$
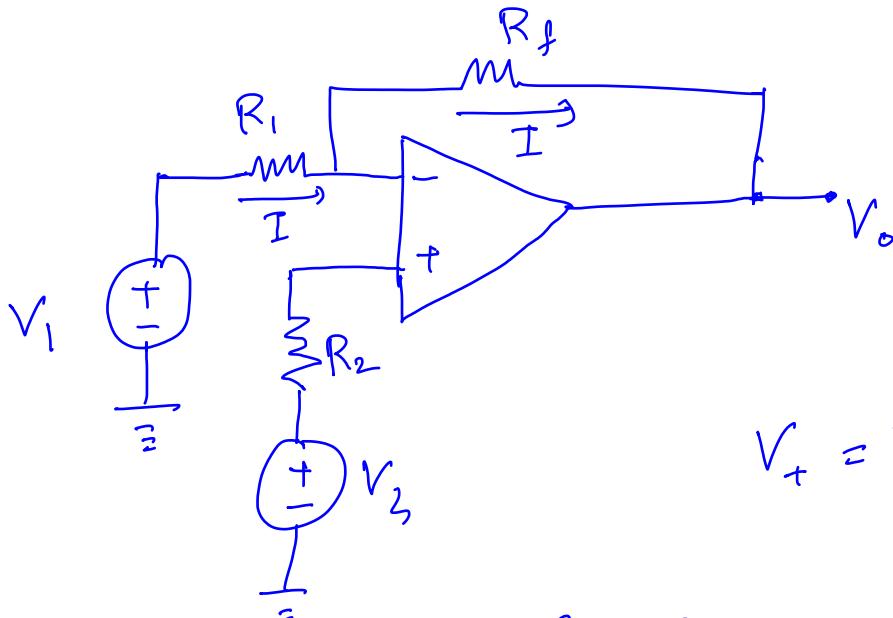
$$I_o = -V_{IN} \frac{R_L + R_f}{R_1 R_2} \quad (\text{dependent on the load resistance})$$




$$V_+ = V_2 = V_-$$

$$\frac{V_1 - V_2}{R_1} = \frac{V_2 - V_0}{R_f}$$

$$V_0 = -\frac{R_f}{R_1} V_1 + V_2 \left(1 + \frac{R_f}{R_1}\right)$$

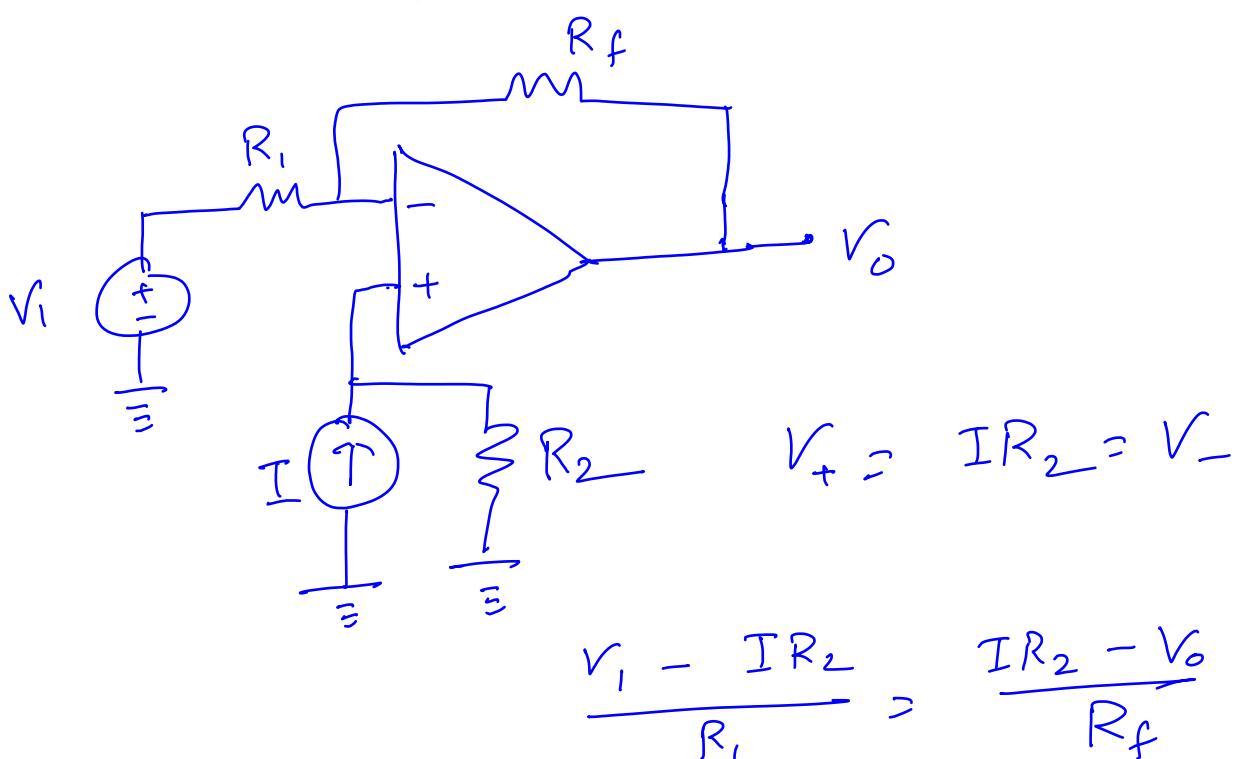
contribution from inverting amplification      contribution from non-inverting amplification




$$V_+ = IR_2 = V_-$$

$$\frac{V_1 - IR_2}{R_1} > \frac{IR_2 - V_0}{R_f}$$
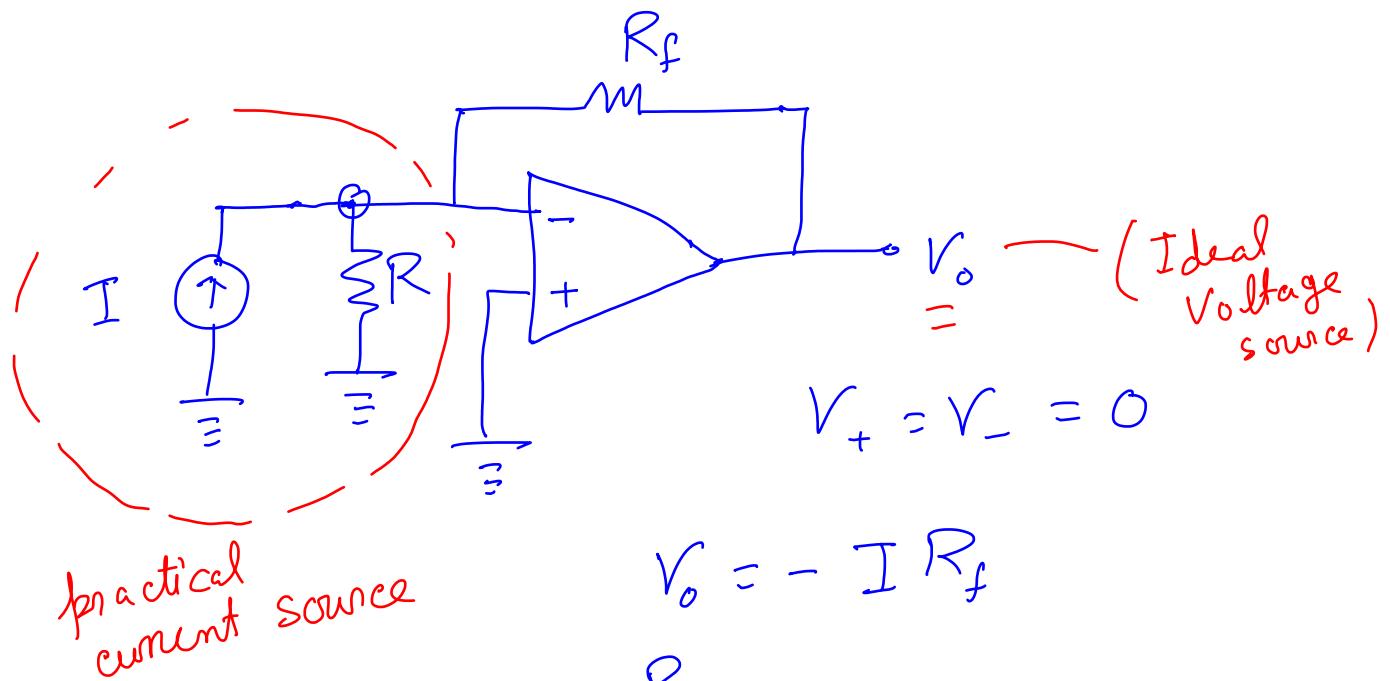
$$V_o = -\frac{R_f}{R_i} V_i + IR_2 \left( 1 + \frac{R_f}{R_i} \right)$$



$$V_o = -I R_f$$

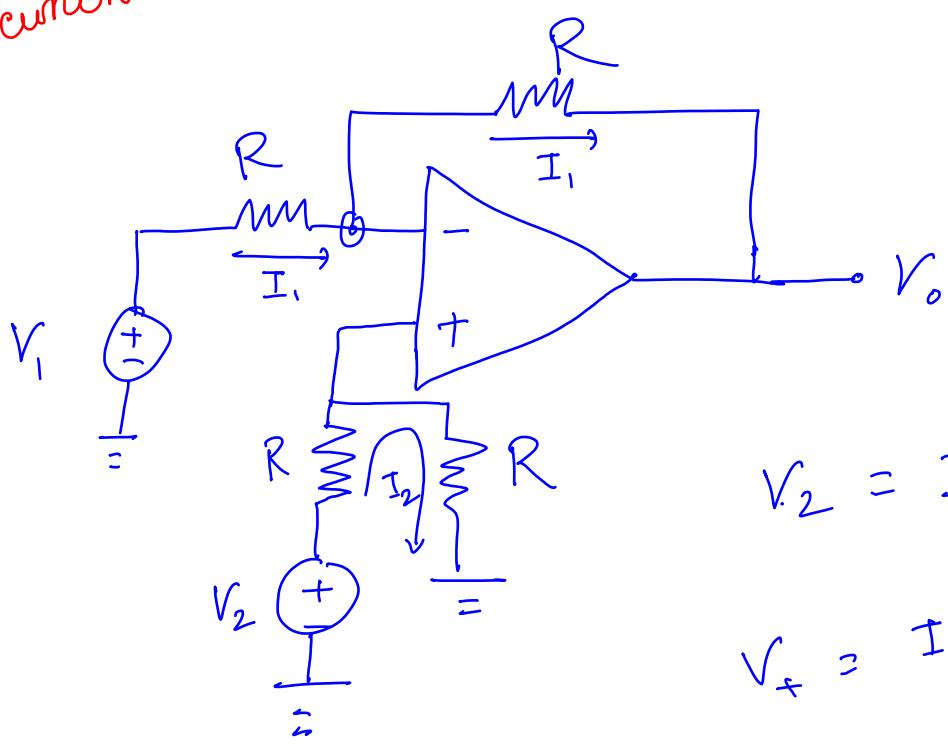


$$V_2 = I_2 2R$$

$$V_+ = I_2 R = \frac{V_2}{2R} R \\ = \frac{V_2}{2}$$

$$\frac{V_1 - \frac{V_2}{2}}{R} = \frac{V_2}{2} - V_o$$

$$\Rightarrow V_- = \frac{V_2}{2}$$
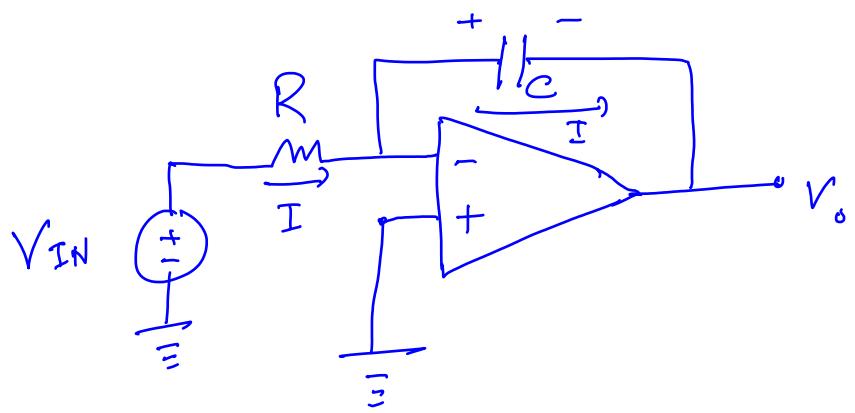
$$V_o = V_2 - V_1 \quad (\text{subtraction})$$




$$V_C(0) = 0$$

$$V_+ = V_- = 0$$

$$\frac{V_{IN}}{R} = -C \frac{dV_o}{dt}$$

$$V_o(t) = -\frac{1}{RC} \int_0^t V_{IN}(z) dz$$

( Integrator )

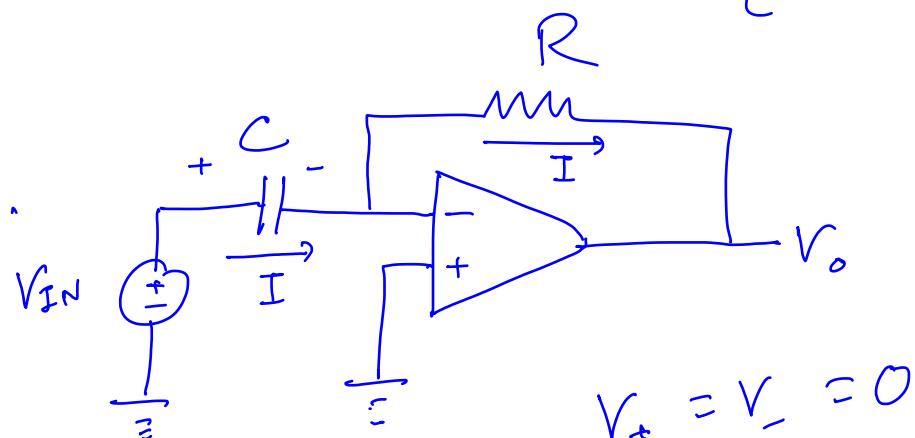


$$V_C(0) = 0$$

$$C \frac{dV_{IN}}{dt} = -\frac{V_o}{R}$$



$$V_o = -RC \frac{dV_{IN}}{dt}$$

( Differentiator )

### Q.3 > (Assignment 1)

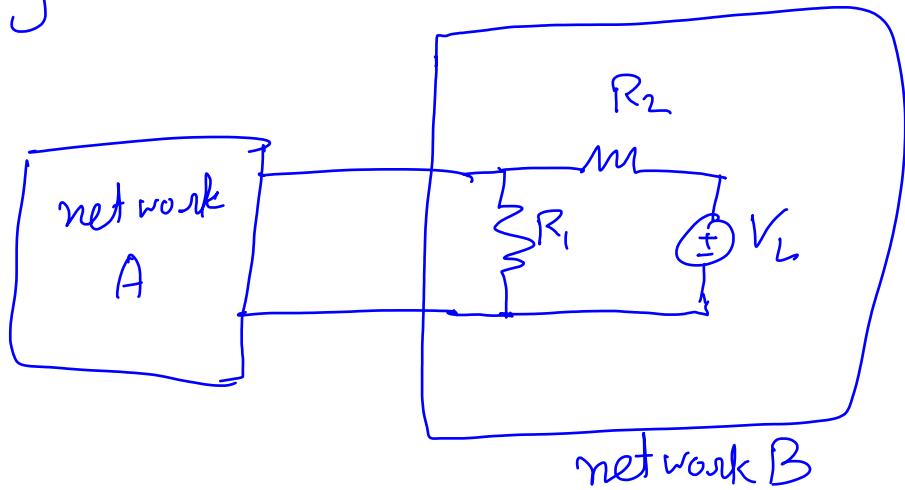

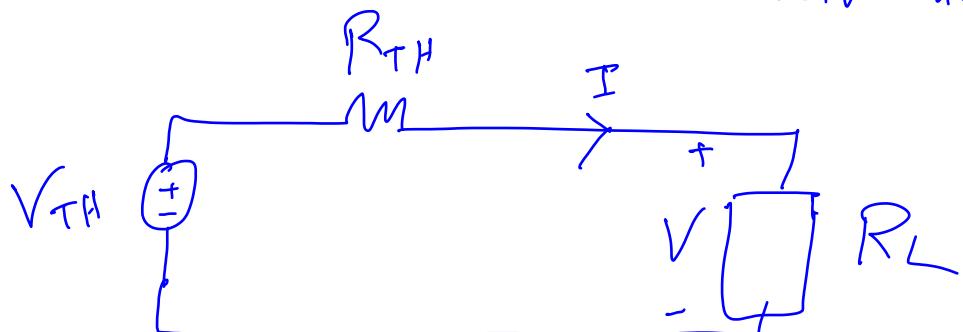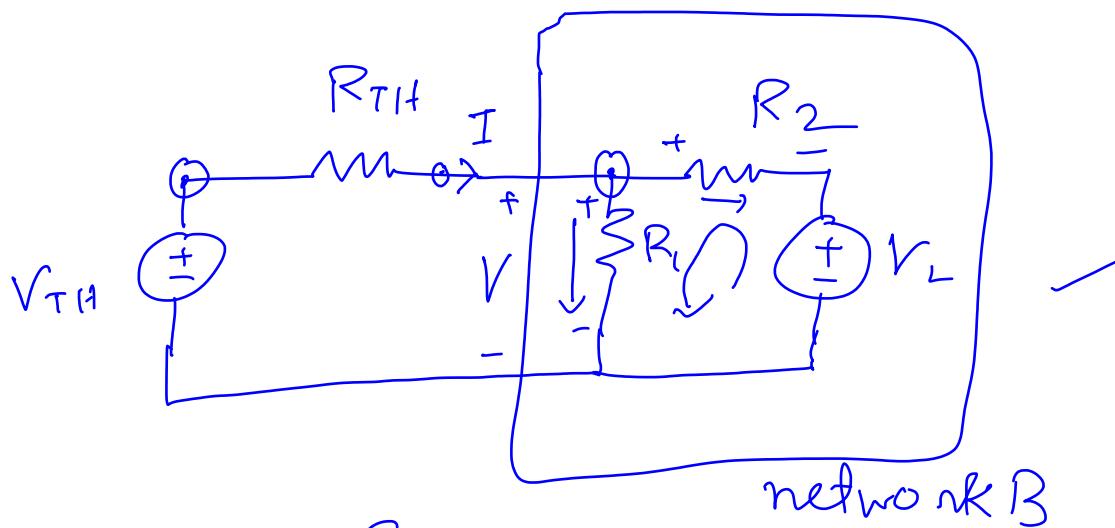What should be the magnitude of  $V_L$  such that maximum power is delivered to network B?



From maximum power transfer  $V = \frac{V_{TH}}{2}$ .

$$\Rightarrow I = \frac{V_{TH}}{2R_{TH}}, \quad I_{R1} = \frac{V_{TH}}{2R_1}$$

$$I = I_{R_1} + I_{R_2}$$

$$I_{R_2} = I - I_{R_1}$$

$$= \frac{V_{TH}}{2} \left( \frac{1}{R_{TH}} - \frac{1}{R_1} \right)$$

$$- V_L - V_{R_2} + V_{R_1} = 0$$

$$V_L = V_{R_1} - V_{R_2}$$

$$= \frac{V_{TH}}{2} - I_{R_2} \cdot R_2$$

$$= \frac{V_{TH}}{2} - \frac{V_{TH}}{2} \left( \frac{1}{R_{TH}} - \frac{1}{R_1} \right) \cdot R_2$$

