

Quick Recap

Resistance (R)
Inductance (L)
Capacitance (C)

Passive Elements

Voltage source
Current source

Active Elements

Independent source
Dependent source


Current-controlled

Voltage
controlled


$$R = \frac{\rho l}{A} \} \checkmark$$

Algebraic Sum

KCL \rightarrow }
KVL \rightarrow }

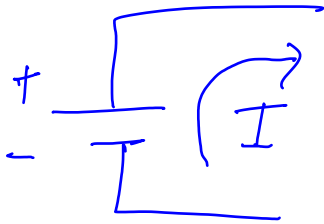


Power generated

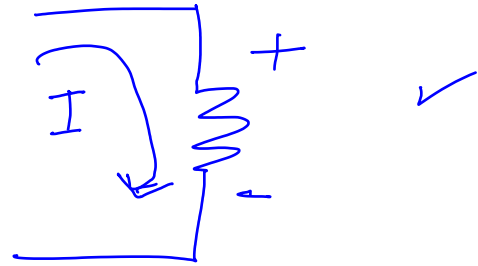


Power absorbed

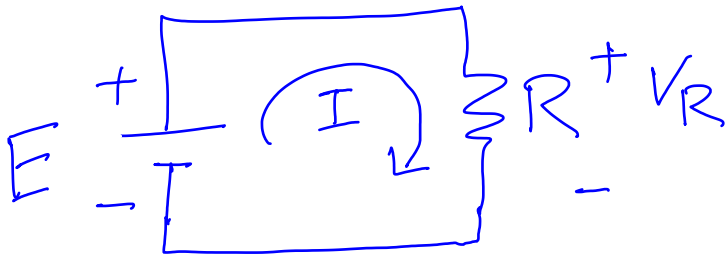KCL and KVL are also
applicable to circuits having
C and L.



$$E - V_R = 0 \Rightarrow E = V_R = IR$$


$$\underline{I} = E/R$$

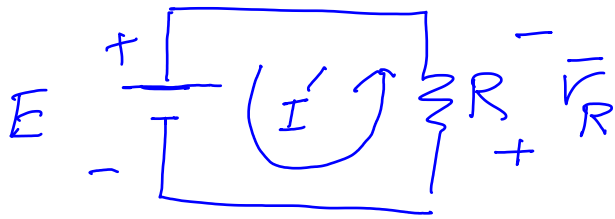

$$E + \bar{V}_R = 0 \Rightarrow I' = -E/R$$

Initial choice of current direction
can be arbitrary ...
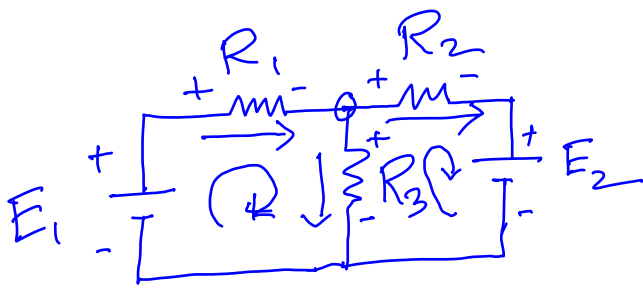
$$I = -I' \quad (\text{in the above example})$$



$$\begin{array}{ccc} I_1, & I_2, & I_3 \\ \downarrow & \downarrow & \downarrow \\ R_1 & R_2 & R_3 \end{array}$$

$$\left\{ \begin{array}{l} I_1 = I_2 + I_3 \quad \text{--- ① (KCL)} \\ E_1 = I_1 R_1 + I_3 R_3 \quad \text{--- ② (KVL)} \\ I_3 R_3 = I_2 R_2 + E_2 \quad \text{--- ③ (KVL)} \end{array} \right.$$

System of Linear Equations . .

$$\underbrace{A}_{3 \times 3} \underbrace{x}_{3 \times 1} = \underbrace{b}_{3 \times 1} \quad x = \underbrace{\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}}_{3 \times 1}$$

$$A = \begin{bmatrix} 1 & -1 & -1 \\ R_1 & 0 & R_3 \\ 0 & -R_2 & R_3 \end{bmatrix} \quad b = \begin{bmatrix} 0 \\ E_1 \\ E_2 \end{bmatrix}$$

check for $\det(A) \neq 0$
for unique sol.

$$x = A^{-1} b$$

$$\begin{cases} a_{11}x_1 + a_{12}x_2 = b_1 \\ a_{21}x_1 + a_{22}x_2 = b_2 \end{cases}$$

Diagram illustrating the matrix representation of the system:

$$\begin{bmatrix} a_{11} \\ a_{21} \end{bmatrix} C_1 + \begin{bmatrix} a_{12} \\ a_{22} \end{bmatrix} C_2 = \begin{bmatrix} b_1 \\ b_2 \end{bmatrix}$$

Labels: A (matrix of coefficients), x (vector of variables), b (vector of constants).

Condition for infinitely many solutions:


$$\frac{a_{11}}{a_{21}} = \frac{a_{12}}{a_{22}} = \frac{b_1}{b_2}$$

$$\frac{a_{11}}{a_{21}} = \frac{a_{12}}{a_{22}} \longrightarrow \text{no solution (parallel lines)}$$

$$\alpha_1 C_1 + \alpha_2 C_2 = 0 \Rightarrow \alpha_1 = 0 \text{ and } \alpha_2 = 0$$

C_1, C_2 are linearly independent.

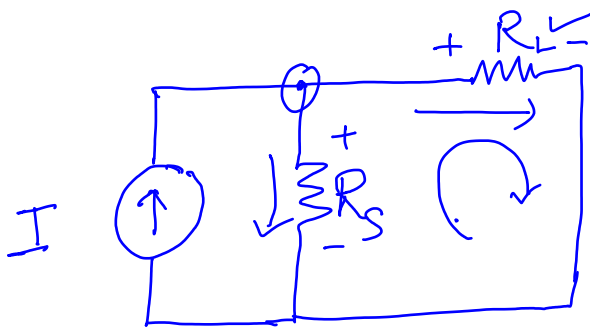Same concept can be extended to "n" equations. . .



I_s, I_L

$$I = I_s + I_L \quad (\text{KCL})$$

$$I_s R_s = I_L R_L \quad (\text{KVL})$$

$$I_L = \frac{R_s}{R_L} I_s$$

$$I_L \left(1 + \frac{R_s}{R_L}\right) = I$$


$$I_L = \frac{R_L}{R_s + R_L} I$$

$$A = \begin{bmatrix} 1 & 1 \\ R_s & -R_L \end{bmatrix}$$

$$b = \begin{bmatrix} I \\ 0 \end{bmatrix}$$

$$x = A^{-1} b$$
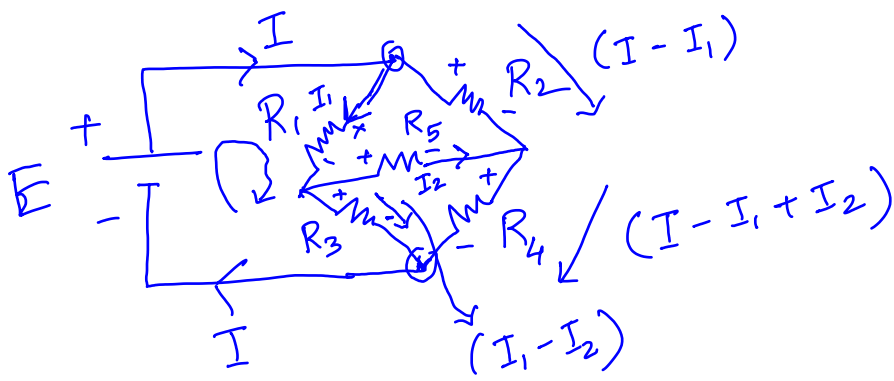
$$x = \begin{bmatrix} I_s \\ I_L \end{bmatrix}$$



$$A x = b$$

$$E = I_1 R_1 + (I_1 - I_2) R_3$$

$$I_1 R_1 + I_2 R_5 = (I - I_1) R_2 \quad \checkmark$$

$$I_2 R_5 + (I - I_1 + I_2) R_4 = (I_1 - I_2) R_3$$

$$x = \begin{bmatrix} I \\ I_1 \\ I_2 \end{bmatrix}$$

$$A \rightarrow 3 \times 3$$

$$b \rightarrow 3 \times 1$$

A circuit having " b " no. of branches

How many minimum no. variables you need to compute " b " branch voltages and " b " branch currents?


b no. of unknowns!

Let's use the following notations throughout...

b = no. of branches/elements

n = no. of nodes

(in a circuit)

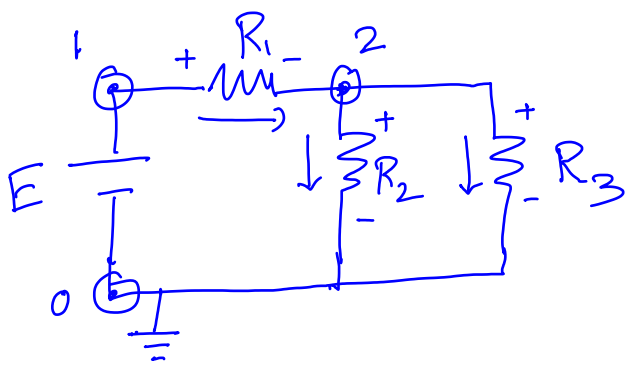

$$n = 3$$

$$b = 4$$

$$V_1 \text{ and } V_2$$

$V_1 \rightarrow$ voltage of node 1 w.r.t node 0.

$$V_2 \rightarrow \dots$$

V_{R_1}
 V_{R_2}
 V_{R_3}
 V_E
 branch voltages

$\left\{ \begin{matrix} V_1 \\ V_2 \end{matrix} \right\}$
 node-to-reference voltages

$$V_1 = E$$

$$\frac{V_1 - V_2}{R_1} = \frac{V_2}{R_2} + \frac{V_2}{R_3}$$

Independent variables
 KCL

Here, node "0" is considered as reference node.

$(n-1)$ voltage variables to solve for
a linear circuit problem.

(node-to-reference voltages)
(datum)

