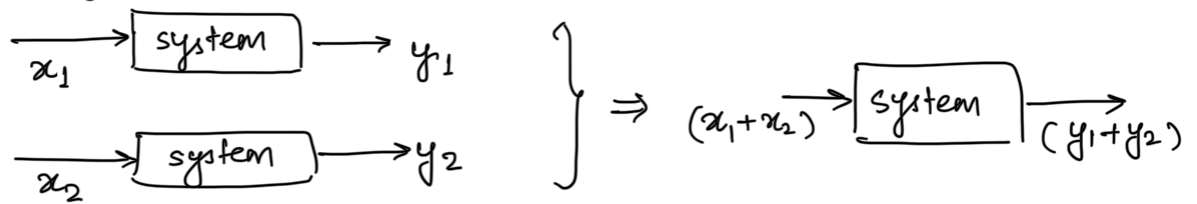


Superposition Principle:-


linearity \leftrightarrow superposition




* Multiple independent sources

- consider separate independent sources "acting alone"
- add all responses.

Example

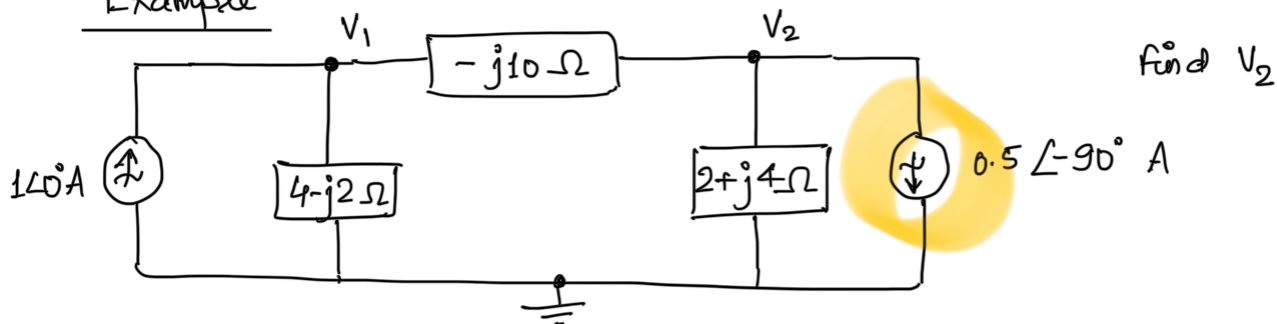

Consider left side source:


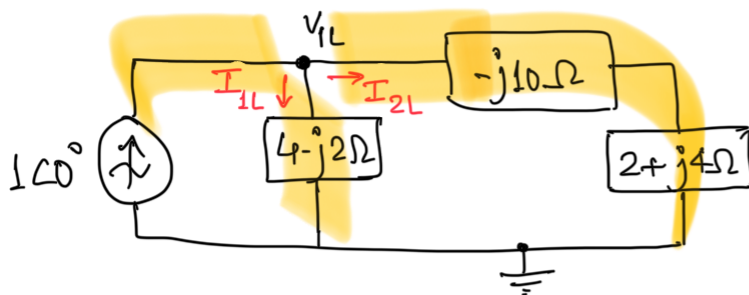


$$V_{1L} = I_{1L} (4 - j2) \leftarrow \text{ohm's law}$$

$$= 1\angle 0^\circ \frac{(-j10 + 2 + j4)}{(4 - j2) + (-j10 + 2 + j4)} (4 - j2)$$

current division
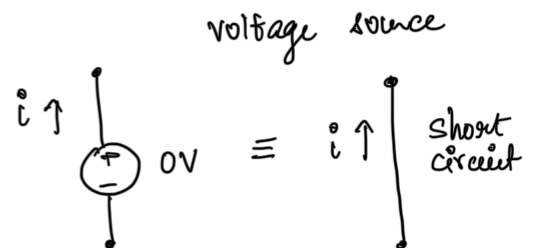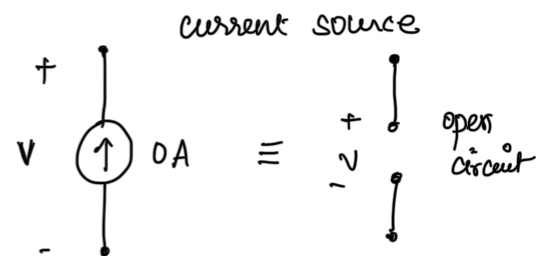
$$= \frac{-4 - j28}{6 - j8} = 2 - j2 \text{ V}$$




$$1\angle 0^\circ$$

$$= 1 \cos 0^\circ + j 1 \sin 0^\circ$$

$$= 1$$

Consider right side source

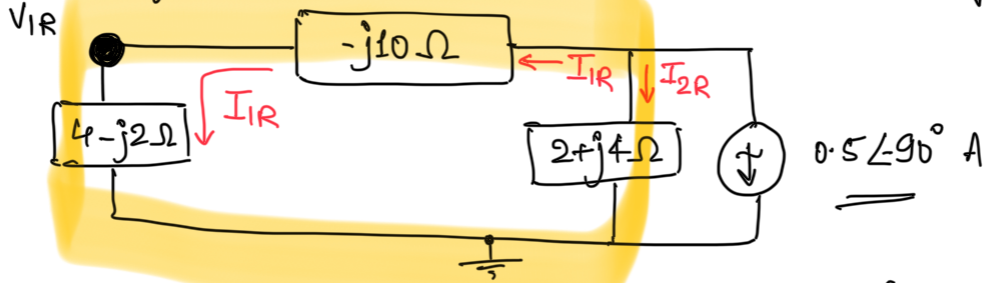

$$V_1 = V_{1L} + V_{1R}$$


$$\begin{aligned} V_{1R} &= I_{1R} (4 - j2) \\ &= \frac{(j0.5)(2 + j4)(4 - j2)}{(6 - j8)} \\ &= -1V \end{aligned}$$

$$I_{1R} = \frac{(-0.5 \angle -90^\circ)(2 + j4)}{(-j10 + 4 - j2 + 2 + j4)}$$


current division

Applying superposition:
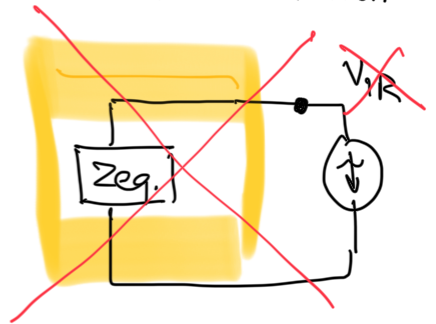
$$\begin{aligned} V_1 &= V_{1L} + V_{1R} \\ &= 2 - j2 - 1 \\ &= 1 - j2 \text{ V} \end{aligned}$$




Example :-

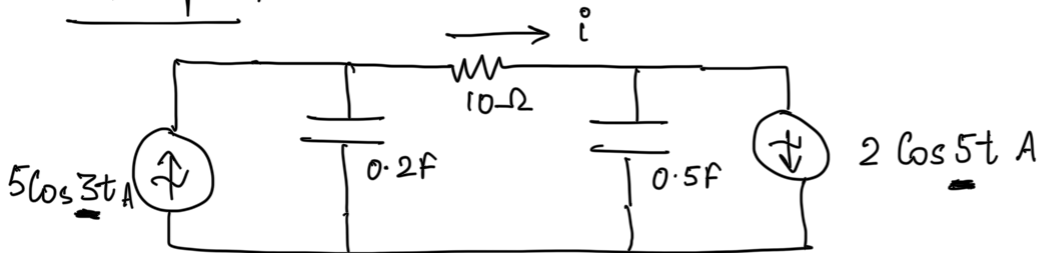

find $i(t)$

$$\frac{1}{j\omega C}$$

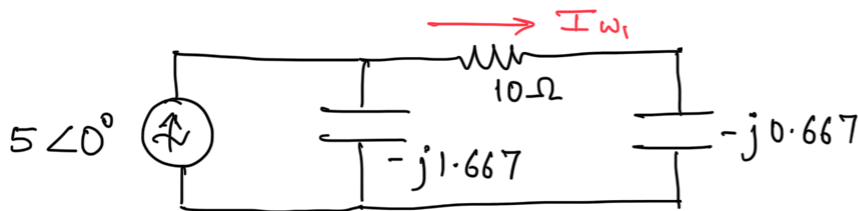Consider left source: $\omega_1 = 3 \text{ rad/s}$




$$\frac{1}{j(3)(0.2)} = \frac{-j}{0.6}$$

$$\frac{1}{j(3)(0.5)} = \frac{-j}{1.5}$$

$$I_{w_1} = 5 \angle 0^\circ \left(\frac{-j1.667}{-j1.667 + 10 - j0.667} \right) = 811.7 \angle -76.86^\circ \text{ mA}$$

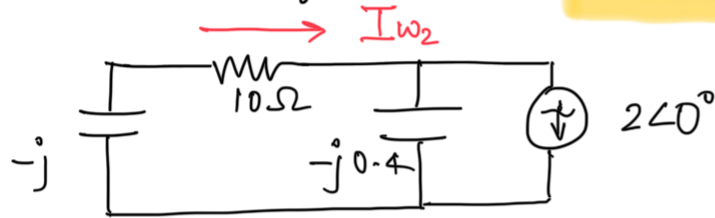Consider right source: $\omega_2 = 5 \text{ rad/s}$



$$\frac{1}{j(5)(0.2)} = -j$$

$$\frac{1}{j(5)(0.5)} = -j0.4$$

$$I_{w_2} = +2\angle 0^\circ \left(\frac{-j0.4}{-j + 10 - j0.4} \right) = 79.2 \angle -82.03^\circ \text{ mA}$$

Applying superposition:

$$\underline{I} = \underline{I_{w_1}} + \underline{I_{w_2}}$$

~~3 rad/s 5 rad/s~~

$$i(t) = i_{w_1}(t) + i_{w_2}(t)$$

$$i_{w_1}(t) = 811.7 \cos(3t - 76.86^\circ) \text{ mA}$$

$$i_{w_2}(t) = 79.23 \cos(5t - 82.03^\circ) \text{ mA}$$

$$i(t) = [811.7 \cos(3t - 76.86^\circ) + 79.23 \cos(5t - 82.03^\circ)] \text{ mA}$$

Phasors can only be added when they correspond to same frequency

Phasor


$$i(t) = I_m \cos(\omega t + \phi)$$

$$= \text{Re} \{ I_m e^{j\omega t + j\phi} \}$$


↓ Remove $e^{j\omega t}$
Re { }

$$I_m e^{j\phi} = I_m \angle \phi$$



Source Transformation :-

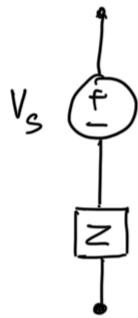




\equiv

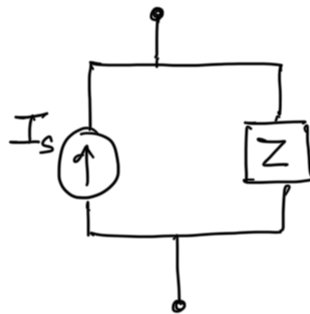


$$I_s = V_s / Z$$

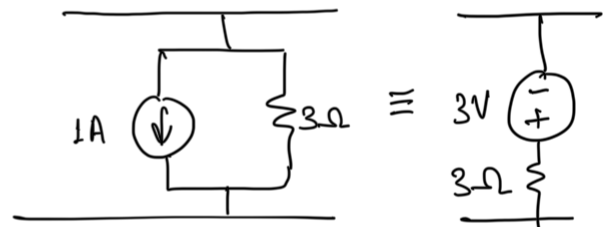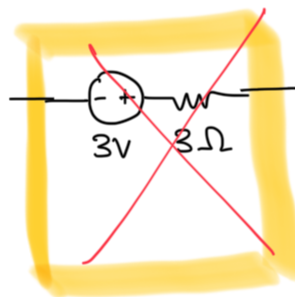


Theremin & Norton Equivalent Circuits :

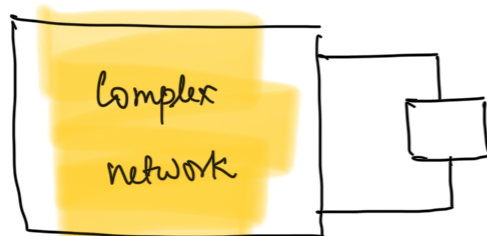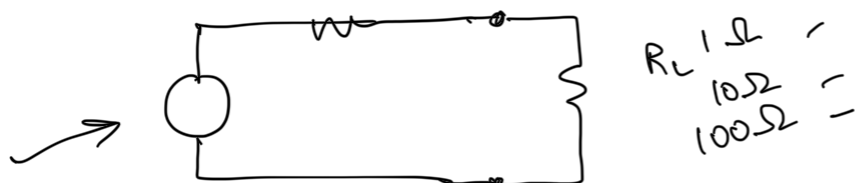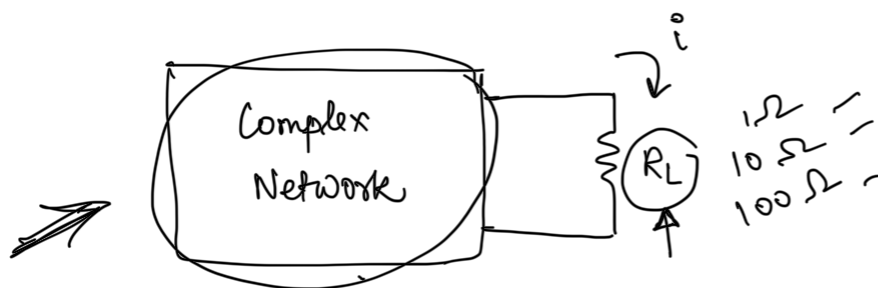

$$Z_L \equiv$$

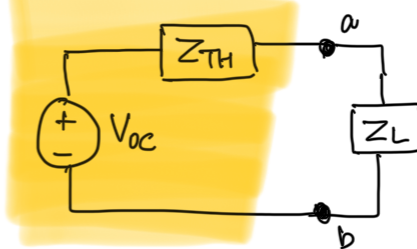


$$\equiv$$

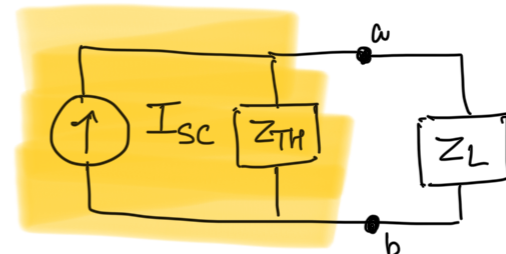


$$V_{oc} = I_{sc} \cdot Z_{TH}$$

- | | V_{oc} | I_{sc} | Z_{TH} |
|-----------------------------------|----------------------------|----------|----------|
| ① Independent sources only | ✓ | ✓ | ✓ |
| ② Independent + dependent sources | ✓ | ✓ | ✓ |
| ③ Dependent sources only | \Rightarrow Test sources | | |

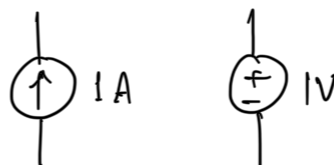

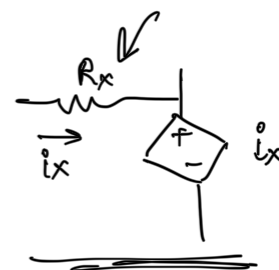
$$V_{oc}, I_{sc}, Z_{TH} = V_{oc} / I_{sc}$$




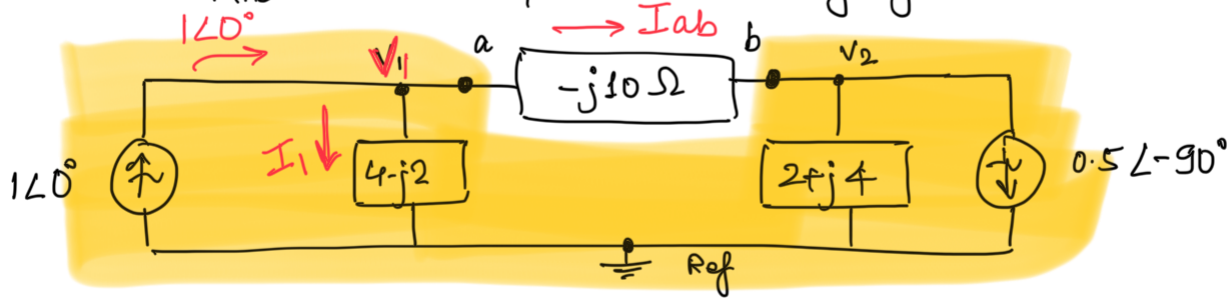Example :

Find Thevenin Equivalent seen by $-j10\Omega$. Find V_1 .



Find V_{oc}

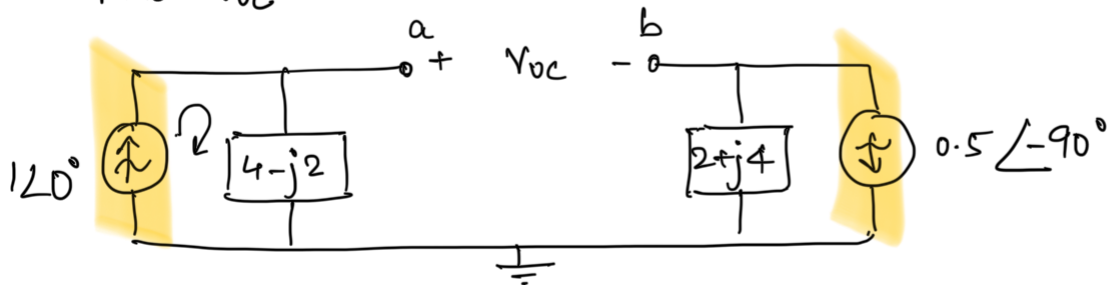

$$V_{oc} = V_a - V_b = 120^\circ (4-j2) - (-0.5\angle-90^\circ)(2+j4)$$

$$= 4-j2 + 2-j1 = 6-j3 \text{ V}$$

Find Z_{TH}


$V_s \rightarrow$ short circuit
 $I_s \rightarrow$ open circuit



$$Z_{TH} = (4-j2) \parallel (2+j4)$$

$$= 6+j2 \Omega$$

Equivalent circuit

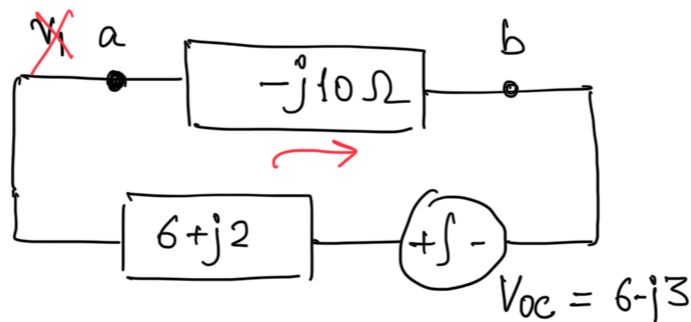

$$I_{ab} = \frac{V_{oc}}{(6+j2) + (-j10)}$$

$$I_1 = 1 \angle 0^\circ - I_{ab}$$

$$\text{Then } V_1 = I_1 (4-j2) = 1-j2 \text{ V}$$