

## Review

Instantaneous Power :  $p(t) = v(t) i(t)$

Average Power :  $P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) = \frac{1}{2} \operatorname{Re}\{VI^*\}$

$$P_{avg, sources} = \sum P_{avg, elements}$$


$P_{avg}$  for resistive load :  $P_{avg} \neq 0$

$P_{avg}$  for reactive load :  $P_{avg} = 0$



$$Z = R + jX$$

↑ resistive  
↓ reactive

Max. power transfer :

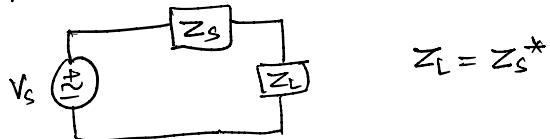

$$Z_L = Z_S^*$$

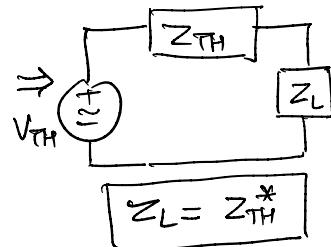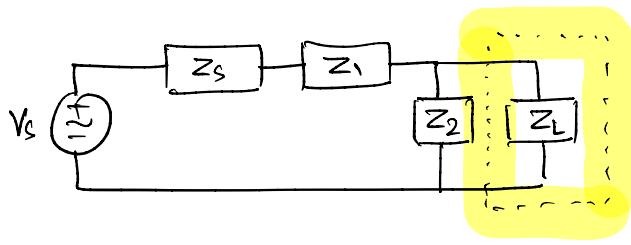

$$Z_L = Z_{TH}^*$$

Effective V and I values (RMS values)

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_{eff} = \frac{I_m}{\sqrt{2}}, \quad V_{eff} = \frac{V_m}{\sqrt{2}}$$

$$I = I_m \angle \phi = \sqrt{2} I_{eff} \angle \phi$$

Apparent Power

$$P_{apparent} = I_{eff} \cdot V_{eff}$$

$$\begin{array}{ll} I_{eff} & A_{rms} \\ V_{eff} & V_{rms} \\ \hline VA & (\text{volt-Ampere}) \end{array}$$

## Power Factor

$$PF = \cos(\theta - \phi) = \frac{\text{Power}}{\text{Apparent}}$$

for purely resistive load:  $PF = 1$  (max)

for purely reactive load:  $PF = 0$  (min)

$$\begin{array}{ll} \theta - \phi & 90^\circ \\ \theta - \phi & -90^\circ \end{array}$$

Assume PF of a load = 0.5


$$\cos(\theta - \phi) = 0.5$$

$$\Rightarrow (\theta - \phi) = \pm 60^\circ$$

$PF = 0.5$  leading  $\rightarrow$  capacitive  $(\theta - \phi) < 0$   
 $0.5$  lagging  $\rightarrow$  inductive  $(\theta - \phi) > 0$

$I$  w.r.t.  $V$

## Example

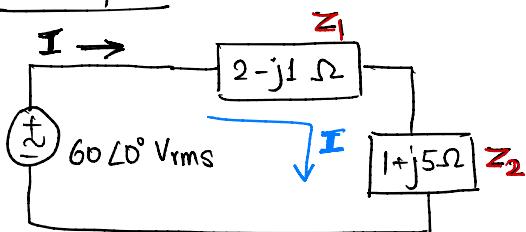


Find

- ① Average power delivered to each loads
- ② Average power supplied by source
- ③ Apparent power supplied by source
- ④ PF of combined load.

$$\text{① } P_{\text{avg}, z_1} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} \text{Re}\{VI^*\}$$

$$= I_{\text{eff}}^2 R$$

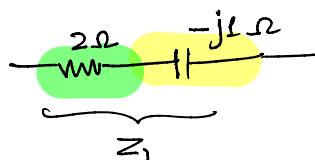

$$I =$$

Writing KVL:

$$- 60\angle 0^\circ V_{\text{rms}} + I (2 - j1 + 1 + j5) = 0$$

$$\Rightarrow I = \frac{60\angle 0^\circ V_{\text{rms}}}{3 + j4 \Omega} = \underbrace{12}_{I_{\text{eff}}} \angle -53.13^\circ A_{\text{rms}}$$

$$P_{\text{avg}, z_1} = (12)^2 2 = 288 \text{ W}$$

$$I = 12 \angle -53^\circ \text{ A rms}$$

$$i(t) = \frac{12}{I_{\text{eff}}} \cos(\omega t - 53^\circ) \text{ A rms}$$

$I_{\text{eff}}$  (A rms) versus  $I_m$  (A)

$$I_{\text{eff}} = \frac{I_m}{\sqrt{2}} \Rightarrow I_m = I_{\text{eff}} \sqrt{2}$$


$$I_{\text{eff}} = 12$$

$$I_m = I_{\text{eff}} \sqrt{2} = \frac{12\sqrt{2}}{1}$$

$$i(t) = \frac{12\sqrt{2}}{I_m} \cos(\omega t - 53^\circ) \text{ A}$$

$$P_{\text{avg}} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{\text{eff}} I_{\text{eff}} \cos(\theta - \phi)$$
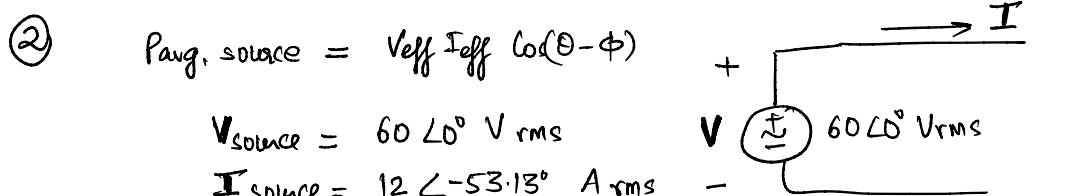
$$P_{\text{avg}, z_2} = I_{\text{eff}}^2 R = (12)^2 1 = 144 \text{ W}$$



$$P_{\text{avg, source}} = (60)(12) \cos(0 - (-53.13^\circ)) = 432 \text{ W}$$

$$P_{\text{avg}, z_1} = 288 \text{ W}, \quad P_{\text{avg}, z_2} = 144 \text{ W}$$

$$P_{\text{avg}, z_1} + P_{\text{avg}, z_2} = 432 \text{ W}$$

③  $P_{\text{apparent, source}} = I_{\text{eff}} V_{\text{eff}} = (60)(12) = 720 \text{ VA}$


④ PF of combined loads = PF of source

$$\text{PF} = \cos(\theta - \phi) = \cos(\theta + 53.13^\circ) = 0.6 \text{ lagging}$$

$(\theta - \phi) > 0 \rightarrow \text{lagging}$

$(\theta - \phi) < 0 \rightarrow \text{leading}$

$$P_{avg, Z_1} = I_{eff}^2 R$$

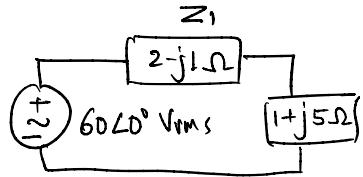

$$P_{avg, Z_1} = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$\begin{aligned} V_{Z_1} &= 60\angle 0^\circ \text{ V}_\text{rms} \times \frac{2-j1}{3+j4} \\ &= 26.83 \angle -79.7^\circ \text{ V}_\text{rms} \end{aligned}$$

$$I_{Z_1} = I = 12 \angle -53.13^\circ \text{ A}_\text{rms}$$

$$P_{avg, Z_1} = 26.83 \times 12 \times \cos(-79.7^\circ - (-53.13^\circ)) = 288 \text{ W}$$

$$P_{avgage} = \frac{1}{2} \operatorname{Re} \{ V I^* \} ; \quad V = V_m \angle \theta \\ I = I_m \angle \phi$$

$$V_{eff} = V_{eff} \angle \theta = \frac{V_m}{\sqrt{2}} \angle \theta$$

$$I_{eff} = I_{eff} \angle \phi = \frac{I_m}{\sqrt{2}} \phi$$

$$P_{avgage} = \operatorname{Re} \{ V_{eff} I_{eff}^* \}$$

### Complex Power

$$S = V_{eff} I_{eff}^* \quad (\text{unit: VA})$$

↙ { Not a phasor of power.  
This is a complex number.

$$S = (V_{eff} \angle \theta) (I_{eff} \angle -\phi) = V_{eff} \cdot I_{eff} e^{j(\theta-\phi)}$$

$$\Rightarrow S = \underbrace{V_{eff} I_{eff} \cos(\theta - \phi)}_{\text{average power (W)}} + j \underbrace{V_{eff} I_{eff} \sin(\theta - \phi)}_{\text{reactive power (VAR)}}$$

$$S = P + jQ$$

$$|S| = V_{\text{eff}} I_{\text{eff}} = \text{Papparent (VA)}$$

$$Z = R + jX$$

Purely resistive load  $Z = R, X = 0$

$$S = P + jQ \rightarrow V_{\text{eff}} I_{\text{eff}} \frac{\sin(\theta - \phi)}{0}$$

$\downarrow$   
 $V_{\text{eff}} I_{\text{eff}} \cos(\theta - \phi)$

$$P \neq 0$$

$$Q = 0$$

Purely reactive load  $Z = jX, R = 0$


$$S = P + jQ$$

$$P = 0$$

$$Q \neq 0$$

$Q$  signifies energy flow rate into or out of reactive component of load.

### Example

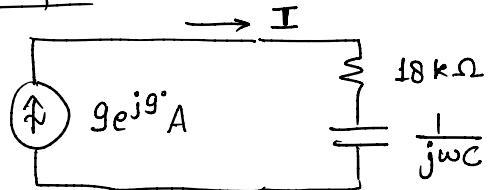

Assume  $C = 1 \mu\text{F}, \omega = 45 \text{ rad/s}$

Find:

- (1) Complex power provided by source
- (2) Time-average power absorbed by combined load.

Find

- (3) Reactive power absorbed by combined load
- (4) Apparent power absorbed by " "
- (5) Power factor of " "

$$S = 1.158 \times 10^6 \angle -50.99^\circ \text{ VA}$$

$$P_{\text{avg}} = 7.29 \times 10^5 \text{ W}$$

$$Q = -9 \times 10^5 \text{ VAR}$$

$$|S| = P_{\text{apparent}} = 1.158 \times 10^6 \text{ VA}$$

$$\text{PF} = 0.629 \text{ leading}$$

$$p(t) = 7.29 \times 10^5 + 1.158 \times 10^6 \cos(90t - 33^\circ) \text{ W}$$