

tr5frbj 12/08/24

## Circuit Theory and Devices

Lab: LT Spice (2nd week onwards)

book: Engineering Circuit Analysis (9th edition)

### Relative grading


Labs	20%
Quiz	20%
Midsem	30%

Scientific calc

Course: 9 modules chapter 10 onwards  
{continuation of BE3}

### Lecture 1

⇒ Linear Circuits

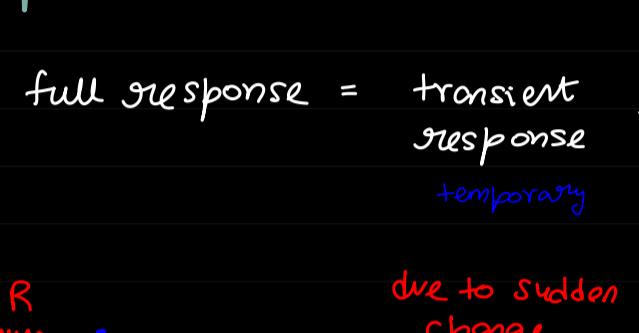

System is linear if

$$Kx \rightarrow [\text{sys}] \rightarrow Ky$$

where  $K$  is constant

"R" Resistor: linear element ✓  
 $V = iR$

"L" Inductor: linear element ✓  
 $V = L \frac{di}{dt}$


### \* Linear Electric Circuits:

consists of ⇒

①  $R, L, C \rightarrow$  linear elements

② Independent voltage & current sources



③ Linear dependent sources

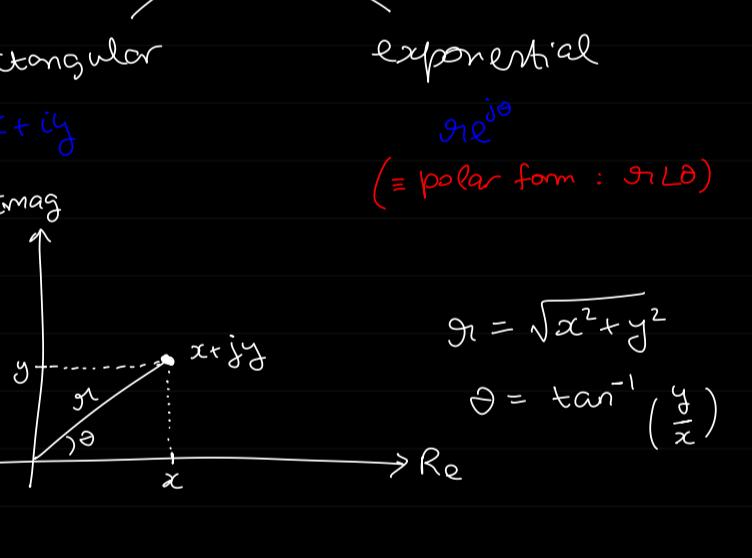

Note: diode and transistors are non-linear elements
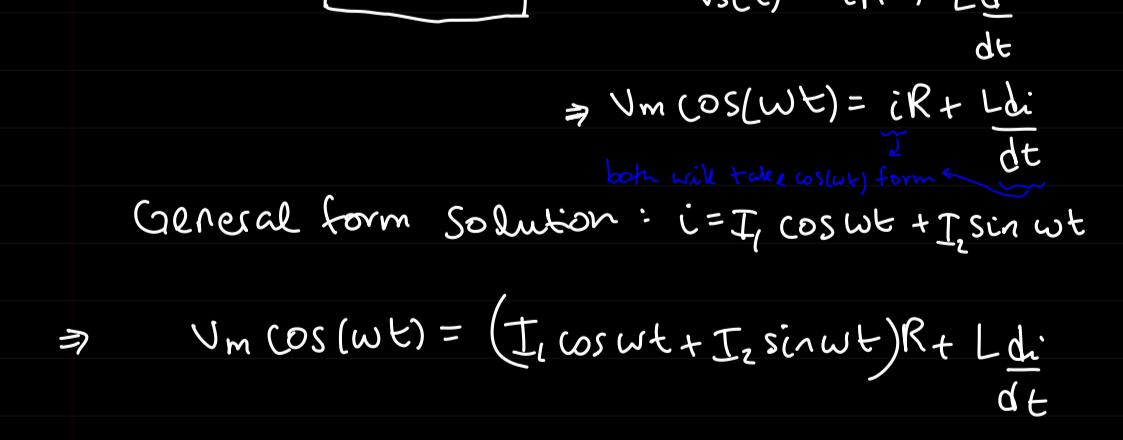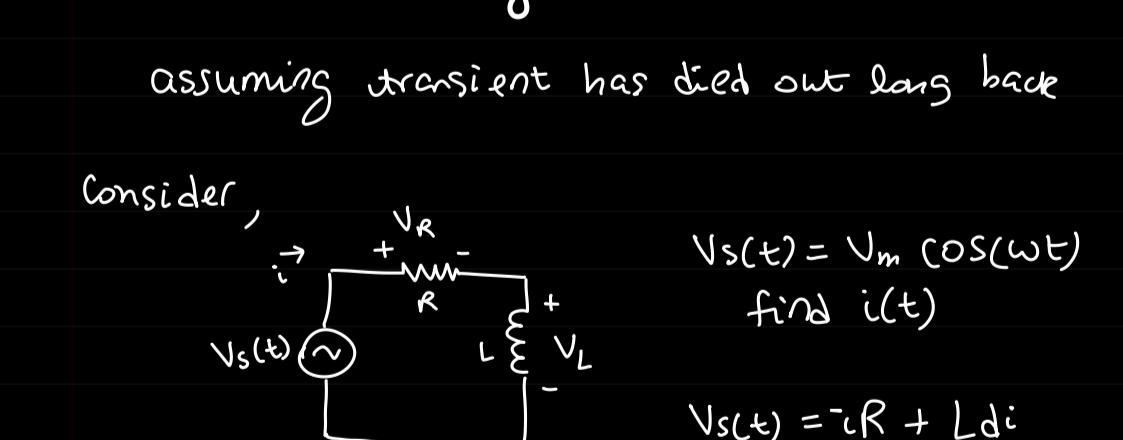
### \* Response of a linear circuit

① full response = transient response + steady state  
transient temporary persists  $t \rightarrow \infty$



$$i_{\text{final}} = i_{\text{transient}} + i_{\text{steady state}}$$

$$\text{as } t \rightarrow \infty, i_{\text{final}} = i_{\text{steady state}}$$

$$V_s(t) = V_m \cos(\omega t)$$

$$V_s(t) = V_m \sin(\omega t)$$

$$V_s(t) = V_m \sin(\omega t + \phi)$$

$$V_s(t) = V_m \cos(\omega t + \phi)$$







## \* Section 10.1

(a)  $Q_1 y \quad 5\sin(5t - 9^\circ)$

$$t=0 \Rightarrow 5\sin(-9^\circ) = -5\sin(9^\circ) = -0.782$$

$$t=0.01 \Rightarrow 5\sin(0.05 - 9^\circ) = -5\sin(8.95^\circ) \quad X$$

$\Downarrow$   
radians

$$5\sin\left(\frac{0.05 \times 80}{\pi} - 9^\circ\right) = 5\sin(2.86^\circ - 9^\circ)$$

$$\Rightarrow -5\sin(6.14^\circ) = -0.534$$

$$t=0.1 \Rightarrow 5\sin(0.5 - 9^\circ) = 5\sin(28.64^\circ - 9^\circ) = 5\sin(19.64^\circ)$$

$$\Rightarrow 1.6805$$

(b)  $4\cos 2t$

$$t=0 \Rightarrow 4\cos(0) = 4$$

$$t=1 \Rightarrow 4\cos(2) = 3.997$$

$$t=1.5 \Rightarrow 4\cos(3) = 3.994$$

(c)  $3.2 \cos(6t + 15^\circ)$

$$t=0 \Rightarrow 3.2 \cos(15^\circ) = 3.09$$

$$t=0.01 \Rightarrow 3.2 \cos(0.06 + 15^\circ) = 3.2 \cos(3.43^\circ + 15^\circ)$$

$$\Rightarrow 3.2 \cos(18.43^\circ)$$

$$\Rightarrow 3.035$$

$$t=0.1 \Rightarrow 3.2 \cos(0.6 + 15^\circ) = 3.2 \cos(34.3^\circ + 15^\circ)$$

$$= 3.2 \cos(49.3^\circ)$$

$$= 2.086$$

Q2) (a)  $300\sin(628t) \rightarrow 300 \cdot \cos(628t - 90^\circ)$


$$4\sin(3\pi t + 30^\circ) \rightarrow 4\cos(3\pi t - 60^\circ)$$

$$14\sin(50t - 8^\circ) - 10\cos 50t \rightarrow$$

Q3)  $V_L = 10\cos(10t - 45^\circ)$


(a)  $i_L = 5\cos 10t$

$$-45^\circ$$

 



## ⇒ AC Power Analysis {Module: 3}

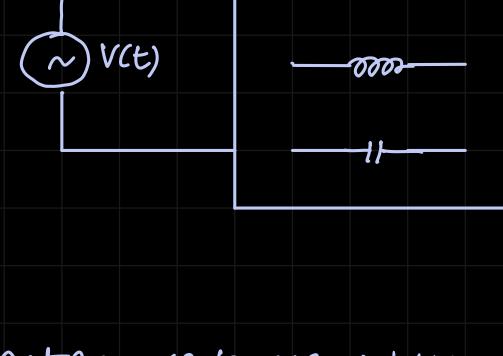

$$\cos(A) \cos(B) =$$

$$\frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

Instantaneous power:  $p(t) = v(t) \cdot i(t)$

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$p(t) = V_m \cos(\omega t + \theta) \cdot I_m \cos(\omega t + \phi)$$

$$p(t) = \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{constant}} + \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)}_{\text{twice frequency}}$$

(DC term)

(harmonic)

## • Average Power

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{real part}} dt + \underbrace{\frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) dt}_{\text{imaginary part}}$$

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

## \* Avg. Power absorbed

## • by a purely resistive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

here, phase diff = 0°




$$P_{avg} = \frac{V_m \cdot I_m}{2} = \frac{I_m^2 R}{2} = \frac{V_m^2}{2R}$$

## • by a purely inductive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

here, phase diff = 90°

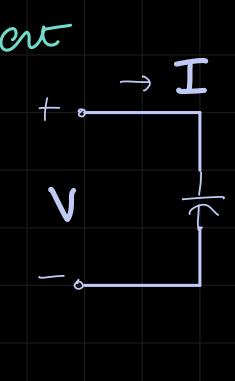

$$P_{avg} = 0 \text{ for inductor}$$

## • by a purely capacitive element

$$P_{avg} = \frac{V_m \cdot I_m}{2} \cos(-90^\circ)$$



## \* Lecture: 6

$$v(t) = V_m \cos(\omega t + \phi) \quad \leftarrow \text{Revision}$$

$$\downarrow$$


$$v(t) = R \Re \{ V_m e^{j\omega t} e^{j\phi} \}$$

$$\downarrow -e^{j\omega t}$$

$$V_m e^{j\phi} = V_m \angle \phi$$

exponential polar

• eq)

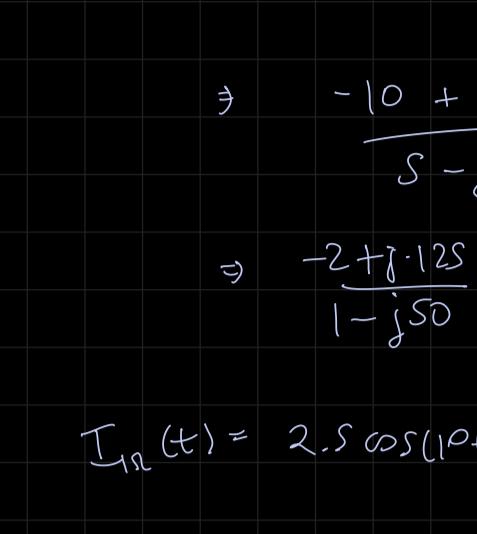


① find power delivered to each element at  $t = 0, 10, 20 \text{ ms}$

② find  $P_{avg}$  to each element

(ans) convert to freq. domain

$$V_{1\text{R}} = V_{u\text{R}} + V_c$$

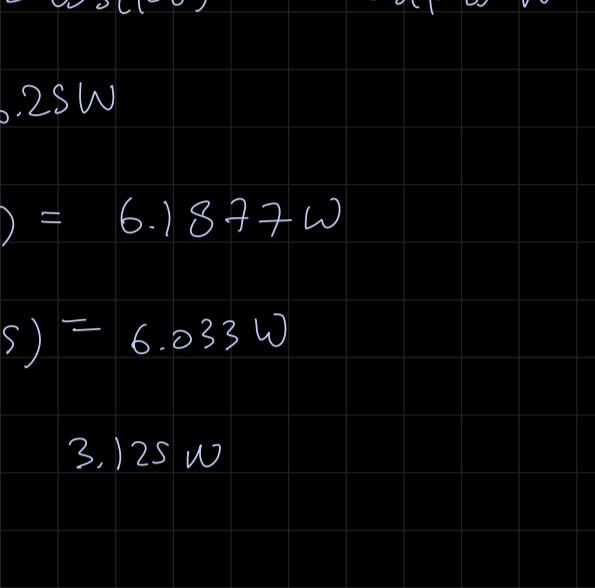

$$\textcircled{1} \quad P_{inst} = \frac{V_m I_m \cos(\theta - \phi)}{2} + \frac{V_m I_m}{2} \cos(2\omega t + \phi + \theta)$$

$$\textcircled{1} \quad I_1 = -2.5 \times \left( \frac{4 - j2.5 \times 10^4}{1 + j - j2.5 \times 10^4} \right) \approx -2.5 \text{ A}$$

$$\Rightarrow \frac{-10 + j62.5 \times 10^4}{5 - j2.5 \times 10^4} \rightarrow \frac{-2 + j12.5}{1 - j50}$$

$$\Rightarrow \frac{-2 + j12.5}{1 - j50} \times \frac{1 + j50}{1 + j50} =$$

$$I_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$V_{1\text{R}} = (I_{1\text{R}})(2 \Omega) \Rightarrow V_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$\cos^2(\theta) = \frac{1 + \cos(2\theta)}{2}$$

$$P_{1\text{R}}(t) = 2.5 \cos(10t) \cdot 2.5 \cos(10t) \text{ W}$$

$$P_{1\text{R}}(t=0) = 6.25 \text{ W}$$

$$P_{1\text{R}}(t=20 \text{ ms}) = 6.033 \text{ W}$$

$$(P_{avg})_{1\text{R}} = 3.125 \text{ W}$$

$\Rightarrow$  P delivered to 4 ohm

$$P_{4\text{R}}(t) = V_{u\text{R}}(t) \times I_{u\text{R}}(t)$$

$$\textcircled{2} \quad I_{4\text{R}} = I_s \times \frac{1}{5 - j2.5 \times 10^4} = 10^{-4} \angle 90^\circ \text{ A}$$

$$V_{u\text{R}} = 4 \times I_{4\text{R}} = 4 \times 10^{-4} \angle 90^\circ \text{ V}$$

convert to time domain

$$P_{4\text{R}}(t) = 2 \times 10^{-8} + 2 \times 10^{-8} \cos(20t) \text{ W}$$

$$t=0^- \quad 4 \times 10^{-8} \text{ W}$$

$$t=10 \text{ ms} = 3.96 \times 10^{-8} \text{ W}$$

$$P_{4\text{R}}(t=20 \text{ ms}) = 2 \times 10^{-8} \text{ W}$$

$\Rightarrow$  P delivered to capacitor

$$P_c(t) = V_c(t) \cdot I_c(t)$$

$$\textcircled{3} \quad P_{avg,c} = 0 \quad \text{since phase diff} = 90^\circ$$

$$I_c = I_2 = 10^{-4} \angle 90^\circ \text{ A} \Rightarrow I_c(t) = 10^{-4} \cos(10t + 90^\circ)$$

$$V_c = (-j2.5 \times 10^4) \times 10^{-4} \angle 90^\circ$$

$$-j2.5 \times 10^4 \times (+j10^4) = 2.5 \text{ V}$$

$$P_c(t) = 1.25 \times 10^{-4} \cos(20t + 90^\circ) \text{ W}$$

$$t=0 \Rightarrow P=0 \text{ W}$$

$$t=10 \text{ ms} \Rightarrow P=2.48 \times 10^{-5} \text{ W}$$

$$P_{avg,c} = 1.25 \times 10^{-4} \text{ W}$$

$$\text{Note: we cannot multiply } I_c \text{ and } V_c \text{ in phasor form and then convert to time domain for getting } P_c \text{ (power) because power does not have a phasor part. It is a real value.}$$

\* Correct or not?

$$\textcircled{1} \quad P_{1\text{R}}(t) + P_{4\text{R}}(t) + P_c(t) = \text{constant 1}$$

$$\textcircled{2} \quad P_{avg,1\text{R}} + P_{avg,4\text{R}} + P_{avg,c} = \text{constant 2}$$

$\Rightarrow$  Pavg source

active sign convention



passive sign convention



\* Maximum Power Transfer Theorem

maximum power delivered to load when

$$Z_L = Z_S^*$$

complex conjugate of  $Z_S$



$\Rightarrow$  Impedance Matching

$$100 \Omega \quad \text{source} \quad \text{load} \quad \text{impedance matching circuit}$$

$$100 \Omega \quad \text{source} \quad \text{load} \quad \text{impedance matching circuit}$$

$$100 \Omega \quad \text{source} \quad \text{load} \quad \text{impedance matching circuit}$$

$$100 \Omega \quad \text{source} \quad \text{load} \quad \text{impedance matching circuit}$$
</div

## \* Lecture: 7


- Instantaneous Power:  $p(t) = v(t)i(t)$
- Average Power:  $P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) = \frac{1}{2} R_{eff} \{VI^*\}$
- $P_{avg, sources} = \sum P_{avg, elements}$

\* Note:  $Z = R + jX$   
 $\downarrow$  resistive      reactive


$P_{avg, resistive} : P \neq 0$

$P_{avg, reactive} : P = 0$


## \* Max Power Transfer:

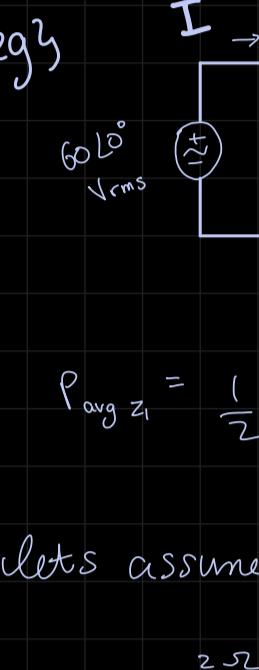

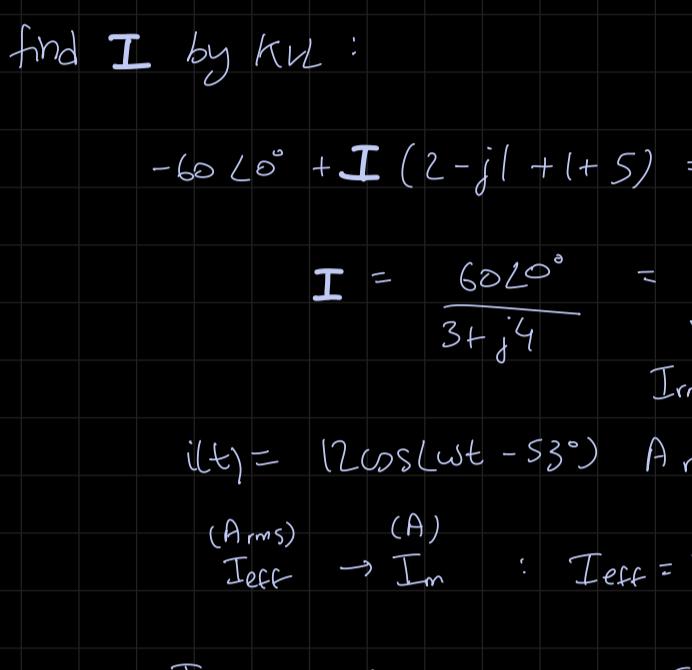Circuit has max. power when  $Z_L = Z_s^*$  complex conjugate



↓ apply Thevenin's theorem

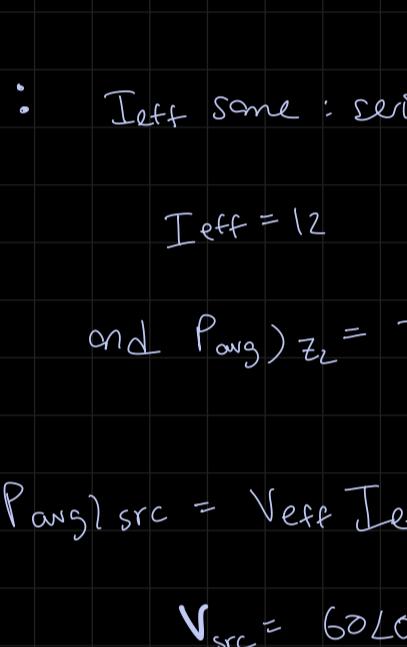

$$Z_L = Z_{th}$$


## \* Power Factor

$$PF = \cos(\theta - \phi) = \frac{\text{Power active}}{\text{Power apparent}}$$

angle of voltage phasor  
↑ angle of current phasor

for purely resistive load:  $PF = 1$  {Max}  $\theta - \phi = 0^\circ$   
 for purely reactive load:  $PF = 0$  {min}

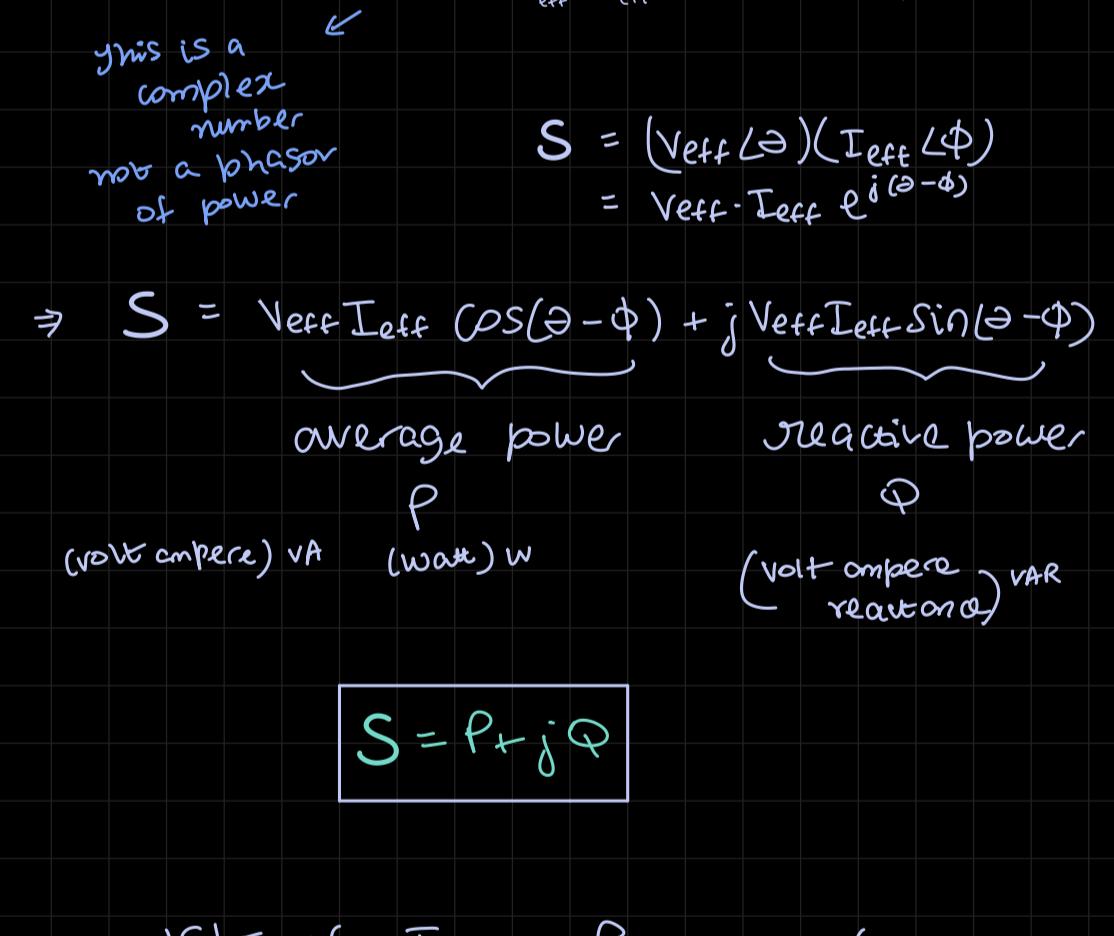Note  $\rightarrow PF = 0.5$  leading  $\rightarrow$  capacitive  $(\theta - \phi) < 0^\circ$   
 $PF = 0.5$  lagging  $\rightarrow$  inductive  $(\theta - \phi) > 0^\circ$



$$\text{Ans}) P_{avg, Z_1} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} R_{eff} \{VI^*\}$$

voltage across  $Z_1$ , not the src

lets assume  $Z_1 = ?$

$$\frac{2-j2}{j1} \parallel \frac{-j2}{j1} \quad \text{so, } P_{avg, Z_1} = \text{Power delivered to } 2\Omega \text{ resistor}$$

$$= I_{eff}^2 R$$

find  $I$  by KVL:

$$-60 \angle 0^\circ + I(2 - j1 + j1) = 0$$

$$I = \frac{60 \angle 0^\circ}{3 + j4} = 12 \angle -53.13^\circ \text{ Arms}$$

$$i(t) = 12 \cos(\omega t - 53.13^\circ) \text{ A rms}$$

$$\frac{(A_{rms})}{I_{eff}} \rightarrow \frac{(A)}{I_m} : I_{eff} = I_m \Rightarrow I_m = I_{eff} \sqrt{2}$$

$$I_{eff} = 12 \text{ Arms} \Rightarrow I_m = 12\sqrt{2} \text{ A}$$

$$i(t) = 12\sqrt{2} \cos(\omega t - 53^\circ) \text{ A}$$

$$P_{avg, Z_1} = (12)^2 \times 2 = 288 \text{ W}$$

$$\text{note: } P_{avg} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$Z_2 : I_{eff} \text{ same : series circuit}$$

$$I_{eff} = 12$$

$$\text{and } P_{avg, Z_2} = I_{eff}^2 R = (144)(1) = 144 \text{ W}$$

$$(2) P_{avg, src} = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$V_{src} = 60 \angle 0^\circ \text{ V rms} \Rightarrow V_{eff} = 60 \text{ V rms}$$

$$I_{src} = 12 \angle -53.13^\circ \text{ V rms} \Rightarrow I_{eff} = 12 \text{ Arms}$$

$$\theta = 0^\circ, \phi = -53.13^\circ$$

$$P_{avg, src} = [60 \times 12] \cos(53.13^\circ) = 432 \text{ W}$$

We can observe that  $288 + 144 = 432$

and hence,

$$P_{avg, sources} = \sum P_{avg, elements} \text{ holds}$$

$$(3) P_{apparent} = V_{eff} \cdot I_{eff} = (60)(12) = 720 \text{ W}$$

$$(4) PF of combined loads = PF of source$$

$$PF = \cos(\theta - \phi) = \cos(0 + 53.13^\circ) = 0.6$$

$\theta - \phi > 0^\circ$  lagging

$\theta - \phi < 90^\circ$  lagging

$$S = V_{eff} I_{eff} \{VI^*\}$$

$$V = V_m \angle \theta \quad I = I_m \angle \phi$$

$$V_{eff} = V_m \angle \theta$$

$$I_{eff} = I_m \angle \phi$$


$$S = P + jQ$$

$$S = P + jQ</$$

## \* Lecture - 8

### • Polyphase Circuits (Chp 12)

⇒ Three Phase Source

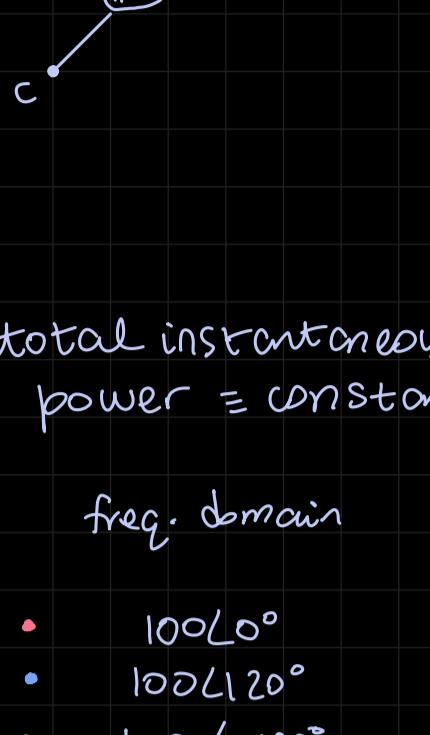

$$V_{an} = 100\angle 0^\circ \text{ V}$$

$$V_{bn} = 100\angle 120^\circ \text{ V}$$

$$V_{cn} = 100\angle -120^\circ \text{ V}$$

if  $|V_{an}| = |V_{bn}| = |V_{cn}|$   
 &  $V_{an} + V_{bn} + V_{cn} = 0$   
 then it is a

Balanced Source


total instantaneous power = constant

freq. domain

- $100\angle 0^\circ$
- $100\angle 120^\circ$
- $100\angle -120^\circ$

time domain

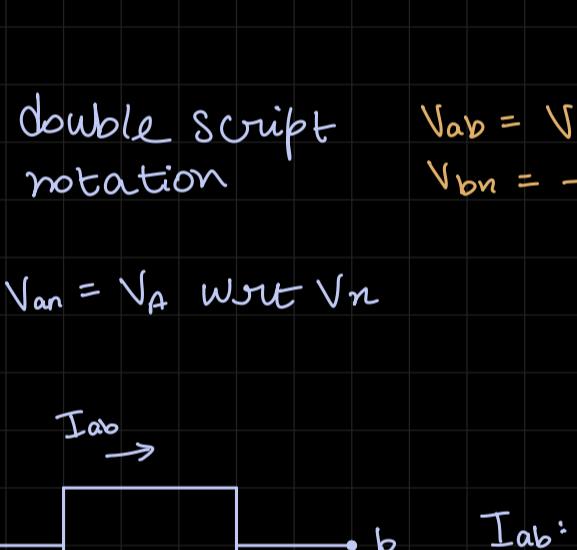
- $100 \cos(\omega t)$
- $100 \cos(\omega t + 120^\circ)$
- $100 \cos(\omega t - 120^\circ)$



total  $p(t) \rightarrow \text{constant}$

## \* Single Phase Three-wire Source

≡ Two phase source

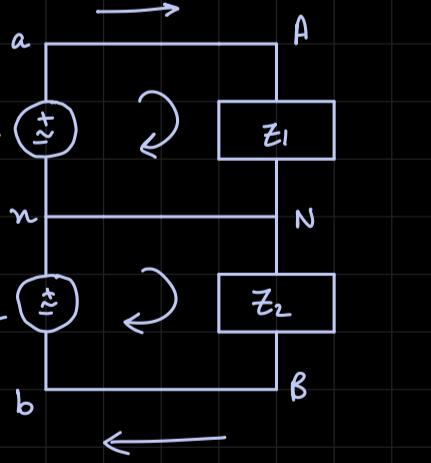

$$V_1 = V_m \angle 0^\circ$$

$$V_{an} = V_1 = V_m \angle 0^\circ$$

$$V_{bn} = -V_1 = V_m \angle 0^\circ - 180^\circ$$

$$V_{bn} \leftarrow \xrightarrow{180^\circ} V_{an}$$

double script notation

$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} = V_{an} + V_{nb} \\ V_{bn} &= -V_{nb} \end{aligned}$$

$$V_{an} = V_A \text{ wrt } V_n$$



$$I_{aa} = \frac{V_1}{Z_1}$$

$$I_{bb} = \frac{V_1}{Z_2}$$

$$I_{nn} = -I_{aa} + I_{bb}$$

$$\Rightarrow \frac{V_1}{Z_1} - \frac{V_1}{Z_2}$$

Assume  $Z_1 = Z_2$

$$I_{nn} = \frac{V_1}{Z_1} - \frac{V_1}{Z_1} = 0$$

when both srcs &  
and loads are equal

Balanced Load : current in neutral line is equal to zero.



all terms are phasors

even with resistance,  
 $I_{nn} = 0 = I_{bb} - I_{aa}$

due to

① Balanced Load  
 ≡ Symmetry



all terms are phasors

even with resistance,  
 $I_{nn} = 0 = I_{bb} - I_{aa}$

due to

① Balanced Load  
 ≡ Symmetry

## \* Lecture: 9

09/09/29

time domain      freq. domain

$$\begin{array}{ll} \sqrt{V_p} \cos(\omega t + \theta^\circ) & \sqrt{V_p} L^{\theta^\circ} \\ \sqrt{V_p} \cos(\omega t + \theta^\circ - 180^\circ) & \sqrt{V_p} L^{\theta^\circ - 180^\circ} \end{array}$$

We cannot directly say,

$$P_{avg} = \sqrt{I} \quad \times$$

$$\text{but } P_{avg} = \frac{1}{2} \operatorname{Re}\{ \sqrt{I} I^* \} \quad \checkmark$$

$$\begin{aligned} \textcircled{2} \quad a) \quad I_{AB} &= \frac{115 L^{\theta^\circ} + 115 L^{\theta^\circ}}{2(10 + j^2)} = \frac{230 L^{\theta^\circ}}{2(10 + j^2)} \\ &= 11.27 / (\theta^\circ - 11.3^\circ) A \end{aligned}$$


$$\phi = \theta - 11.3^\circ$$

$$PF = \cos(\theta - \phi + 11.3^\circ) = 0.98 \text{ lagging}$$

because PF angle is true

$$b) \quad PF = 1 \Rightarrow \cos(\theta - \phi) = 1 \Rightarrow \theta - \phi = 0$$

$$\Rightarrow \theta = \phi$$

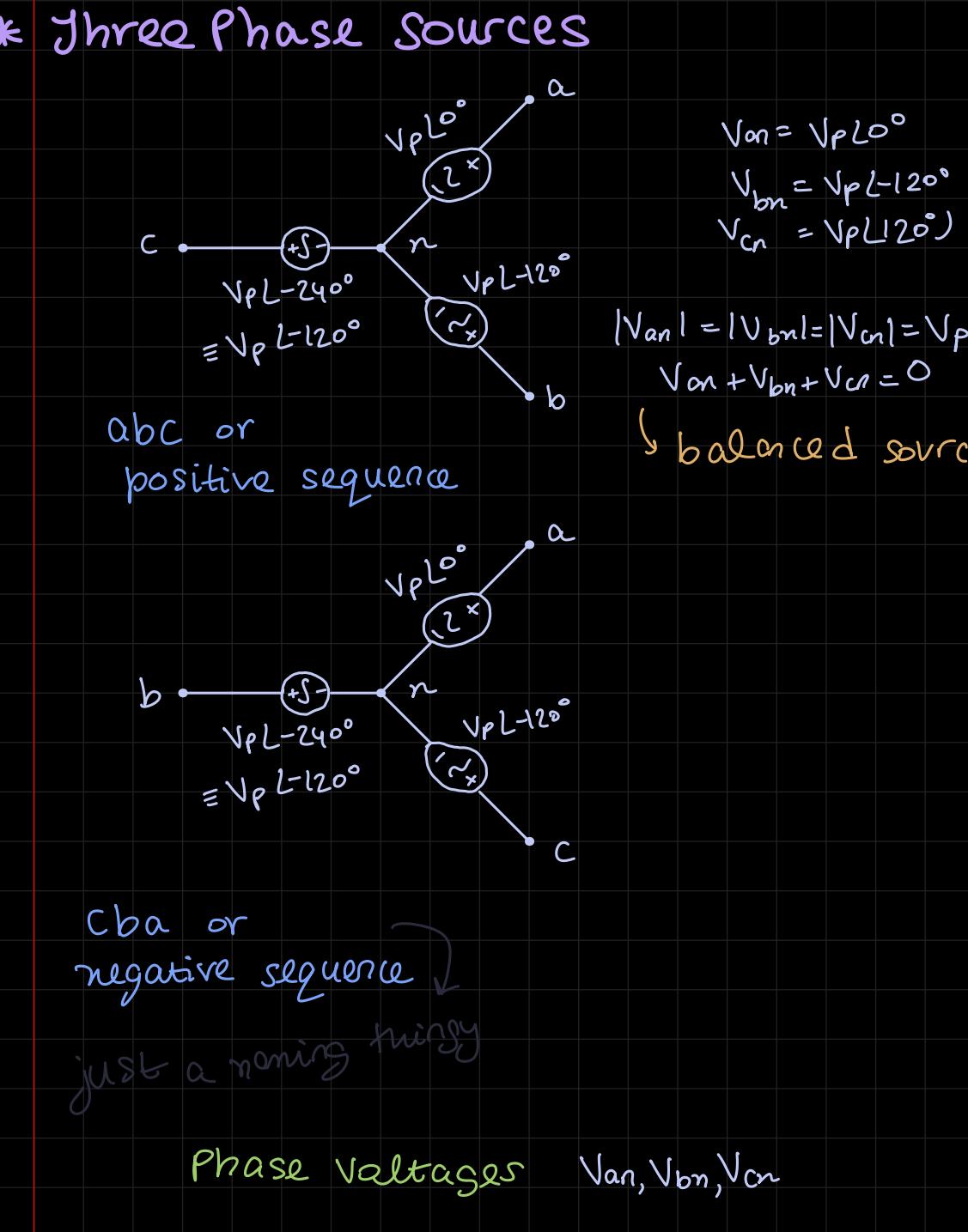

Note that this is still a balanced load, so we can remove MN since  $I_{MN} = 0$

using complex power

$S = \text{complex power of total load}$

$$S = \frac{1}{2} \sqrt{I} I^*$$

$$PF = \frac{\operatorname{Re}\{S\}}{|S|} = 1 \Rightarrow \operatorname{Re}\{S\} = |S|$$

so,  $\operatorname{Im}\{S\} = 0$  here

$$S = \frac{1}{2} V_{an} I_{An}^* + \frac{1}{2} V_{nb} I_{Nb}^* + \frac{1}{2} V_{ab} I_{Ab}^*$$

$$\Rightarrow \frac{1}{2} V_{an} \left( \frac{V_{an}}{Z_p} \right)^* + \frac{1}{2} V_{nb} \left( \frac{V_{nb}}{Z_p} \right)^* + \frac{1}{2} V_{ab} \left( \frac{V_{ab}}{Z_p} \right)^*$$

$$\Rightarrow \frac{1}{2} \frac{|V_{an}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{nb}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{ab}|^2}{|Z_p|^2} Z_p$$

$$\Rightarrow \frac{115^2}{10^4} (10 + j^2) + \frac{1}{2} \left( \frac{230^2}{(j\omega C)^2} \right) \left( \frac{-j}{\omega C} \right) = \frac{1}{j\omega C} \times \frac{-1}{j\omega C}$$

$$\Rightarrow 115^2 \left( \frac{10 + j^2}{10^4} - \frac{1}{j\omega C} \right)$$

$$\Rightarrow 2 \times 115^2 \left( \frac{j}{10^4} - \frac{1}{j\omega C} \right)$$

$$\Rightarrow 2 \times 115^2 \left( \frac{1}{10^4} - \omega C \right) = 0$$

$$\frac{1}{10^4} - 100\pi C = 0$$

$$C = \frac{1}{10400\pi} = 30.6 \mu F \quad \checkmark$$

## \* Three Phase Sources



just a naming thingy

Phase Voltages  $V_{an}, V_{bn}, V_{cn}$

Line-to-line Voltages  $V_{ab}, V_{bc}, V_{ca}$  OR line voltages

$$V_{ab} = V_{an} - V_{bn} = V_{an} + V_{nb}$$

$$V_{ab} = \sqrt{3} V_p L^{30^\circ}$$

$$V_{bc} = \sqrt{3} V_p L^{-90^\circ}$$

$$V_{ca} = \sqrt{3} V_p L^{-210^\circ}$$

## \* Y-Y connection



used for easier analysis

e.g. to find total power by CRT, just add the three individual power obtained from above CRTs.

going back to the Y-Y connection  $\rightarrow$

$$I_{aa} = \frac{V_{an}}{Z_p}$$

$$I_{bb} = \frac{V_{bn}}{Z_p} = \frac{V_{an} L^{-120^\circ}}{Z_p} = I_{aa} L^{-120^\circ}$$



$$I_{cc} = \frac{V_{cn}}{Z_p} = \frac{V_{an} L^{+120^\circ}}{Z_p} = I_{aa} L^{+120^\circ}$$

$$\Rightarrow I_{aa} + I_{bb} + I_{cc} = 0$$

$$\frac{1}{10^4} - 100\pi C = 0$$

$$C = \frac{1}{10400\pi} = 30.6 \mu F \quad \checkmark$$
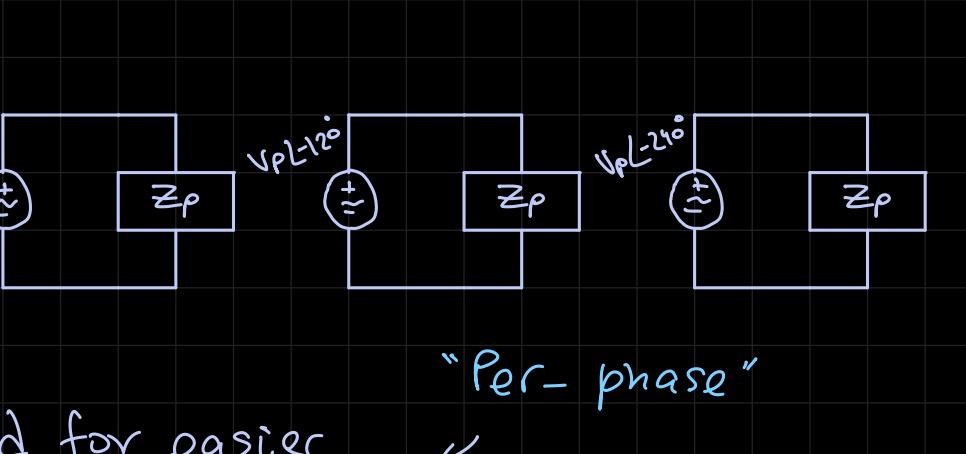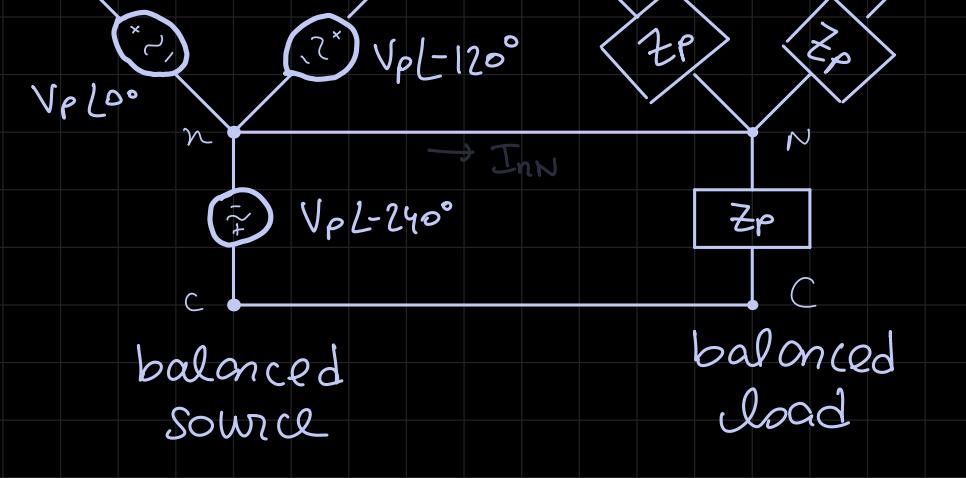
## \* Three Phase Balanced Y-Y Connected System



just a naming thingy

Phase Voltages  $V_{an}, V_{bn}, V_{cn}$

Line-to-line Voltages  $V_{ab}, V_{bc}, V_{ca}$  OR line voltages

$$V_{ab} = V_{an} - V_{bn} = V_{an} + V_{nb}$$

$$V_{ab} = \sqrt{3} V_p L^{30^\circ}$$

$$V_{bc} = \sqrt{3} V_p L^{-90^\circ}$$

$$V_{ca} = \sqrt{3} V_p L^{-210^\circ}$$

## \* Line Currents:

$$I_{aa} = \frac{V_{an}}{Z_p} = \frac{200 L^{\theta^\circ}}{100 L^{60^\circ}} = 2 L^{-60^\circ} A_{rms}$$

$$I_{bb} = 2 L^{-180^\circ} A_{rms}$$

$$I_{cc} = 2 L^{-300^\circ} A_{rms} = 2 L^{60^\circ} A_{rms}$$

$$\text{total avg. power: } P_{avg} = \frac{1}{2} \operatorname{Re}\{ \sqrt{I} I^* \}$$

in phase A:

$$P_{avg,A} = \frac{1}{2} \operatorname{Re}\{ \sqrt{I} I^* \}$$

$$= \operatorname{Re}\{ \sqrt{I} \operatorname{Re}\{ I \} \}$$

$$= \operatorname{Re}\{ 200 L^{\theta^\circ} \times 2 L^{-60^\circ} \}$$


$$\Rightarrow \operatorname{Re}\{ 400 L^{-60^\circ} \} \Rightarrow 400 \cos(-60^\circ) = 200 W$$

$$P_{avg,B} = 200 W$$

$$P_{avg,C} = 200 W$$

$$\Rightarrow P_{avg,\text{total}} = 600 W$$

→ Y-Y connection

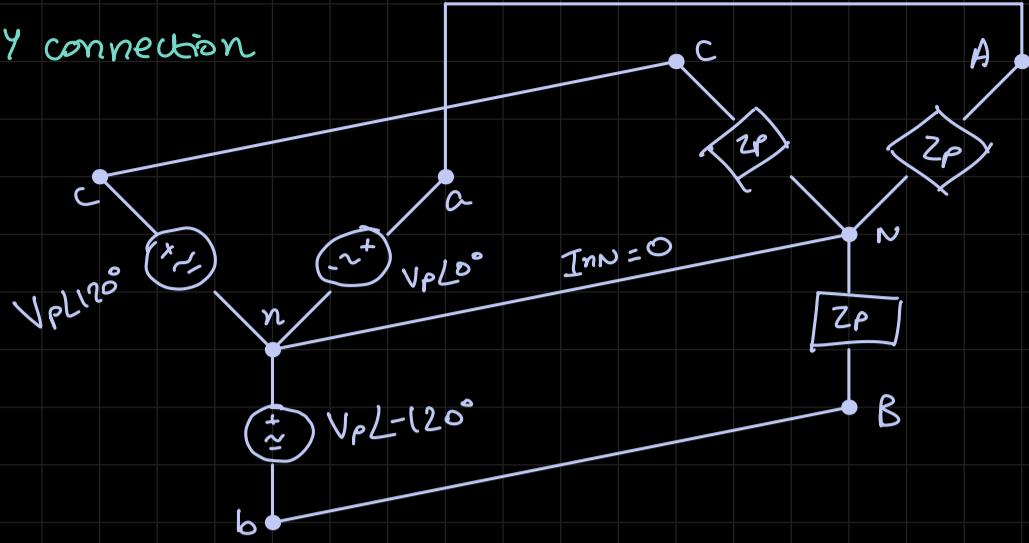

balanced load: all load are same

balanced src: all src magnitudes are equal

line: lines connecting load to src

aa cC

bb nn

Phase Voltages: V<sub>AN</sub> = V<sub>aN</sub>, V<sub>BN</sub> = V<sub>bN</sub>, V<sub>CN</sub> = V<sub>cN</sub>line voltages: V<sub>ab</sub>, V<sub>bc</sub>, V<sub>ca</sub>line currents: I<sub>aA</sub>, I<sub>bB</sub>, I<sub>cC</sub>phase currents: I<sub>AN</sub> = I<sub>aA</sub>, I<sub>BN</sub> = I<sub>bB</sub>, I<sub>CN</sub> = I<sub>cC</sub>

$$V_{an} = V_p L 0^\circ$$

$$V_{bn} = V_p L -120^\circ$$


$$V_{cn} = V_p L -240^\circ$$

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_p L 30^\circ$$

$$V_{bc} = \sqrt{3} V_p L -90^\circ$$

$$V_{ca} = \sqrt{3} V_p L -210^\circ$$

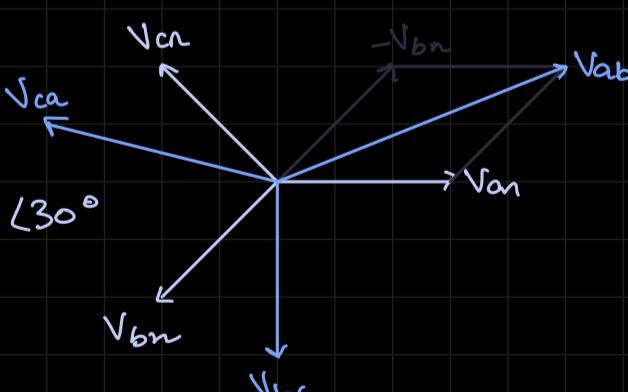

line voltages

$$V_{\text{line}} = \sqrt{3} V_{\text{phase}}$$

line currents = phase currents

\* Total Instantaneous Power

$$P_{\text{total}}(t) = P_A(t) + P_B(t) + P_C(t)$$

# Classes & Attribs

interface (entity)

~~ ~~~

Bird

↓

dmg  
(chits)

Pig

↓

health  
(units)

User

↓

save  
stage

level mg

blocks

pigs

type

→ max-score

→ no. of pigs

center point

Game

update score

wood

glass

steel

Score

level-status

Slingshot

angle

stretch

↙

$b^\circ$



$$v = 10 \text{ m/s}$$

0°

180°

S, P

$$\sqrt{v \cos \theta, v \sin \theta}$$

per second


/ rate

-1 → 0


\* TODO: revise lecture 11 (missed due to SNS quiz)

## \* Lecture 12:

eg 3

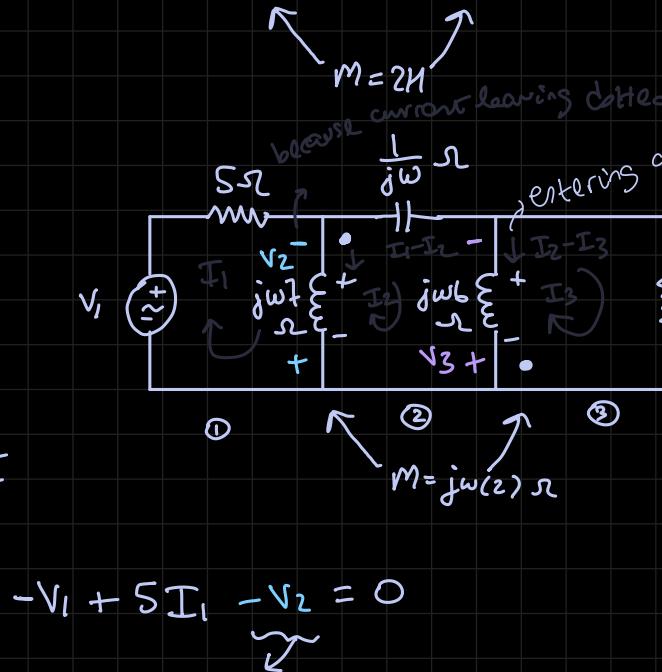

ans 3

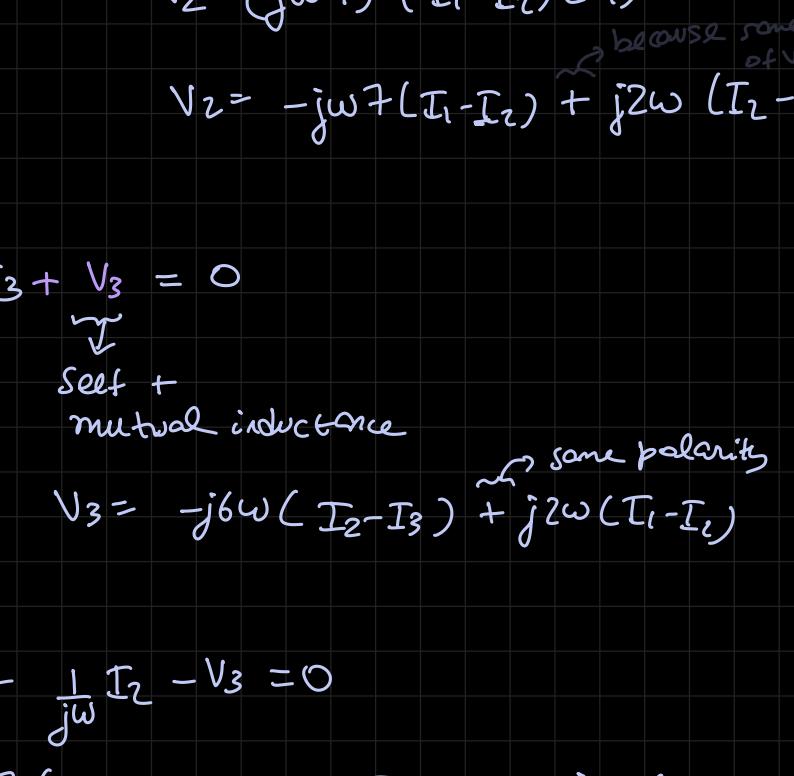

$$\textcircled{1} \quad -V_1 + 5I_1 - V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)(-1)$$

$$V_2 = -j\omega 7(I_1 - I_2) + j2\omega(I_2 - I_3)$$

$$\textcircled{3} \quad 3I_3 + V_3 = 0$$

Self + mutual inductance


$$V_3 = -j6\omega(I_2 - I_3) + j2\omega(I_1 - I_2) \quad \text{some polarity}$$

$$\textcircled{2} \quad V_2 + \frac{1}{j\omega} I_2 - V_3 = 0$$

$$-j\omega 7(I_1 - I_2) + j2\omega(I_2 - I_3) + j6\omega(I_2 - I_3) - j2\omega(I_1 - I_2) + \frac{I_2}{j\omega} = 0$$

$$I_1(-j5\omega) + I_2(j17\omega) + I_3(-j8\omega) + \frac{I_2}{j\omega} = 0$$

eg 3

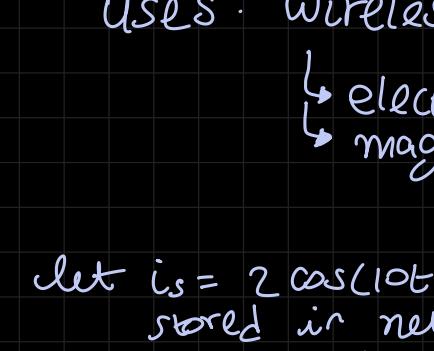

$$-V_1 + 5I_1 + V_2 = 0$$


$$V_2 = (j\omega 7)(I_1 - I_2)$$

+ (j\omega 2)(I\_2 - I\_3)

We don't need to care about this sign if we use  $V_2, V_3$  method.
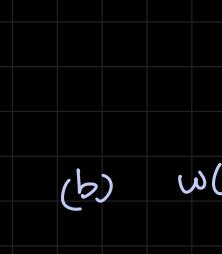
## \* ENERGY STORED

$$W(t) = \frac{1}{2} L(i(t))^2 \quad \text{for only one inductor}$$



$$W(t) = \frac{1}{2} L(i_1)^2 + \frac{1}{2} L(i_2)^2 \pm M i_1(t) i_2(t)$$

[+ve] sign with occur iff both  $i_1$  and  $i_2$  are entering either dotted or undotted

[-ve] sign iff both enter different (dotted/undotted)

- Coupling coefficient ( $K$ )

$$M \leq \sqrt{L_1 L_2}$$

$$K = \frac{M}{\sqrt{L_1 L_2}} \Rightarrow 0 \leq K \leq 1$$

$K \rightarrow 0$

poor coupling or no coupling

$K \rightarrow 1$

Strong coupling (very close to each other)

$\Rightarrow K$  depends on: distance; size; ferrite b/w coils; of coils core

$$y \propto \frac{1}{x}$$

$$y \propto x$$

$$y \propto x$$


uses: wireless power transfer  $\leftarrow$  (inductively coupled)

↳ electric vehicle charging

↳ magSafe charging

eg 3 let  $i_s = 2 \cos(10t)$  A. find total energy stored in network at  $t=0$  if  $K=0.6$  and

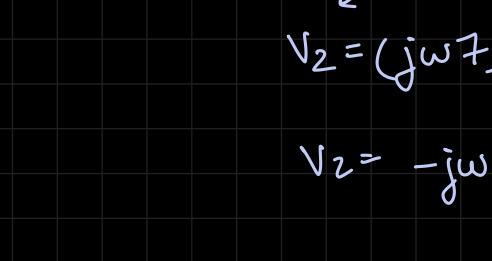- (a) if  $x_y$  terminals are open circuited
- (b) if  $x_y$  are short circuited



$$j\omega L_1 = j^4 \Rightarrow L_1 = \frac{4}{\omega} = 0.4 \text{ H}$$


$$i_1 = i_s = 2 \cos(10t)$$

$$W(t) = \frac{1}{2} L_1(i_1)^2 + \frac{1}{2} L_2(i_2)^2 - M i_1(t) i_2(t)$$

$$i_2 = \frac{V_x}{j2S} \quad \text{and} \quad V_x = -j\omega M I_1$$

$$i_2 = -0.6 \frac{(2 \cos 10t)}{2.5} = -0.48A$$
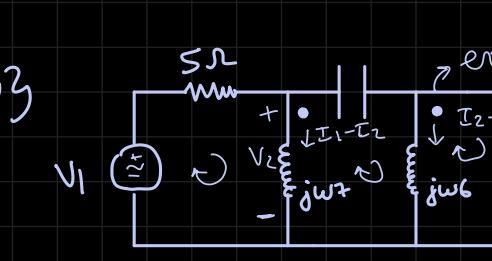
$$W(t=0) = \frac{1}{2} (0.4) (2^2) + \frac{1}{2} (0.4) (-0.48)^2$$




$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

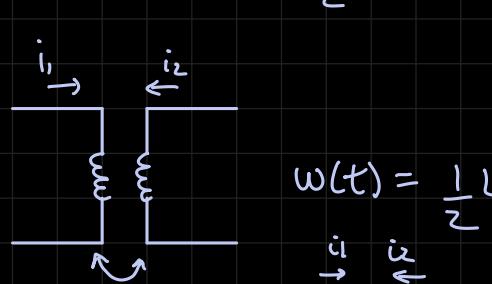We don't need to care about this sign if we use  $V_2, V_3$  method.




$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

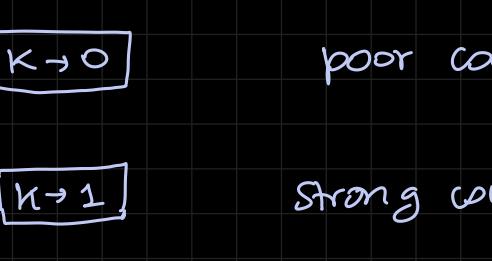We don't need to care about this sign if we use  $V_2, V_3$  method.




$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

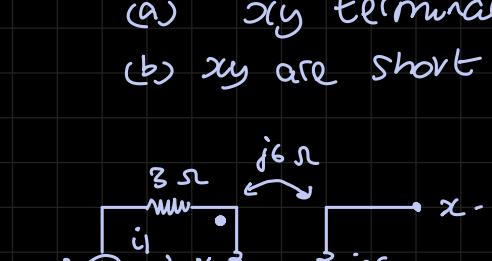We don't need to care about this sign if we use  $V_2, V_3$  method.




$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

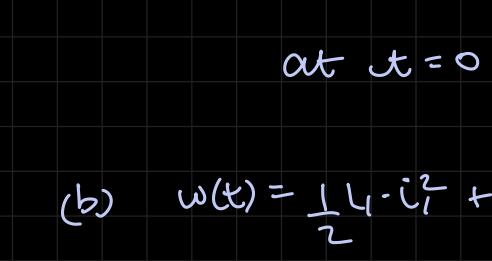We don't need to care about this sign if we use  $V_2, V_3$  method.




$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

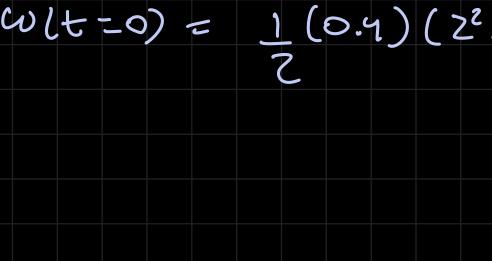We don't need to care about this sign if we use  $V_2, V_3$  method.



$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

We don't need to care about this sign if we use  $V_2, V_3$  method.



$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

We don't need to care about this sign if we use  $V_2, V_3$  method.



$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

We don't need to care about this sign if we use  $V_2, V_3$  method.



$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

We don't need to care about this sign if we use  $V_2, V_3$  method.



$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

We don't need to care about this sign if we use  $V_2, V_3$  method.



$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

We don't need to care about this sign if we use  $V_2, V_3$  method.



$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

We don't need to care about this sign if we use  $V_2, V_3$  method.



$$-V_1 + 5I_1 + V_2 = 0$$


$$V_2 = (j\omega 7)(I_1 - I_2)$$

$$+ (j\omega 2)(I_2 - I_3)$$

We don't need to care about this sign if we use  $V_2, V_3$  method.


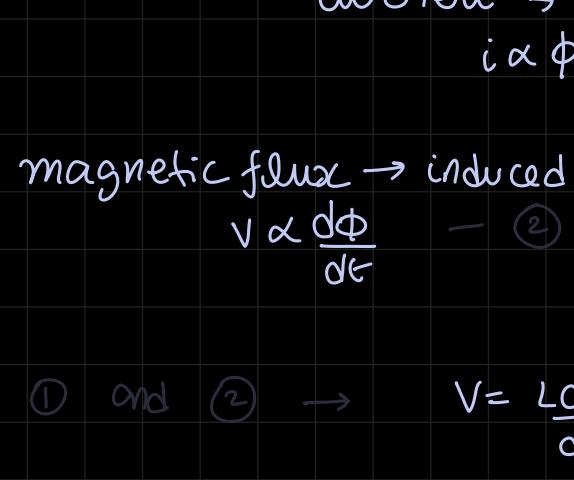
## • MODULE 5: Magnetically coupled circuits



current  $\rightarrow$  magnetic flux  
 $i \propto \phi$  — ①

magnetic flux  $\rightarrow$  induced voltage



$$V \propto \frac{d\phi}{dt} \quad \text{— ②}$$

① and ②  $\rightarrow V = L \frac{di}{dt}$

for DC source: current is constant

hence  $\frac{di}{dt} = 0$  and  $\therefore V = 0$   
 (induced)

## • Mutual Inductance

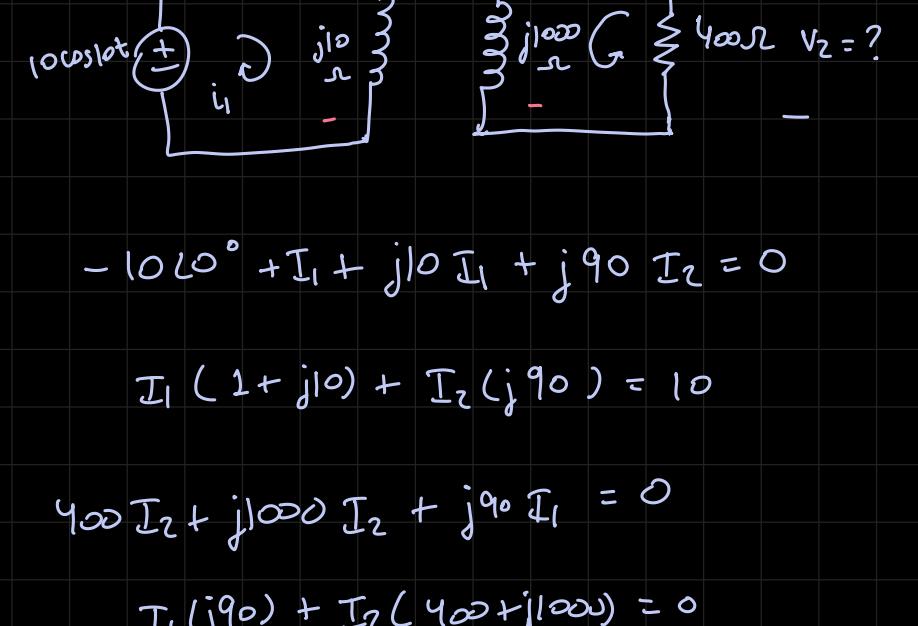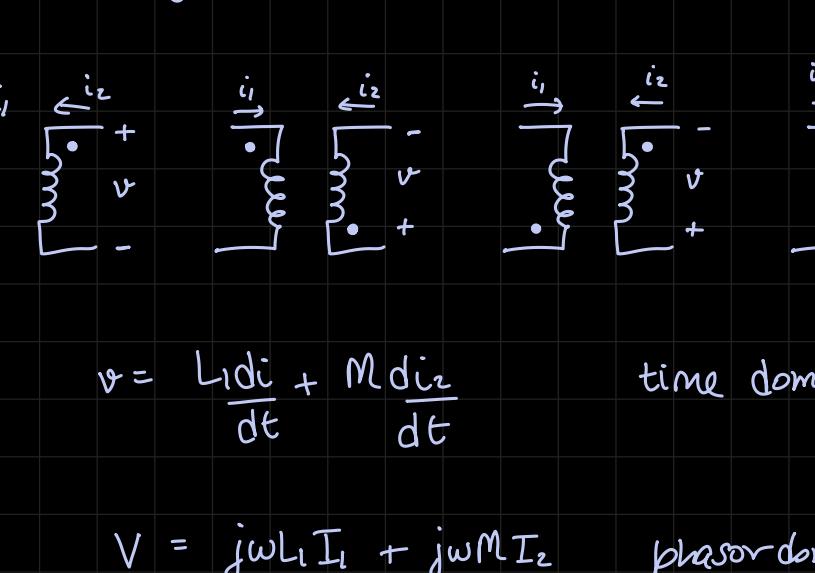

\* Additive/Subtractive Property {two different coils?}

$$i_1 \text{ (clockwise)} \quad i_2 \text{ (counter-clockwise)} \quad v_2 = L \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$i_1 \text{ (clockwise)} \quad i_2 \text{ (clockwise)} \quad v_2 = L \frac{di_2}{dt} - M \frac{di_1}{dt}$$

## • Dotted Notation

Current entering + terminal means  
 +ve voltage reference at -

$$v = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \text{time domain}$$

$$V = j\omega L_1 I_1 + j\omega M I_2 \quad \text{phasor domain}$$

$$\text{eg: } \begin{array}{c} 1 \Omega \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{c} M \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{c} M \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{c} 4 \Omega \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{c} + \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{c} - \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{c} + \\ \text{---} \\ \text{---} \end{array} \quad \begin{array}{c} - \\ \text{---} \\ \text{---} \end{array}$$

$$\Delta = \begin{vmatrix} 1+j10 & j1000 \\ j90 & 400+j1000 \end{vmatrix} = -400 - j10.000 = 10770 \angle -111.8^\circ$$

$$\Delta_1 = \begin{vmatrix} j1000 & 10 \\ 400+j1000 & 0 \end{vmatrix} = -400 - j10.000 = 10770 \angle -111.8^\circ$$

$$\Delta_2 = \begin{vmatrix} 10 & 1+j10 \\ 0 & j90 \end{vmatrix} = j900 = 900 \angle 90^\circ$$

$$I_1 = \frac{\Delta}{\Delta_1} = -3.2 + 6.75j$$

full current part

wrong because I took  $M = L_2 = j1000$  above

$$\Delta_0 = \begin{vmatrix} 1+j10 & j90 \\ j90 & 400+j1000 \end{vmatrix} = 400+j1000 - j4000 - 10.000 + 8100 = j5000 - 1500 = 5220 \angle 106.69^\circ$$

Energy stored in the circuit?

$$w(t) = \frac{1}{2} L_1 i_1(t)^2 + \frac{1}{2} L_2 i_2(t)^2 + M i_1(t) i_2(t)$$

+: current entering same: • and • OR - and -

-: current entering different: • and - OR - and •

## Coupling Coefficient ( $k$ )

$$k = \frac{M}{\sqrt{L_1 L_2}} \quad ; \quad \text{note } M \leq \sqrt{L_1 L_2}$$

$$\therefore 0 \leq k \leq 1$$

$$I_1 = \frac{\Delta}{\Delta_1} = -3.2 + 6.75j$$

full current part

wrong because I took  $M = L_2 = j1000$  above

$$\Delta_0 = \begin{vmatrix} 1+j10 & j90 \\ j90 & 400+j1000 \end{vmatrix} = 400+j1000 - j4000 - 10.000 + 8100 = j5000 - 1500 = 5220 \angle 106.69^\circ$$

$$\Delta_1 = \begin{vmatrix} j1000 & 10 \\ 400+j1000 & 0 \end{vmatrix} = -400 - j10.000 = 10770 \angle -111.8^\circ$$

$$\Delta_2 = \begin{vmatrix} 10 & 1+j10 \\ 0 & j90 \end{vmatrix} = j900 = 900 \angle 90^\circ$$

$$I_1 = \frac{\Delta}{\Delta_1} = -3.2 + 6.75j$$

full current part

wrong because I took  $M = L_2 = j1000$  above

$$\Delta_0 = \begin{vmatrix} 1+j10 & j90 \\ j90 & 400+j1000 \end{vmatrix} = 400+j1000 - j4000 - 10.000 + 8100 = j5000 - 1500 = 5220 \angle 106.69^\circ$$

$$I_1 = \frac{\Delta}{\Delta_1} = -3.2 + 6.75j$$

full current part

wrong because I took  $M = L_2 = j1000$  above

$$\Delta_0 = \begin{vmatrix} 1+j10 & j90 \\ j90 & 400+j1000 \end{vmatrix} = 400+j1000 - j4000 - 10.000 + 8100 = j5000 - 1500 = 5220 \angle 106.69^\circ$$

$$I_1 = \frac{\Delta}{\Delta_1} = -3.2 + 6.75j$$


full current part

wrong because I took  $M = L_2 = j1000$  above

$$\Delta_0 = \begin{vmatrix} 1+j10 & j90 \\ j90 & 400+j1000 \end{vmatrix} = 400+j1000 - j4000 - 10.000 + 8100 = j5000 - 1500 = 5220 \angle 106.69^\circ$$
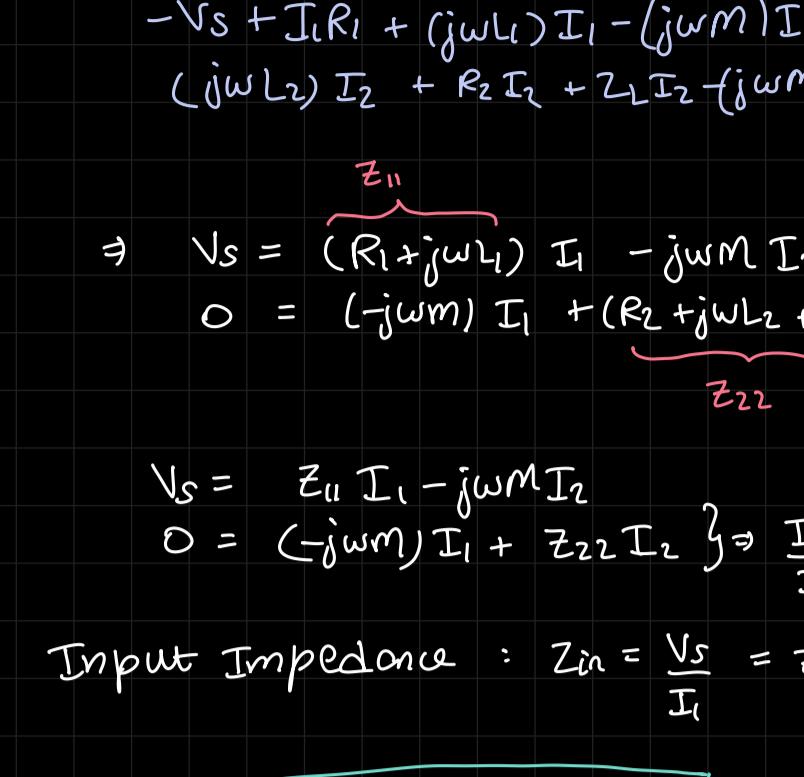
## • LINEAR TRANSFORMER

When  $V \propto \frac{di}{dt} \Rightarrow$  no magnetic core



$$-Vs + I_1 R_1 + (j\omega L_1) I_1 - (j\omega M) I_2 = 0$$

$$(j\omega L_2) I_2 + R_2 I_2 + Z_L I_2 - (j\omega M) I_1 = 0$$

$$\Rightarrow V_s = (R_1 + j\omega L_1) I_1 - j\omega M I_2$$

$$0 = (-j\omega M) I_1 + (R_2 + j\omega L_2 + Z_L) I_2$$

$$V_s = Z_{11} I_1 - j\omega M I_2$$

$$0 = (-j\omega M) I_1 + Z_{22} I_2 \Rightarrow \frac{I_2}{I_1} = \frac{j\omega M}{Z_{22}}$$

$$\text{Input Impedance : } Z_{in} = \frac{V_s}{I_1} = Z_{11} - j\omega M \frac{I_2}{I_1}$$

$$Z_{in} = Z_{11} + \underbrace{\frac{\omega^2 M^2}{Z_{22}}}_{\text{Reflective Impedance}}$$


where

$$Z_{11} = R_1 + j\omega L_1, \quad Z_{22} = R_2 + j\omega L_2 + Z_L$$

- if  $K = \frac{M}{\sqrt{L_1 L_2}} = 0 \Rightarrow Z_{in} = Z_{11}$  i.e. no coupling

## • T EQUIVALENT NETWORK

(no mutual coupling)

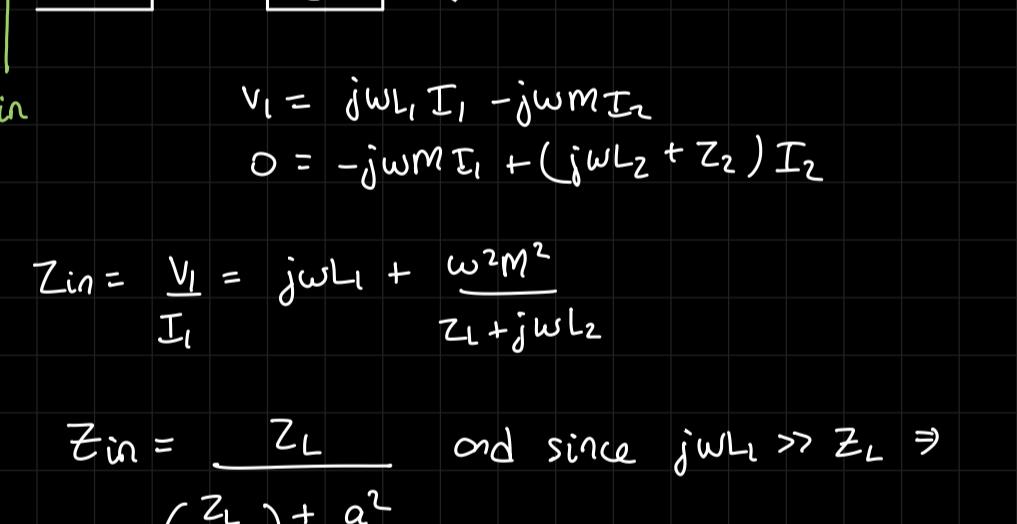


$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

Note: no mutual coupling since there is no arrow for it

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$V_1 = (L_1 - M) \frac{di_1}{dt} + M \left( \frac{di_1}{dt} + \frac{di_2}{dt} \right)$$

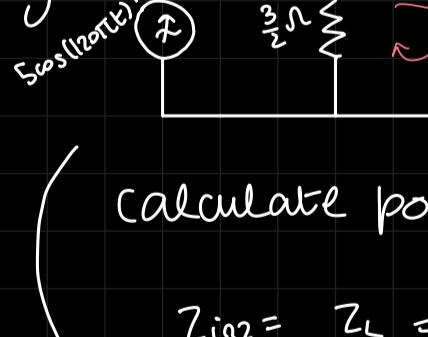Note: if dots are on opposite sides, replace M with -M



similarly, we get  
V2 same as we got  
in the left circuit  
Hence, both circuits  
are equivalent.

## • π EQUIVALENT NETWORK

$$Z_{in} = \frac{V_1}{I_1} = j\omega L_1 + \frac{\omega^2 M^2}{Z_L + j\omega L_2}$$

use nodal analysis to prove this

$$L_B = \frac{L_1 L_2 - M^2}{M}$$

$$V = L \frac{di}{dt} \Rightarrow i = \frac{1}{L} \int_v dt$$

$$L_C = \frac{L_1 L_2 - M^2}{L_1 - M}$$

$$i = i(0) u(t) + \frac{1}{L} \int_v dt$$

if dots are on opposite sides:  $M \rightarrow -M$

## • IDEAL TRANSFORMER

$$K=1 \Rightarrow \text{achieved only with ferrite core (iron)}$$

$$+ \xrightarrow{K=1} \left| \begin{array}{c} \bullet \\ \circ \end{array} \right| \parallel \left| \begin{array}{c} \bullet \\ \circ \end{array} \right| \xrightarrow{+} V_2$$

$$Z_{in} = \frac{V_1}{I_1} = j\omega L_1, \quad V_1 = j\omega L_1 I_1 - j\omega M I_2$$

$$0 = -j\omega M I_1 + (j\omega L_2 + Z_L) I_2$$

$$Z_{in} = \frac{V_1}{I_1} = j\omega L_1 + \frac{\omega^2 M^2}{Z_L + j\omega L_2}$$

$$Z_{in} = \frac{Z_L}{a^2}$$

$$Z_{in} = \frac{Z_L}{a^2} + a^2$$

$$Z_{in} = \frac{Z_L}{a^2} + a^2 = \frac{Z_L}{a^2} + \frac{Z_L}{a^2} = \frac{2Z_L}{a^2}$$

$$Z_{in} = \frac{Z_L}{a^2} + a^2 = \frac{Z_L}{a^2} + \frac{Z_L}{a^2} = \frac{2Z_L}{a^2}$$

$$Z_{in} = \frac{Z_L}{a^2} + a^2 = \frac{Z_L}{a^2} + \frac{Z_L}{a^2} = \frac{2Z_L}{a^2}$$

$$Z_{in} = \frac{Z_L}{a^2} + a^2 = \frac{Z_L}{a^2} + \frac{Z_L}{a^2} = \frac{2Z_L}{a^2}$$




# \* CTD Practice

## ① Quiz: 1 (set A)

mesh analysis: current  
nodal analysis: voltage

## • midsem : 2023

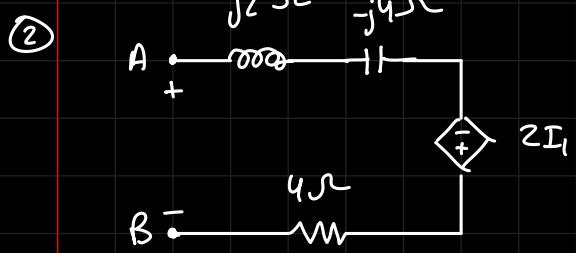

mesh analysis voltage:

# \* Lecture 15

13/10/24

## • Phasor vs S-domain

Assumptions:


zero initial conditions

sinusoidally varying source

"steady state"

<u>time domain</u>	<u>freq. domain</u>
$v(t) = V_m \cos(\omega t + \phi)$ $= \operatorname{Re} \{ V_m e^{j\omega t} e^{j\phi} \}$	$V = V_m e^{j\phi}$
$v(t) = V_m e^{\sigma t} \cos(\omega t + \phi)$ $= \operatorname{Re} \{ V_m e^{\sigma t} e^{j\phi} e^{j\omega t} \}$	$V = V_m e^{j\phi}$ where $s = \sigma + j\omega$ complex frequency
$R$	$R$
$L$	$L(s) = sL$
$C$	$\frac{1}{(s + j\omega)C} = \frac{1}{sC}$

e.g.

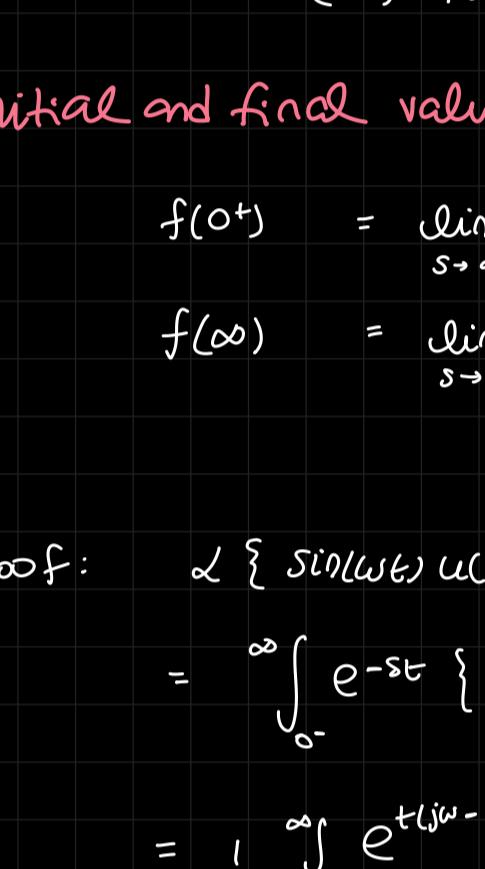

$$V_{in}(s) = 5e^{-2t} \cos(3t + 45^\circ)$$

$$s = \sigma + j\omega$$

$$s = -2 + j3$$

$$V_{in} = 5e^{-j45^\circ} = 5/45^\circ V$$

Voltage divider  
for finding  $V_{out}$

$$V_{out} = \frac{5/45^\circ \times (-0.02)(-2+j3) \times (-0.01)(-2+j3)}{10 + (-0.02)(-2+j3) + (-0.01)(-2+j3)}$$

$$V_{out}(t) = \operatorname{Re} \{ 5.86 e^{j(-24.4)} e^{(s+j\omega)t} \}$$

$$= 5.86 e^{-2t} \cos(3t - 24.4) V$$

for zero initial condition, we can use phasors  
for  $e^{\sigma t} \cos(\omega t + \phi)$

Can we still use phasors for  $\delta(t)$ ,  $u(t)$ ,  $\sin(\omega t)$ ,  $\cos(\omega t)$ ?

NO

but Laplace transform works ✓

$$\mathcal{L}\{f(t)\} = \int_0^\infty e^{-st} f(t) dt \Rightarrow F(s)$$

variable ↴

$$\begin{array}{lll} \mathcal{S}(t) & \downarrow & f_1(t) \pm f_2(t) & F_1(t) \pm F_2(t) \\ u(t) & \frac{1}{s} & kf(t) & kF(t) \\ tu(t) & \frac{1}{s^2} & \frac{d}{dt} f(t) & sF(s) - f(0) \\ e^{-at} u(t) & \frac{1}{s+a} & \frac{1}{s} \int_0^t f(t) dt & F(s)/s \\ te^{-at} u(t) & \frac{1}{(s+a)^2} & & \end{array}$$

$$\begin{array}{lll} \sin(\omega t) u(t) & \frac{\omega}{s^2 + \omega^2} & f_1(t) * f_2(t) & F_1(t) \cdot F_2(t) \\ \cos(\omega t) u(t) & \frac{s}{s^2 + \omega^2} & f(t-a) u(t-a) & e^{-as} F(s) \\ e^{-at} \sin(\omega t) u(t) & \frac{\omega}{(s+a)^2 + \omega^2} & f(t) e^{-at} & F(s+a) \end{array}$$

$$e^{-at} \cos(\omega t) u(t) = \frac{s}{(s+a)^2 + \omega^2}$$

$$f(t) = \delta(t) - \frac{1}{\sqrt{7}} \sin(\sqrt{7}t) u(t)$$

$$f(0^+) = \lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \frac{4e^{-2s}(s+50)}{s} \times \cancel{s}$$

$$= \lim_{s \rightarrow \infty} \frac{4(s+50)}{e^{2s}} \underset{\infty}{\cancel{s}} = \frac{4}{\infty} = 0$$

$$f(\infty) = \lim_{s \rightarrow 0} sF(s) = \lim_{s \rightarrow 0} \frac{4s^2 + 10}{s^2 + 7s + 10} = \frac{4}{10} = 0.4$$

$$f(t) = \frac{1}{\sqrt{7}} \cos(\sqrt{7}t) u(t)$$

$$f(t) = \frac{1}{\sqrt{7}} \cos(\sqrt{7}t) u(t)$$