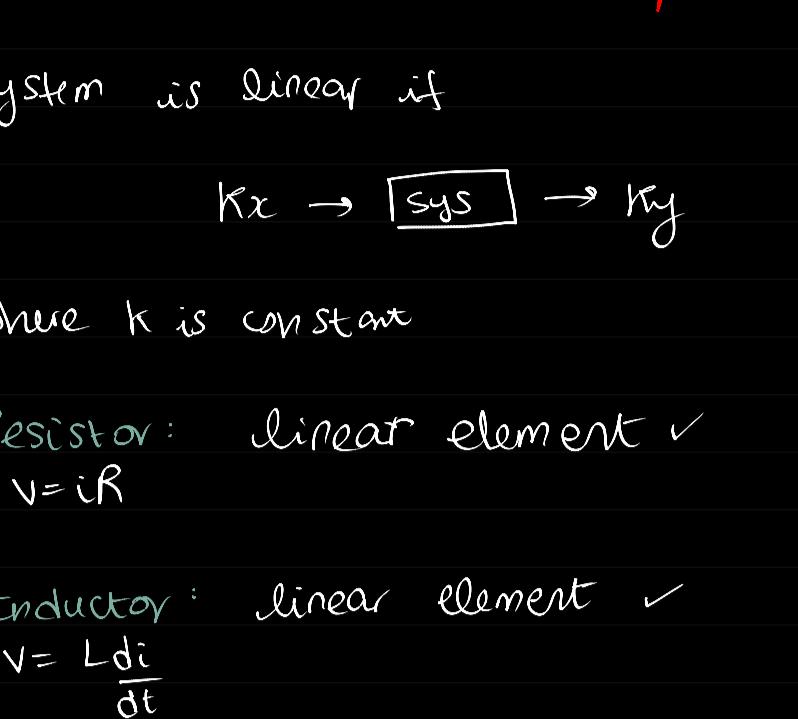


Circuit Theory and Devices

Lab: LT Spice (2nd week onwards)

book: Engineering Circuit Analysis (9th edition)

Course: 9 modules chapter 10 onwards
{continuation of BE3}

* Lecture: 1

⇒ Linear Circuits



System is linear if

$$Kx \rightarrow [\text{sys}] \rightarrow Ky$$

where K is constant

"R" Resistor: linear element ✓
 $V = iR$ "L" Inductor: linear element ✓
 $V = L \frac{di}{dt}$ "C" Capacitor: linear element ✓
 $i = C \frac{dv}{dt}$


* Linear Electric Circuits:

consists of ⇒

① R, L, C → linear elements


② Independent voltage & current sources

③ Linear dependent sources

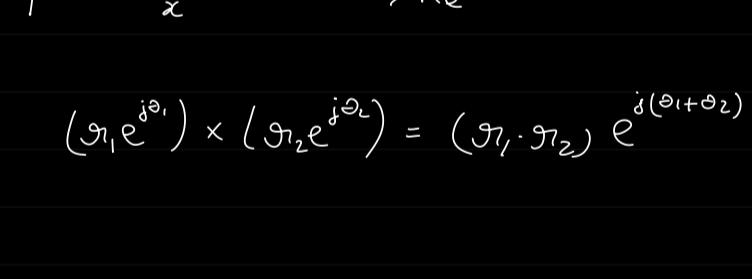

Note: diode and transistors are non-linear elements

* Response of a linear circuit

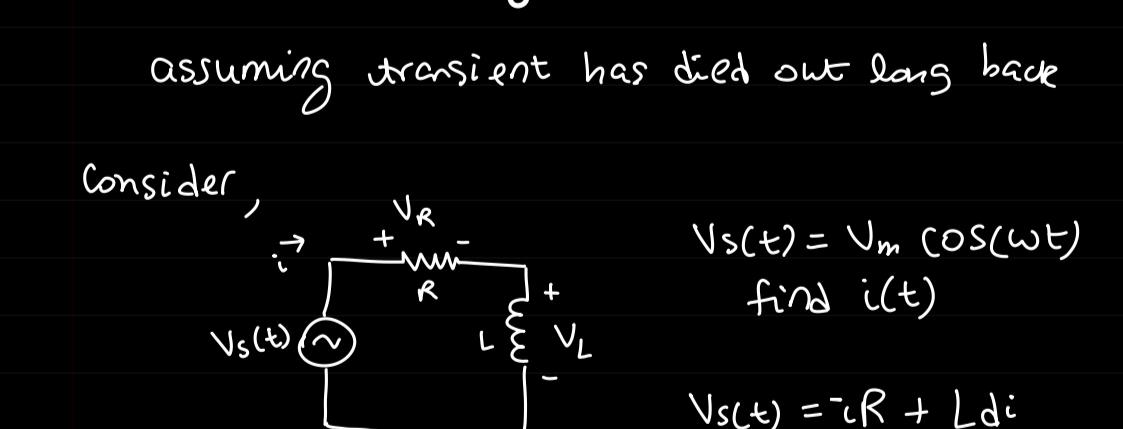① full response = transient response + steady state
transient persists $t \rightarrow \infty$ 

$$i_{\text{final}} = i_{\text{transient}} + i_{\text{steady state}}$$

as $t \rightarrow \infty$, $i_{\text{final}} = i_{\text{steady state}}$


* Sinusoids & complex numbers

sinusoidally varying voltage source

$$V_s(t) = V_m \cos(\omega t)$$

$$V_s(t) = V_m \sin(\omega t)$$

$$V_s(t) = V_m \sin(\omega t + \phi)$$

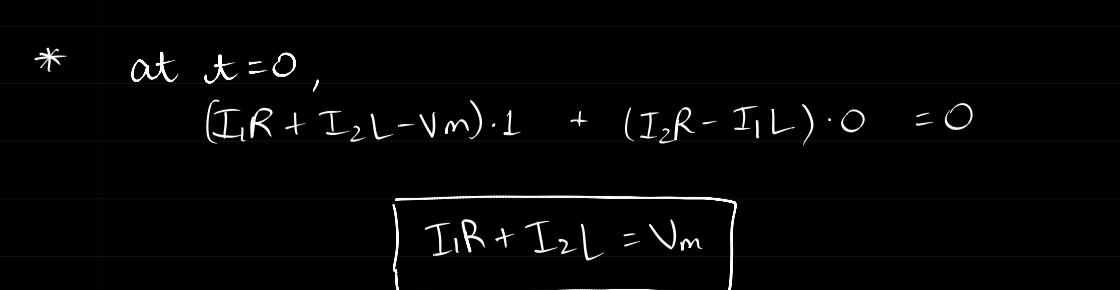② is leading ① by angle ϕ
① is lagging ② by angle ϕ

Nodes

* Section 10.1

(a) $Q_1 y \quad 5\sin(5t - 9^\circ)$

$$t=0 \Rightarrow 5\sin(-9^\circ) = -5\sin(9^\circ) = -0.782$$

$$t=0.01 \Rightarrow 5\sin(0.05 - 9^\circ) = -5\sin(8.95^\circ) \quad X$$

\Downarrow
radians

$$5\sin\left(\frac{0.05 \times 80}{\pi} - 9^\circ\right) = 5\sin(2.86^\circ - 9^\circ)$$

$$\Rightarrow -5\sin(6.14^\circ) = -0.534$$

$$t=0.1 \Rightarrow 5\sin(0.5 - 9^\circ) = 5\sin(28.64^\circ - 9^\circ) = 5\sin(19.64^\circ)$$

$$\Rightarrow 1.6805$$

(b) $4\cos 2t$

$$t=0 \Rightarrow 4\cos(0) = 4$$

$$t=1 \Rightarrow 4\cos(2) = 3.997$$

$$t=1.5 \Rightarrow 4\cos(3) = 3.994$$

(c) $3.2 \cos(6t + 15^\circ)$

$$t=0 \Rightarrow 3.2 \cos(15^\circ) = 3.09$$

$$t=0.01 \Rightarrow 3.2 \cos(0.06 + 15^\circ) = 3.2 \cos(3.43^\circ + 15^\circ)$$

$$\Rightarrow 3.2 \cos(18.43^\circ)$$

$$\Rightarrow 3.035$$

$$t=0.1 \Rightarrow 3.2 \cos(0.6 + 15^\circ) = 3.2 \cos(34.3^\circ + 15^\circ)$$

$$= 3.2 \cos(49.3^\circ)$$

$$= 2.086$$

Q2) (a) $300\sin(628t) \rightarrow 300 \cdot \cos(628t - 90^\circ)$


$$4\sin(3\pi t + 30^\circ) \rightarrow 4\cos(3\pi t - 60^\circ)$$

$$14\sin(50t - 8^\circ) - 10\cos 50t \rightarrow$$


Q3) $V_L = 10\cos(10t - 45^\circ)$

(a) $i_L = 5\cos 10t$

$$-45^\circ$$

 

⇒ AC Power Analysis {Module: 3}

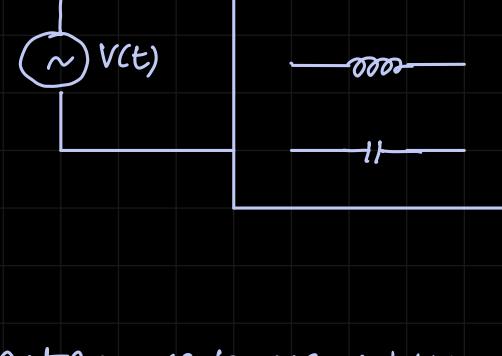

$$\cos(A) \cos(B) =$$

$$\frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

Instantaneous power: $p(t) = v(t) \cdot i(t)$

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$p(t) = V_m \cos(\omega t + \theta) \cdot I_m \cos(\omega t + \phi)$$

$$p(t) = \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{constant}} + \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)}_{\text{twice frequency}}$$

(DC term)

(harmonic)

• Average Power

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{real part}} dt + \underbrace{\frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) dt}_{\text{imaginary part}}$$

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

* Avg. Power absorbed

• by a purely resistive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

here, phase diff = 0°




$$P_{avg} = \frac{V_m \cdot I_m}{2} = \frac{I_m^2 R}{2} = \frac{V_m^2}{2R}$$

• by a purely inductive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$


here, phase diff = 90°

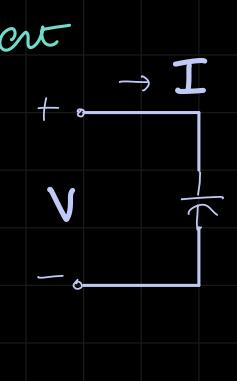

$$P_{avg} = 0 \text{ for inductor}$$

• by a purely capacitive element
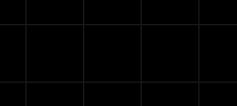
$$P_{avg} = \frac{V_m \cdot I_m}{2} \cos(-90^\circ)$$



* Lecture: 6

$$v(t) = V_m \cos(\omega t + \phi) \quad \leftarrow \text{Revision}$$

$$\downarrow$$


$$v(t) = R \Re \{ V_m e^{j\omega t} e^{j\phi} \}$$

$$\downarrow -e^{j\omega t}$$

$$V_m e^{j\phi} = V_m \angle \phi$$

exponential polar

• eq)

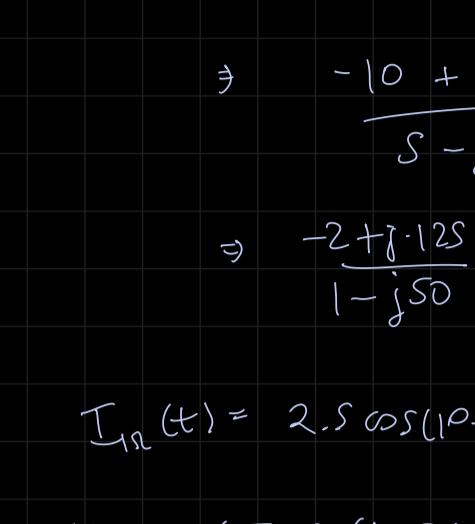


① find power delivered to each element at $t = 0, 10, 20 \text{ ms}$

② find P_{avg} to each element

(ans) convert to freq. domain

$$V_{1\text{R}} = V_{u\text{R}} + V_c$$

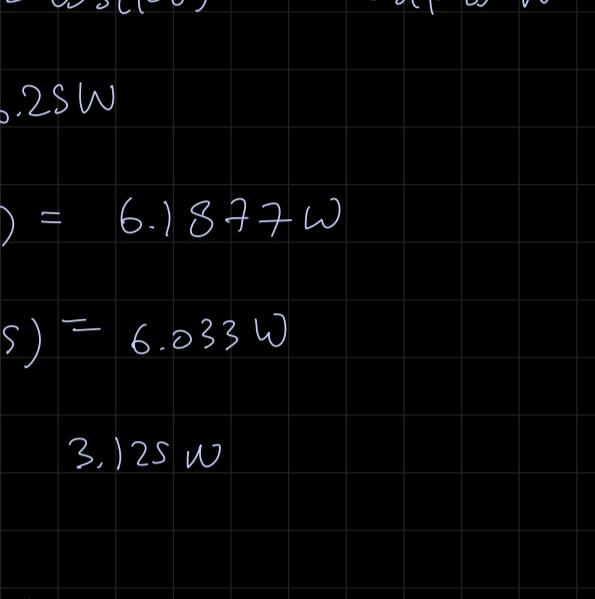

$$\textcircled{1} \quad P_{inst} = \frac{V_m I_m \cos(\theta - \phi)}{2} + \frac{V_m I_m}{2} \cos(2\omega t + \phi + \theta)$$

$$I_i = -2.5 \times \left(\frac{4 - j2.5 \times 10^4}{1 + j - j2.5 \times 10^4} \right) \approx -2.5 \text{ A}$$

$$\Rightarrow \frac{-10 + j62.5 \times 10^4}{5 - j2.5 \times 10^4} \Rightarrow \frac{-2 + j12.5}{1 - j50}$$

$$\Rightarrow \frac{-2 + j1.25}{1 - j50} \times \frac{1 + j50}{1 + j50} =$$

$$I_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$V_{1\text{R}} = (I_{1\text{R}})(2 \Omega) \Rightarrow V_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$\cos^2(\theta) = \frac{1 + \cos(2\theta)}{2}$$

$$P_{1\text{R}}(t) = 2.5 \cos(10t) \cdot 2.5 \cos(10t) \text{ W}$$

$$P_{1\text{R}}(t=0) = 6.25 \text{ W}$$

$$P_{1\text{R}}(t=20 \text{ ms}) = 6.033 \text{ W}$$

$$(P_{avg})_{1\text{R}} = 3.125 \text{ W}$$

\Rightarrow P delivered to 4 ohm

$$P_{4\text{R}}(t) = V_{u\text{R}}(t) \times I_{u\text{R}}(t)$$

$$\Rightarrow I_{4\text{R}} = I_s \times \frac{1}{5 - j2.5 \times 10^4} = 10^{-4} \angle 90^\circ \text{ A}$$

$$V_{u\text{R}} = 4 \times I_{4\text{R}} = 4 \times 10^{-4} \angle 90^\circ \text{ V}$$

convert to time domain

$$P_{4\text{R}}(t) = 2 \times 10^{-8} + 2 \times 10^{-8} \cos(20t) \text{ W}$$

$$t=0^- \quad 4 \times 10^{-8} \text{ W}$$

$$t=10 \text{ ms} = 3.96 \times 10^{-8} \text{ W}$$

$$P_{4\text{R}}(t=20 \text{ ms}) = 2 \times 10^{-8} \text{ W}$$

\Rightarrow P delivered to capacitor

$$P_c(t) = V_c(t) \cdot I_c(t)$$

$$\left(P_{avg} \right)_c = 0 \quad \text{since phase diff} = 90^\circ$$

$$I_c = I_2 = 10^{-4} \angle 90^\circ \text{ A} \Rightarrow I_c(t) = 10^{-4} \cos(10t + 90^\circ)$$

$$V_c = (-j2.5 \times 10^4) \times 10^{-4} \angle 90^\circ$$

$$-j2.5 \times 10^4 \times (+j10^{-4}) = 2.5 \text{ V}$$

$$P_c(t) = 1.25 \times 10^{-4} \cos(20t + 90^\circ) \text{ W}$$

$$t=0 \Rightarrow P=0 \text{ W}$$

$$t=10 \text{ ms} \Rightarrow P=2.48 \times 10^{-5} \text{ W}$$

$$(P_{avg})_c = 1.25 \times 10^{-5} \text{ W}$$

Note: we cannot multiply I_c and V_c in phasor form and then convert to time domain for getting P_c (power) because power does not have a phasor part. It is a real value.

* Correct or not?

$$\text{depends on } \times \quad \textcircled{1} \quad P_{1\text{R}}(t) + P_{4\text{R}}(t) + P_c(t) = \text{constant 1}$$

$$\checkmark \quad \textcircled{2} \quad P_{avg\ 1\text{R}} + P_{avg\ 4\text{R}} + P_{avg\ c} = \text{constant 2}$$

\Rightarrow Pavg source

active sign convention

passive sign convention

maximum power delivered to load when

$$Z_L = Z_S^*$$

complex conjugate of Z_S

\Rightarrow Impedance Matching

$$100 \Omega \quad 100 \Omega \quad j50 \Omega \quad 50 \Omega \quad \text{impedance matching circuit}$$

$$\Rightarrow Z_L = Z_S^* = 50 \Omega$$

$$\Rightarrow Z_L = 5$$

* Lecture: 7


- Instantaneous Power: $p(t) = v(t)i(t)$
- Average Power: $P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) = \frac{1}{2} R_{eff} \{VI^*\}$
- $P_{avg, sources} = \sum P_{avg, elements}$

* Note: $Z = R + jX$
 \downarrow resistive reactive


$P_{avg, resistive} : P \neq 0$

$P_{avg, reactive} : P = 0$


* Max Power Transfer:

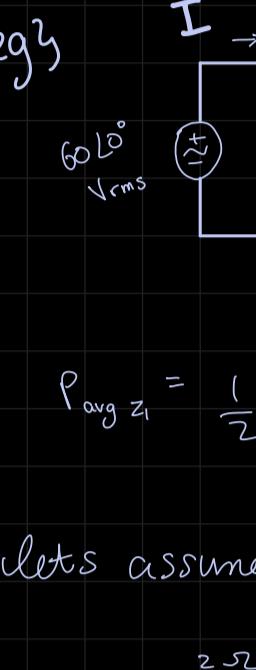

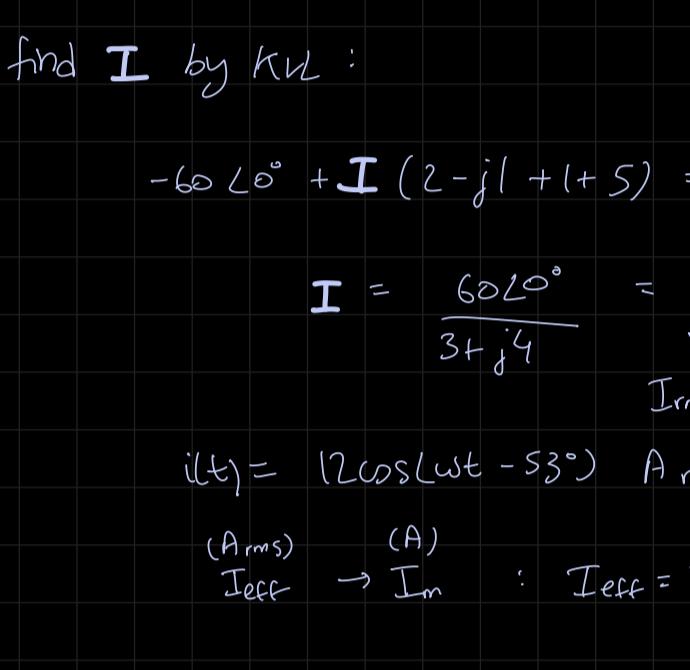Circuit has max. power when $Z_L = Z_s^*$ complex conjugate



↓ apply Thevenin's theorem

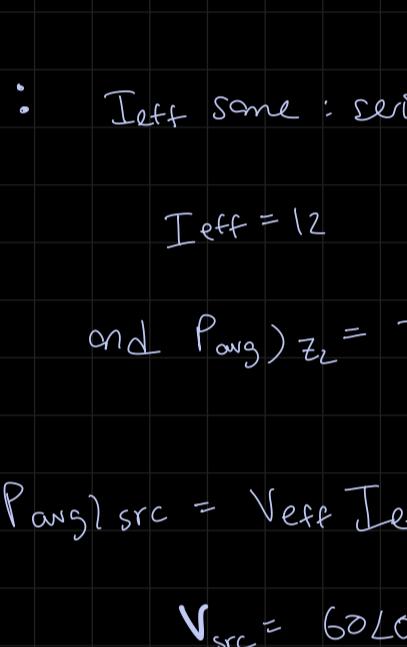

$$Z_L = Z_{th}$$

* Power Factor

$$PF = \cos(\theta - \phi) = \frac{P_{average}}{P_{apparent}}$$

angle of voltage phasor
↑ angle of current phasor

for purely resistive load: $PF = 1$ {Max} $\theta - \phi = 0^\circ$
 for purely reactive load: $PF = 0$ {min}

Note $\rightarrow PF = 0.5$ leading \rightarrow capacitive $(\theta - \phi) < 0^\circ$
 $PF = 0.5$ lagging \rightarrow inductive $(\theta - \phi) > 0^\circ$

eg)
 find
 ① Average power delivered to each load
 ② $P_{avg, source} = ?$
 ③ $P_{apparent, src} = ?$
 ④ PF of combined load = ?

$$(Ans) P_{avg, Z_1} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} R_{eff} \{VI^*\}$$

\downarrow
voltage across Z_1 , not the src

lets assume Z_1 :

$$\frac{2-j2}{j2} \quad \text{so, } P_{avg, Z_1} = \text{Power delivered to } 2\Omega \text{ resistor}$$

find I by KVL:

$$-60 \angle 0^\circ + I(2 - j1 + j5) = 0$$

$$I = \frac{60 \angle 0^\circ}{3 + j4} = 12 \angle -53.13^\circ \text{ Arms}$$

$$i(t) = 12 \cos(\omega t - 53.13^\circ) \text{ A rms}$$

$$(A_{rms}) \xrightarrow{I_{eff}} \xrightarrow{I_m} I_{eff} = \frac{I_m}{\sqrt{2}} = \frac{12}{\sqrt{2}} \text{ A}$$

$$I_{eff} = 12 \text{ Arms} \Rightarrow I_m = 12\sqrt{2} \text{ A}$$

$$i(t) = 12\sqrt{2} \cos(\omega t - 53^\circ) \text{ A}$$

$$P_{avg, Z_1} = (12)^2 \times 2 = 288 \text{ W}$$

$$\text{note: } P_{avg} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{eff} I_{eff} \cos(\theta - \phi)$$

Z_2 : I_{eff} same: series circuit

$$I_{eff} = 12$$

$$\text{and } P_{avg, Z_2} = I_{eff}^2 R = (12)^2 \times 1 = 144 \text{ W}$$

$$(2) P_{avg, src} = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$V_{src} = 60 \angle 0^\circ \text{ V rms} \Rightarrow V_{eff} = 60 \text{ V rms}$$

$$I_{src} = 12 \angle -53.13^\circ \text{ V rms} \Rightarrow I_{eff} = 12 \text{ Arms}$$

$$\theta = 0^\circ, \phi = -53.13^\circ$$

$$P_{avg, src} = [60 \times 12] \cos(53.13^\circ) = 432 \text{ W}$$

We can observe that $288 + 144 = 432$

and hence,

$$P_{avg, sources} = \sum P_{avg, elements} \text{ holds}$$

$$(3) P_{apparent} = V_{eff} \cdot I_{eff} = (60)(12) = 720 \text{ W}$$

$$(4) PF of combined loads = PF of source$$

$$PF = \cos(\theta - \phi) = \cos(0 + 53.13^\circ) = 0.6$$

$\sim \sim$
 $\theta - \phi > 0^\circ$
 lagging \downarrow

$$* P_{avg} = \frac{1}{2} R_{eff} \{VI^*\}$$

$$V_{eff} = V_{eff} \angle \theta$$

$$I_{eff} = I_{eff} \angle \phi$$

$$P_{avg} = Re \{ V_{eff} I_{eff}^* \}$$

$$Q_{reactive} = Im \{ V_{eff} I_{eff}^* \}$$

$$S = P + jQ$$

$$S = P + jQ = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$S = P + jQ = V_{eff} I_{eff} \sin(\theta - \phi)$$

$$S = P + jQ = V_{eff} I_{eff} \sin(\theta - \phi)$$

$$S = P + jQ = V_{eff} I_{eff} \sin(\theta - \phi)$$


$$S = P + jQ = V_{eff} I_{eff} \sin(\theta - \phi)$$

$$$$

* Lecture - 8

• Polyphase Circuits (Chp 12)

⇒ Three Phase Source

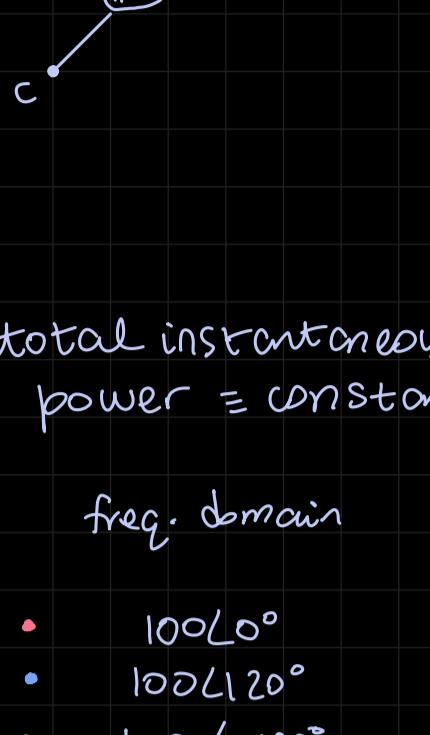

$$V_{an} = 100 \angle 0^\circ V$$

$$V_{bn} = 100 \angle 120^\circ V$$

$$V_{cn} = 100 \angle -120^\circ V$$

if $|V_{an}| = |V_{bn}| = |V_{cn}|$
 & $V_{an} + V_{bn} + V_{cn} = 0$
 then it is a

Balanced Source


total instantaneous power = constant

freq. domain

- $100 \angle 0^\circ$
- $100 \angle 120^\circ$
- $100 \angle -120^\circ$

time domain

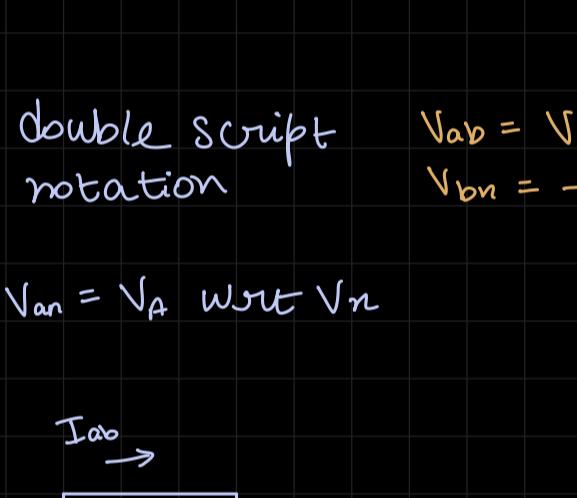
- $100 \cos(\omega t)$
- $100 \cos(\omega t + 120^\circ)$
- $100 \cos(\omega t - 120^\circ)$



total $p(t) \rightarrow \text{constant}$

* Single Phase Three-wire Source

≡ Two phase source

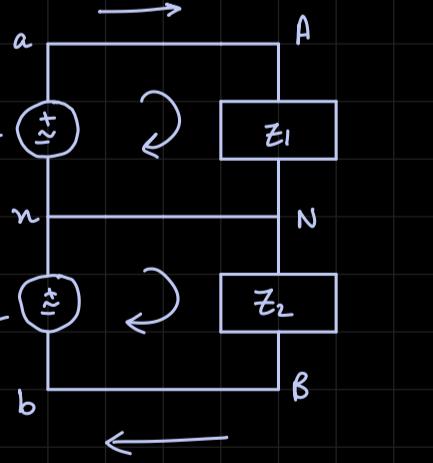

$$V_1 = V_m \angle 0^\circ$$

$$V_{an} = V_1 = V_m \angle 0^\circ$$


$$V_{bn} = -V_1 = V_m \angle 0^\circ - 180^\circ$$

$$V_{an} \leftarrow \xrightarrow{180^\circ} V_{bn} \rightarrow V_{an}$$

double script notation

$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} = V_{an} + V_{nb} \\ V_{bn} &= -V_{nb} \end{aligned}$$

$$V_{an} = V_A \text{ wrt } V_n$$

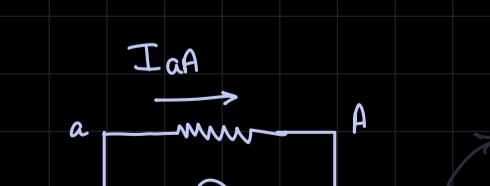

$$I_{ab} = \frac{V_{ab}}{Z_L}$$

$$I_{nn} = -I_{aa} + I_{bb}$$

$$\Rightarrow \frac{V_1}{Z_1} - \frac{V_2}{Z_1}$$

$$\text{Assume } Z_1 = Z_2$$

$$I_{nn} = \frac{V_1}{Z_1} - \frac{V_2}{Z_1} = 0$$

when both srcs &
and loads are equal

Balanced Load : current in neutral line is equal to zero.

all terms are phasors

even with resistance,
 $I_{nn} = 0 = I_{bb} - I_{aa}$

due to

① Balanced Load
 ≡ Symmetry

all terms are phasors

even with resistance,
 $I_{nn} = 0 = I_{bb} - I_{aa}$

due to

① Balanced Load
 ≡ Symmetry

* Lecture: 9

09/09/29

time domain freq. domain

$$\begin{array}{ll} \sqrt{V_p} \cos(\omega t + \theta^\circ) & \sqrt{V_p} L^{\theta^\circ} \\ \sqrt{V_p} \cos(\omega t + \theta^\circ - 180^\circ) & \sqrt{V_p} L^{\theta^\circ - 180^\circ} \end{array}$$

We cannot directly say,

$$P_{avg} = \sqrt{I} \quad \times$$

$$\text{but } P_{avg} = \frac{1}{2} \operatorname{Re}\{ \sqrt{I} I^* \} \quad \checkmark$$

$$\begin{aligned} \textcircled{2} \quad a) \quad I_{AB} &= \frac{115 L^{\theta^\circ} + 115 L^{\theta^\circ}}{2(10 + j^2)} = \frac{230 L^{\theta^\circ}}{2(10 + j^2)} \\ &= 11.27 / (\theta^\circ - 11.3^\circ) A \end{aligned}$$


$$\phi = \theta - 11.3^\circ$$

$$PF = \cos(\theta - \phi + 11.3^\circ) = 0.98 \text{ lagging}$$

because PF angle is true

$$b) \quad PF = 1 \Rightarrow \cos(\theta - \phi) = 1 \Rightarrow \theta - \phi = 0$$

$$\Rightarrow \theta = \phi$$

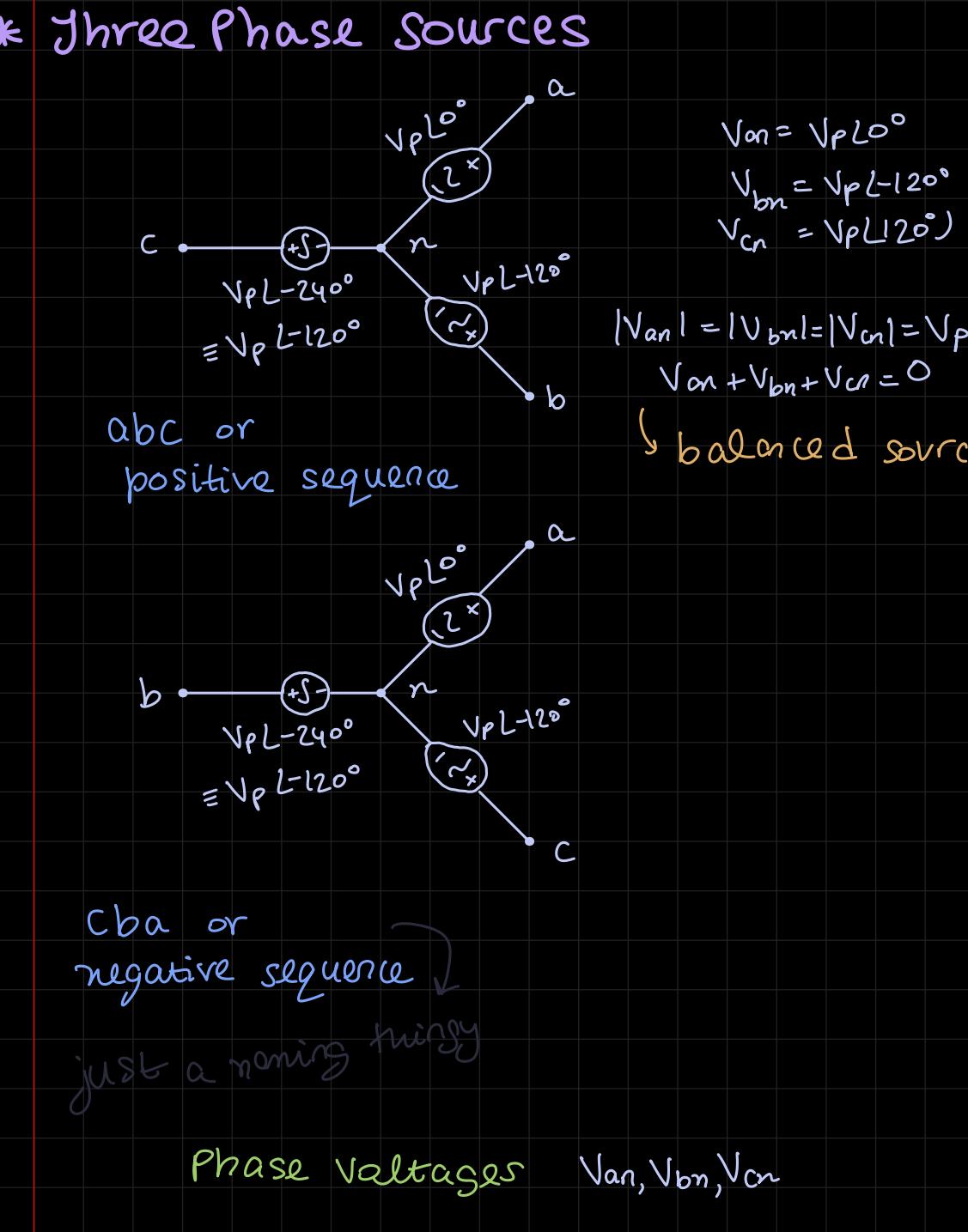

Note that this is still a balanced load, so we can remove MN since $I_{MN} = 0$

using complex power

$S = \text{complex power of total load}$

$$S = \frac{1}{2} \sqrt{I} I^*$$

$$PF = \frac{\operatorname{Re}\{ S \}}{|S|} = 1 \Rightarrow \operatorname{Re}\{ S \} = |S|$$

so, $\operatorname{Im}\{ S \} = 0$ here

$$S = \frac{1}{2} V_{an} I_{An}^* + \frac{1}{2} V_{nb} I_{Nb}^* + \frac{1}{2} V_{ab} I_{Ab}^*$$

$$\Rightarrow \frac{1}{2} V_{an} \left(\frac{V_{an}}{Z_p} \right)^* + \frac{1}{2} V_{nb} \left(\frac{V_{nb}}{Z_p} \right)^* + \frac{1}{2} V_{ab} \left(\frac{V_{ab}}{Z_p} \right)^*$$

$$\Rightarrow \frac{1}{2} \frac{|V_{an}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{nb}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{ab}|^2}{|Z_p|^2} Z_p$$

$$\Rightarrow \frac{115^2}{10^4} (10 + j^2) + \frac{1}{2} \left(\frac{230^2}{(j\omega C)^2} \right) \left(\frac{-j}{\omega C} \right) = \frac{1}{j\omega C} \times \frac{-1}{j\omega C}$$


$$\Rightarrow 115^2 \left(\frac{10 + j^2}{10^4} - \frac{1}{j\omega C} \right)$$

$$\Rightarrow 2 \times 115^2 \left(\frac{j}{10^4} - \frac{1}{j\omega C} \right)$$

$$\Rightarrow 2 \times 115^2 \left(\frac{1}{10^4} - \omega C \right) = 0$$

$$\frac{1}{10^4} - 100\pi C = 0 \quad C = \frac{1}{10400\pi} = 30.6 \mu F \quad \checkmark$$

* Three Phase Sources

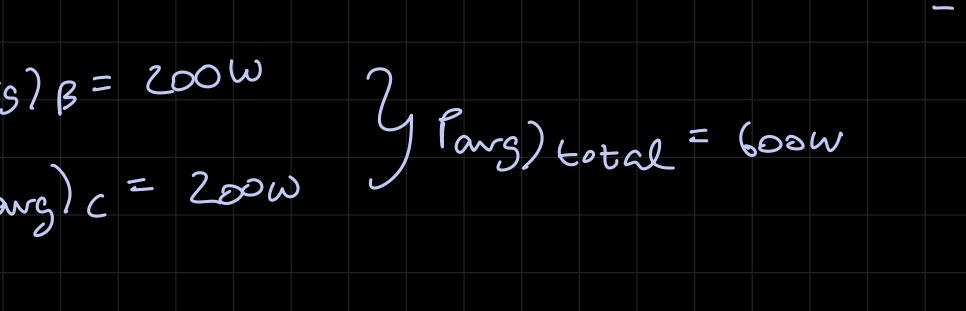

$$V_{an} = V_p L^{\theta^\circ}$$

$$V_{bn} = V_p L^{-120^\circ}$$

$$V_{cn} = V_p L^{+120^\circ}$$

abc or positive sequence

cba or negative sequence

just a naming thingy

Phase Voltages V_{an}, V_{bn}, V_{cn}

Line-to-line Voltages V_{ab}, V_{bc}, V_{ca} OR line voltages

$$V_{ab} = V_{an} - V_{bn} = V_{an} + V_{nb}$$


$$V_{ab} = \sqrt{3} V_p L^{30^\circ}$$

$$V_{bc} = \sqrt{3} V_p L^{-90^\circ}$$

$$V_{ca} = \sqrt{3} V_p L^{-210^\circ}$$

* Y-Y connection

→ Y-Y connection

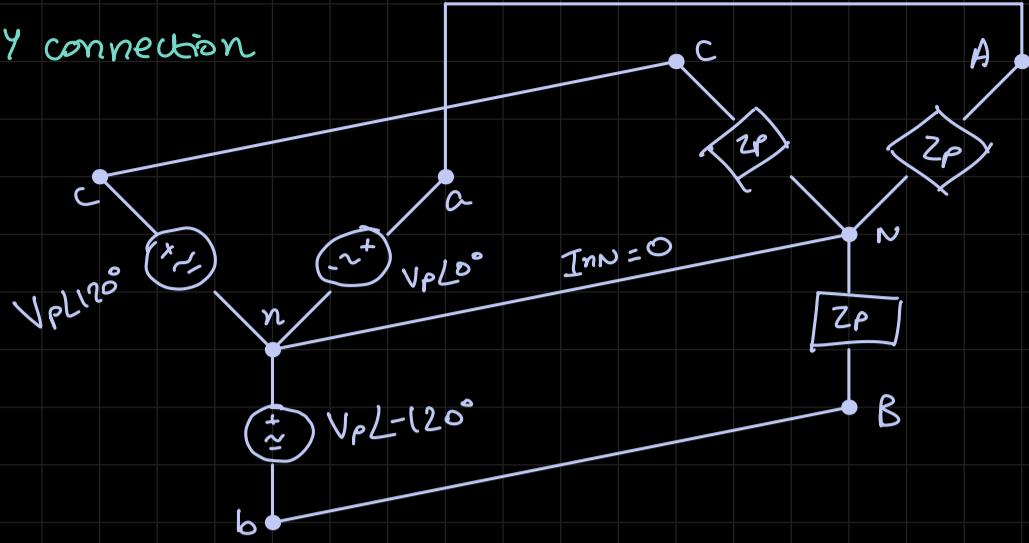

balanced load: all load are same

balanced src: all src magnitudes are equal

line: lines connecting load to src

aa cC

bb nn

Phase Voltages: $V_{AN} = V_{an}$, $V_{BN} = V_{bn}$, $V_{CN} = V_{cn}$ line voltages: V_{ab} , V_{ba} , V_{ca} , V_{ac} line currents: I_{aA} , I_{bB} , I_{cC} phase currents: $I_{AN} = I_{aA}$, $I_{BN} = I_{bB}$, $I_{CN} = I_{cC}$

$$V_{an} = V_p L 0^\circ$$

$$V_{bn} = V_p L -120^\circ$$


$$V_{cn} = V_p L -240^\circ$$

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_p L 30^\circ$$

$$V_{bc} = \sqrt{3} V_p L -90^\circ$$

$$V_{ca} = \sqrt{3} V_p L -210^\circ$$

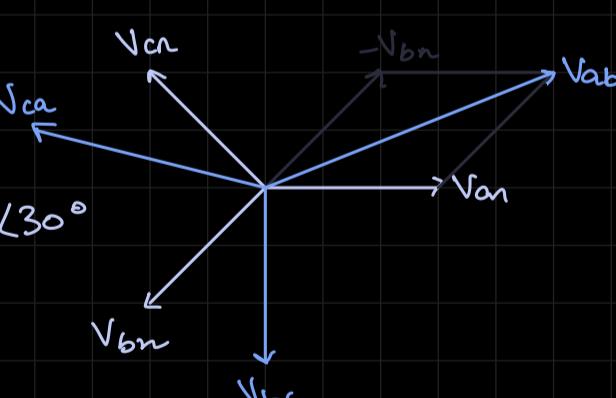

line voltages

$$V_{\text{line}} = \sqrt{3} V_{\text{phase}}$$

line currents = phase currents

* Total Instantaneous Power

$$P_{\text{total}}(t) = P_A(t) + P_B(t) + P_C(t)$$

Classes & Attribs

interface (entity)

~~ ~~~

Bird

↓

dmg
(chits)

Pig

↓

health
(units)

User

↓

save
stage

level mg

blocks

pigs

type

→ max-score

→ no. of pigs

center point

Game

update score

wood

glass

steel

Score

level-status

Slingshot

angle

stretch

↙

b°



$$v = 10 \text{ m/s}$$

0°

90°

S, P


$$\frac{\sqrt{v \cos \theta}, \sqrt{v \sin \theta}}{\text{per second / rate}}$$

-1 → 0


* TODO: revise lecture 11 (missed due to SNS quiz)

* Lecture 12:

eg 3

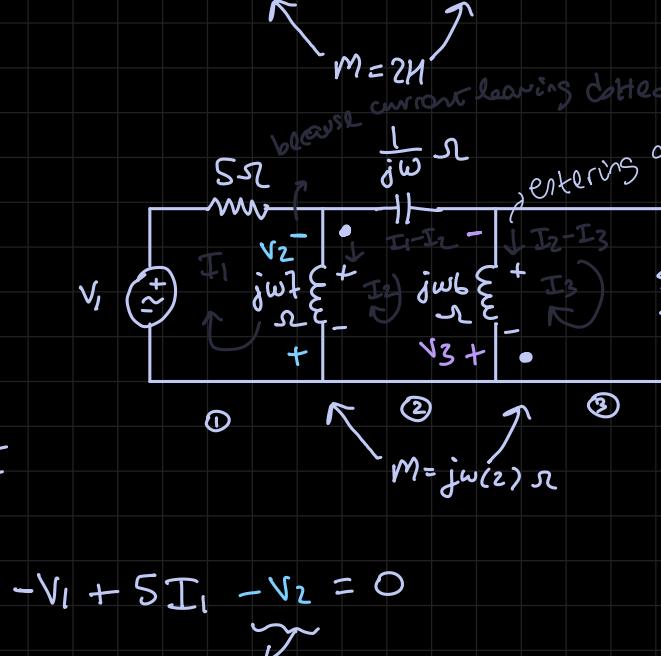

ans 3

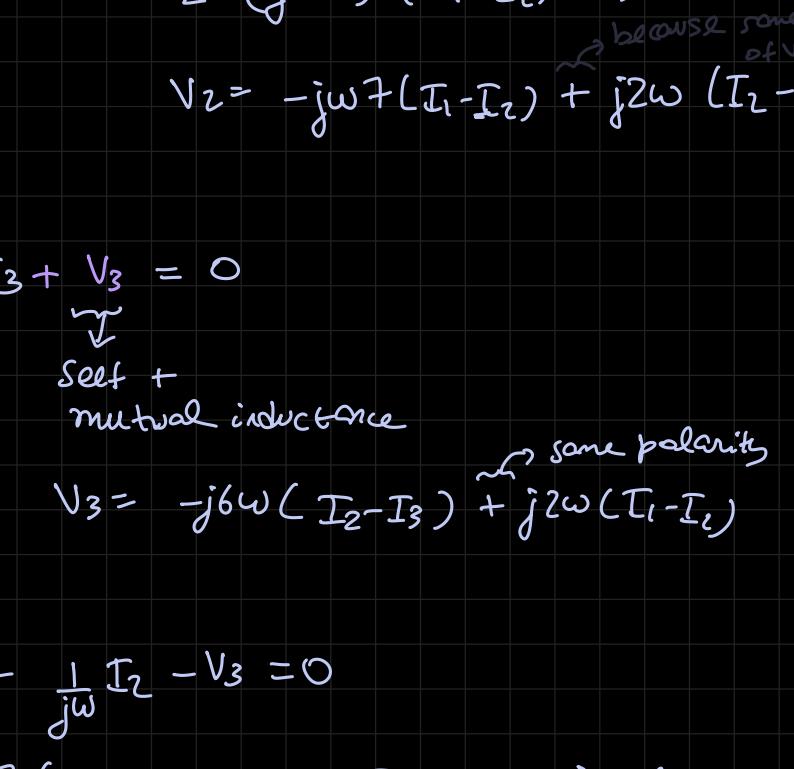

$$\textcircled{1} \quad -V_1 + 5I_1 - V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)(-1)$$

$$V_2 = -j\omega 7(I_1 - I_2) + j2\omega(I_2 - I_3)$$

$$\textcircled{3} \quad 3I_3 + V_3 = 0$$

Self + mutual inductance


$$V_3 = -j6\omega(I_2 - I_3) + j2\omega(I_1 - I_2)$$

$$\textcircled{2} \quad V_2 + \frac{1}{j\omega} I_2 - V_3 = 0$$

$$-j\omega 7(I_1 - I_2) + j2\omega(I_2 - I_3) + j6\omega(I_2 - I_3) - j^2\omega(I_1 - I_2) + \frac{I_2}{j\omega} = 0$$

$$I_1(-j5\omega) + I_2(j17\omega) + I_3(-j8\omega) + \frac{I_2}{j\omega} = 0$$

eg 3

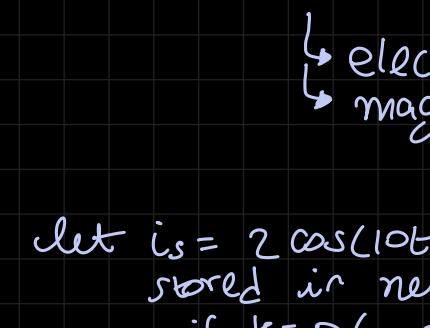

$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

We don't need to care about this sign if we use V_2, V_3 method.

* ENERGY STORED

$$w(t) = \frac{1}{2} L(i(t))^2 \quad \text{for only one inductor}$$



$$w(t) = \frac{1}{2} L(i_1)^2 + \frac{1}{2} L(i_2)^2 \pm M i_1(t) i_2(t)$$

[+ve] sign with occur iff both i_1 and i_2 are entering either dotted or undotted

[-ve] sign iff both enter different (dotted/undotted)

- Coupling coefficient (K)

$$M \leq \sqrt{L_1 L_2}$$

$$K = \frac{M}{\sqrt{L_1 L_2}} \Rightarrow 0 \leq K \leq 1$$

$K \rightarrow 0$

poor coupling or no coupling

$K \rightarrow 1$

Strong coupling (very close to each other)

$\Rightarrow K$ depends on: distance; size; ferrite b/w coils; of coils core

$$y \propto \frac{1}{x}$$

$$y \propto x$$

$$y \propto x$$

(inductively coupled) uses: wireless power transfer

- ↳ electric vehicle charging
- ↳ magsafe charging

eg 3 let $i_s = 2 \cos(10t)$ A. find total energy stored in network at $t=0$ if $K=0.6$ and

- (a) if x_y terminals are open circuited
- (b) x_y are short circuited

$$\text{Ans 3} \quad w(t) = \frac{1}{2} L_1(i_1)^2 + \frac{1}{2} L_2(i_2)^2 \pm M i_1(t) i_2(t)$$

$$j\omega L_1 = j4 \Rightarrow L_1 = \frac{4}{\omega} = 0.4 \text{ H}$$

- (a) if x_y are open: $i_2 = 0$

$$\therefore w(t) = \frac{1}{2} \times 0.4 \times (2 \cos 10t)^2$$

$$w(t) = 0.8 \cos^2(10t)$$

$$\text{at } t=0 \Rightarrow w(t) = 0.8 \text{ J}$$

$$(b) \quad w(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$


$$i_1 = i_s = 2 \cos 10^\circ$$

$$i_2 = \frac{V_2}{j2S} \quad \text{and} \quad V_x = -j\omega M I_1$$

$$i_2 = -0.6 \frac{(2 \cos 10^\circ)}{2.5} = -0.48 A$$

$$w(t=0) = \frac{1}{2} (0.4) (2^2) + \frac{1}{2} (-0.48)^2$$

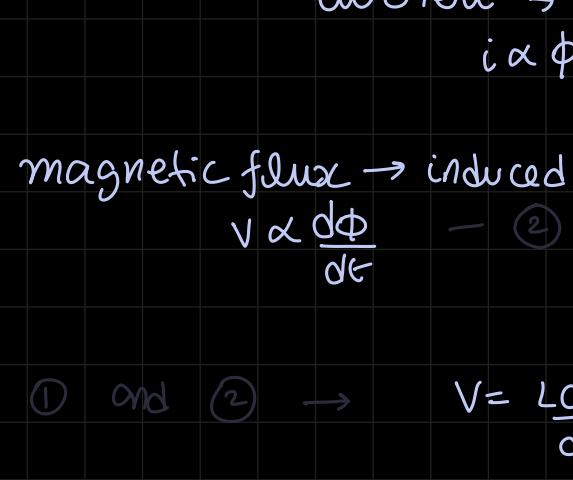• MODULE 5: Magnetically coupled circuits



current \rightarrow magnetic flux
 $i \propto \phi$ — ①

magnetic flux \rightarrow induced voltage


$$V \propto \frac{d\phi}{dt} \quad \text{— ②}$$

① and ② $\rightarrow V = L \frac{di}{dt}$


for DC source: current is constant

hence $\frac{di}{dt} = 0$ and $\therefore V = 0$
 (induced)

• Mutual Inductance

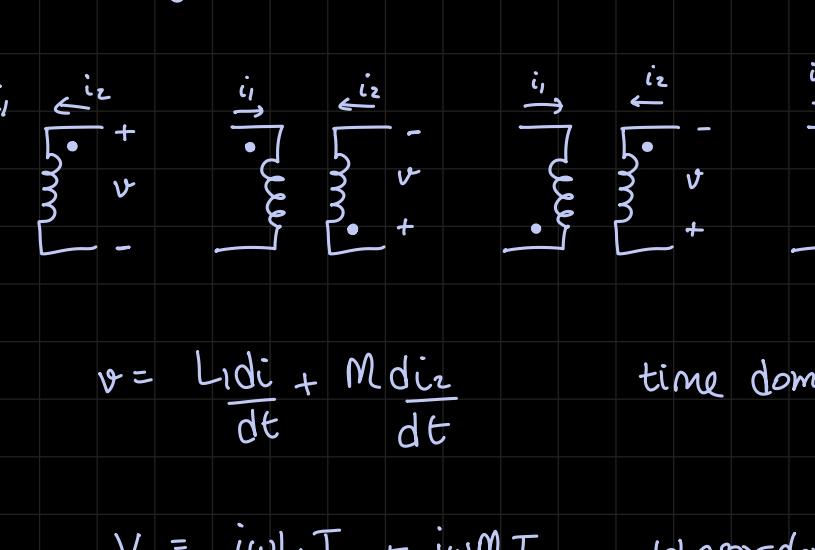


L : self inductance mutual inductance

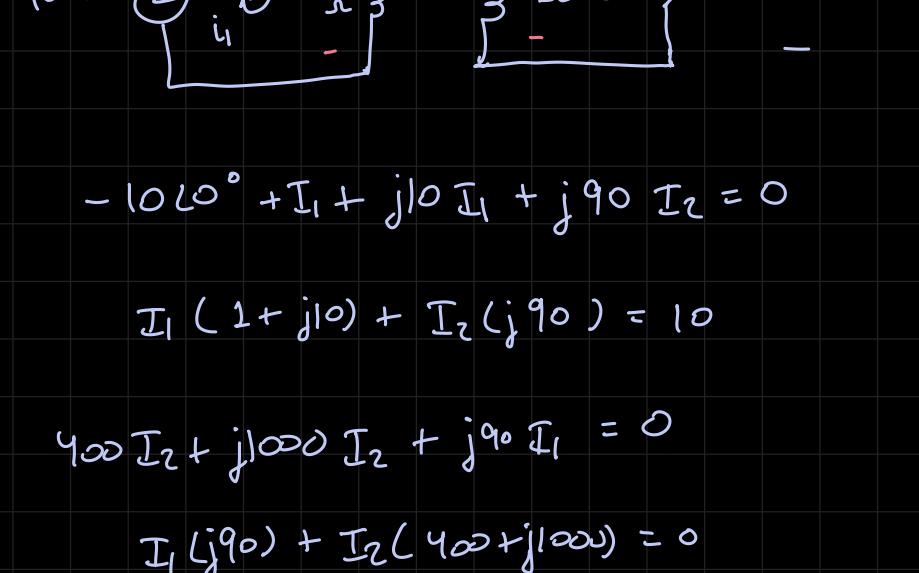

$$v_2 = L \frac{di_2}{dt} - M \frac{di_1}{dt}$$

• Dotted Notation

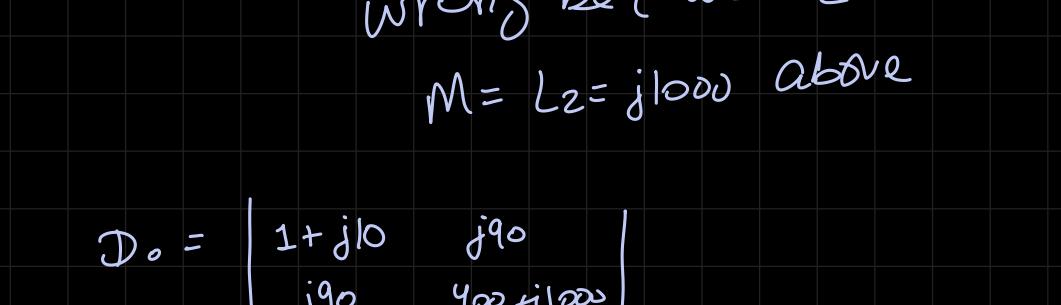Current entering terminal means
 +ve voltage reference at



$$v = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \text{time domain}$$

$$V = j\omega L_1 I_1 + j\omega M I_2 \quad \text{phasor domain}$$

$$\text{eg} \quad \begin{array}{c} 1 \Omega \\ \text{AC source} \\ 10 \cos(\omega t) \end{array} \quad \begin{array}{c} i_1 \\ i_2 \end{array} \quad \begin{array}{c} M \\ \text{M} = j90^\circ \end{array} \quad \begin{array}{c} 4 \Omega \\ \text{AC source} \\ 4 \cos(90^\circ) \end{array} \quad \begin{array}{c} i_1 \\ i_2 \end{array} \quad \begin{array}{c} 4 \Omega \\ \text{AC source} \\ 4 \cos(90^\circ) \end{array} \quad \begin{array}{c} v_2 = ? \end{array}$$

$$\textcircled{1} \quad -10 \cos(90^\circ) + I_1 + j10 I_1 + j90 I_2 = 0$$

$$I_1 (1 + j10) + I_2 (j90) = 10$$

$$\textcircled{2} \quad 4 \cos(90^\circ) + j1000 I_2 + j90 I_1 = 0$$

$$I_1 (j90) + I_2 (4 + j1000) = 0$$

CURRENTS :

$$\Delta = \begin{vmatrix} 1+j10 & j90 \\ j90 & 400+j1000 \end{vmatrix}$$

$$= (1+j10)(400+j1000) + 90000$$

$$= 400 + j1000 + j4000 - 10.000 + 90.000$$

$$= j5000 + 80,400 = 80555 \angle 3.55^\circ$$

$$\Delta_1 = \begin{vmatrix} j1000 & 10 \\ 400+j1000 & 0 \end{vmatrix} = -4000 - j10.000 = 10770 \angle -111.8^\circ$$

$$\Delta_2 = \begin{vmatrix} 10 & 1+j10 \\ 0 & j90 \end{vmatrix} = j900 = 900 \angle 90^\circ$$

$$I_1 = \frac{\Delta}{\Delta_1} = -3.2 + 6.75j$$

full current part

wrong because I took $M = L_2 = j1000$ above

$$\Delta_0 = \begin{vmatrix} 1+j10 & j90 \\ j90 & 400+j1000 \end{vmatrix}$$

$$= 400 + j1000 + j4000 - 10.000 + 8100$$

$$= j5000 - 1500 = 5220 \angle 106.69^\circ$$

ENERGY STORED IN THE CIRCUIT

$$w(t) = \frac{1}{2} L_1 i_1(t)^2 + \frac{1}{2} L_2 i_2(t)^2$$

$$\pm M i_1(t) i_2(t)$$

+: current entering same: • and • OR - and -

-: current entering different: • and - OR - and •

COUPLING COEFFICIENT (k)

$$k = \frac{M}{\sqrt{L_1 L_2}} \quad ; \quad \text{note } \Rightarrow M \leq \sqrt{L_1 L_2}$$

$$\therefore 0 \leq k \leq 1$$