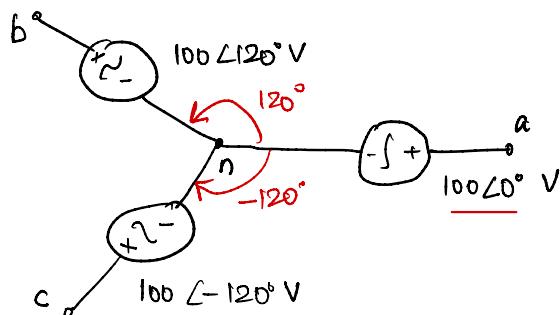


Module 4

Polyphase Circuits

(Chapter 12 of textbook)

Three-phase source



$$V_{an} = 100\angle 0^\circ \text{ V}$$

$$V_{bn} = 100\angle 120^\circ \text{ V}$$

$$V_{cn} = 100\angle -120^\circ \text{ V}$$

$$\begin{aligned} |V_{an}| &= |V_{bn}| = |V_{cn}| \\ \rightarrow V_{an} + V_{bn} + V_{cn} &= 0 \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{Balanced Source}$$

Freq. Domain

$$100\angle 0^\circ$$

$$100\angle 120^\circ$$


$$100\angle -120^\circ$$

Time Domain

$$100 \cos(\omega t)$$


$$100 \cos(\omega t + 120^\circ)$$

$$100 \cos(\omega t - 120^\circ)$$

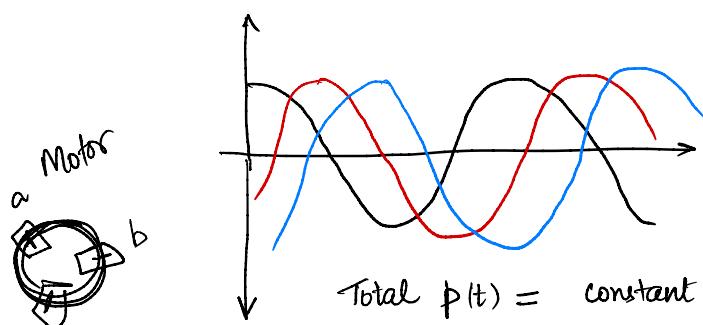

Total $p(t) = \text{constant}$ for three-phase sources
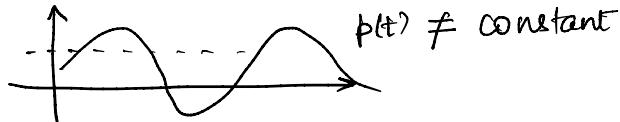
$$\text{for single phase source: } p(t) = \frac{1}{2} V_m I_m \cos(\theta - \phi) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta - \phi)$$




Advantages of three-phase sources are


- constant power and constant torque to large motors.
- more economical since motors are more efficient.

$\theta^\circ, \theta - 180^\circ$

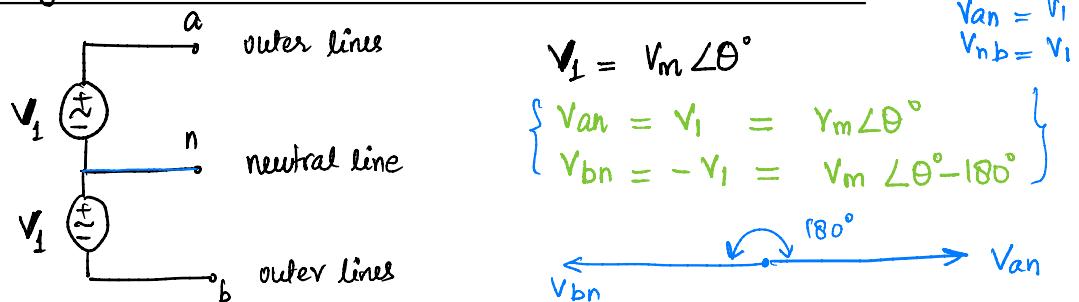Single-Phase Three-Wire Source (Two-phase source)



Double Script Notations:

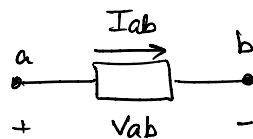

V_{an} = voltage at point a w.r.t. voltage at point n


$$V_{ab} = V_{an} - V_{bn} = V_{an} + V_{nb}$$

$$V_{bn} = -V_{nb}$$

I_{ab} = current flowing from point a to point b.

Balanced Single-Phase Three-Wire Source:


$$\left. \begin{array}{l} |V_{an}| = |V_{bn}| \\ V_{an} + V_{bn} = 0 \end{array} \right\} \text{Balanced source}$$

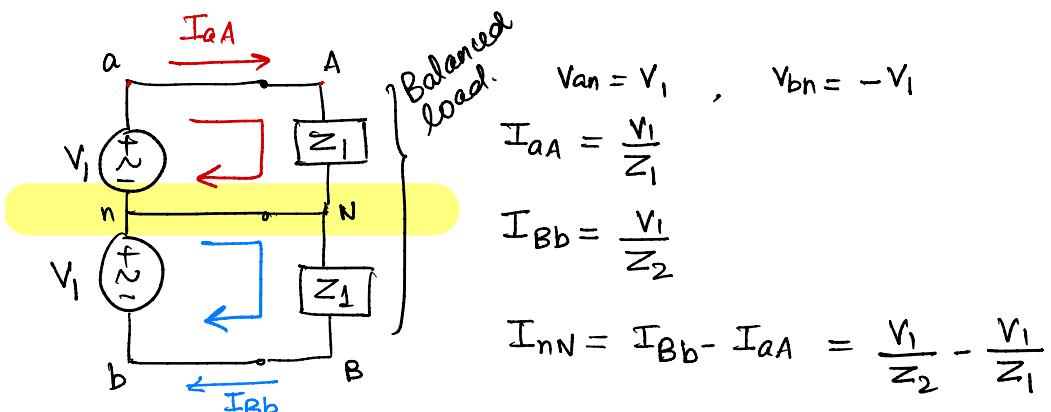

Assume $Z_1 = Z_2$ (Balanced load)

$$I_{nN} = \frac{V_1}{Z_1} - \frac{V_1}{Z_1} = 0$$

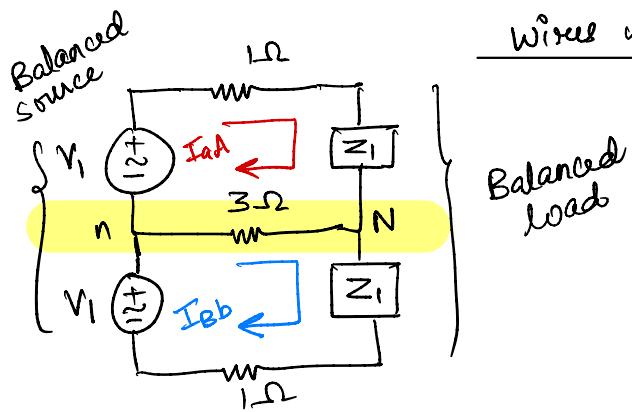
For balanced source } current in neutral line $I_{nN} = 0$
and balanced load }



Wires with non-zero resistance

$$I_{BN} = 0 = I_{Bb} - I_{aA}$$

Example

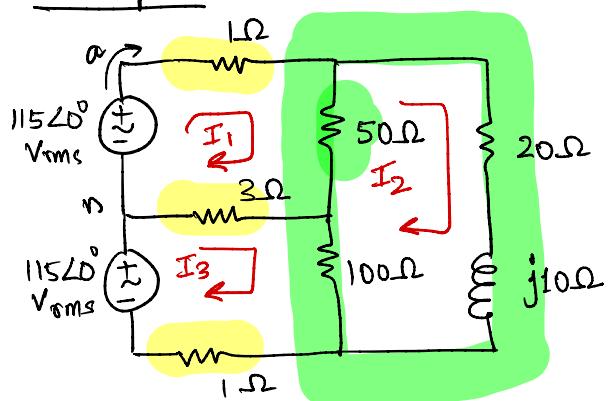

Line resistances

loads

Find

- ① Average power delivered to each of three loads
- ② Avg power lost in outerlines and neutral line.
- ③ Avg power provided by source.

Using mesh analysis

$$-115\angle 0^\circ + 1(I_1) + 50(I_1 - I_2) + 3(I_1 - I_3) = 0$$

$$50(I_2 - I_1) + (20 + j10)I_2 + 100(I_2 - I_3) = 0$$

$$-115\angle 0^\circ + (I_3 - I_1)3 + (I_3 - I_2)100 + I_3(1) = 0$$

$$\rightarrow I_1 = 11.24 \angle -19.83^\circ \text{ Arms}$$

$$I_2 = 9.389 \angle -24.47^\circ \text{ Arms}$$

$$I_3 = 10.37 \angle -21.80^\circ \text{ Arms}$$

$$I_1 - I_2 = 11.24 - 9.389$$

Avg power delivered to loads:

$$P_{avg, 50\Omega} = |I_2 - I_1|^2 (50) \\ = 206 \text{ W}$$

$$P_{avg, 100\Omega} = 117 \text{ W}$$

$$P_{avg, 20+j10\Omega} = I_2^2 (20) = 1763 \text{ W}$$

$$\text{Total power delivered to loads} = 2086 \text{ W}$$

Avg power lost in lines

$$P_{avg, aa} = |I_1|^2 1 = 126 \text{ W}$$

$$P_{avg, bb} = |I_3|^2 1 = 108 \text{ W}$$

$$P_{avg, nn} = |I_3 - I_1|^2 3 = 3 \text{ W}$$

$$\text{Total power lost in lines} = 237 \text{ W}$$

Power supplied by sources

$$P_{avg, an} = V_{an} I_{na} \cos(\theta - \phi) \\ = 115 \times 11.24 \cos(0 - (-19.83^\circ)) \\ = 1216 \text{ W}$$

$$V_{an} = 115 \angle 0^\circ \text{ V}_{rms}$$

$$I_{na} = I_1$$

$$P_{avg, nb} = 115 \times 10.37 \cos(21.80^\circ) \\ = 1107 \text{ W}$$

$$\text{Total power supplied} = 2323 \text{ W}$$

$$P_{supplied} = P_{delivered} + P_{loss}$$

① Example : Consider $V_{12} = 9 \angle 30^\circ$, $V_{32} = 3 \angle 130^\circ$
 find $V_{21} = 9 \angle -150^\circ$, $V_{13} = V_{12} + V_{23}$

② Consider a single-phase three-wire balanced source connected to a balanced load. $f = 50 \text{ Hz}$, $V_{an} = 115 \angle 0^\circ \text{ V}$

- Find power factor of the load if capacitor is omitted.
- find value of C that will lead to a unity power factor of total load.

