

14. In the three-wire system of Fig. 12.32, (a) replace the  $50\ \Omega$  resistor with a  $200\ \Omega$  resistor, and calculate the current flowing through the neutral wire. (b) Determine a new value for the  $50\ \Omega$  resistor such that the neutral wire current magnitude is 25% that of line current  $I_{aA}$ .

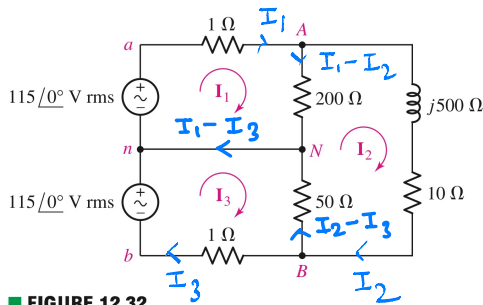


FIGURE 12.32

Sol<sup>n</sup>: (a) KVL .  $-115 + I_1 + 200(I_1 - I_2) = 0$   
 $\Rightarrow 201I_1 - 200I_2 = 115 \quad -(1)$

$-115 - 200(I_2 - I_3) + I_3 = 0$   
 $\Rightarrow -115 - 200I_2 + 201I_3 = 0$   
 $\Rightarrow 201I_3 - 200I_2 = 115 \quad -(2)$

subtracting (1) - (2)

$201(I_1 - I_3) = 0$

$\therefore I_1 - I_3 = 0$  : current through neutral wire

$$(6) \quad I_1 - I_3 = 0.25 I_1$$

$$\Rightarrow 0.75 I_1 = I_3 \quad \text{---(1)}$$

$$\text{as} \quad 201 I_1 - 200 I_2 = 115 \quad \text{---(2)}$$

let new value for  $50\Omega = R$

$$- R(I_1 - I_3) + I_3 = 115$$

$$\Rightarrow (R+1) I_3 - R I_2 = 115 \quad \text{---(3)}$$

$$\Rightarrow 0.75(R+1) I_1 - R I_2 = 201 I_1 - 200 I_2$$

$$\Rightarrow (0.75(R+1) - 201) I_1 + (200 - R) I_2 = 0 \quad \text{---(4)}$$

$$\underline{\text{KVL:}} \quad (10 + 500j) I_2 + R(I_2 - I_3) - 200(I_1 - I_2) = 0$$

$$\Rightarrow (210 + R + 500j) I_2 - 0.75R I_1 - 200 I_1 = 0$$

$$\Rightarrow (210 + R + 500j) I_2 - (0.75R + 200) I_1 = 0 \quad \text{---(5)}$$

from (4) and (5)

$$\Rightarrow (1.5R + 1.75) I_1 = (1 + 2R + 500j) I_2$$

$$\Rightarrow I_2 = \frac{(1.5R + 1.75) I_1}{(2R + 1 + 500j)}$$

substituting  $I_2$  in (5)

$$\Rightarrow \left\{ (210 + R + 500j) - \frac{(0.75R + 200)(1.5R + 1.75)}{(2R + 1 + 500j)} \right\} I_1 = 0$$

$$\Rightarrow \left\{ (210 + R + 500j) - \frac{(0.75R + 200)(1.5R + 1.75)}{(2R + 1 + 500j)} \right\} I_1 = 0$$

$$\text{Since } I_1 \neq 0 \text{ A}$$

$$\Rightarrow (210 + R + 500j)(2R + 1 + 500j) - (0.75R + 200)(1.5R + 1.75) = 0$$

$$\begin{aligned} \Rightarrow & 420R + 210 + 105000j + 2R^2 + R + 500Rj \\ & + 1000Rj + 500j - 250000 \\ & - \{ 1.125R^2 + 1.31R + 300R + 350 \} = 0 \end{aligned}$$


$$\Rightarrow (421 + 1500j - 301.31)R + 0.875R^2 + 105500j - 249650 = 0$$

$$\Rightarrow 0.875R^2 + 119.69R - 249650 + j(1500R + 105500) = 0$$

|   |                      |
|---|----------------------|
| $\Rightarrow 0.875R^2 + 119.69R - 249650 = 0$ | $1500R + 105500 = 0$ |
|   | (Not Possible)       |

$$\therefore R = 470.11 \Omega$$

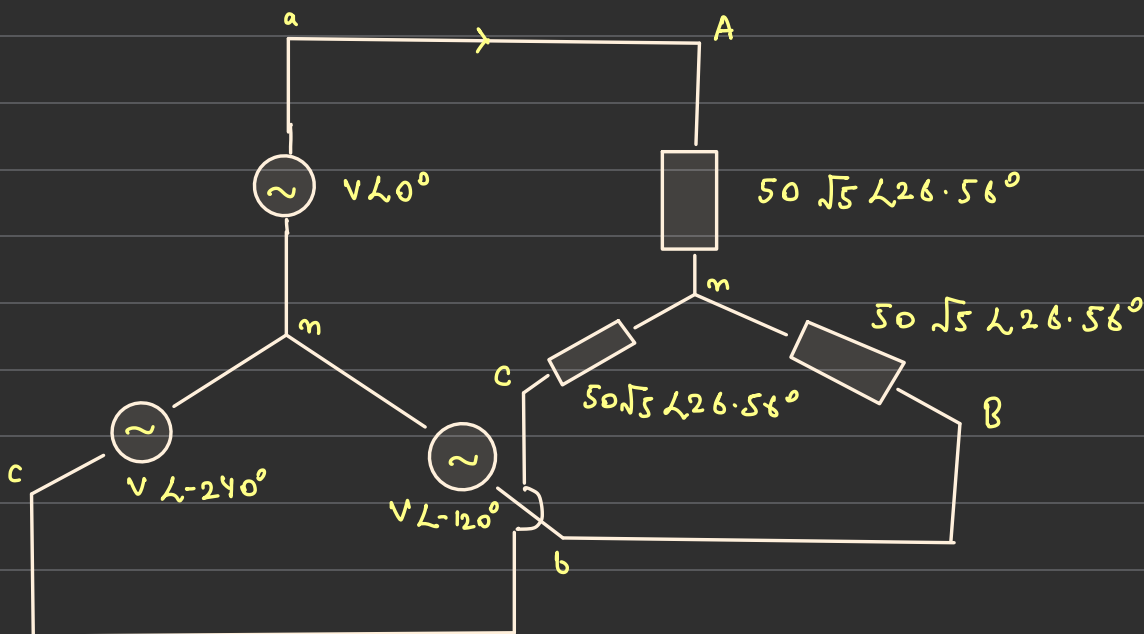22. A balanced Y-connected load of  $100 + j50 \Omega$  is connected to a balanced three-phase source. If the line current is 42 A and the source supplies 12 kW, determine (a) the line voltage; (b) the phase voltage.



Line voltages:  $V_{ab}, V_{bc}, V_{ca}$

Phase voltages:  $V_{an}, V_{bn}, V_{cn}$

Line currents:  $I_{aA}, I_{bB}, I_{cC}$

also

$$V_{line} = \sqrt{3} V_{phase} \angle \alpha + 30^\circ$$

some angle

$$I_{aA} = I_0 \angle -\theta, \quad I_{bB} = I_0 \angle -\theta - 120^\circ$$

$$I_{cC} = I_0 \angle -\theta - 240^\circ$$

$$\theta = 26.56^\circ$$

$$|I_{QA}| = \left| \frac{V}{50\sqrt{3}} \right| = \left| \frac{V}{50\sqrt{3}} \right| = 42$$

$$V = 2100\sqrt{3}$$

$$V = 4695.74 \text{ watt}$$

↳ phase voltage

$$\sqrt{3} V_{\text{phase}} = V_{\text{line}} \Rightarrow 4695.74\sqrt{3}$$

$$\therefore V_{\text{phase}} = 4695.74\sqrt{3}$$

↳ line voltage

Q. Two  $\Delta$  connected load are connected in parallel and powered by a balanced Y-connected system.

Smaller of the two load draws 10 KVA at a lagging voltage & PF of 0.75. larger 25 KVA at a leading PF of 0.80. The line voltage is 400 V.

- (a) Power factor at which the source is operating
- (b) The total power drawn by the two loads
- (c) The phase current of each load.

Smaller load,

$$\text{Apparent Power } S_1 = 10 \text{ KVA} = 10,000 \text{ VA}$$

$$\text{Power factor } PF_1 = 0.75 \text{ (lagging)}$$

larger load,

$$\text{Apparent Power } S_2 = 25 \text{ KVA} = 25,000 \text{ VA}$$

$$\text{Power factor } PF_2 = 0.80 \text{ (leading)}$$

Line voltage

$$V_{\text{line}} = 400 \text{ V}$$

(a) Power factor of the source:

Real Power (P)  $\Rightarrow$  for the smaller load

$$P_1 = S_1 \times PF_1 = 10,000 \times 0.75 = 7,500 \text{ W}$$

$\Rightarrow$  for the larger load

$$P_2 = S_2 \times PF_2 = 25,000 \times 0.80 = 20,000 \text{ W}$$

Reactive Power (Q)

$\Rightarrow$  for the smaller load (lagging, inductive).

$$Q_1 = S_1 \times \sin(\cos^{-1}(PF_1)) = 10,000 \times \sin(\cos^{-1}(0.75)) \\ = 10,000 \times 0.6614$$

$$Q_1 = 6,614 \text{ VAR}$$



→ for the larger load (leading, Capacitive);

$$Q_2 = S_2 \times \sin(\cos^{-1}(PF_2)) = 25,000 \times \sin(\cos^{-1}(0.80))$$

$$Q_2 = 25,000 \times 0.6 = 15,000 \text{ VAR}$$

$$\text{Total Real Power } (P_{\text{total}}) = P_1 + P_2 = 7,500 + 20,000 = 27,500 \text{ W}$$

$$\text{Total Reactive Power } (Q_{\text{total}}) = Q_1 - Q_2 = 6614 - 15,000 = -8,386 \text{ VAR}$$

Total Apparent Power  $S_{\text{total}}$ :

$$S_{\text{total}} = \sqrt{P_{\text{total}}^2 + Q_{\text{total}}^2} = \sqrt{(27,500)^2 + (-8386)^2}$$

$$S_{\text{total}} = \sqrt{756,250,000 + 70,307,396} = \sqrt{826,557,396} \approx 28,742 \text{ VA}$$

$$\text{Power factor of the source } (PF_{\text{total}}) = \frac{P_{\text{total}}}{S_{\text{total}}} = \frac{27,500}{28,742} \approx 0.956$$

(b) Total Power drawn by the two loads

$$S_{\text{total}} = 28,742 \text{ VA}$$

(c) Phase Current of Each load


$$I = \frac{S}{\sqrt{3} \times V_{\text{line}}}$$

$$\text{for the smaller load:- } I_1 = \frac{S_1}{\sqrt{3} \times V_{\text{line}}} = \frac{10,000}{\sqrt{3} \times 400} = \frac{10,000}{692.82} \approx 14.44 \text{ A}$$

$$\text{for the larger load:- } I_2 = \frac{S_2}{\sqrt{3} \times V_{\text{line}}} = \frac{25,000}{\sqrt{3} \times 400} \approx \frac{25,000}{692.82} \approx 36.1 \text{ A}$$



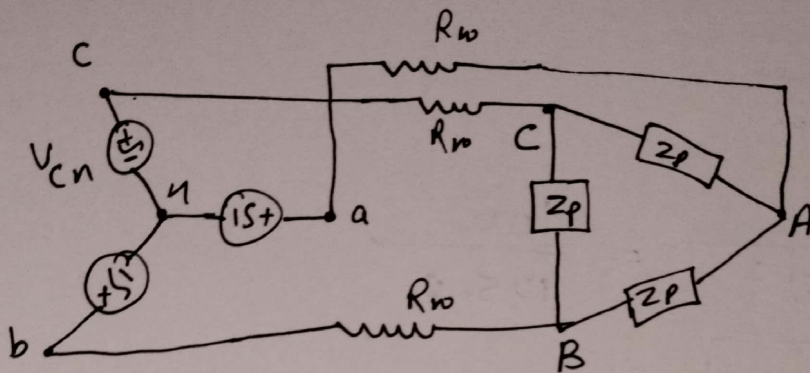Q. For the balanced three-phase system shown in Fig. It is determined that 1000 W is lost in each wire. If the phase voltage of the source is 400 V and the load draws 12 kW at a lagging PF of 0.83. determine the wire resistance  $R_w$ .



Power loss in each wire  $P_{loss} = 1000 \text{ W}$

Phase Voltage  $V_{an} = 400 \text{ V}$

Load Power  $P_{load} = 12 \text{ kW} = 12000 \text{ W}$

Power factor of the load  $PF = 0.83$  (lagging)

Determine the total current in the system

$$P_{load} = \sqrt{3} \times V_{line} \times I \times PF$$

$$V_{line} = \sqrt{3} \times V_{phase}$$

$$P_{load} = 3 \times V_{phase} \times I_{phase} \times PF$$

$$I_{phase} = \frac{P_{load}}{3 \times V_{phase} \times PF}$$

$$I_{phase} = \frac{12000}{3 \times 400 \times 0.83} = \frac{12000}{996}$$

$$I_{phase} \approx 12.05 \text{ A}$$



use power loss to find  $R_w$

$$P_{loss} = I^2 R$$

$$P_{loss} = I_{phase}^2 \times R_w$$

$$R_w = \frac{P_{loss}}{I^2_{phase}}$$

$$R_w = \frac{100}{(12.05)^2} = \frac{100}{145.2}$$

$$\boxed{R_w \approx 0.688 \Omega}$$