

tr5frbj 12/08/24

Circuit Theory and Devices

Lab: LT Spice (2nd week onwards)

book: Engineering Circuit Analysis (9th edition)

Relative grading


Labs	20%
Quiz	20%
Midsem	30%

Scientific calc

Course: 9 modules chapter 10 onwards
{continuation of BE3}

Lecture 1

⇒ Linear Circuits

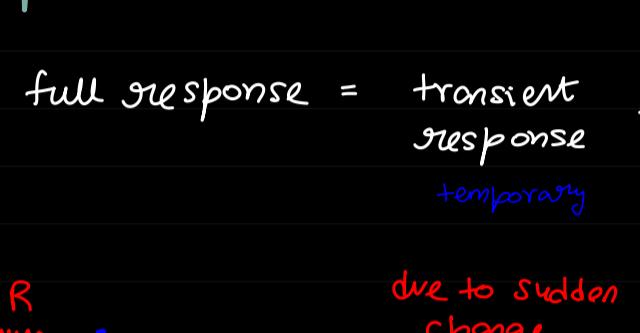

System is linear if

$$Kx \rightarrow [\text{sys}] \rightarrow Ky$$

where K is constant

"R" Resistor: linear element ✓
 $V = iR$

"L" Inductor: linear element ✓

$$V = L \frac{di}{dt}$$

"C" Capacitor: linear element ✓

$$i = C \frac{dv}{dt}$$


* Linear Electric Circuits:

consists of ⇒

① $R, L, C \rightarrow$ linear elements

② Independent voltage & current sources

③ Linear dependent sources

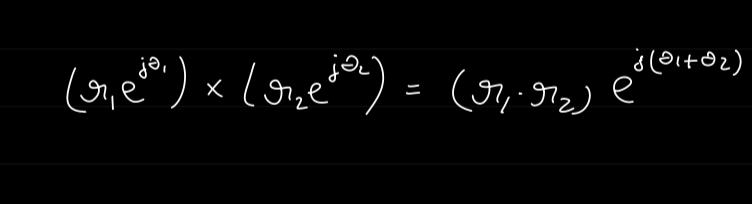

example would not have been

linear if $V_s = kV_x^2$

Note: diode and transistors are non-linear elements

Non-linear elements

Non-linear response

depends on current/voltage source

* Response of a linear circuit

① full response = transient response + steady state

transient temporary persists

steady state $t \rightarrow \infty$

Nodes

due to sudden change

also called natural response

depends on R, L, C

due to source

also called forced response

depends on current/voltage source

Nodes

due to source

also called forced response

depends on current/voltage source

Nodes

due to source

also called forced response

depends on current/voltage source

Nodes

due to source

also called forced response

depends on current/voltage source

Nodes

due to source

also called forced response

* Section 10.1

(a) $Q_1 y \quad 5\sin(5t - 9^\circ)$

$$t=0 \Rightarrow 5\sin(-9^\circ) = -5\sin(9^\circ) = -0.782$$

$$t=0.01 \Rightarrow 5\sin(0.05 - 9^\circ) = -5\sin(8.95^\circ) \quad X$$

\Downarrow
radians

$$5\sin\left(\frac{0.05 \times 80}{\pi} - 9^\circ\right) = 5\sin(2.86^\circ - 9^\circ)$$

$$\Rightarrow -5\sin(6.14^\circ) = -0.534$$

$$t=0.1 \Rightarrow 5\sin(0.5 - 9^\circ) = 5\sin(28.64^\circ - 9^\circ) = 5\sin(19.64^\circ)$$

$$\Rightarrow 1.6805$$

(b) $4\cos 2t$

$$t=0 \Rightarrow 4\cos(0) = 4$$

$$t=1 \Rightarrow 4\cos(2) = 3.997$$

$$t=1.5 \Rightarrow 4\cos(3) = 3.994$$

(c) $3.2 \cos(6t + 15^\circ)$

$$t=0 \Rightarrow 3.2 \cos(15^\circ) = 3.09$$

$$t=0.01 \Rightarrow 3.2 \cos(0.06 + 15^\circ) = 3.2 \cos(3.43^\circ + 15^\circ)$$

$$\Rightarrow 3.2 \cos(18.43^\circ)$$

$$\Rightarrow 3.035$$

$$t=0.1 \Rightarrow 3.2 \cos(0.6 + 15^\circ) = 3.2 \cos(34.3^\circ + 15^\circ)$$

$$= 3.2 \cos(49.3^\circ)$$

$$= 2.086$$

Q2) (a) $300\sin(628t) \rightarrow 300 \cdot \cos(628t - 90^\circ)$


$$4\sin(3\pi t + 30^\circ) \rightarrow 4\cos(3\pi t - 60^\circ)$$

$$14\sin(50t - 8^\circ) - 10\cos 50t \rightarrow$$


Q3) $V_L = 10\cos(10t - 45^\circ)$

(a) $i_L = 5\cos 10t$

$$-45^\circ$$

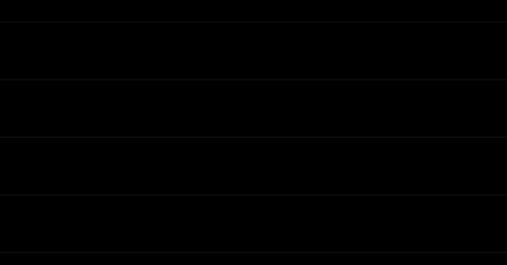

⇒ AC Power Analysis {Module: 3}

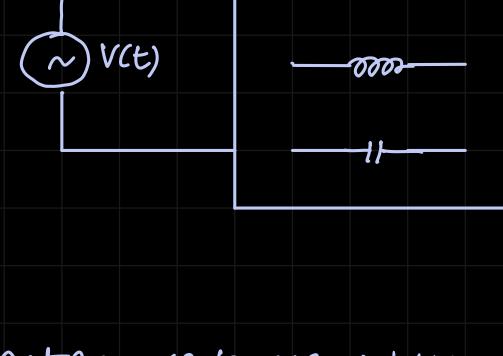

$$\cos(A) \cos(B) =$$

$$\frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

Instantaneous power: $p(t) = v(t) \cdot i(t)$

$$v(t) = V_m \cdot \cos(\omega t + \theta)$$

$$i(t) = I_m \cdot \cos(\omega t + \phi)$$

$$p(t) = V_m \cdot \cos(\omega t + \theta) \cdot I_m \cdot \cos(\omega t + \phi)$$

$$p(t) = \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{constant}} + \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)}_{\text{twice frequency}}$$

(DC term)

(harmonic)

• Average Power

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{real part}} dt + \underbrace{\frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) dt}_{\text{imaginary part}}$$

$$P_{avg} = \frac{V_m I_m}{2} \cdot \cos(\theta - \phi)$$

* Avg. Power absorbed

• by a purely resistive element

$$P_{avg} = \frac{V_m I_m}{2} \cdot \cos(\theta - \phi)$$

here, phase diff = 0°




$$P_{avg} = \frac{V_m \cdot I_m}{2} = \frac{I_m^2 R}{2} = \frac{V_m^2}{2R}$$

• by a purely inductive element

$$P_{avg} = \frac{V_m I_m}{2} \cdot \cos(\theta - \phi)$$

here, phase diff = 90°

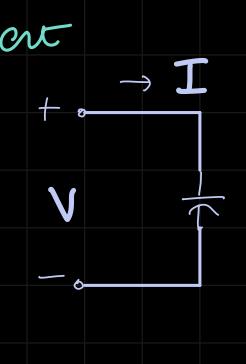

$$P_{avg} = 0 \text{ for inductor}$$

• by a purely capacitive element

$$P_{avg} = \frac{V_m \cdot I_m}{2} \cdot \cos(-90^\circ)$$



$$P_{avg} = 0 \text{ for capacitor}$$

* Lecture: 6

$$v(t) = V_m \cos(\omega t + \phi) \quad \leftarrow \text{Revision}$$

$$\downarrow$$


$$v(t) = R \Re \{ V_m e^{j\omega t} e^{j\phi} \}$$

$$\downarrow -e^{j\omega t}$$

$$V_m e^{j\phi} = V_m \angle \phi$$

exponential polar

• eq)

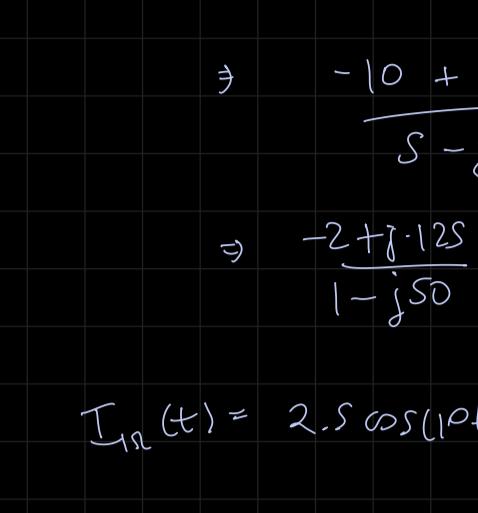


① find power delivered to each element at $t = 0, 10, 20 \text{ ms}$

② find P_{avg} to each element

(ans) convert to freq. domain

$$V_{1\text{R}} = V_{u\text{R}} + V_c$$

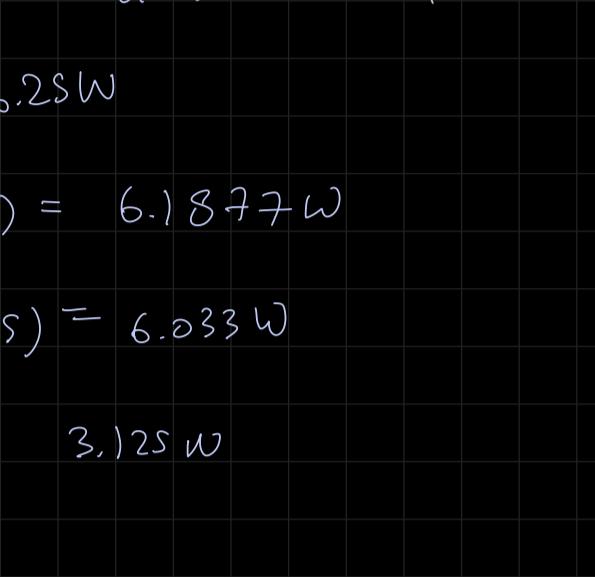

$$\textcircled{1} \quad P_{inst} = \frac{V_m I_m \cos(\theta - \phi)}{2} + \frac{V_m I_m}{2} \cos(2\omega t + \phi + \theta)$$

$$I_1 = -2.5 \times \left(\frac{4 - j2.5 \times 10^4}{1 + j - j2.5 \times 10^4} \right) \approx -2.5 \text{ A}$$

$$\Rightarrow \frac{-10 + j62.5 \times 10^4}{5 - j2.5 \times 10^4} \Rightarrow \frac{-2 + j12.5}{1 - j50}$$

$$\Rightarrow \frac{-2 + j1.25}{1 - j50} \times \frac{1 + j50}{1 + j50} =$$

$$I_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$V_{1\text{R}} = (I_{1\text{R}})(2 \Omega) \Rightarrow V_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$\cos^2(\theta) = \frac{1 + \cos(2\theta)}{2}$$

$$P_{1\text{R}}(t) = 2.5 \cos(10t) \cdot 2.5 \cos(10t) \text{ W}$$

$$P_{1\text{R}}(t=0) = 6.25 \text{ W}$$

$$P_{1\text{R}}(t=20 \text{ ms}) = 6.033 \text{ W}$$

$$(P_{avg})_{1\text{R}} = 3.125 \text{ W}$$

\Rightarrow P delivered to 4 ohm

$$P_{4\text{R}}(t) = V_{u\text{R}}(t) \times I_{u\text{R}}(t)$$

$$\Rightarrow I_{4\text{R}} = I_s \times \frac{1}{5 - j2.5 \times 10^4} = 10^{-4} \angle 90^\circ \text{ A}$$

$$V_{u\text{R}} = 4 \times I_{4\text{R}} = 4 \times 10^{-4} \angle 90^\circ \text{ V}$$

convert to time domain

$$P_{1\text{R}}(t) = 2 \times 10^{-8} + 2 \times 10^{-8} \cos(20t) \text{ W}$$

$$t=0^- \quad 4 \times 10^{-8} \text{ W}$$

$$t=10 \text{ ms} = 3.96 \times 10^{-8} \text{ W}$$

$$P_{4\text{R}}(t=0) = 2 \times 10^{-8} \text{ W}$$

\Rightarrow P delivered to capacitor

$$P_c(t) = V_c(t) \cdot I_c(t)$$

$$\left(P_{avg} \right)_c = 0 \quad \text{since phase diff} = 90^\circ$$

$$I_c = I_2 = 10^{-4} \angle 90^\circ \text{ A} \Rightarrow I_c(t) = 10^{-4} \cos(10t + 90^\circ)$$

$$V_c = (-j2.5 \times 10^4) \times 10^{-4} \angle 90^\circ$$

$$-j2.5 \times 10^4 \times (+j10^{-4}) =$$

$$P_c(t) = 1.25 \times 10^{-4} \cos(20t + 90^\circ) \text{ W}$$

$$t=0 \Rightarrow P=0 \text{ W}$$

$$t=10 \text{ ms} \Rightarrow P=2.48 \times 10^{-5} \text{ W}$$

Note: we cannot multiply I_c and V_c in phasor form and then convert to time domain for getting P_c (power) because power does not have a phasor part. It is a real value.

* Correct or not?

$$\text{depends on } \times \quad \textcircled{1} \quad P_{1\text{R}}(t) + P_{4\text{R}}(t) + P_c(t) = \text{constant 1}$$

$$\checkmark \quad \textcircled{2} \quad P_{avg\ 1\text{R}} + P_{avg\ 4\text{R}} + P_{avg\ c} = \text{constant 2}$$

$\Rightarrow P_{avg\ source}$

active sign convention

passive sign convention

maximum power delivered to load when

$$Z_L = Z_S^*$$

complex conjugate of Z_S

\Rightarrow Impedance Matching

$$100 \Omega \quad \text{impedance matching circuit} \quad j50 \Omega$$

$$100 \Omega \quad 50 \Omega \quad j50 \Omega$$

$$Z_L = Z_S^*$$

$i(t) \xrightarrow{\text{square}} i^2(t) \xrightarrow{\text{mean}} \frac{1}{T} \int_0^T i^2(t) dt \xrightarrow{\text{current}} \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$

$v(t) \xrightarrow{\text{square}} v^2(t) \xrightarrow{\text{mean}} \frac{1}{T} \int_0^T v^2(t) dt \xrightarrow{\text{voltage}} \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$

$\Rightarrow I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} \quad \text{Root mean square value}$

$\Rightarrow V_{eff} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \quad \text{Root mean square value}$

$\Rightarrow I_{eff} = \frac{I_m}{\sqrt{2}} \quad \text{current rms value unit: A rms}$

$\Rightarrow V_{eff} = \frac{V_m}{\sqrt{2}} \quad \text{voltage rms value unit: V rms}$

$\Rightarrow I = 10 \angle 90^\circ \text{ A} \Rightarrow I = 5\sqrt{2} \angle 90^\circ \text{ A rms}$

or $V = 100 \sqrt{2} \angle -60^\circ \text{ V} \Rightarrow V = 100 \angle -60^\circ \text{ V rms}$

* Apparent Power

$$P_{apparent} = I_{eff} V_{eff} \quad \text{volt amperes}$$

unit: VA, not W

* Power factor

$$PF = \frac{\text{avg power}}{\text{apparent power}} = \frac{(V_m \cdot I_m)/2 \cos(\theta - \phi)}{V_{eff} \cdot I_{eff}}$$

$$PF = \cos(\theta - \phi)$$

$\xrightarrow{5}$ power factor angle

\Rightarrow Power factor angle

\Rightarrow Power factor angle

* Lecture: 7


- Instantaneous Power: $p(t) = v(t)i(t)$
- Average Power: $P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) = \frac{1}{2} R_{eff} \{VI^*\}$
- $P_{avg, sources} = \sum P_{avg, elements}$

* Note: $Z = R + jX$
 \downarrow resistive reactive


$P_{avg, resistive} : P \neq 0$

$P_{avg, reactive} : P = 0$


* Max Power Transfer:

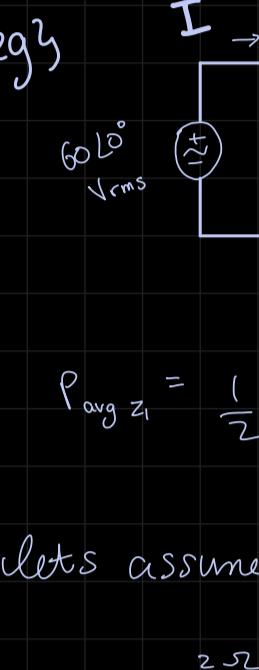

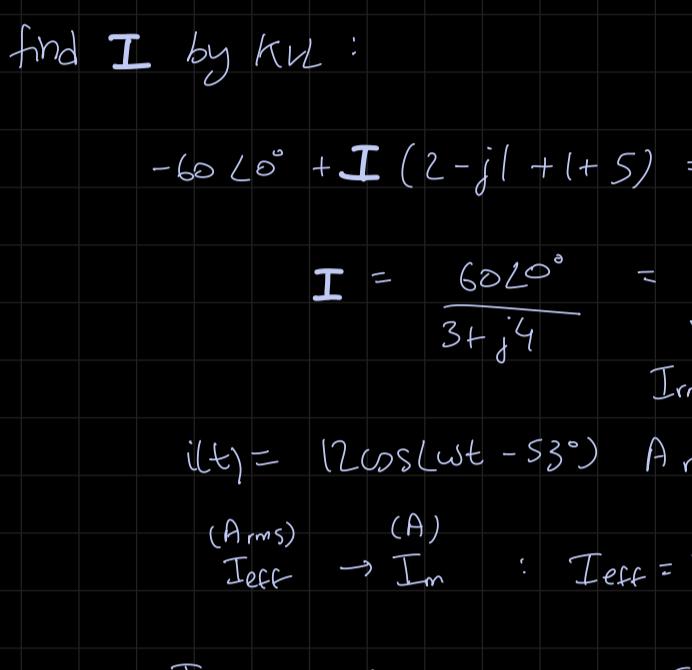Circuit has max. power when $Z_L = Z_s^*$ complex conjugate



↓ apply Thevenin's theorem

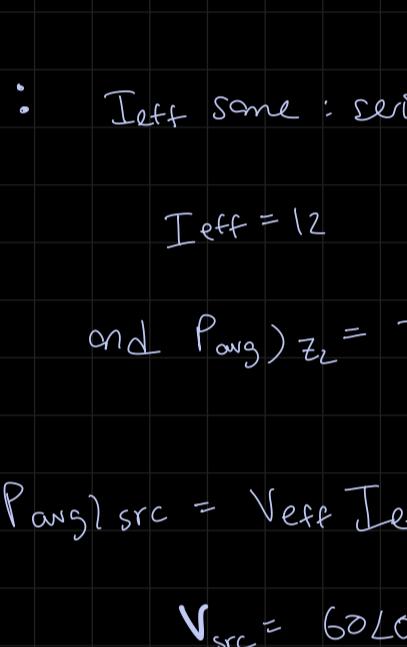

$$Z_L = Z_{th}$$


* Power Factor

$$PF = \cos(\theta - \phi) = \frac{\text{Power active}}{\text{Power apparent}}$$

angle of voltage phasor
↑ angle of current phasor

for purely resistive load: $PF = 1$ {Max} $\theta - \phi = 0^\circ$
 for purely reactive load: $PF = 0$ {min}

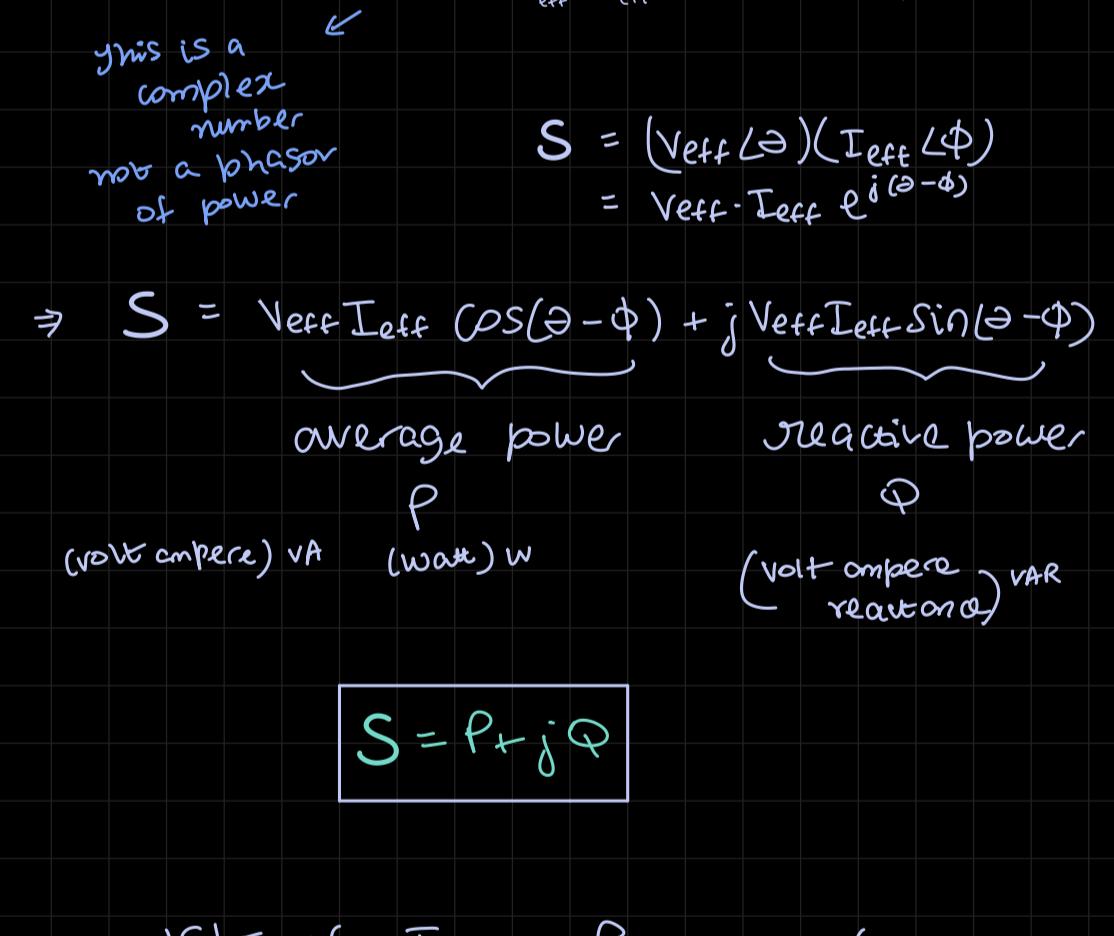Note $\rightarrow PF = 0.5$ leading \rightarrow capacitive $(\theta - \phi) < 0^\circ$
 $PF = 0.5$ lagging \rightarrow inductive $(\theta - \phi) > 0^\circ$



(Ans) $P_{avg, Z_1} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} R_{eff} \{VI^*\}$

voltage across Z_1 , not the src

lets assume Z_1 :

$$\frac{2-j1}{2+j4} = \frac{-j2}{3+j4} \quad \text{so, } P_{avg, Z_1} = \text{Power delivered to } 2\Omega \text{ resistor}$$

$$= I_{eff}^2 R$$

find I by KVL:

$$-60 \angle 0^\circ + I(2 - j1 + 1 + j5) = 0$$

$$I = \frac{60 \angle 0^\circ}{3 + j4} = 12 \angle -53.13^\circ \text{ Arms}$$

$$i(t) = 12 \cos(\omega t - 53.13^\circ) \text{ A rms}$$

$$\frac{(A_{rms})}{I_{eff}} \rightarrow \frac{(A)}{I_m} : I_{eff} = I_m \Rightarrow I_m = I_{eff} \sqrt{2}$$

$$I_{eff} = 12 \text{ Arms} \Rightarrow I_m = 12\sqrt{2} \text{ A}$$

$$i(t) = 12\sqrt{2} \cos(\omega t - 53^\circ) \text{ A}$$

$$P_{avg, Z_1} = (12)^2 \times 2 = 288 \text{ W}$$

$$\text{note: } P_{avg} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{eff} I_{eff} \cos(\theta - \phi)$$


$$S = V_{eff} I_{eff} \cos(\theta - \phi) = V_{eff} I_{eff} \sin(\theta - \phi)$$

$$S = P + jQ$$

* Lecture - 8

• Polyphase Circuits (Chp 12)

⇒ Three Phase Source

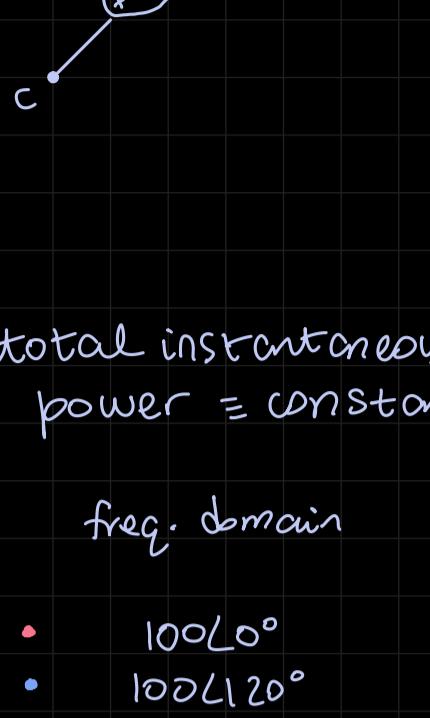

$$V_{an} = 100 \angle 0^\circ V$$

$$V_{bn} = 100 \angle 120^\circ V$$

$$V_{cn} = 100 \angle -120^\circ V$$

if $|V_{an}| = |V_{bn}| = |V_{cn}|$
 & $V_{an} + V_{bn} + V_{cn} = 0$
 then it is a

Balanced Source


total instantaneous power = constant

freq. domain

- $100 \angle 0^\circ$
- $100 \angle 120^\circ$
- $100 \angle -120^\circ$

time domain

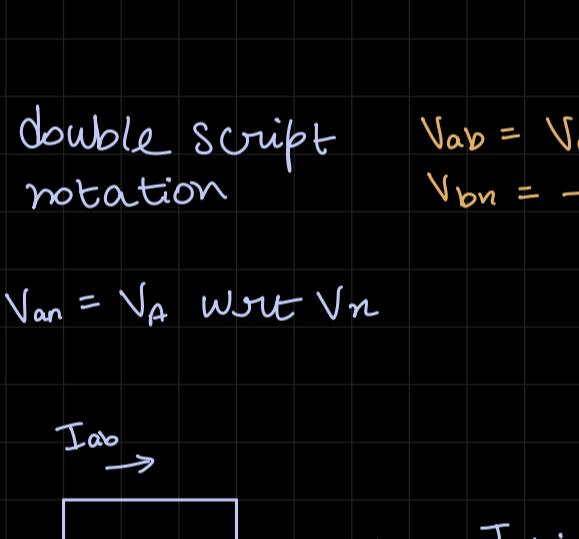
- $100 \cos(\omega t)$
- $100 \cos(\omega t + 120^\circ)$
- $100 \cos(\omega t - 120^\circ)$



total $p(t) \rightarrow \text{constant}$

* Single Phase Three-wire Source

≡ Two phase source

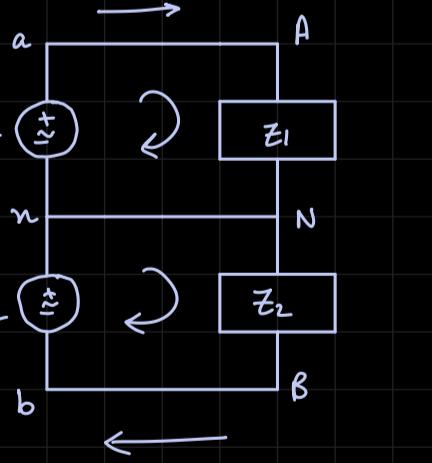

$$V_1 = V_m \angle 0^\circ$$

$$V_{an} = V_1 = V_m \angle 0^\circ$$

$$V_{bn} = -V_1 = V_m \angle 0^\circ - 180^\circ$$


$$V_{bn} \leftarrow \xrightarrow{180^\circ} V_{an}$$

double script notation

$$V_{ab} = V_{an} - V_{bn} = V_{an} + V_{nb}$$

$$V_{bn} = -V_{nb}$$

$$V_{an} = V_A \text{ wrt } V_n$$

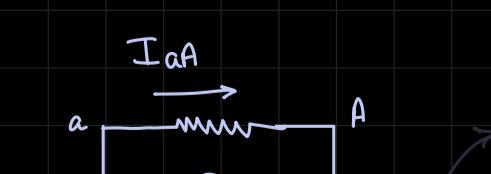

$$I_{aa} = \frac{V_1}{Z_1}$$

$$I_{bb} = \frac{V_1}{Z_2}$$

$$I_{nn} = -I_{aa} + I_{bb}$$

$$\Rightarrow \frac{V_1}{Z_1} - \frac{V_1}{Z_2}$$

Assume $Z_1 = Z_2$

$$I_{nn} = \frac{V_1}{Z_1} - \frac{V_2}{Z_1} = 0$$

when both srcs &
and loads are equal

Balanced Load : current in neutral line is equal to zero.

all terms are phasors

even with resistance,

$$I_{nn} = 0 = I_{bb} - I_{aa}$$

due to

① Balanced Load

≡ Symmetry

* Lecture: 9

09/09/29

time domain freq. domain

$$\begin{array}{ll} \sqrt{V_p} \cos(\omega t + \theta^\circ) & \sqrt{V_p} L^{\theta^\circ} \\ \sqrt{V_p} \cos(\omega t + \theta^\circ - 180^\circ) & \sqrt{V_p} L^{\theta^\circ - 180^\circ} \end{array}$$

We cannot directly say,

$$P_{avg} = \sqrt{I} \quad \times$$

$$\text{but } P_{avg} = \frac{1}{2} \operatorname{Re}\{ \sqrt{I} I^* \} \quad \checkmark$$

$$\begin{aligned} \textcircled{2} \quad a) \quad I_{AB} &= \frac{115 L^{\theta^\circ} + 115 L^{\theta^\circ}}{2(10 + j^2)} = \frac{230 L^{\theta^\circ}}{2(10 + j^2)} \\ &= 11.27 / (\theta^\circ - 11.3^\circ) A \end{aligned}$$


$$\phi = \theta - 11.3^\circ$$

$$PF = \cos(\theta - \phi + 11.3^\circ) = 0.98 \text{ lagging}$$

because PF angle is true

$$b) \quad PF = 1 \Rightarrow \cos(\theta - \phi) = 1 \Rightarrow \theta - \phi = 0$$

$$\Rightarrow \theta = \phi$$

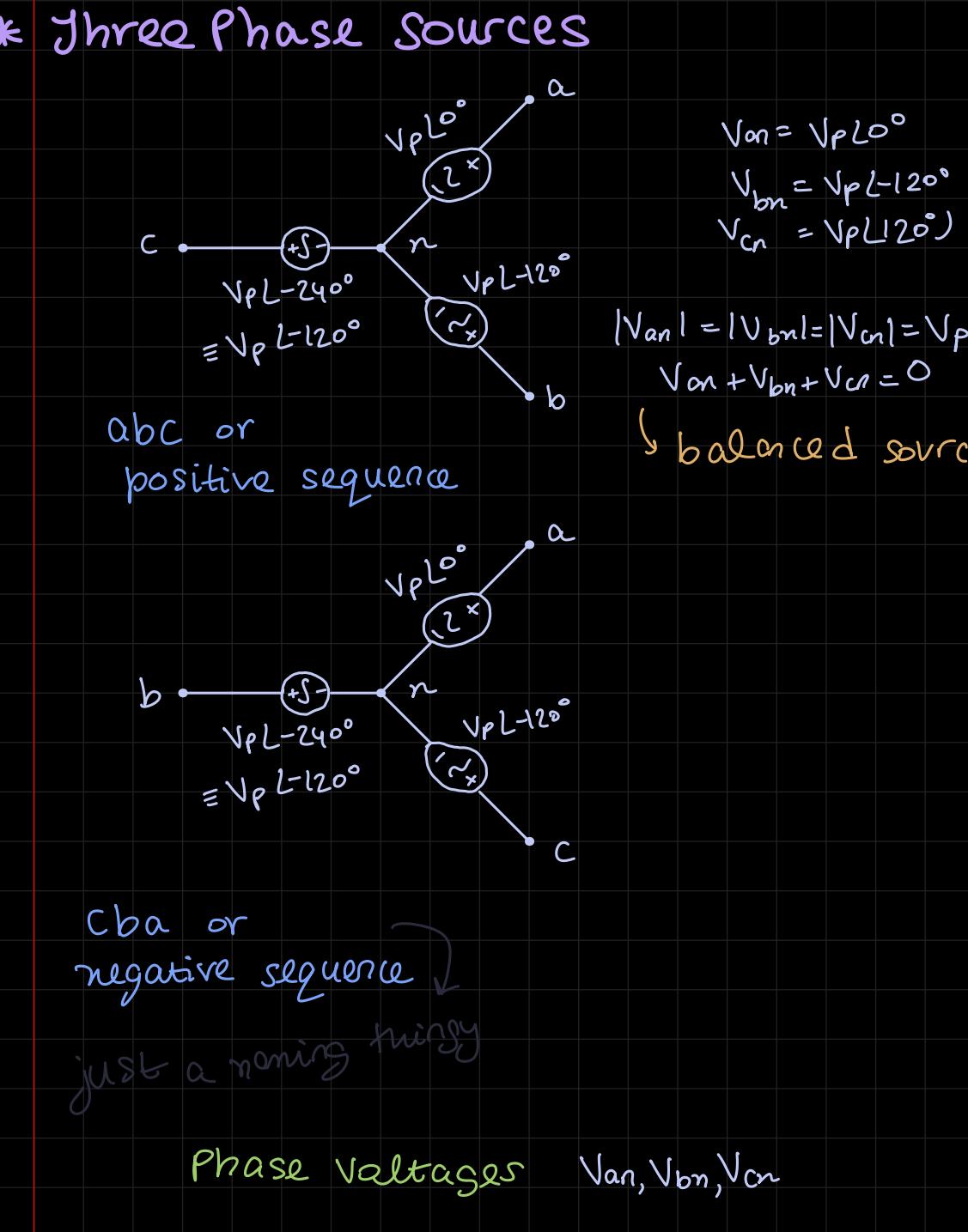

Note that this is still a balanced load, so we can remove NN since $I_{NN} = 0$

using complex power

$S = \text{complex power of total load}$

$$S = \frac{1}{2} \sqrt{I} I^*$$

$$PF = \frac{\operatorname{Re}\{S\}}{|S|} = 1 \Rightarrow \operatorname{Re}\{S\} = |S|$$

so, $\operatorname{Im}\{S\} = 0$ here

$$S = \frac{1}{2} V_{an} I_{an}^* + \frac{1}{2} V_{nb} I_{nb}^* + \frac{1}{2} V_{ab} I_{ab}^*$$

$$\Rightarrow \frac{1}{2} V_{an} \left(\frac{V_{an}}{Z_p} \right)^* + \frac{1}{2} V_{nb} \left(\frac{V_{nb}}{Z_p} \right)^* + \frac{1}{2} V_{ab} \left(\frac{V_{ab}}{Z_p} \right)^*$$

$$\Rightarrow \frac{1}{2} \frac{|V_{an}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{nb}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{ab}|^2}{|Z_p|^2} Z_p$$

$$\Rightarrow \frac{115^2}{10^4} (10 + j^2) + \frac{1}{2} \left(\frac{230^2}{(j\omega C)^2} \right) \left(\frac{-j}{\omega C} \right) = \frac{1}{j\omega C} = \frac{1}{j\omega} \times \frac{-1}{j\omega C}$$


$$\Rightarrow 115^2 \left(\frac{10 + j^2}{10^4} - \frac{-j}{\omega C} \right)$$

$$\Rightarrow 2 \times 115^2 \left(\frac{j}{10^4} - \frac{1}{\omega C} \right)$$

$$\Rightarrow 2 \times 115^2 \left(\frac{1}{10^4} - \frac{1}{\omega C} \right) = 0$$

$$\frac{1}{10^4} - \frac{1}{\omega C} = 0 \Rightarrow C = \frac{1}{10400 \pi} = 30.6 \mu F$$


* Three Phase Sources

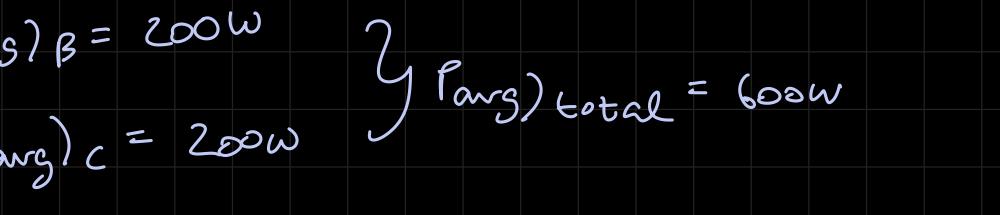

balanced source

balanced source

→ Y-Y connection

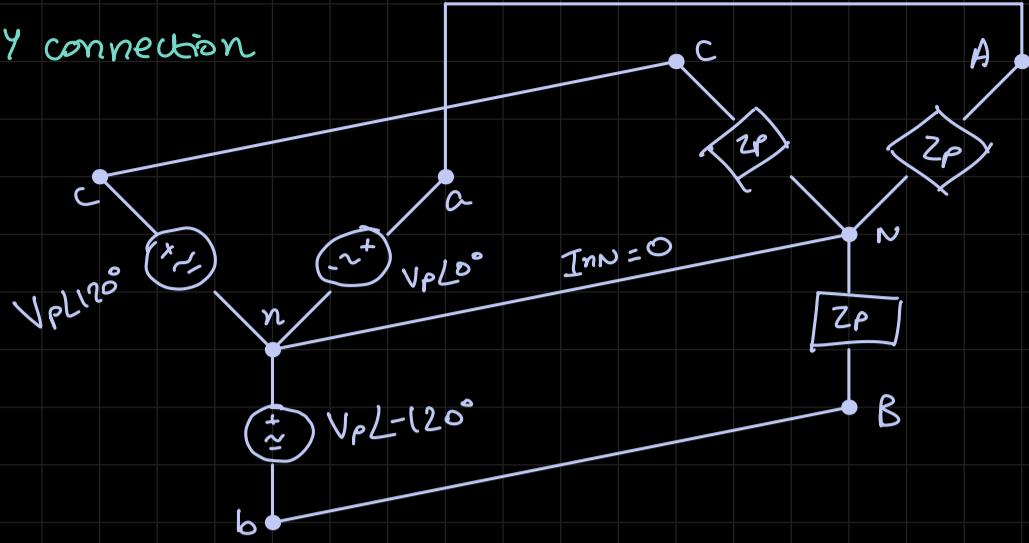

balanced load: all load are same

balanced src: all src magnitudes are equal

line: lines connecting load to src

aa cC

bb nn

Phase Voltages: V_{AN} = V_{aN}, V_{BN} = V_{bN}, V_{CN} = V_{cN}line voltages: V_{ab}, V_{bc}, V_{ca}line currents: I_{aA}, I_{bB}, I_{cC}phase currents: I_{AN} = I_{aA}, I_{BN} = I_{bB}, I_{CN} = I_{cC}

$$V_{an} = V_p L 0^\circ$$

$$V_{bn} = V_p L -120^\circ$$


$$V_{cn} = V_p L -240^\circ$$

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_p L 30^\circ$$

$$V_{bc} = \sqrt{3} V_p L -90^\circ$$

$$V_{ca} = \sqrt{3} V_p L -210^\circ$$

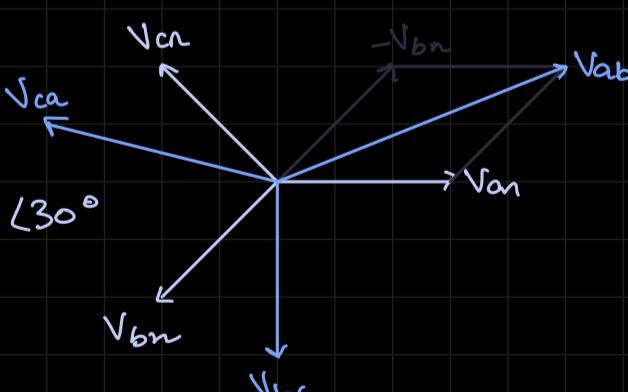

line voltages

$$V_{\text{line}} = \sqrt{3} V_{\text{phase}}$$

line currents = phase currents

* Total Instantaneous Power

$$P_{\text{total}}(t) = P_A(t) + P_B(t) + P_C(t)$$

Classes & Attribs

interface (entity)

~~ ~~~

Bird

↓

dmg
(chits)

Pig

↓

health
(units)

User

↓

save
stage

level mg

blocks

pigs

type

→ max-score

→ no. of pigs

center point

Game

update score

wood

glass

steel

Score

level-status

Slingshot

angle

stretch

↙

b°



$$v = 10 \text{ m/s}$$

0°

①

S, P

$$\sqrt{v \cos \theta, v \sin \theta}$$

per second


/ rate

-l → 0


* TODO: revise lecture 11 (missed due to SNS quiz)

* Lecture 12:

eg 3

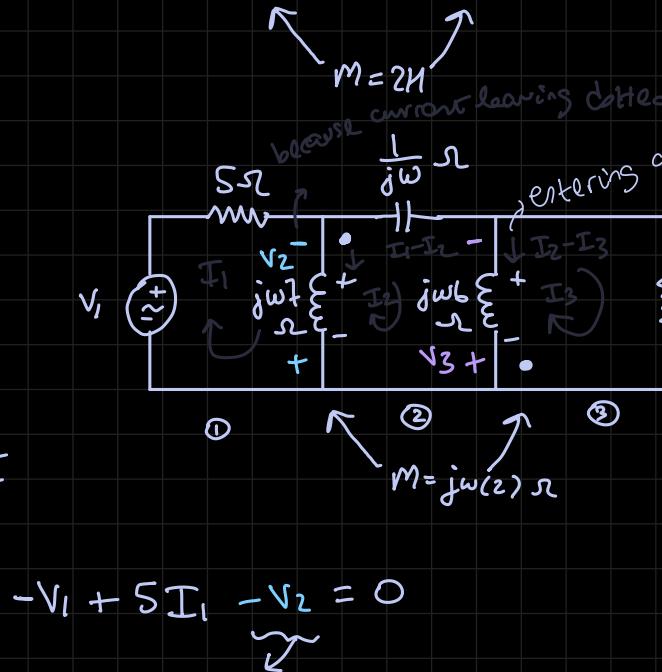

ans 3

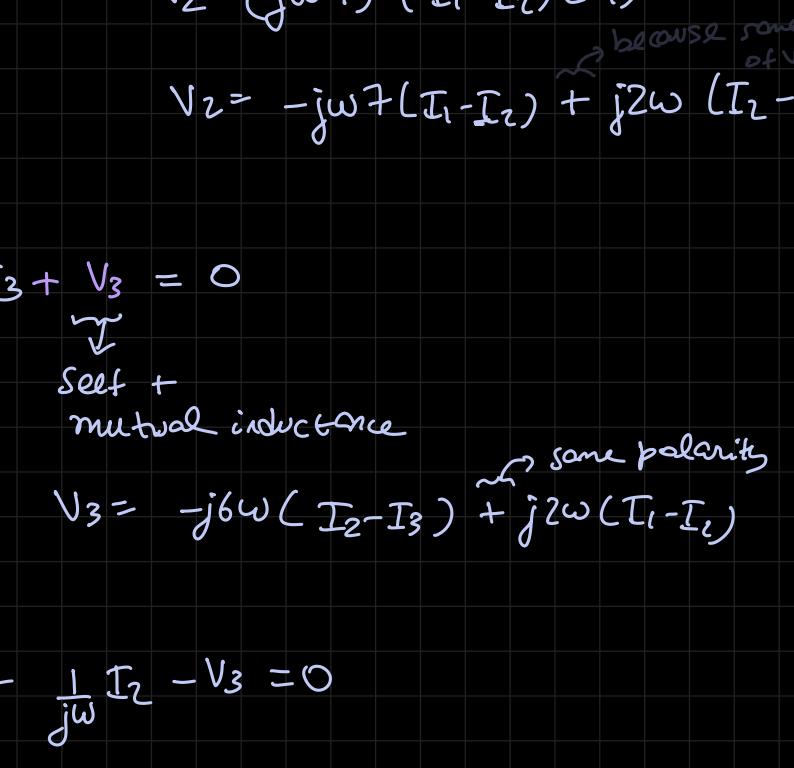

$$\textcircled{1} \quad -V_1 + 5I_1 - V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)(-1)$$

$$V_2 = -j\omega 7(I_1 - I_2) + j2\omega(I_2 - I_3)$$

$$\textcircled{3} \quad 3I_3 + V_3 = 0$$

\downarrow
Self + mutual inductance


$$V_3 = -j6\omega(I_2 - I_3) + j2\omega(I_1 - I_2)$$

$$\textcircled{2} \quad V_2 + \frac{1}{j\omega} I_2 - V_3 = 0$$

$$-j\omega 7(I_1 - I_2) + j2\omega(I_2 - I_3) + j6\omega(I_2 - I_3) - j^2\omega(I_1 - I_2) + \frac{I_2}{j\omega} = 0$$

$$I_1(-j5\omega) + I_2(j17\omega) + I_3(-j8\omega) + \frac{I_2}{j\omega} = 0$$

eg 3

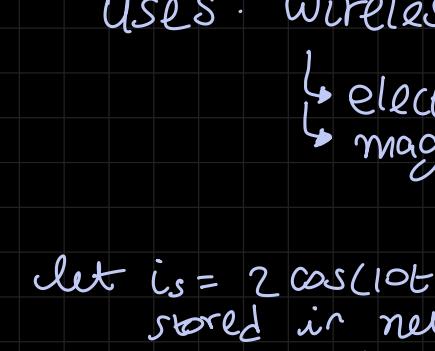


$$-V_1 + 5I_1 + V_2 = 0$$

$$V_2 = (j\omega 7)(I_1 - I_2)$$

\downarrow
we don't need to care about this sign if we use V_2, V_3 method.

* ENERGY STORED
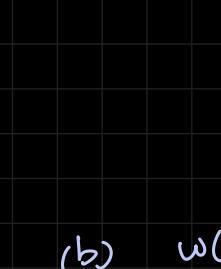
$$w(t) = \frac{1}{2} L(i(t))^2 \quad \text{for only one inductor}$$



$$w(t) = \frac{1}{2} L_1(i_1)^2 + \frac{1}{2} L_2(i_2)^2 \pm M_i_1(t)i_2(t)$$

\downarrow [+] sign with occur iff both i_1 and i_2 are entering either dotted or undotted

\downarrow [-] sign iff both enter different (dotted/undotted)

- Coupling coefficient (K)

$$M \leq \sqrt{L_1 L_2}$$

$$K = \frac{M}{\sqrt{L_1 L_2}} \Rightarrow 0 \leq K \leq 1$$

$[K \rightarrow 0]$

poor coupling or no coupling

$[K \rightarrow 1]$

Strong coupling (very close to each other)

$\Rightarrow K$ depends on: distance ; size ; ferrite b/w coils of coils core

$$y \propto \frac{1}{x}$$

$$y \propto x$$

$$y \propto x$$

uses: wireless power transfer \nwarrow inductively coupled

\nwarrow electric vehicle charging
 \nwarrow magsafe charging

eg 3 let $i_s = 2 \cos(10t)$ A. find total energy stored in network at $t=0$ if $K=0.6$ and

- (a) if x_y terminals are open circuited
- (b) x_y are short circuited

$$\text{Ans 3} \quad w(t) = \frac{1}{2} L_1(i_1)^2 + \frac{1}{2} L_2(i_2)^2 \pm M i_1(t) i_2(t)$$

$$j\omega L_1 = j4 \Rightarrow L_1 = \frac{4}{\omega} = 0.4 \text{ H}$$

- (a) if x_y are open: $i_2 = 0$

$$\therefore w(t) = \frac{1}{2} \times 0.4 \times (2 \cos 10t)^2$$

$$w(t) = 0.8 \cos^2(10t)$$

$$\text{at } t=0 \Rightarrow w(t) = 0.8 \text{ J}$$

$$(b) \quad w(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$


$$i_1 = i_s = 2 \cos 10^\circ$$

$$i_2 = \frac{v_x}{j2s} \quad \text{and} \quad v_x = -j\omega M i_1$$

$$i_2 = -0.6 \frac{(2 \cos 10^\circ)}{2.5} = -0.48 \text{ A}$$

$$w(t=0) = \frac{1}{2} (0.4) (2^2) + \frac{1}{2} (-0.48)^2$$

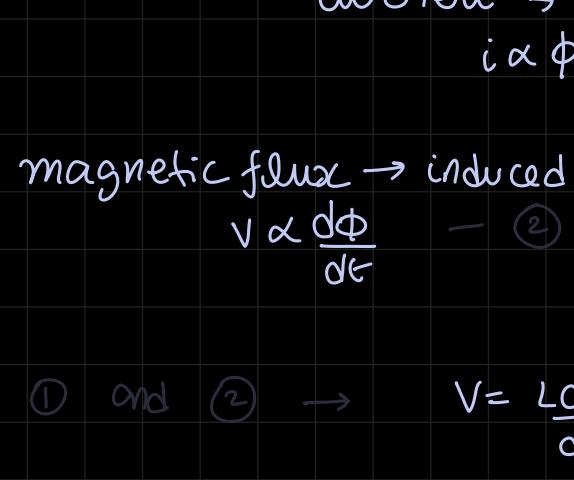• MODULE 5: Magnetically coupled circuits



current \rightarrow magnetic flux
 $i \propto \phi$ — ①

magnetic flux \rightarrow induced voltage



$$V \propto \frac{d\phi}{dt} \quad \text{— ②}$$

$$\textcircled{1} \text{ and } \textcircled{2} \rightarrow V = L \frac{di}{dt}$$

for DC source: current is constant

hence $\frac{di}{dt} = 0$ and $\therefore V = 0$
 (induced)

• Mutual Inductance

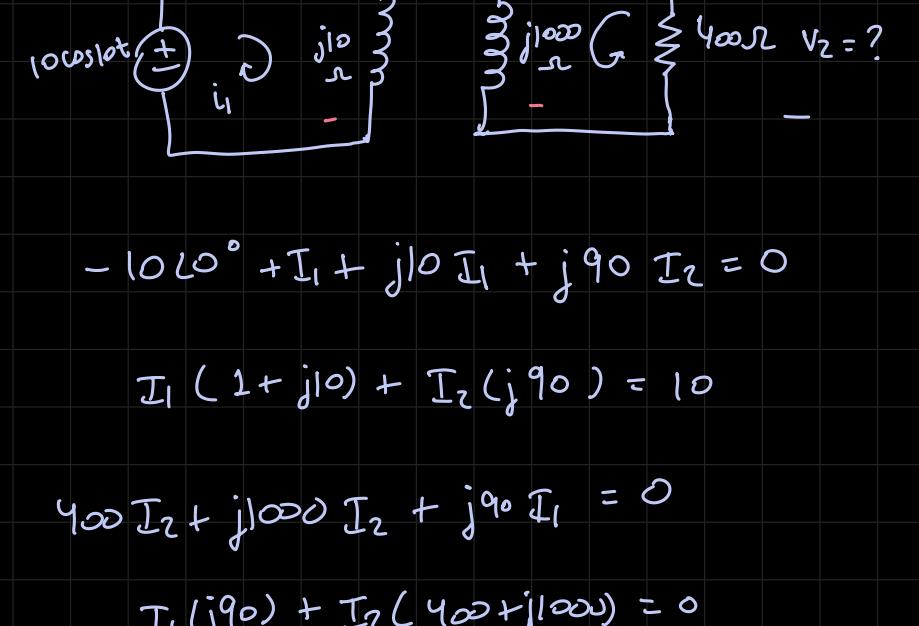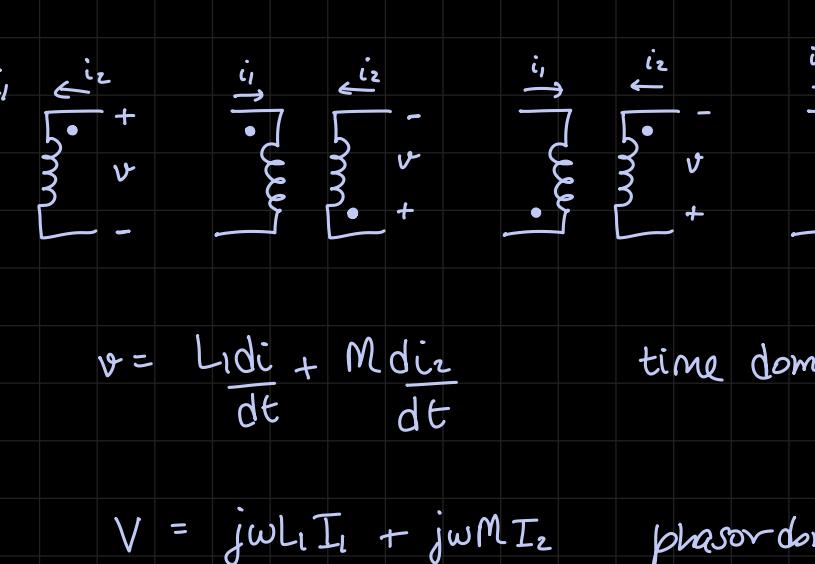

* Additive/Subtractive Property {two different coils?}

$$i_1 \text{ (clockwise)} \quad i_2 \text{ (counter-clockwise)} \quad v_2 = L \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$i_1 \text{ (clockwise)} \quad i_2 \text{ (clockwise)} \quad v_2 = L \frac{di_2}{dt} - M \frac{di_1}{dt}$$

• Dotted Notation

Current entering + terminal means
 +ve voltage reference at -

$$v = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \text{time domain}$$

$$V = j\omega L_1 I_1 + j\omega M I_2 \quad \text{phasor domain}$$

$$\text{eg: } \begin{array}{c} 1 \Omega \\ \text{10cos}(\omega t) \end{array} \quad \begin{array}{c} i_1 \\ \text{+} \\ \text{-} \end{array} \quad \begin{array}{c} i_2 \\ \text{+} \\ \text{-} \end{array} \quad \begin{array}{c} M=j90 \\ \text{+} \\ \text{-} \end{array} \quad \begin{array}{c} 4 \Omega \\ \text{+} \\ \text{-} \end{array} \quad \begin{array}{c} i_2 \\ \text{+} \\ \text{-} \end{array} \quad \begin{array}{c} 4 \Omega \\ \text{+} \\ \text{-} \end{array} \quad \begin{array}{c} i_2 \\ \text{+} \\ \text{-} \end{array}$$

$$\textcircled{1} \quad -10\cos(\omega t) + I_1 + j10I_1 + j90I_2 = 0$$

$$I_1(1+j10) + I_2(j90) = 10$$

$$\textcircled{2} \quad 4\Omega I_2 + j1000I_2 + j90I_1 = 0$$

$$I_1(j90) + I_2(4\Omega + j1000) = 0$$

CURRENTS:

$$\Delta = \begin{vmatrix} 1+j10 & j90 \\ j90 & 4\Omega + j1000 \end{vmatrix}$$

$$= (1+j10)(4\Omega + j1000) + 90000$$

$$= 400 + j1000 + j4000 - 10.000 + 90.000$$

$$= j5000 + 80,400 = 80555 \angle 3.55^\circ$$

$$\Delta_1 = \begin{vmatrix} j1000 & 10 \\ 4\Omega + j1000 & 0 \end{vmatrix} = -4000 - j10.000 = 10770 \angle -111.8^\circ$$

$$\Delta_2 = \begin{vmatrix} 10 & 1+j10 \\ 0 & j90 \end{vmatrix} = j900 = 900 \angle 90^\circ$$

$$I_1 = \frac{\Delta}{\Delta_1} = -3.2 + 6.75j$$

full current part

wrong because I took $M = L_2 = j1000$ above

$$\Delta_0 = \begin{vmatrix} 1+j10 & j90 \\ j90 & 4\Omega + j1000 \end{vmatrix}$$

$$= 400 + j1000 + j4000 - 10.000 + 8100$$

$$= j5000 - 1500 = 5220 \angle 106.69^\circ$$

ENERGY STORED IN THE CIRCUIT

$$w(t) = \frac{1}{2} L_1 i_1(t)^2 + \frac{1}{2} L_2 i_2(t)^2$$

$$\pm M i_1(t) i_2(t)$$

+: current entering same: • and • OR - and -

-: current entering different: • and - OR - and •


COUPLING COEFFICIENT (k)

$$k = \frac{M}{\sqrt{L_1 L_2}} \quad ; \quad \text{note } \Rightarrow M \leq \sqrt{L_1 L_2}$$

$$\therefore 0 \leq k \leq 1$$

• LINEAR TRANSFORMER

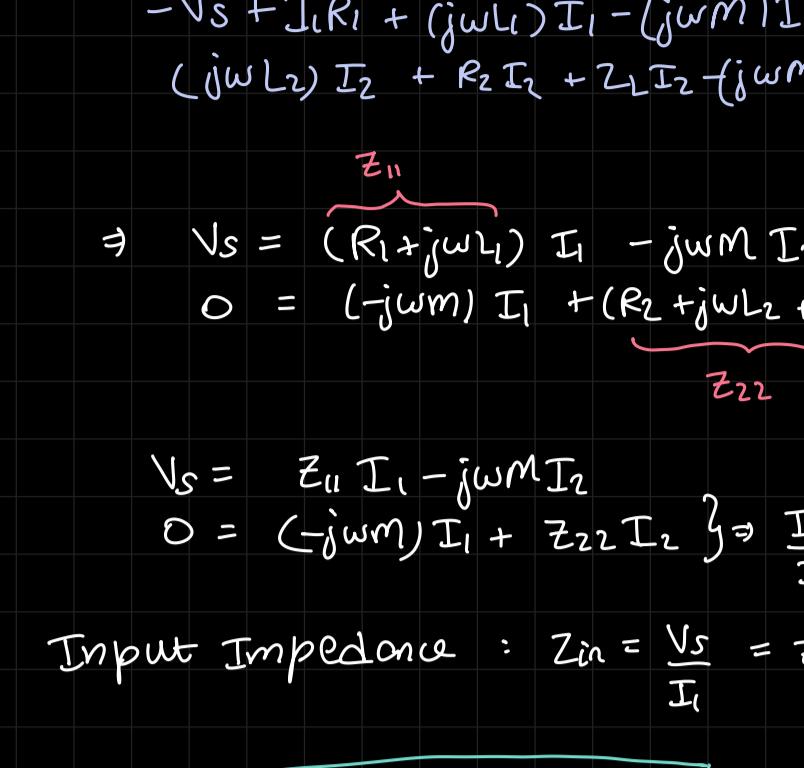When $V \propto \frac{di}{dt} \Rightarrow$ no magnetic core



$$-Vs + I_1 R_1 + (j\omega L_1) I_1 - (j\omega M) I_2 = 0$$

$$(j\omega L_2) I_2 + R_2 I_2 + Z_L I_2 - (j\omega M) I_1 = 0$$

$$\Rightarrow V_s = (R_1 + j\omega L_1) I_1 - j\omega M I_2$$

$$0 = (-j\omega M) I_1 + (R_2 + j\omega L_2 + Z_L) I_2$$

$$V_s = Z_{11} I_1 - j\omega M I_2$$

$$0 = (-j\omega M) I_1 + Z_{22} I_2 \Rightarrow \frac{I_2}{I_1} = \frac{j\omega M}{Z_{22}}$$

$$\text{Input Impedance : } Z_{in} = \frac{V_s}{I_1} = Z_{11} - j\omega M \frac{I_2}{I_1}$$

$$Z_{in} = Z_{11} + \underbrace{\frac{\omega^2 M^2}{Z_{22}}}_{\text{Reflective Impedance}}$$


where

$$Z_{11} = R_1 + j\omega L_1, \quad Z_{22} = R_2 + j\omega L_2 + Z_L$$

- if $K = \frac{M}{\sqrt{L_1 L_2}} = 0 \Rightarrow Z_{in} = Z_{11}$ i.e. no coupling

• T EQUIVALENT NETWORK

(no mutual coupling)

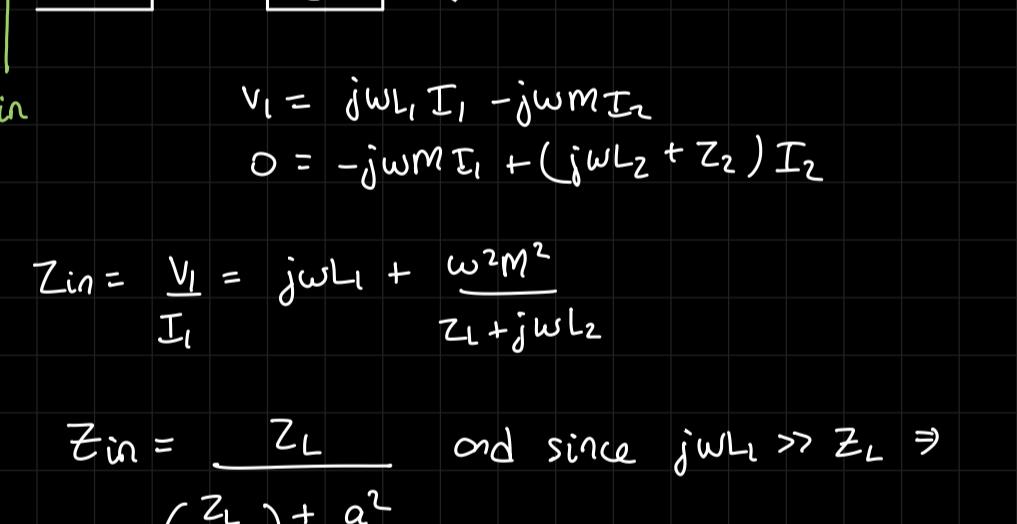

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

Note: no mutual coupling since there is no arrow for it

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$V_1 = (L_1 - M) \frac{di_1}{dt} + M \left(\frac{di_1}{dt} + \frac{di_2}{dt} \right)$$

Note: if dots are on opposite sides, replace M with -M

$$V_1 = \frac{L_1 di_1}{dt} + \frac{M di_2}{dt}$$

$$V_2 = \frac{L_2 di_2}{dt} + \frac{M di_1}{dt}$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$


$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

* CTD Practice

① Quiz: 1 (set A)

mesh analysis: current
nodal analysis: voltage

• midsem : 2023

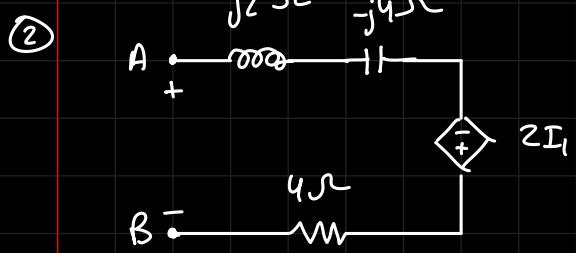

mesh analysis voltage:

- Phasor vs Assumptions:
zero initial condition

time domain

=

R

L
C

eg 3

$$V_{in}(t) = 5e^{-2t} \cos(3t + 45^\circ)$$

$$S = \sigma + j\omega$$

$$S = -2 + j3$$

$$V_{in} = 5e^{j45^\circ} = 5 \angle 45^\circ \text{ V}$$

Voltage divider
for finding V_{out}

$$V_{out} = \frac{5 \angle 45^\circ \times (0.02)(-2+j3) \times \frac{1}{(0.01)(-2+j3)}}{(10 + (0.02)(-2+j3)) + \frac{1}{(0.01)(-2+j3)}}$$

$$= 5.86 \angle -24.4^\circ$$

$$V_{out}(t) = \operatorname{Re} \{ 5.86 e^{j(-24.4)} e^{(\sigma + j\omega)t} \}$$

$$= 5.86 e^{-2t} \cos(3t - 24.4) \text{ V}$$

for zero initial condition, we can use phasors
for $e^{\sigma t} \cos(\omega t + \theta)$

Can we still use phasors for $\delta(t)$, $u(t)$, $\sin(\omega t)$
 $u(t)$
NO

but Laplace transform works ✓

$$\mathcal{L}\{f(t)\} = \int_0^\infty e^{-st} f(t) dt \Rightarrow F(s)$$

Variable ↴

$$\delta(t)$$

$$1$$

$$f_1(t) \pm f_2(t)$$

$$F_1(t) \pm F_2(t)$$

$$u(t)$$

$$1/s$$

$$kf(t)$$

$$kF(t)$$

$$tu(t)$$

$$1/s^2$$

$$\frac{d}{dt} f(t)$$

$$sF(s) - f(0^+)$$

$$\begin{aligned}
 &= \frac{1}{z_j} \mathcal{L}\{e^{j\omega t}\} - \mathcal{L}\{e^{-j\omega t}\} \\
 &= \frac{1}{2i} \left[\left(\frac{1}{s-j\omega} \right) - \left(\frac{1}{s+j\omega} \right) \right] \\
 &= \frac{1}{2i} \frac{2j\omega}{s^2 + \omega^2} = \frac{\omega}{s^2 + \omega^2}
 \end{aligned}$$

$$z_j \quad s^2 + \omega^2 \quad s^2 + \omega^2$$

Complex

$$f(0^+) = \lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \frac{4e^{-2s}(s+50)}{s}$$

use L'Hopital's rule

$$\Rightarrow f(0^+) = \lim_{s \rightarrow \infty} \frac{4}{2e^{2s}} = \frac{1}{\infty} \text{ form} = \underline{\underline{0}}$$

final value : $f(\infty) = \lim_{s \rightarrow 0} 4e^{-2s}(s+50)$

$$= 4(50) = \underline{\underline{200}}$$

$$\Rightarrow f(0^+) = \lim_{s \rightarrow \infty} sF(s) = \frac{5s^2 + 10}{2s^2 + 6s + 10}$$

$$f(\infty) = \lim_{s \rightarrow 0} \frac{s^2 + s}{s^2 + 3s + 5} = 1$$

Complex : find LCT of $F(s) = \frac{s^2 + 6}{s^2 + 7}$

$$f(t) = \delta(t) - \frac{1}{\sqrt{7}} \sin(\sqrt{7}t) u(t)$$

∴ find ILT of $\frac{s+2}{s^2+2s+4}$

$$\Rightarrow \frac{(s+1) + 1}{(s+1)^2 + (\sqrt{3})^2} \Rightarrow \frac{s+1}{(s+1)^2 + (\sqrt{3})^2} + \frac{1}{s^2+s+5}$$

\Downarrow

$$\cos(\sqrt{3}t) u(t)$$

impedances in S-domain

A circuit diagram showing a voltage source $V(s)$ connected in series with a resistor R and an inductor $I(s)$. The inductor is represented by a coil symbol.

$$V(s) = L(sI(s) - i(0^-))$$

$$i(t) = C \frac{dv}{dt}$$

$i(x) \rightarrow$

$$I(s) = C [sV(s) - v(0^-)]$$


$$I(s) = CsV(s) - Cv(0^-)$$

$$V(s) = \frac{1}{s} I(s) + \frac{v(0^-)}{s}$$


* Lecture 1b {missed}

Transfer function :

lets consider :

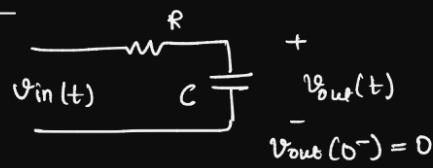

Freq. domain

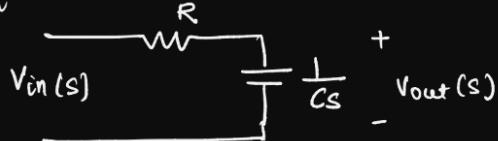

$$V_{out}(s) = \frac{1/Cs}{R + 1/Cs} V_{in}(s)$$

$$\Rightarrow \underbrace{\frac{V_{out}(s)}{V_{in}(s)}}_{\text{transfer function. } H(s)} = \frac{1}{sRC+1}$$

transfer function. $H(s)$

$$V_{out}(t) = \mathcal{L}^{-1} \left\{ V_{out}(s) \right\} = \mathcal{L}^{-1} \left\{ \underbrace{H(s)}_{\text{defines the system.}} \cdot V_{in}(s) \right\}$$

• Stability

Stable: bounded o/p for bounded i/p

Unstable: unbounded o/p for bounded i/p

marginally stable: oscillating OR bounded offset

let: $e^{\sigma t} \cos(\omega_0 t) u(t)$ ① $\sigma > 0$: unstable② $\sigma < 0$: stable③ $\sigma = 0$: marginally stable

* Stability Criterion

System transfer fn $H(s) = k \frac{(s-z_1)(s-z_2)(s-z_3) \dots (s-z_n)}{(s-p_1)(s-p_2)(s-p_3) \dots (s-p_n)}$

- system is stable if

All poles of $SH(s)$ lie on LHS of complex plane

- Marginally stable if

1st order pole at $s=0$ OR 1st order complex conjugate pole pair


- Unstable system if

All other cases

→ 1st pole on RHS OR

→ 2nd or higher order pole at $s=0$ OR












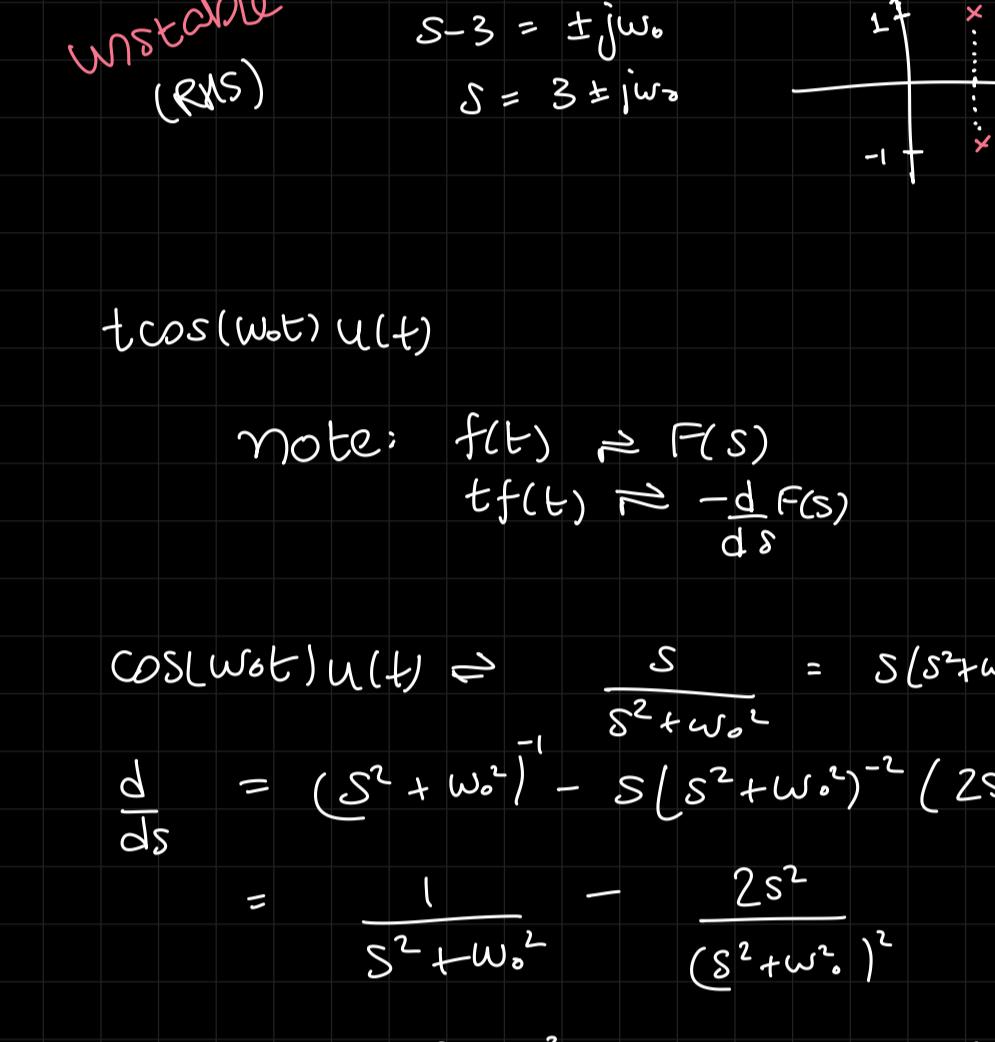
→ 2nd or higher order conjugate pole pair at jw-axis



at jω axis:

could be unstable

or marginally stable

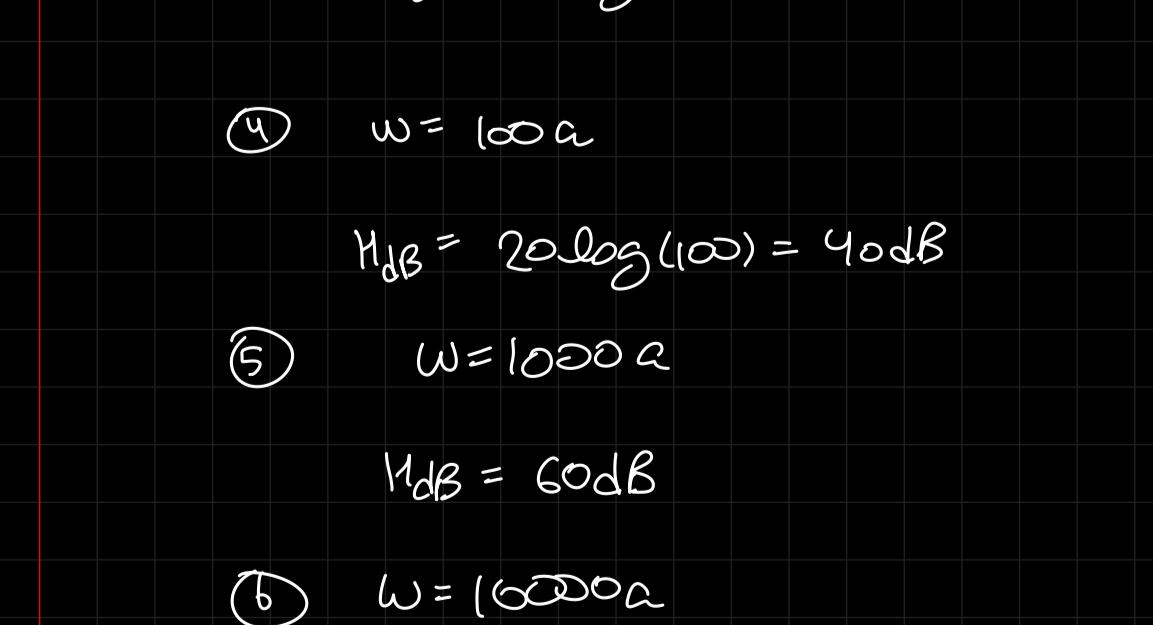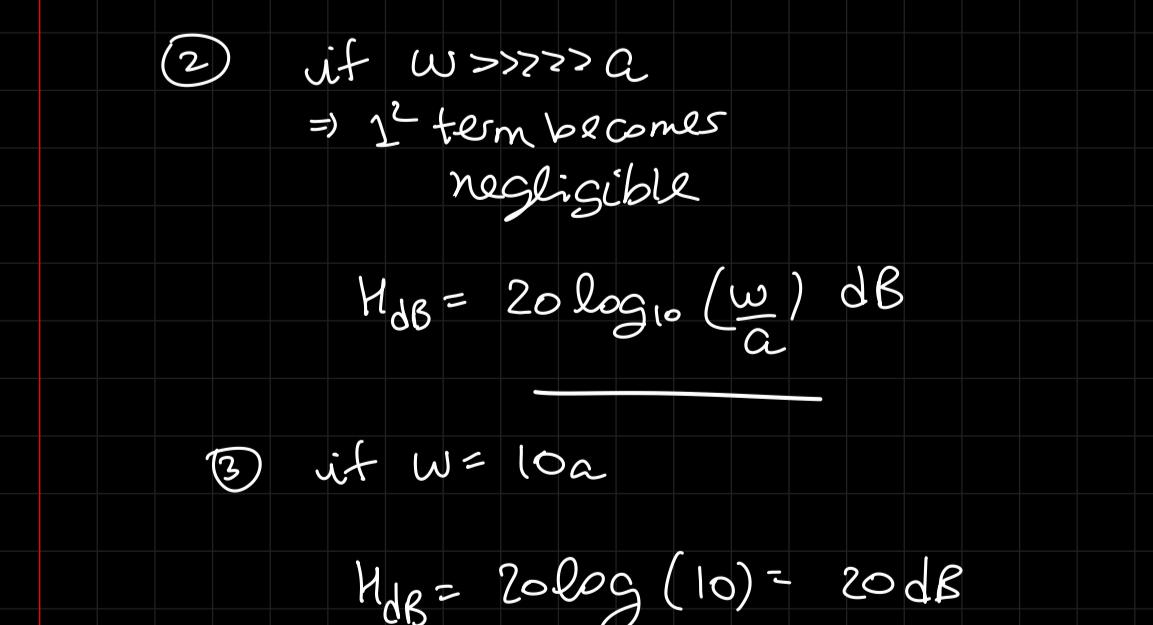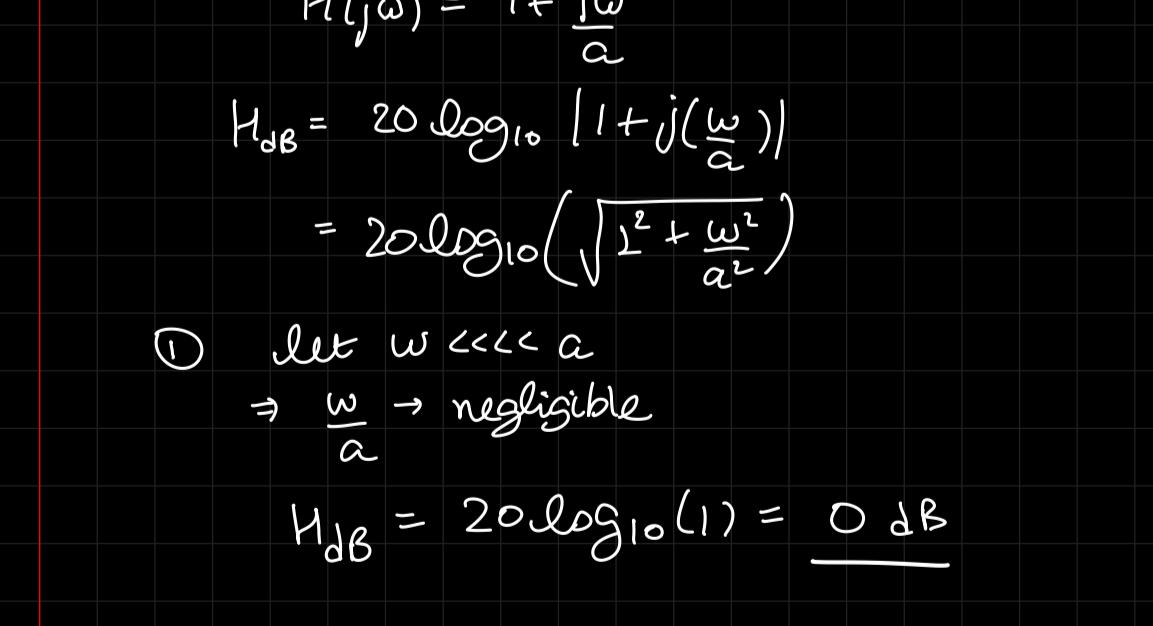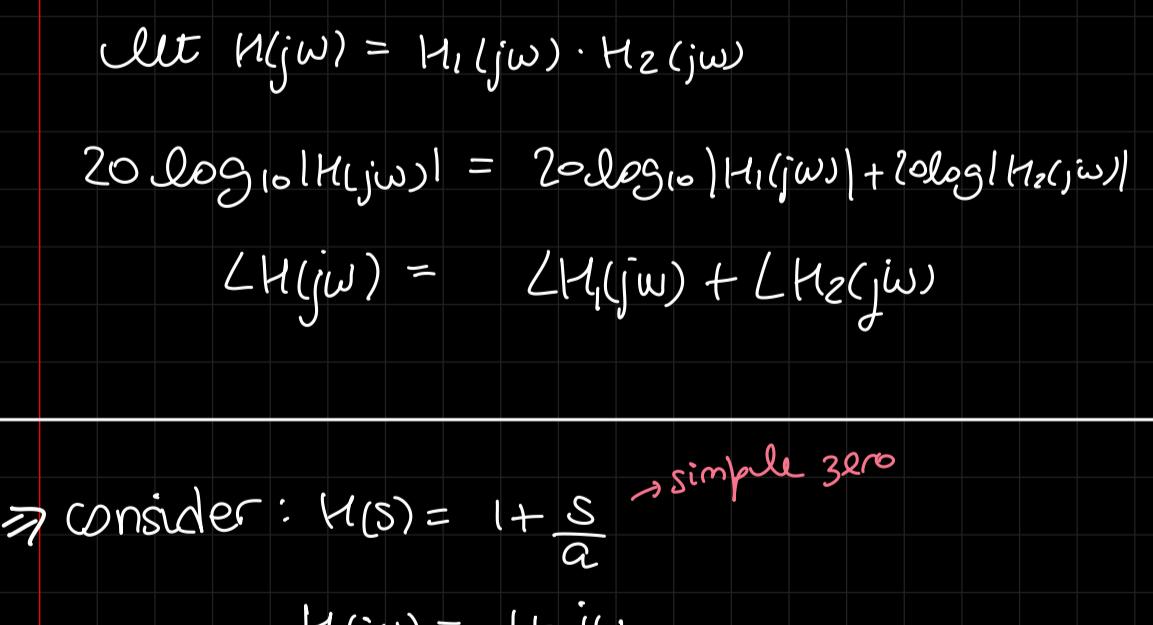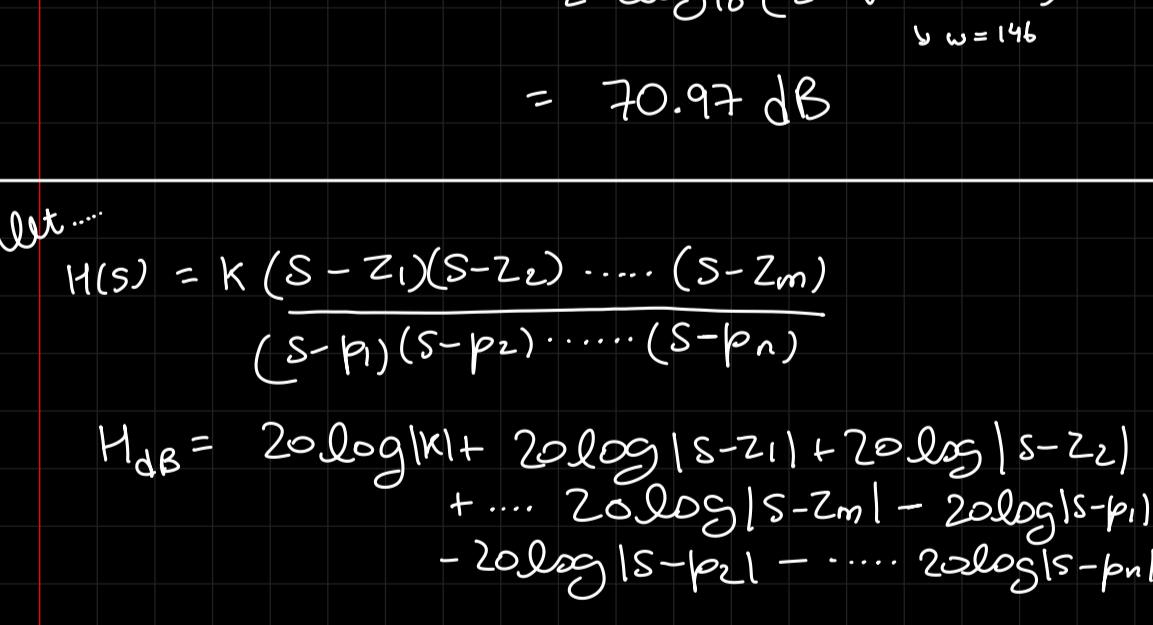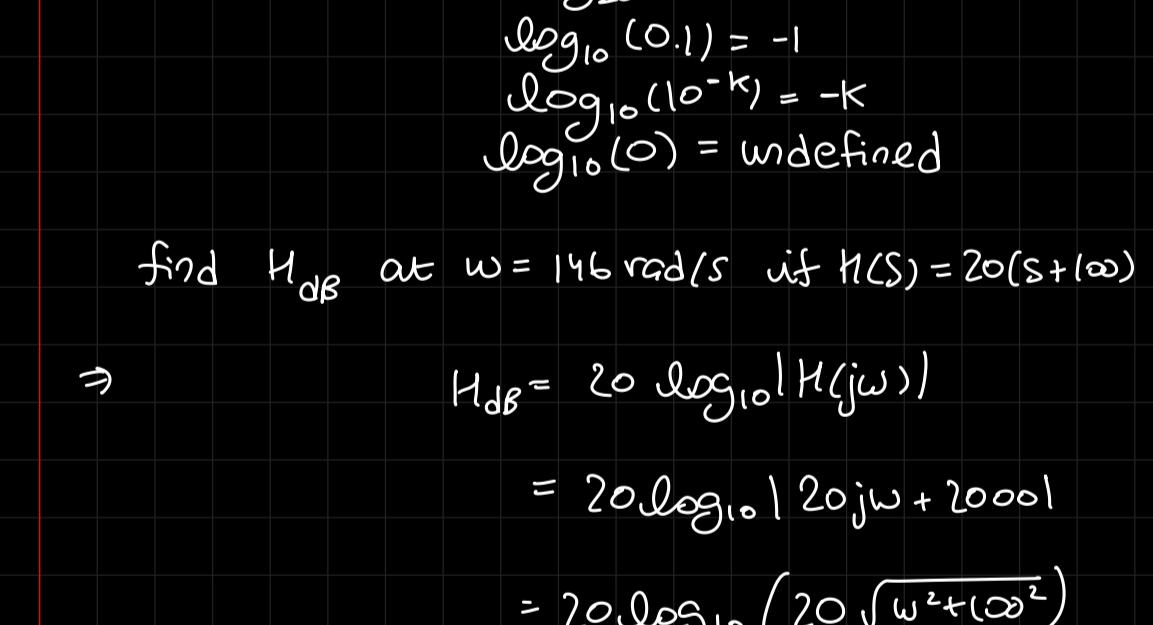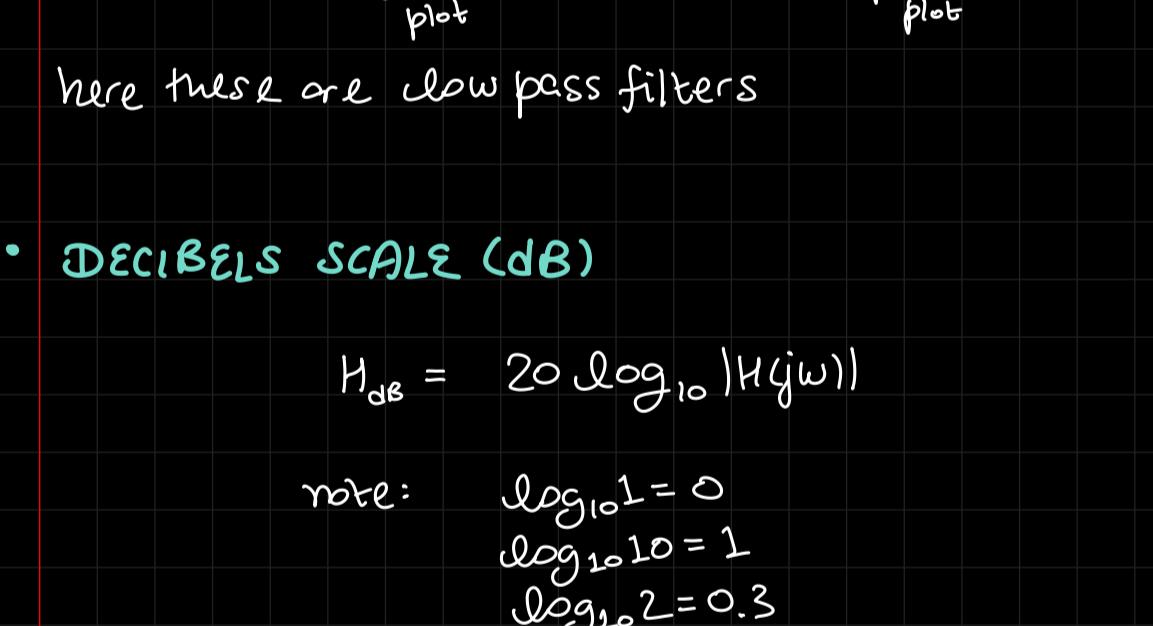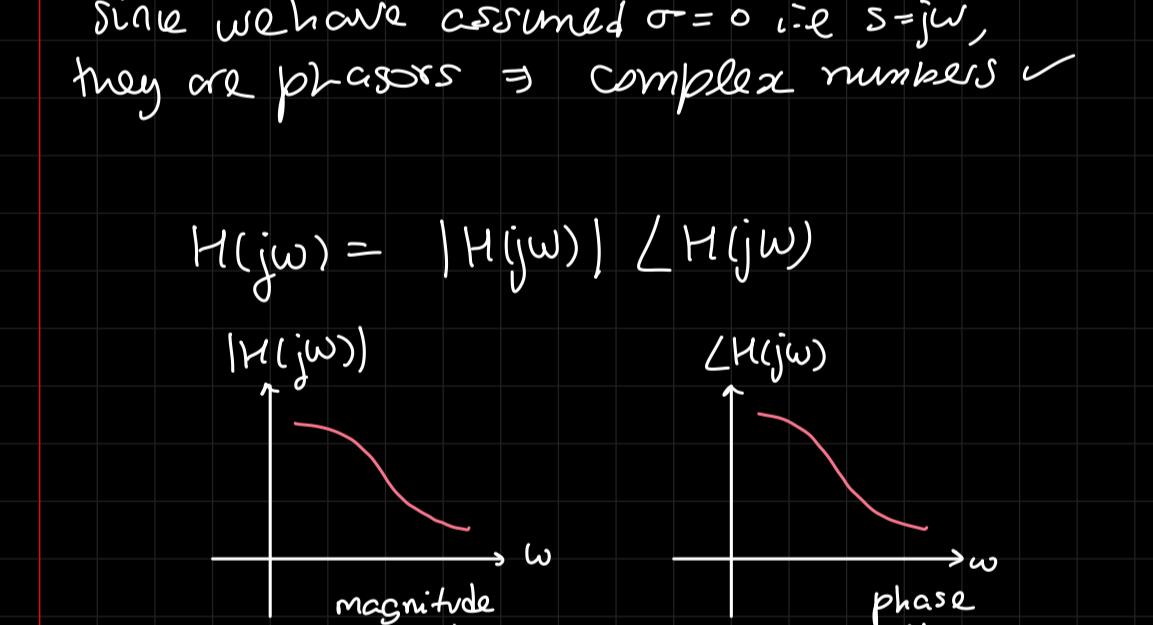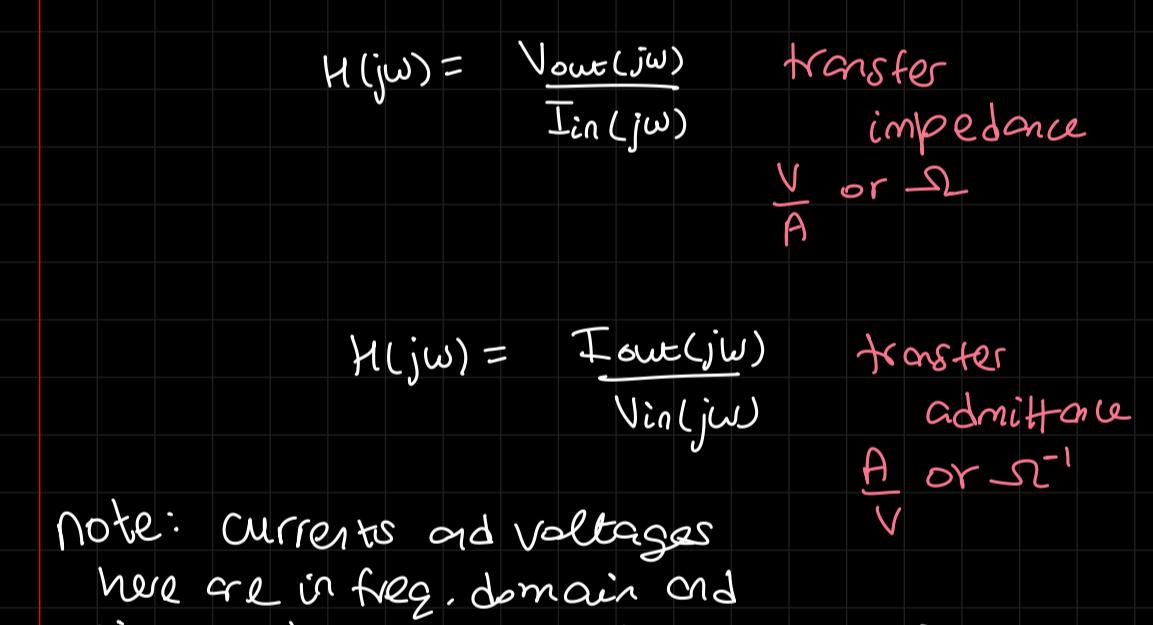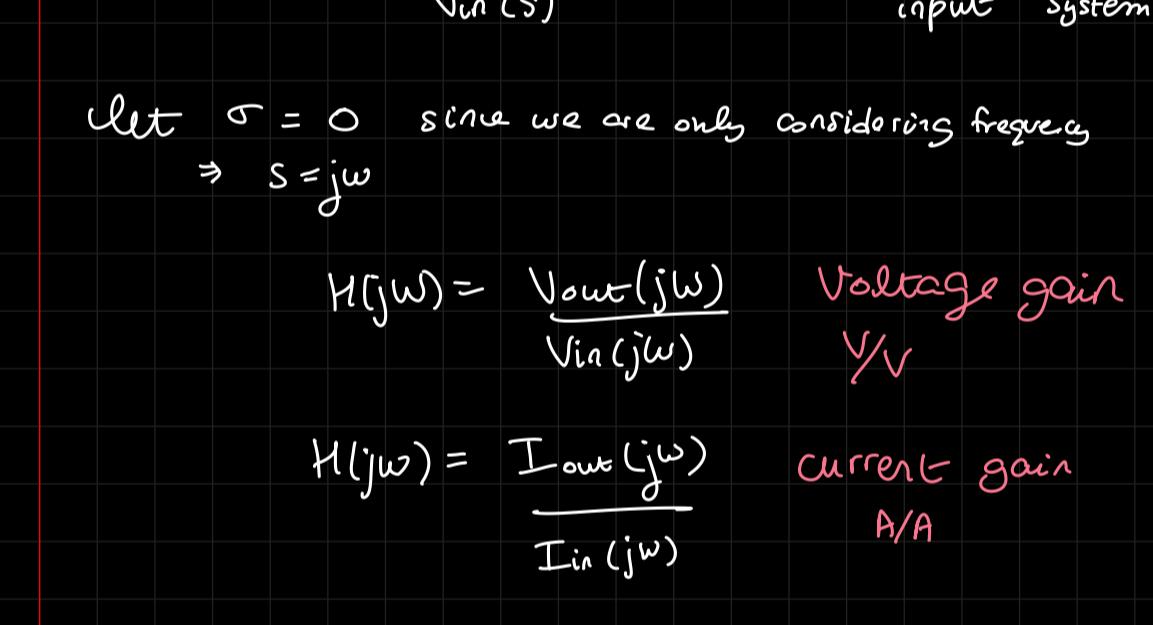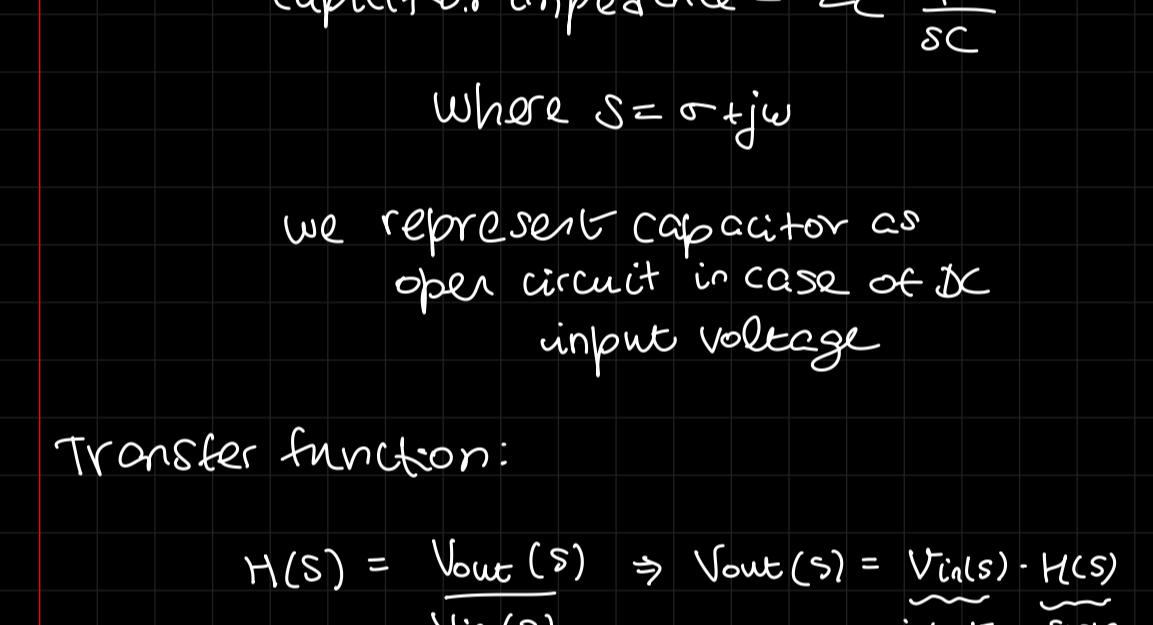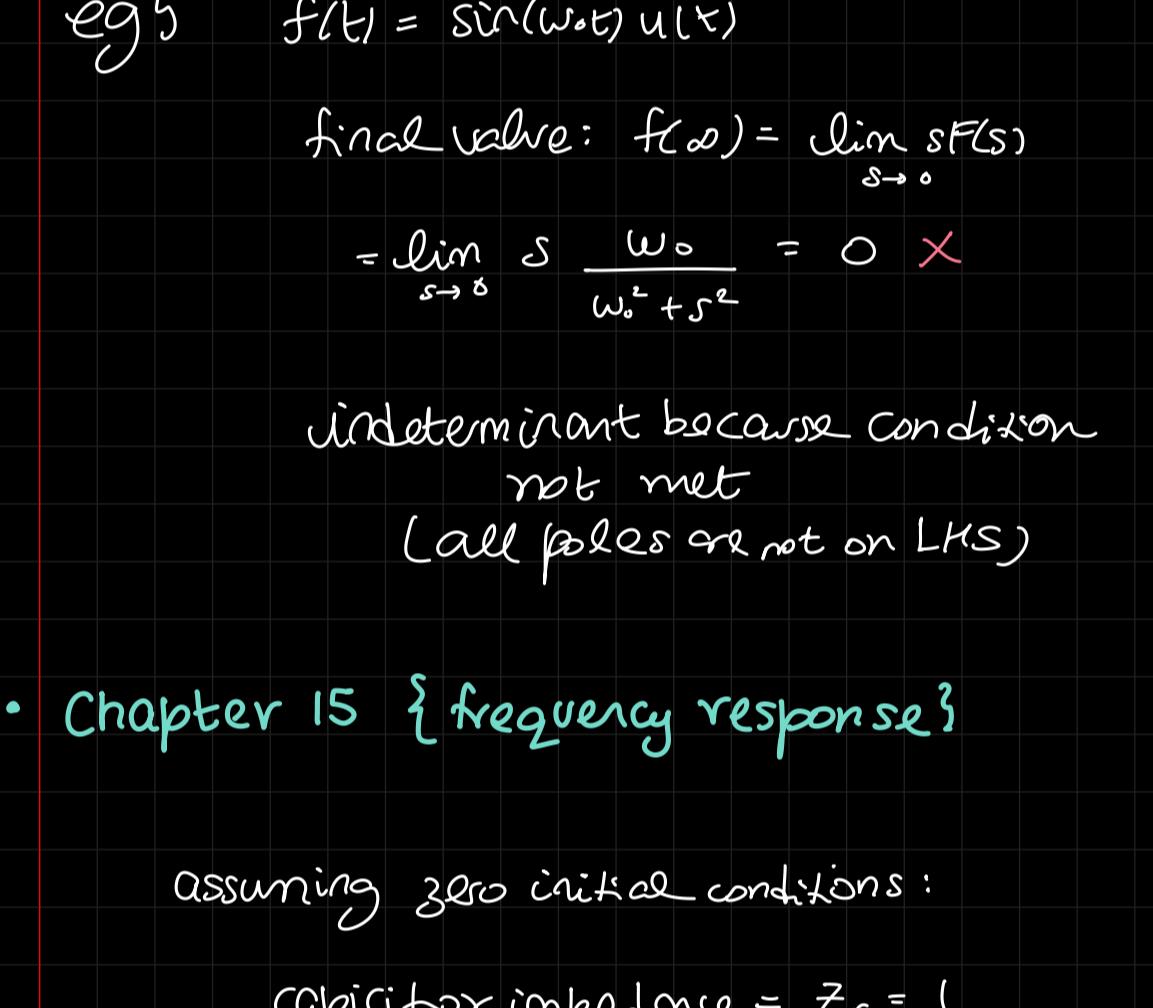

$$\text{cos}(\omega_0 t) u(t) \Rightarrow \frac{s}{s^2 + \omega_0^2} = s(s^2 + \omega_0^2)^{-1}$$

$$\frac{d}{ds} = (s^2 + \omega_0^2)^{-1} - s(s^2 + \omega_0^2)^{-2} (2s)$$

$$= \frac{1}{s^2 + \omega_0^2} - \frac{2s^2}{(s^2 + \omega_0^2)^2}$$

$$= \frac{s^2 + \omega_0^2 - 2s^2}{(s^2 + \omega_0^2)^2} = \frac{\omega_0^2 - s^2}{(s^2 + \omega_0^2)^2}$$

$$H(j\omega) = \frac{s = \pm j\omega_0}{(s^2 + \omega_0^2)^2} \quad (\text{2nd order})$$

$$\text{note: } \log_{10} 1 = 0$$

$$\log_{10} 10 = 1$$

$$\log_{10} 2 = 0.3$$

$$\log_{10}(0.1) = -1$$

$$\log_{10}(10^{-k}) = -k$$

$$\log_{10}(0) = \text{undefined}$$

$$\text{find } H_{dB} \text{ at } \omega = 146 \text{ rad/s if } H(s) = 20(s+100)$$

$$\Rightarrow H_{dB} = 20 \log_{10} |H(j\omega)|$$

$$= 20 \log_{10} (20 \sqrt{\omega^2 + 100^2})$$

$$= 70.97 \text{ dB}$$

$$H_{dB} = 20 \log_{10} |K| + 20 \log_{10} |s-z_1| + 20 \log_{10} |s-z_2| + \dots + 20 \log_{10} |s-z_m| - 20 \log_{10} |s-p_1| - \dots - 20 \log_{10} |s-p_n|$$

$$\text{let } H(j\omega) = H_1(j\omega) \cdot H_2(j\omega)$$

$$20 \log_{10} |H(j\omega)| = 20 \log_{10} |H_1(j\omega)| + 20 \log_{10} |H_2(j\omega)|$$

$$\angle H(j\omega) = \angle H_1(j\omega) + \angle H_2(j\omega)$$

$$\text{here these are low pass filters}$$

$$\text{note: } \log_{10} 1 = 0$$

$$\log_{10} 10 = 1$$

$$\log_{10} 2 = 0.3$$

$$\log_{10}(0.1) = -1$$

$$\log_{10}(10^{-k}) = -k$$

$$\log_{10}(0) = \text{undefined}$$

$$\text{if } \omega = 100 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10) = 20 \text{ dB}$$

$$\text{if } \omega = 1000 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (100) = 40 \text{ dB}$$

$$\text{if } \omega = 10 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-1}) = -20 \text{ dB}$$

$$\text{if } \omega = 1 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-6}) = -60 \text{ dB}$$

$$\text{if } \omega = 0.1 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-10}) = -100 \text{ dB}$$

$$\text{if } \omega = 0.01 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-12}) = -120 \text{ dB}$$

$$\text{if } \omega = 0.001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-14}) = -140 \text{ dB}$$

$$\text{if } \omega = 0.0001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-16}) = -160 \text{ dB}$$

$$\text{if } \omega = 0.00001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-18}) = -180 \text{ dB}$$

$$\text{if } \omega = 0.000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-20}) = -200 \text{ dB}$$

$$\text{if } \omega = 0.0000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-22}) = -220 \text{ dB}$$

$$\text{if } \omega = 0.00000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-24}) = -240 \text{ dB}$$

$$\text{if } \omega = 0.000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-26}) = -260 \text{ dB}$$

$$\text{if } \omega = 0.0000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-28}) = -280 \text{ dB}$$

$$\text{if } \omega = 0.00000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-30}) = -300 \text{ dB}$$

$$\text{if } \omega = 0.000000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-32}) = -320 \text{ dB}$$

$$\text{if } \omega = 0.0000000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-34}) = -340 \text{ dB}$$

$$\text{if } \omega = 0.00000000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-36}) = -360 \text{ dB}$$

$$\text{if } \omega = 0.000000000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-38}) = -380 \text{ dB}$$

$$\text{if } \omega = 0.0000000000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-40}) = -400 \text{ dB}$$

$$\text{if } \omega = 0.00000000000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-42}) = -420 \text{ dB}$$

$$\text{if } \omega = 0.000000000000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-44}) = -440 \text{ dB}$$

$$\text{if } \omega = 0.0000000000000000001 \text{ rad/s}$$

$$H_{dB} = 20 \log_{10} (10^{-46}) = -460 \text{ dB}$$

- Lecture 18 {Bode Plots} Missed
23/10/24

Lecture 19


04/11/24

eg) draw bode plots of $H(s) = \frac{s+1}{s(s+2)^2}$

zeroes: 1 $\rightarrow s = -1$

poles: 3 $\rightarrow s = 0, -2, -2$
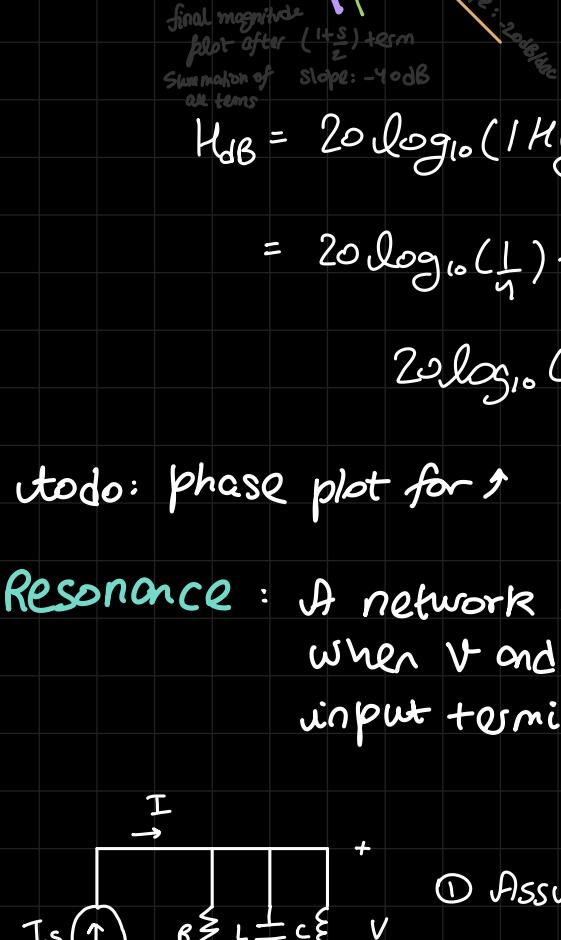
$$H(s) = \frac{(1+s/1)}{s(1+s/2)^2} = \frac{1}{4} \cdot \frac{1}{s} \cdot \left(\frac{1+s/1}{1+s/2}\right) \cdot \left(\frac{1+s/2}{1+s/2}\right)$$



Simple pole case

so, we have corner frequency at $w = \omega$ i.e.

at $w = 1$ & $w = 2$ respectively


$$H_{dB} = 20 \log_{10}(|H(j\omega)|)$$

$$= 20 \log_{10}\left(\frac{1}{\sqrt{1}}\right) + 20 \log_{10}\left(\frac{1}{j\omega}\right)$$

$$20 \log_{10}(1 + \frac{1}{\omega}) + 40 \log_{10}(1 + \frac{1}{\omega^2})$$

todo: phase plot for \rightarrow

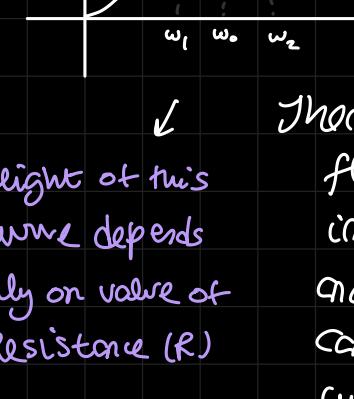- Resonance: A network is in resonance when V and I at network input terminals are in phase



① Assume: $I_S = I_0 \cos(\omega t + \phi)$

$$V(j\omega) = \frac{1}{Z(j\omega)} = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$= \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

for resonance \Rightarrow V and I are in phase
(purely resistive circuits)

$$\text{i.e. } \omega C - \frac{1}{\omega L} = 0$$

$$\Rightarrow \omega = \frac{1}{\sqrt{LC}} = \omega_0 \text{ "resonant frequency"}$$

- ② Assume $I_S = I_0 e^{-rt} \cos(\omega t + \phi)$

$$Y(s) = \frac{1}{Z(s)} = \frac{1}{R} + sC + \frac{1}{sL}$$

$$= \frac{s^2 + s(1/RC) + (1/LC)}{(1/C)s}$$

$V_{out} = V \Rightarrow$ transfer function?

$I_{in} = I_S$

↓

$$\frac{V(s)}{I_S(s)} = Z(s) = \frac{1}{Y(s)}$$

transfer impedance

ω_1, ω_2 : half power frequency

height of this curve depends only on value of Resistance (R)
depends on L & C as well

there will be some current flowing in capacitor & inductor but it is equal and opposite so it cancels out and net total current flows only through the resistor

width of the curve

depends on L & C as well

At resonance:

$$I_S = I_R$$

$$I_C = -I_L \Rightarrow I_C + I_L = 0$$

quality factor

$$Q = 2\pi \frac{\text{max. energy stored}}{\text{total energy lost per period}}$$

$$= 2\pi \frac{[w_L(t) + w_C(t)]_{\text{max}}}{P_R \cdot T}$$

P_R : avg power lost in resistor

$$= \frac{1}{2} |I|^2 R \text{ WATTS}$$

T: time period (sec)

$$w_L(t) : \frac{1}{2} L i_L^2(t) \text{ (J)}$$

$$w_C(t) : \frac{1}{2} C v_C^2(t) \text{ (J)}$$

$$Q = \omega_0 R C = R \sqrt{\frac{C}{L}}$$

$$\alpha = \text{damping factor} = \frac{1}{2RC} = \frac{\omega_0}{2Q}$$

ω_d : damped frequency $= \sqrt{\omega_0^2 - \alpha^2}$

$$= \omega_0 \sqrt{1 - \left(\frac{1}{2Q}\right)^2}$$

HALF POWER BANDWIDTH (BW)

$$BW = \omega_2 - \omega_1 = \frac{\omega_0}{Q}$$

$$\text{where } \omega_c = \sqrt{\omega_1 \omega_2}$$

note: $BW \propto \frac{1}{Q}$.

note: if $Q > 5$: high-Q circuit