

tr5frbj 12/08/24

Circuit Theory and Devices

Lab: LT Spice (2nd week onwards)

book: Engineering Circuit Analysis (9th edition)

Relative grading


Labs	20%
Quiz	20%
Midsem	30%

Scientific calc

Course: 9 modules chapter 10 onwards
{continuation of BE3}

Lecture 1

⇒ Linear Circuits

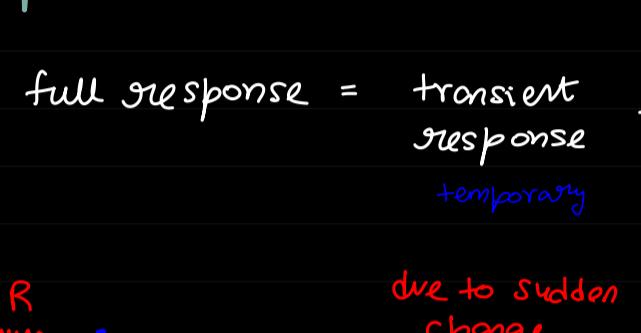

System is linear if

$$Kx \rightarrow [\text{sys}] \rightarrow Ky$$

where K is constant

"R" Resistor: linear element ✓
 $V = iR$

"L" Inductor: linear element ✓
 $V = L \frac{di}{dt}$


* Linear Electric Circuits:

consists of ⇒

① $R, L, C \rightarrow$ linear elements

② Independent voltage & current sources

③ Linear dependent sources

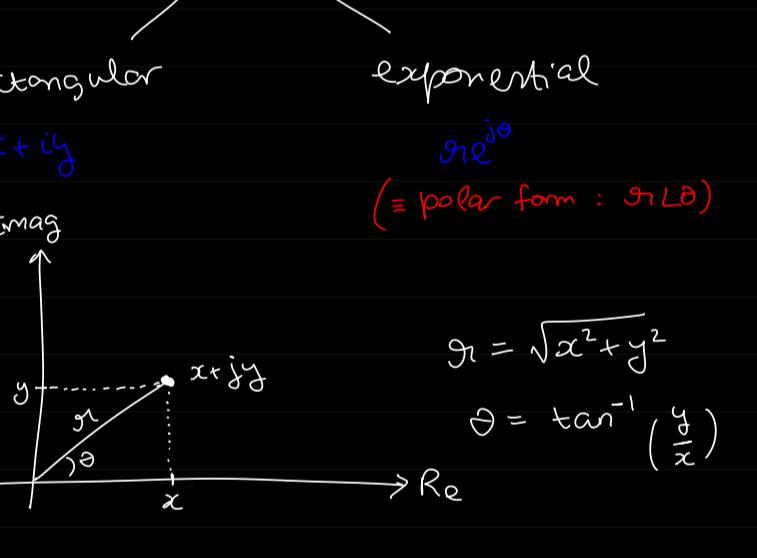


Note: diode and transistors are non-linear elements

* Response of a linear circuit

① full response = transient response + steady state

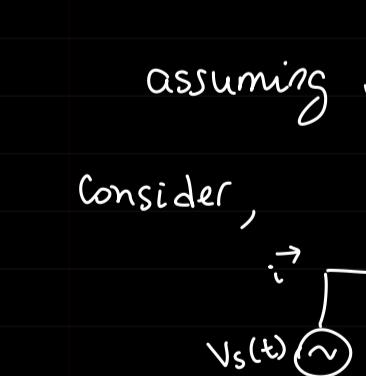transient temporary persists $t \rightarrow \infty$



due to sudden change

due to source

also called natural response

also called forced response

depends on R, L, C

depends on current/voltage source

$$KVL : -V_s + iR + L \frac{di}{dt} = 0$$

depends on R, L, C

depends on current/voltage source

$$i_{\text{final}} = i_{\text{transient}} + i_{\text{steady state}}$$

as $t \rightarrow \infty$, $i_{\text{final}} = i_{\text{steady state}}$

* Sinusoids & complex numbers

Sinusoidally varying voltage source

$$V_s(t) = V_m \cos(\omega t)$$

$$V_s(t) = V_m \sin(\omega t)$$

$$V_s(t) = V_m \sin(\omega t + \phi)$$

General form Solution: $i = I_1 \cos \omega t + I_2 \sin \omega t$

$$\Rightarrow V_m \cos(\omega t) = (I_1 \cos \omega t + I_2 \sin \omega t) R + L \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{d}{dt} (I_1 \cos \omega t + I_2 \sin \omega t)$$

$$\Rightarrow \omega (I_1 (-\sin \omega t) + I_2 \cos \omega t)$$

$$\Rightarrow \omega (I_2 \cos \omega t - I_1 \sin \omega t)$$

$$V_m \cos(\omega t) = (I_1 \cos \omega t + I_2 \sin \omega t) R + (I_2 \cos \omega t - I_1 \sin \omega t) L \omega$$

$$\Rightarrow \cos \omega t \cdot (I_1 R + I_2 L - V_m) + \sin \omega t \cdot (I_2 R - I_1 L) = 0$$

$$\Rightarrow (I_1 R + I_2 L - V_m) \cos \omega t + (I_2 R - I_1 L) \sin \omega t = 0$$

$$\boxed{I_1 R + I_2 L = V_m}$$

$$I_1 = \frac{\sqrt{m} R}{R^2 + L^2}$$

$$\boxed{I_1 = I_2 \cdot \frac{R}{L}}$$

$$\Rightarrow I_2 R + I_1 L = V_m \Rightarrow I_2 = \frac{V_m L}{R^2 + L^2}$$

* Section 10.1

(a) $Q_1 \rightarrow 5\sin(5t - 9^\circ)$

$$t=0 \Rightarrow 5\sin(-9^\circ) = -5\sin(9^\circ) = -0.782$$

$$t=0.01 \Rightarrow 5\sin(0.05 - 9^\circ) = -5\sin(8.95^\circ) \quad X$$

\Downarrow
radians

$$5\sin\left(\frac{0.05 \times 180}{\pi} - 9^\circ\right) = 5\sin(2.86^\circ - 9^\circ)$$

$$\Rightarrow -5\sin(6.14^\circ) = -0.534$$

$$t=0.1 \Rightarrow 5\sin(0.5 - 9^\circ) = 5\sin(28.64^\circ - 9^\circ) = 5\sin(19.64^\circ)$$

$$\Rightarrow 1.6805$$

(b) $4\cos 2t$

$$t=0 \Rightarrow 4\cos(0) = 4$$

$$t=1 \Rightarrow 4\cos(2) = 3.997$$

$$t=1.5 \Rightarrow 4\cos(3) = 3.994$$

(c) $3.2 \cos(6t + 15^\circ)$

$$t=0 \Rightarrow 3.2 \cos(15^\circ) = 3.09$$

$$t=0.01 \Rightarrow 3.2 \cos(0.06 + 15^\circ) = 3.2 \cos(3.43^\circ + 15^\circ)$$

$$\Rightarrow 3.2 \cos(18.43^\circ)$$

$$\Rightarrow 3.035$$

$$t=0.1 \Rightarrow 3.2 \cos(0.6 + 15^\circ) = 3.2 \cos(34.3^\circ + 15^\circ)$$

$$= 3.2 \cos(49.3^\circ)$$

$$= 2.086$$

Q2) (a) $300\sin(628t) \rightarrow 300 \cdot \cos(628t - 90^\circ)$


$$4\sin(3\pi t + 30^\circ) \rightarrow 4\cos(3\pi t - 60^\circ)$$

$$14\sin(50t - 8^\circ) - 10\cos 50t \rightarrow$$


Q3) $V_L = 10\cos(10t - 45^\circ)$

(a) $i_L = 5\cos 10t$

$$-45^\circ$$

 

⇒ AC Power Analysis {Module: 3}

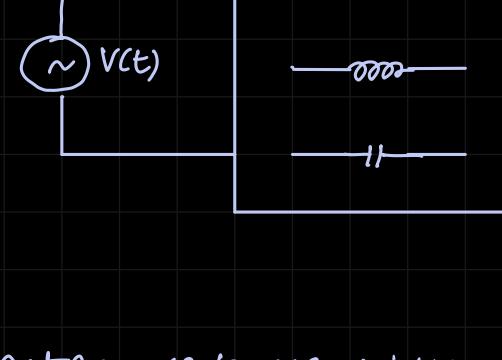

$$\cos(A) \cos(B) =$$

$$\frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

Instantaneous power: $p(t) = v(t) \cdot i(t)$

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$p(t) = V_m \cos(\omega t + \theta) \cdot I_m \cos(\omega t + \phi)$$

$$p(t) = \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{constant}} + \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)}_{\text{twice frequency (harmonic)}}$$

• Average Power

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(\theta - \phi) dt + \underbrace{\frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) dt}_{0}$$

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

* Avg. Power absorbed

• by a purely resistive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

here, phase diff = 0°

$$\mathbf{I} = I_m e^{j\phi}$$

$$\mathbf{I}^* = I_m e^{-j\phi}$$

(conjugate)



$$P_{avg} = \frac{V_m \cdot I_m}{2} = \frac{I_m^2 R}{2} = \frac{V_m^2}{2R}$$

• by a purely inductive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$


here, phase diff = 90°



$$P_{avg} = 0 \text{ for inductor}$$

• by a purely capacitive element
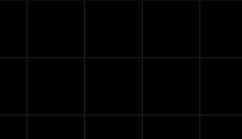
$$P_{avg} = \frac{V_m \cdot I_m}{2} \cos(-90^\circ)$$



$$P_{avg} = 0 \text{ for capacitor}$$

* Lecture: 6

$$v(t) = V_m \cos(\omega t + \phi) \quad \leftarrow \text{Revision}$$

$$\downarrow$$


$$v(t) = R \Re \{ V_m e^{j\omega t} e^{j\phi} \}$$

$$\downarrow -e^{j\omega t}$$

$$V_m e^{j\phi} = V_m \angle \phi$$

exponential polar

• eq)

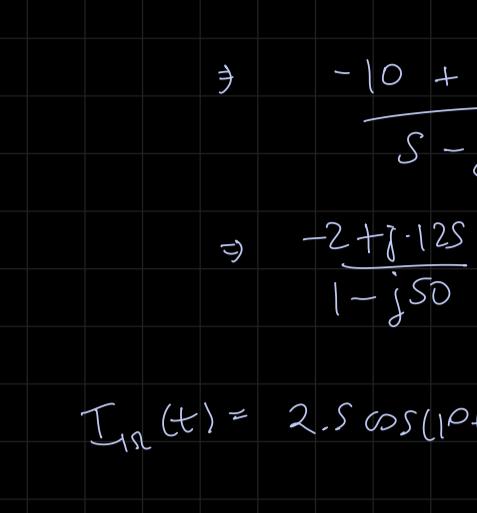


① find power delivered to each element at $t = 0, 10, 20 \text{ ms}$

② find P_{avg} to each element

(ans) convert to freq. domain

$$V_{1\text{R}} = V_{u\text{R}} + V_c$$

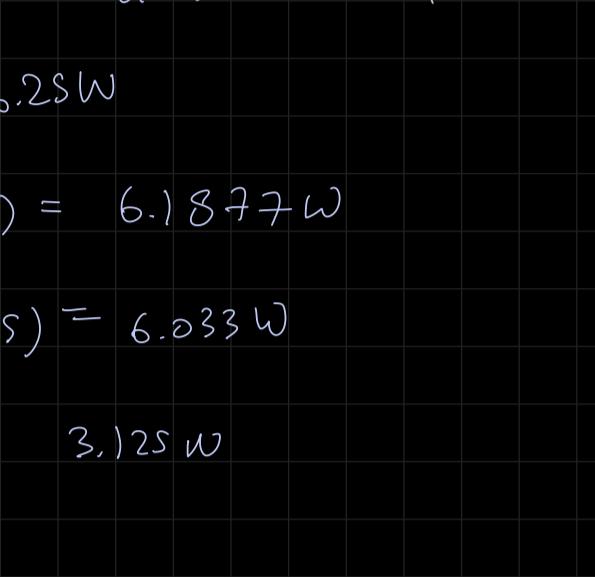

$$\textcircled{1} \quad P_{inst} = \frac{V_m I_m \cos(\theta - \phi)}{2} + \frac{V_m I_m}{2} \cos(2\omega t + \phi + \theta)$$

$$I_1 = -2.5 \times \left(\frac{4 - j2.5 \times 10^4}{1 + j - j2.5 \times 10^4} \right) \approx -2.5 \text{ A}$$

$$\Rightarrow \frac{-10 + j62.5 \times 10^4}{5 - j2.5 \times 10^4} \Rightarrow \frac{-2 + j12.5}{1 - j50}$$

$$\Rightarrow \frac{-2 + j1.25}{1 - j50} \times \frac{1 + j50}{1 + j50} =$$

$$I_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$V_{1\text{R}} = (I_{1\text{R}})(2 \Omega) \Rightarrow V_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$\cos^2(\theta) = \frac{1 + \cos(2\theta)}{2}$$

$$P_{1\text{R}}(t) = 2.5 \cos(10t) \cdot 2.5 \cos(10t) \text{ W}$$

$$P_{1\text{R}}(t=0) = 6.25 \text{ W}$$

$$P_{1\text{R}}(t=20 \text{ ms}) = 6.033 \text{ W}$$

$$(P_{avg})_{1\text{R}} = 3.125 \text{ W}$$

\Rightarrow P delivered to 4 ohm

$$P_{4\text{R}}(t) = V_{u\text{R}}(t) \times I_{u\text{R}}(t)$$

$$\Rightarrow I_{4\text{R}} = I_s \times \frac{1}{5 - j2.5 \times 10^4} = 10^{-4} \angle 90^\circ \text{ A}$$

$$V_{u\text{R}} = 4 \times I_{4\text{R}} = 4 \times 10^{-4} \angle 90^\circ \text{ V}$$

convert to time domain

$$P_{1\text{R}}(t) = 2 \times 10^{-8} + 2 \times 10^{-8} \cos(20t) \text{ W}$$

$$t=0^- \quad 4 \times 10^{-8} \text{ W}$$

$$t=10 \text{ ms} = 3.96 \times 10^{-8} \text{ W}$$

$$P_{4\text{R}}(t=0) = 2 \times 10^{-8} \text{ W}$$

\Rightarrow P delivered to capacitor

$$P_c(t) = V_c(t) \cdot I_c(t)$$

$$\left(P_{avg} \right)_c = 0 \quad \text{since phase diff} = 90^\circ$$

$$I_c = I_2 = 10^{-4} \angle 90^\circ \text{ A} \Rightarrow I_c(t) = 10^{-4} \cos(10t + 90^\circ)$$

$$V_c = (-j2.5 \times 10^4) \times 10^{-4} \angle 90^\circ$$

$$-j2.5 \times 10^4 \times (+j10^{-4})$$

$$P_c(t) = 1.25 \times 10^{-4} \cos(20t + 90^\circ) \text{ W}$$

$$t=0 \Rightarrow P=0 \text{ W}$$

$$t=10 \text{ ms} \Rightarrow P=2.48 \times 10^{-5} \text{ W}$$

Note: we cannot multiply I_c and V_c in phasor form and then convert to time domain for getting P_c (power) because power does not have a phasor part. It is a real value.

* Correct or not?

$$\text{depends on } \times \quad \textcircled{1} \quad P_{1\text{R}}(t) + P_{4\text{R}}(t) + P_c(t) = \text{constant 1}$$

$$\checkmark \quad \textcircled{2} \quad P_{avg\ 1\text{R}} + P_{avg\ 4\text{R}} + P_{avg\ c} = \text{constant 2}$$

$\Rightarrow P_{avg\ source}$

active sign convention

passive sign convention

maximum power delivered to load when

$$Z_L = Z_S^*$$

complex conjugate of Z_S

\Rightarrow Impedance Matching

$$\text{impedance matching circuit}$$

$$100 \Omega \quad 100 \Omega \quad j50 \Omega \quad 50 \Omega$$

$$Z_L = Z_S^*$$

• Sinusoidally varying voltage

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \phi) dt}$$

$$\text{if } P_{avg\ 1} = P_{avg\ 2}$$

$$\Rightarrow I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

= Root mean square

$$i(t) \xrightarrow{\text{square}} i^2(t) \xrightarrow{\text{mean}} \frac{1}{T} \int_0^T i^2(t) dt \xrightarrow{\text{square root}} \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$V_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$I_{eff} = \frac{I_m}{\sqrt{2}}$$

current rms value unit: A rms

$$V_{eff} = \frac{V_m}{\sqrt{2}}$$

voltage rms value unit: V rms

$$\text{eg. } I = 10 \angle 90^\circ \text{ A} \Rightarrow I = 5\sqrt{2} \angle 90^\circ \text{ A rms}$$

$$\text{or } V = 100 \sqrt{2} \angle -60^\circ \text{ V} \Rightarrow V = 100 \angle -60^\circ \text{ V rms}$$

* Apparent Power

$$P_{apparent} = I_{eff} V_{eff}$$

volt amperes
unit: VA, not W

$$PF = \frac{\text{avg power}}{\text{apparent power}} = \frac{(V_m \cdot I_m)/2 \cos(\theta - \phi)}{V_{eff} \cdot I_{eff}}$$

$$PF = \cos(\theta - \phi)$$

\approx power factor angle

$$\text{it is real number}$$

$$\text{not a phasor}$$

$$\text{current/voltage}$$

$$\text{magnitude of current/voltage}$$

$$\text{current/voltage}$$

* Lecture: 7


- Instantaneous Power: $p(t) = v(t)i(t)$
- Average Power: $P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) = \frac{1}{2} R_{eff} \{VI^*\}$
- $P_{avg, sources} = \sum P_{avg, elements}$

* Note: $Z = R + jX$
 \downarrow resistive reactive


$P_{avg, resistive} : P \neq 0$

$P_{avg, reactive} : P = 0$


* Max Power Transfer:

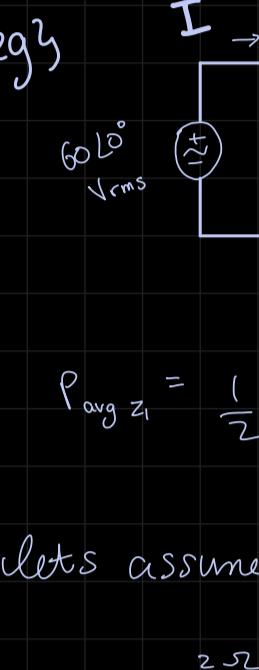

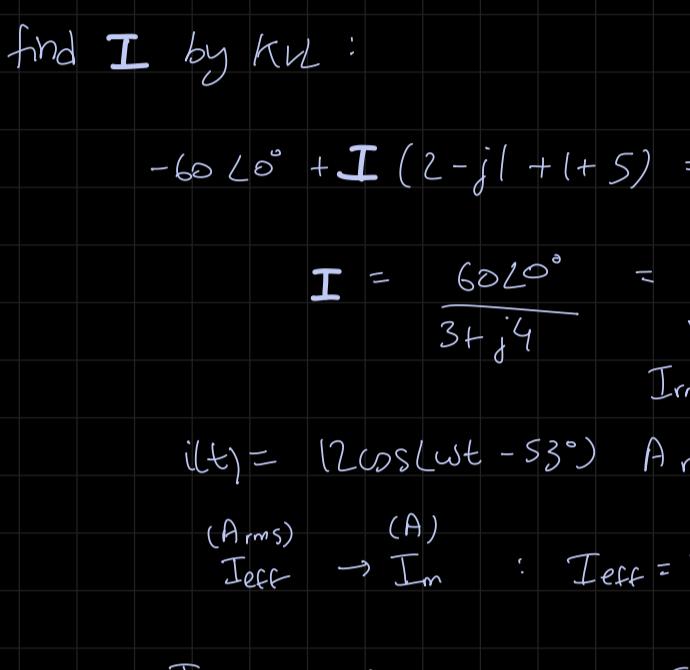Circuit has max. power when $Z_S = Z_L^*$ complex conjugate



↓ apply Thevenin's theorem

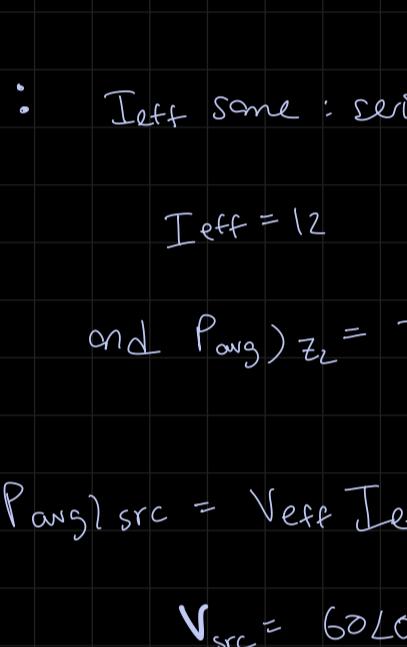

$$Z_L = Z_{th}$$

* Power Factor

$$PF = \cos(\theta - \phi) = \frac{\text{Power active}}{\text{Power apparent}}$$

for purely resistive load: $PF = 1$ {Max} $\theta - \phi = 0^\circ$
 for purely reactive load: $PF = 0$ {min}

Note $\rightarrow PF = 0.5$ leading \rightarrow capacitive $(\theta - \phi) < 0^\circ$
 $PF = 0.5$ lagging \rightarrow inductive $(\theta - \phi) > 0^\circ$

eg) $I \rightarrow$ $z_1 = 2 - j1$ $z_2 = 1 + j5$ \downarrow find
 $V_{rms} = 60^\circ$ \downarrow $\theta = 53.13^\circ$ A_{rms}
 $I_{eff} = 12 A_{rms}$ \downarrow $I_m = 12\sqrt{2} A$
 $P_{avg, z_1} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} R_{eff} \{VI^*\}$
 \downarrow voltage across z_1 , not the src

lets assume z_1 :

$$\frac{2-j1}{2+j1} = \frac{-j2}{1+j4} \quad \text{so, } P_{avg, z_1} = \text{Power delivered to } 2\Omega \text{ resistor}$$

$$= I_{eff}^2 R$$

find I by KVL:

$$-60^\circ + I(2 - j1 + 1 + j5) = 0$$

$$I = \frac{60^\circ}{3 + j4} = 12L - 53.13^\circ A_{rms}$$

$$i(t) = 12 \cos(\omega t - 53.13^\circ) A_{rms}$$

$$\frac{(A_{rms})}{I_{eff}} \rightarrow \frac{(A)}{I_m} : I_{eff} = I_m = \frac{I_{eff} \sqrt{2}}{\sqrt{2}}$$

$$I_{eff} = 12 A_{rms} \Rightarrow I_m = 12\sqrt{2} A$$

$$i(t) = 12\sqrt{2} \cos(\omega t - 53^\circ) A$$

$$P_{avg}(z_1) = (12)^2 \times 2 = 288 W$$

$$\text{note: } P_{avg} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$Z_2 : I_{eff} \text{ same : series circuit}$$

$$I_{eff} = 12$$

$$\text{and } P_{avg, z_2} = I_{eff}^2 R = (144)(1) = 144 W$$

$$(2) P_{avg, src} = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$V_{src} = 60L^\circ V_{rms} \Rightarrow V_{eff} = 60 V_{rms}$$

$$I_{src} = 12L - 53.13^\circ V_{rms} \Rightarrow I_{eff} = 12 A_{rms}$$

$$\theta = 0^\circ, \phi = -53.13^\circ$$

$$P_{avg, src} = [60 \times 12] \cos(53.13^\circ) = 432 W$$

We can observe that $288 + 144 = 432$

and hence,

$$P_{avg, sources} = \sum P_{avg, elements} \text{ holds}$$

$$(3) P_{apparent} = V_{eff} \cdot I_{eff} = (60)(12) = 720 W$$

$$(4) PF of combined loads = PF of source$$

$$PF = \cos(\theta - \phi) = \cos(0 + 53.13^\circ) = 0.6$$

$\theta - \phi > 0^\circ$ lagging

$$S = P + jQ = \frac{1}{2} V_{eff} I_{eff} \sin(\theta - \phi)$$

$$S = P + jQ$$

$$|S| = \sqrt{P^2 + Q^2} = \sqrt{P_{apparent}^2 + Q_{apparent}^2}$$

$$S = P + jQ = \frac{1}{2} V_{eff} I_{eff} \sin(\theta - \phi)$$

$$P = 0, Q \neq 0$$

$$Q \text{ signifies energy flow rate into or out of reactive component of load}$$

$$eg) \quad S = P + jQ = \frac{1}{2} V_{eff} I_{eff} \sin(\theta - \phi)$$

$$V_{src} = 90^\circ A \quad \text{assume } C = 1 \mu F, \omega = 45 \text{ rad/s}$$

$$I_{src} = 9L^\circ V_{rms} \Rightarrow I_{eff} = 9 A_{rms}$$

$$\theta = 90^\circ, \phi = -90^\circ$$

$$P_{avg, src} = \frac{1}{2} V_{eff} I_{eff} \sin(90^\circ - (-90^\circ)) = 81 W$$

$$Q_{avg, src} = \frac{1}{2} V_{eff} I_{eff} \cos(90^\circ - (-90^\circ)) = 162 VAr$$

$$|S| = \sqrt{P_{avg, src}^2 + Q_{avg, src}^2} = \sqrt{81^2 + 162^2} = 189 W$$

$$I_m = 9 A$$

$$I_{eff} = \frac{9}{\sqrt{2}} A_{rms}$$

$$V_{eff} = ? \quad \text{find } V$$

$$V = I(Z_{eq}) = 9L^\circ \left(18 \times 10^3 - j10^6 \right)$$

$$V = I(Z_{eq}) = 9L^\circ \left(18 \times 10^3 - j10^6 \right)$$

$$V = I(Z_{eq}) = 9L^\circ \left(18 \times 10^3 - j10^6 \right)$$

$$V = I(Z_{eq}) = 9L^\circ \left(18 \times 10^3 - j10^6 \right)$$

* Lecture - 8

• Polyphase Circuits (Chp 12)

⇒ Three Phase Source

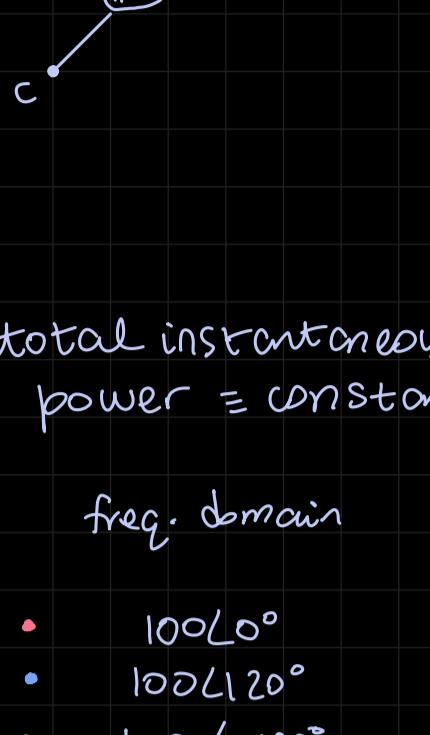

$$V_{an} = 100\angle 0^\circ \text{ V}$$

$$V_{bn} = 100\angle 120^\circ \text{ V}$$

$$V_{cn} = 100\angle -120^\circ \text{ V}$$

if $|V_{an}| = |V_{bn}| = |V_{cn}|$
 & $V_{an} + V_{bn} + V_{cn} = 0$
 then it is a

Balanced Source


total instantaneous power = constant

freq. domain

- $100\angle 0^\circ$
- $100\angle 120^\circ$
- $100\angle -120^\circ$

time domain

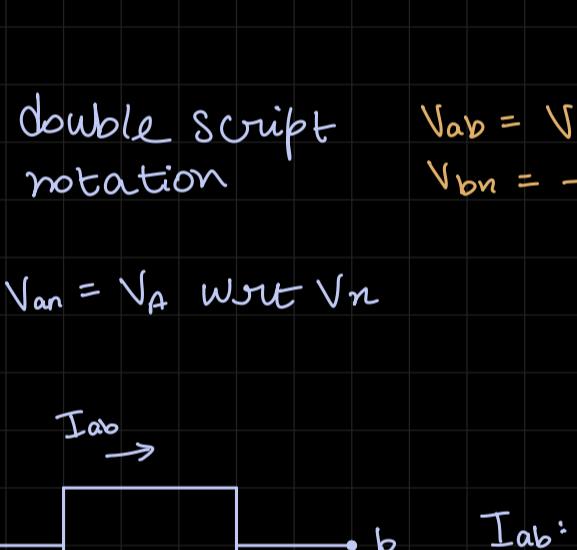
- $100 \cos(\omega t)$
- $100 \cos(\omega t + 120^\circ)$
- $100 \cos(\omega t - 120^\circ)$



total $p(t) \rightarrow \text{constant}$

* Single Phase Three-wire Source

≡ Two phase source

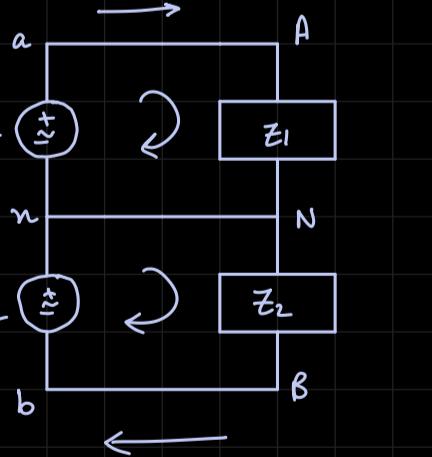

$$V_1 = V_m \angle 0^\circ$$

$$V_{an} = V_1 = V_m \angle 0^\circ$$


$$V_{bn} = -V_1 = V_m \angle 0^\circ - 180^\circ$$

$$V_{bn} \leftarrow \xrightarrow{180^\circ} V_{an}$$

double script notation

$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} = V_{an} + V_{nb} \\ V_{bn} &= -V_{nb} \end{aligned}$$

$$V_{an} = V_A \text{ wrt } V_n$$

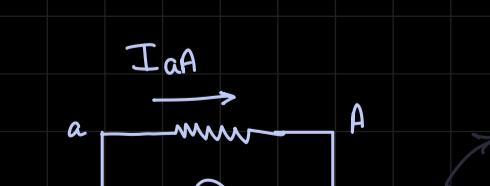

$$I_{aa} = \frac{V_1}{Z_1}$$

$$I_{bb} = \frac{V_1}{Z_2}$$

$$I_{nn} = -I_{aa} + I_{bb}$$

$$\Rightarrow \frac{V_1}{Z_1} - \frac{V_1}{Z_2}$$

Assume $Z_1 = Z_2$

$$I_{nn} = \frac{V_1}{Z_1} - \frac{V_2}{Z_1} = 0$$

when both srcs &
and loads are equal

Balanced Load : current in neutral line is equal to zero.

all terms are phasors

even with resistance, $I_{nn} = 0 = I_{bb} - I_{aa}$

due to

① Balanced Load
 ≡ Symmetry

* Lecture: 9

09/09/29

time domain freq. domain

$$\begin{array}{ll} \sqrt{V_p} \cos(\omega t + \theta^\circ) & \sqrt{V_p} L^{\theta^\circ} \\ \sqrt{V_p} \cos(\omega t + \theta^\circ - 180^\circ) & \sqrt{V_p} L^{\theta^\circ - 180^\circ} \end{array}$$

We cannot directly say,

$$P_{avg} = \sqrt{I} \quad \times$$

$$\text{but } P_{avg} = \frac{1}{2} \operatorname{Re}\{ \sqrt{I} I^* \} \quad \checkmark$$

$$\begin{aligned} \textcircled{2} \quad a) \quad I_{AB} &= \frac{115 L^{\theta^\circ} + 115 L^{\theta^\circ}}{2(10 + j^2)} = \frac{230 L^{\theta^\circ}}{2(10 + j^2)} \\ &= 11.27 / (\theta^\circ - 11.3^\circ) A \end{aligned}$$


$$\phi = \theta - 11.3^\circ$$

$$PF = \cos(\theta - \phi + 11.3^\circ) = 0.98 \text{ lagging}$$

because PF angle is true

$$b) \quad PF = 1 \Rightarrow \cos(\theta - \phi) = 1 \Rightarrow \theta - \phi = 0$$

$$\Rightarrow \theta = \phi$$

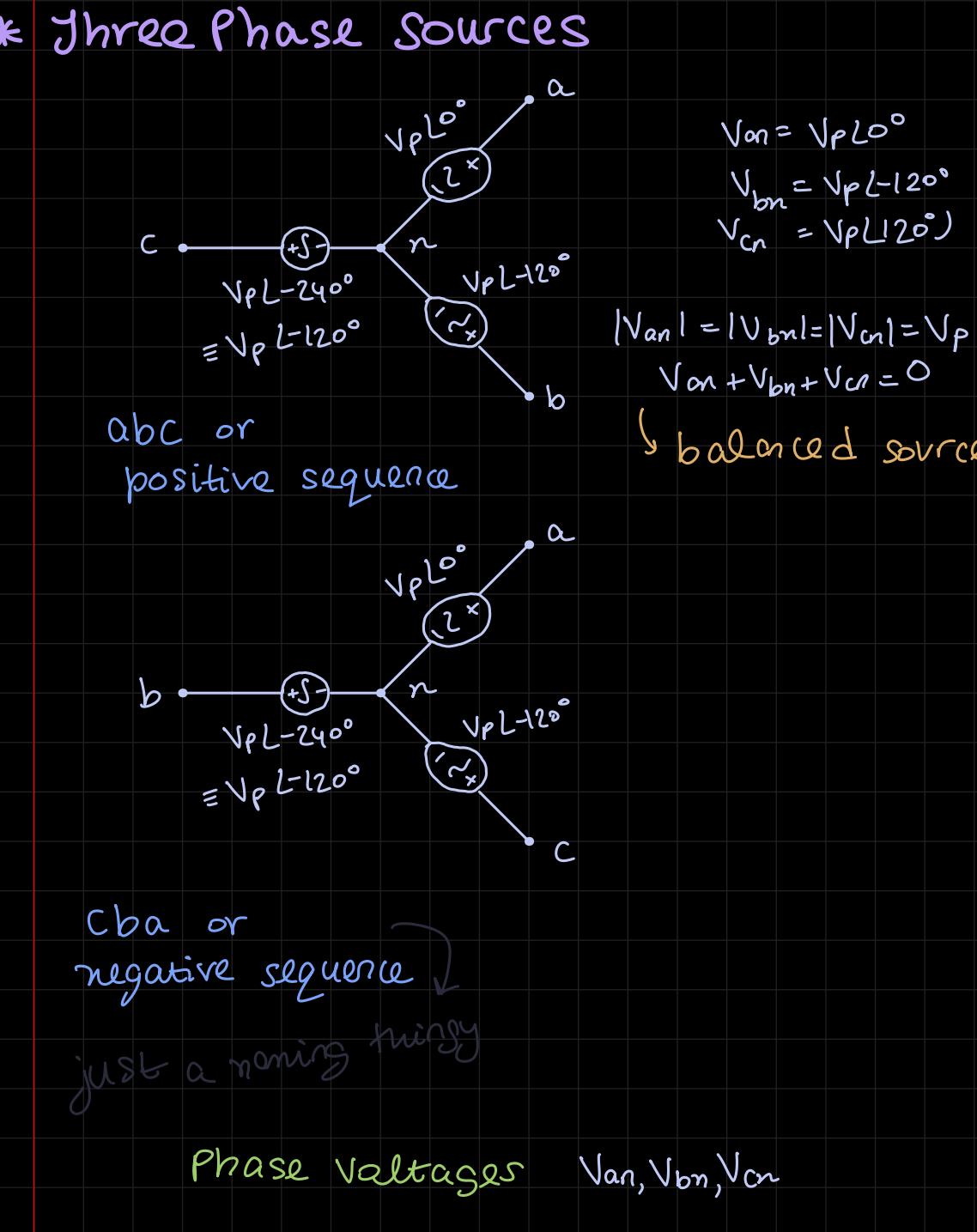

Note that this is still a balanced load, so we can remove NN since $I_{NN} = 0$

using complex power

$S = \text{complex power of total load}$

$$S = \frac{1}{2} \sqrt{I} I^*$$

$$PF = \frac{\operatorname{Re}\{S\}}{|S|} = 1 \Rightarrow \operatorname{Re}\{S\} = |S|$$

so, $\operatorname{Im}\{S\} = 0$ here

$$S = \frac{1}{2} V_{an} I_{an}^* + \frac{1}{2} V_{nb} I_{nb}^* + \frac{1}{2} V_{ab} I_{ab}^*$$

$$\Rightarrow \frac{1}{2} V_{an} \left(\frac{V_{an}}{Z_p} \right)^* + \frac{1}{2} V_{nb} \left(\frac{V_{nb}}{Z_p} \right)^* + \frac{1}{2} V_{ab} \left(\frac{V_{ab}}{Z_p} \right)^*$$

$$\Rightarrow \frac{1}{2} \frac{|V_{an}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{nb}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{ab}|^2}{|Z_p|^2} Z_p$$

$$\Rightarrow \frac{115^2}{10^4} (10 + j^2) + \frac{1}{2} \left(\frac{230^2}{(j\omega C)^2} \right) \left(\frac{-j}{\omega C} \right) = \frac{1}{j\omega C} = \frac{1}{j\omega} \times \frac{-1}{j\omega C}$$


$$\Rightarrow 115^2 \left(\frac{10 + j^2}{10^4} - \frac{-j}{\omega C} \right)$$

$$\Rightarrow 2 \times 115^2 \left(\frac{j}{10^4} - \frac{1}{\omega C} \right)$$

$$\Rightarrow 2 \times 115^2 \left(\frac{1}{10^4} - \frac{1}{\omega C} \right) = 0$$

$$\frac{1}{10^4} - \frac{1}{\omega C} = 0 \Rightarrow C = \frac{1}{10400 \pi} = 30.6 \mu F$$

* Three Phase Sources

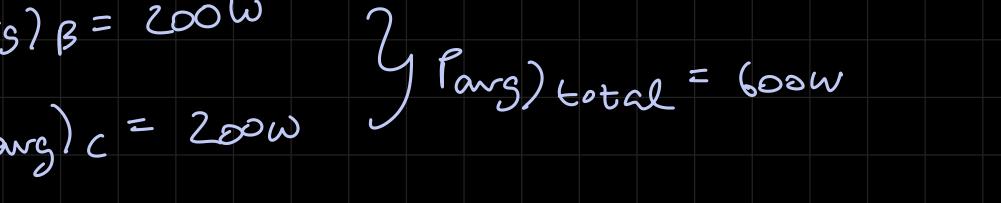

abc or positive sequence

cba or negative sequence

just a naming thingy

Phase Voltages V_{an}, V_{bn}, V_{cn}

Line-to-line Voltages V_{ab}, V_{bc}, V_{ca} OR line voltages

$$V_{ab} = V_{an} - V_{bn} = V_{an} + V_{nb}$$

$$V_{ab} = \sqrt{3} V_p L^{30^\circ}$$

$$V_{bc} = \sqrt{3} V_p L^{-90^\circ}$$

$$V_{ca} = \sqrt{3} V_p L^{-210^\circ}$$

* Y-Y connection

balanced source

cba or negative sequence

just a naming thingy

Phase Voltages V_{an}, V_{bn}, V_{cn}

Line-to-line Voltages V_{ab}, V_{bc}, V_{ca} OR line voltages

$$V_{ab} = V_{an} - V_{bn} = V_{an} + V_{nb}$$

$$V_{ab} = \sqrt{3} V_p L^{30^\circ}$$

$$V_{bc} = \sqrt{3} V_p L^{-90^\circ}$$

$$V_{ca} = \sqrt{3} V_p L^{-210^\circ}$$

going back to the Y-Y connection

$$I_{aa} = \frac{V_{an}}{Z_p} = \frac{200 L^{0^\circ}}{100 L^{60^\circ}} = 2 L^{-60^\circ} A_{rms}$$

$$I_{bb} = \frac{V_{bn}}{Z_p} = \frac{200 L^{-120^\circ}}{100 L^{60^\circ}} = I_{aa} L^{-120^\circ}$$

$$I_{cc} = \frac{V_{cn}}{Z_p} = \frac{200 L^{+120^\circ}}{100 L^{60^\circ}} = I_{aa} L^{+120^\circ}$$

$$I_{nn} = I_{aa} + I_{bb} + I_{cc} = 0$$

e.g. consider three phase balanced Y-Y connected system

$$V_{an} = 200 L^{0^\circ} V_{rms}$$

$$V_{bn} = 200 L^{-120^\circ} V_{rms}$$

$$V_{cn} = 200 L^{+120^\circ} V_{rms}$$

line voltage:

$$V_{ab} = \sqrt{3} V_p L^{30^\circ} = 200 \sqrt{3} L^{30^\circ} V_{rms}$$

$$V_{bc} = 200 \sqrt{3} L^{-90^\circ} V_{rms}$$

$$V_{ca} = 200 \sqrt{3} L^{-210^\circ} V_{rms}$$

line currents:

$$I_{aa} = \frac{V_{an}}{Z_p} = \frac{200 L^{0^\circ}}{100 L^{60^\circ}} = 2 L^{-60^\circ} A_{rms}$$

$$I_{bb} = 2 L^{-120^\circ} A_{rms}$$

$$I_{cc} = 2 L^{-30^\circ} A_{rms} = 2 L^{60^\circ} A_{rms}$$

total avg. power: $P_{avg} = \frac{1}{2} \operatorname{Re}\{ \sqrt{I} I^* \}$

in phase A:

$$P_{avg,A} = \frac{1}{2} \operatorname{Re}\{ \sqrt{I} I^* \}$$

$$= \operatorname{Re}\{ \sqrt{I_{eff}} I_{eff}^* \}$$

$$= \operatorname{Re}\{ 200 L^{0^\circ} \times 2 L^{-60^\circ} \}$$

$$\Rightarrow \operatorname{Re}\{ 400 L^{-60^\circ} \} \Rightarrow 400 \cos(-60^\circ) = 200 W$$

$$P_{avg,B} = 200 W$$

$$P_{avg,C} = 200 W$$

$$\therefore P_{avg,A} + P_{avg,B} + P_{avg,C} = 600 W$$