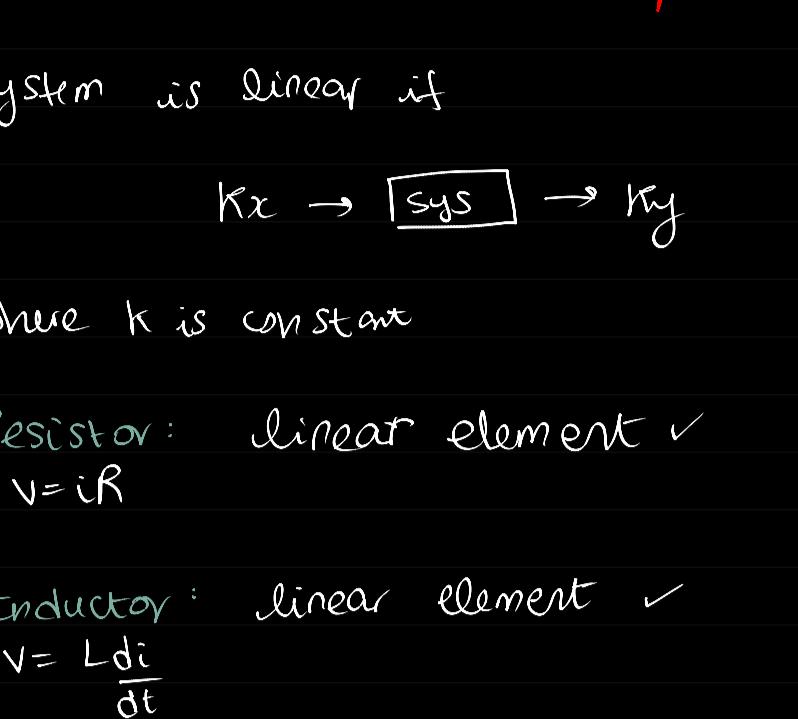


## Circuit Theory and Devices

Lab: LT Spice (2nd week onwards)

book: Engineering Circuit Analysis (9th edition)

Course: 9 modules chapter 10 onwards  
{continuation of BE3}

## \* Lecture: 1

⇒ Linear Circuits



System is linear if

$$Kx \rightarrow [\text{sys}] \rightarrow Ky$$

where K is constant

"R" Resistor: linear element ✓  
 $V = iR$ "L" Inductor: linear element ✓  
 $V = L \frac{di}{dt}$ "C" Capacitor: linear element ✓  
 $i = C \frac{dv}{dt}$ 


## \* Linear Electric Circuits:

consists of ⇒

① R, L, C → linear elements


② Independent voltage &amp; current sources

③ Linear dependent sources

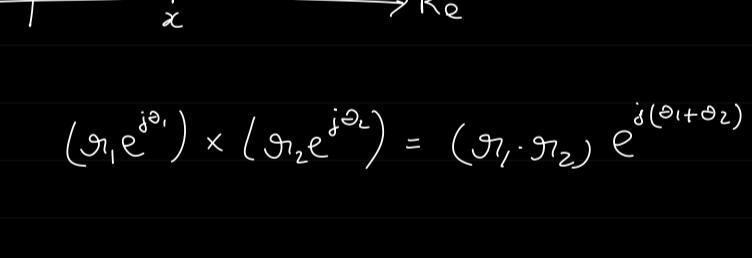

Note: diode and transistors are non-linear elements

## \* Response of a linear circuit

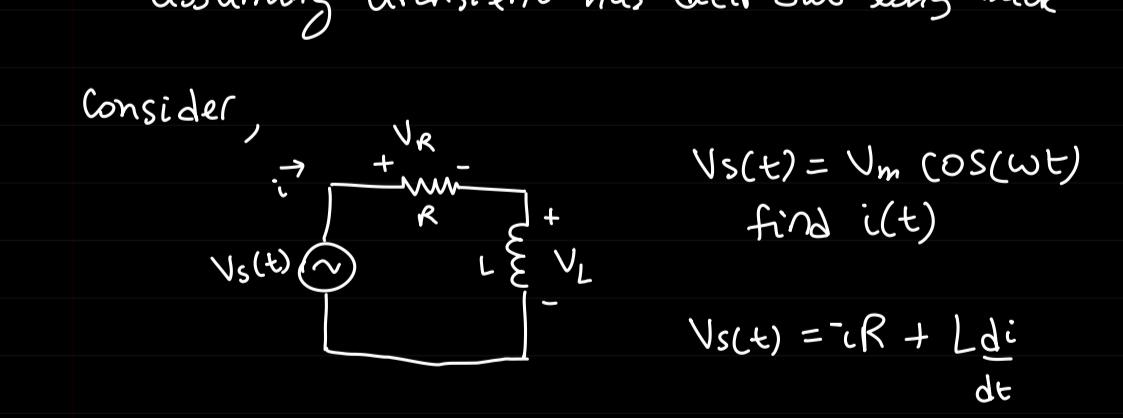① full response = transient response + steady state  
transient persists  $t \rightarrow \infty$ KVL :  $-Vs + iR + L \frac{di}{dt} = 0$ 

$$i_{\text{final}} = i_{\text{transient}} + i_{\text{steady state}}$$

$$\text{as } t \rightarrow \infty, i_{\text{final}} = i_{\text{steady state}}$$


## \* Sinusoids &amp; complex numbers

sinusoidally varying voltage source

$$V_s(t) = V_m \cos(\omega t)$$

$$V_s(t) = V_m \sin(\omega t)$$

$$V_s(t) = V_m \sin(\omega t + \phi)$$

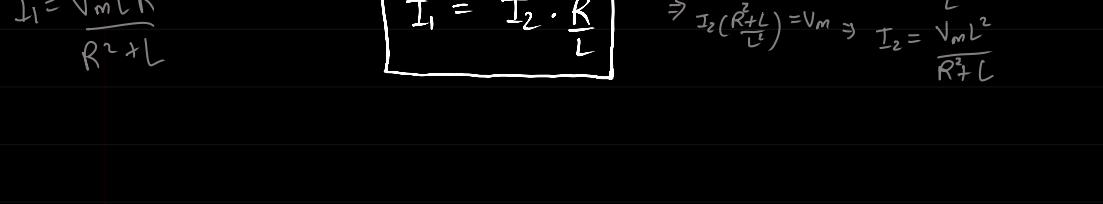

$$\Rightarrow \text{Euler's identity: } e^{j\theta} = \cos\theta + j\sin\theta$$

$$i_{\text{final}} = \frac{d}{dt} (I_1 \cos\omega t + I_2 \sin\omega t)$$

$$\Rightarrow \omega(I_1(-\sin\omega t) + I_2 \cos\omega t)$$

$$\Rightarrow \omega(I_2 \cos\omega t - I_1 \sin\omega t)$$

$$V_m \cos(\omega t) = (I_1 \cos\omega t + I_2 \sin\omega t)R + (I_2 R - I_1 L)$$

$$\Rightarrow (I_1 R + I_2 L - V_m) \cos(\omega t) + (I_2 R - I_1 L) \sin(\omega t) = 0$$

$$* \text{ at } t=0, (I_1 R + I_2 L - V_m) \cdot 1 + (I_2 R - I_1 L) \cdot 0 = 0$$

$$\boxed{I_1 R + I_2 L = V_m}$$

$$* \text{ at } t = \frac{\pi}{2\omega}, (I_1 R + I_2 L - V_m) \cdot 0 + (I_2 R - I_1 L) \cdot 1 = 0$$

$$\boxed{I_1 = I_2 \cdot \frac{R}{L}}$$

$$\Rightarrow \frac{I_1 R + I_2 L}{I_2 \cdot \frac{R}{L}} = V_m \Rightarrow \frac{I_1 R + I_2 L}{I_2 R} = V_m \Rightarrow I_2 = \frac{V_m L}{R(L+R)}$$

