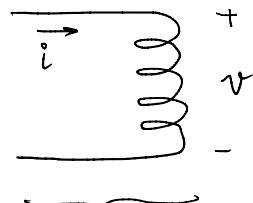


## Module 5

### Magnetically coupled circuits

(Chapter 13 of textbook)



"Pure linear inductors"  
→ no resistance

$$v = L \frac{di}{dt}$$


$i$  leads to magnetic flux  $i \propto \phi$

Magnetic flux leads to induced  $v$   $v \propto d\phi/dt \Rightarrow v \propto di/dt$

$$v = L \frac{di}{dt}$$

DC  $\rightarrow$  const  $i \rightarrow$  const mag. flux  $\rightarrow v = 0$


Mutual Inductance:

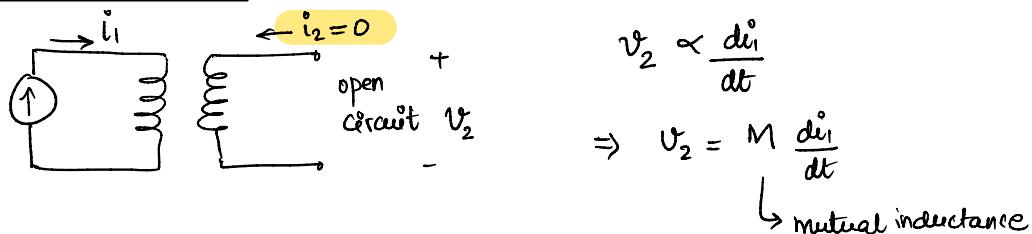


$L$ : self inductance

Henry

Now consider:  $i_2 \neq 0$

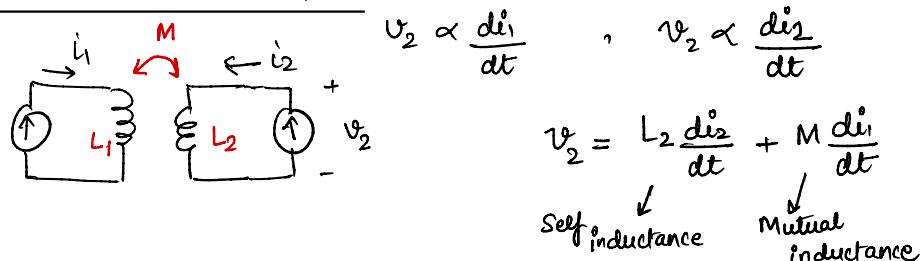

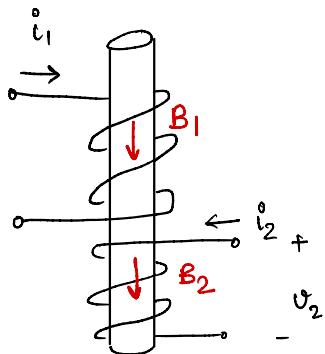


$$v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$B_2$        $B_1$


Top view



Additive magnetic flux

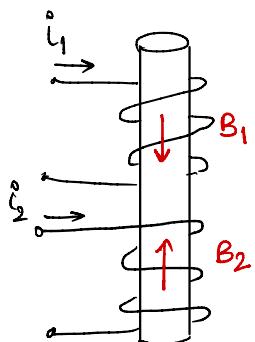


Top view

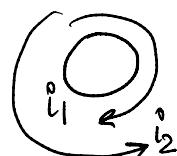


Subtractive magnetic flux
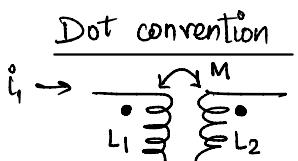
$$v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$




Assume  $i_2 = 0$

$$v_2 = M \frac{di_1}{dt}$$

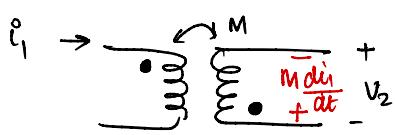


$$v_2 = -M \frac{di_1}{dt}$$

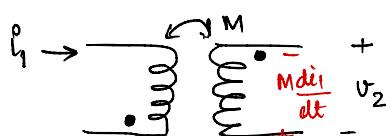} Current entering at dotted terminal leads to +ve voltage reference at dotted terminal.




$$v_2 = -M \frac{di_1}{dt}$$

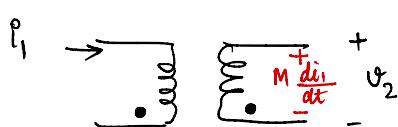

$$v_2 = M \frac{di_1}{dt}$$

} Current entering at undotted terminal leads to +ve voltage reference at undotted terminal.

Example :

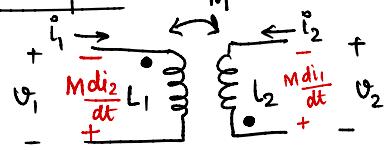

(A) find  $v_2$  if  $i_1 = -8e^{-t} A$ ,  $i_2 = 0$

$$v_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

0

$$v_2 = -M \frac{di_1}{dt} = -2 \frac{d}{dt} (-8e^{-t}) = -2 \times (-8) \times (-1) e^{-t}$$

$$= -16 e^{-t} V$$

(B) find  $v_1$  if  $i_1 = 0$  and  $i_2 = 5 \sin 45t A$ .

$$v_1 = \underbrace{L_1 \frac{di_1}{dt}}_0 - M \frac{di_2}{dt}$$

$$v_1 = -M \frac{d}{dt} (5 \sin 45t) = -2 \times 5 \times 45 \cos 45t$$

$$= -450 \cos 45t V$$

Sign Convention for self inductance:

$$v = L \frac{di}{dt}$$

(current entering from  
+ve terminal)

$$v = -L \frac{di}{dt}$$

(current leaving from  
+ve terminal)

Phasor Representation :

$$V_1 = L_1 \frac{di^*}{dt} + M \frac{di^*}{dt}$$

$$V_2 = L_2 \frac{di^*}{dt} + M \frac{di^*}{dt}$$

$$v = L \frac{di}{dt}$$

time domain

$$V = j\omega L I_1$$


freq.  
domain

for sinusoidally varying sources


$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega L_2 I_2 + j\omega M I_1$$


Example

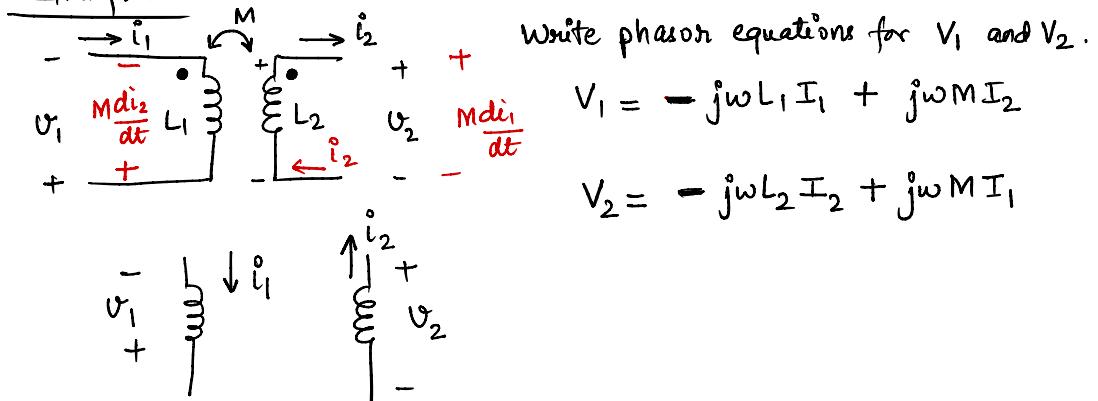

Example :-

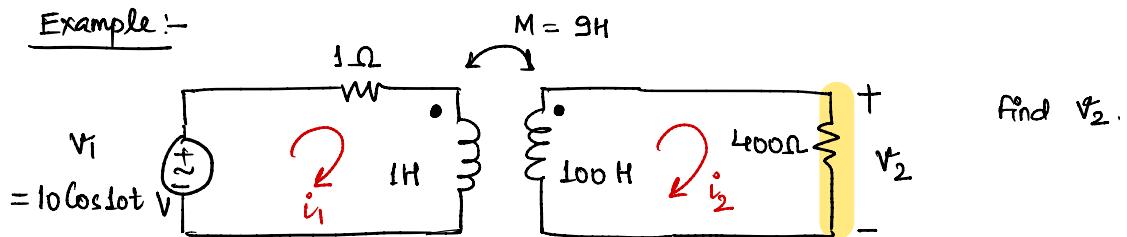


freq. domain representation

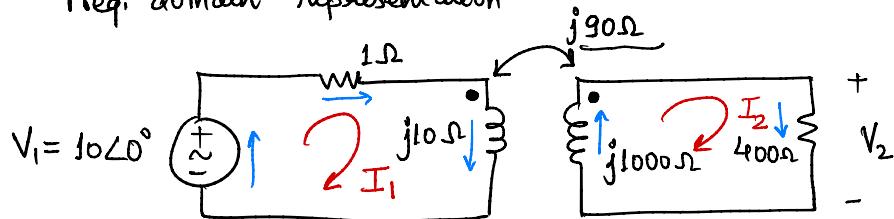

$$\text{Mesh 1: } -10\angle 0^\circ + I_1 (1) + (j10) I_1 - (j90) I_2 = 0$$
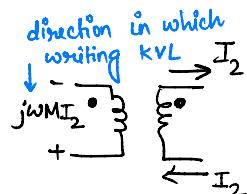
$$\Rightarrow 10\angle 0^\circ = (1 + j10) I_1 - j90 I_2$$



Last term

$$\text{Mesh 2: } -(-j1000)I_2 - (j90)I_1 + (400)I_2 = 0$$

$$\Rightarrow -j90I_1 + (400 + j1000)I_2 = 0$$

Always remember to put a minus sign if while writing KVL terms you encounter a -ve reference terminal first.



$$(1 + j10)I_1 - j90I_2 = 10$$

$$(-j90)I_1 + (400 + j1000)I_2 = 0$$

$$\text{Cramer's rule: } I_1 = \frac{D_1}{D_0}, \quad I_2 = \frac{D_2}{D_0}$$

$$D_0 = \begin{vmatrix} 1+j10 & -j90 \\ -j90 & 400 + j1000 \end{vmatrix}$$

$$D_1 = \begin{vmatrix} 10 & -j90 \\ 0 & 400 + j1000 \end{vmatrix}$$

$$D_2 = \begin{vmatrix} 1+j10 & 10 \\ -j90 & 0 \end{vmatrix}$$

$$V_2 = 400I_2$$