

Quick Recap


Node Analysis (using node-to-reference voltages)

Mesh Analysis (Mesh currents)

$(n-1)$

$(b - n + 1)$

Super node 

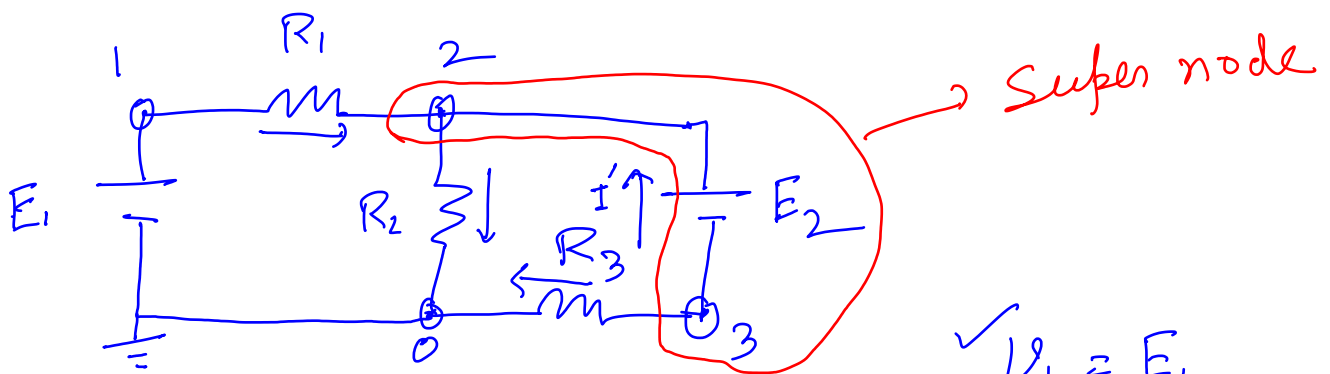

$$\checkmark V_1 = E_1$$

$$\frac{V_1 - V_2}{R_1} + I' = \frac{V_2}{R_2}$$

(KCL at node 2)


$$0 = \frac{V_3}{R_3} + I'$$

(KCL at node 3)

$$\checkmark V_2 - V_3 = E_2$$

$$\Rightarrow \checkmark \frac{V_1 - V_2}{R_1} - \frac{V_3}{R_3} = \frac{V_2}{R_2} \quad (\text{KCL at Super node})$$

Super Mesh

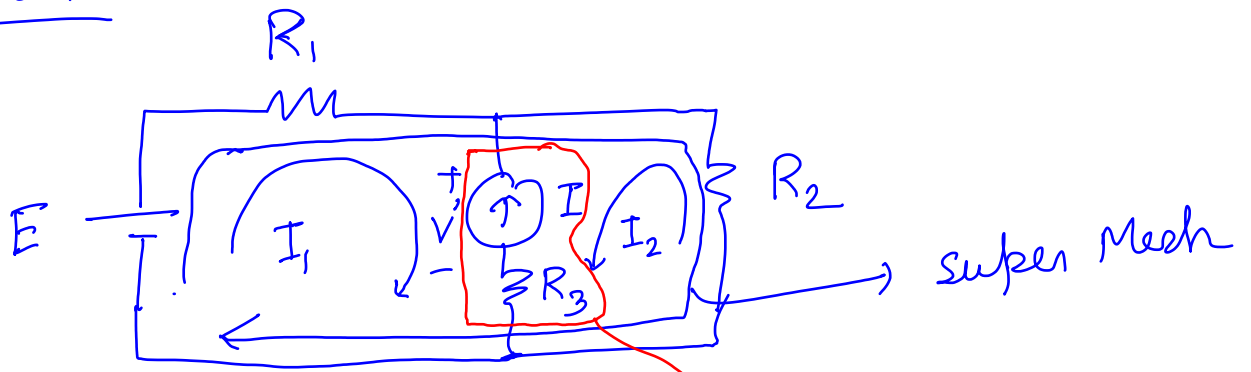

KVL for loop 1,

$$E = I_1 R_1 + \underbrace{V' + (I_1 + I_2) R_3}$$


KVL for loop 2,

$$0 = I_2 R_2 + \underbrace{V' + (I_1 + I_2) R_3}$$


$$E = I_1 R_1 - I_2 R_2 \rightarrow \text{(KVL for Super Mesh)}$$

$$I = -I_1 - I_2$$

Series Resistances


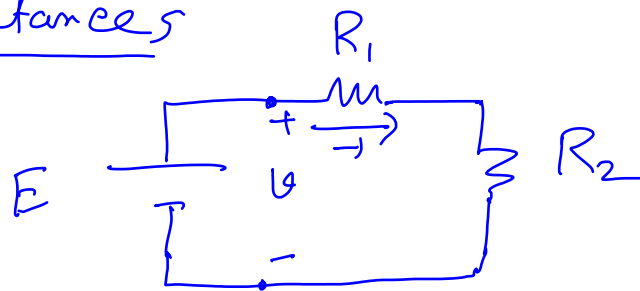


\Downarrow




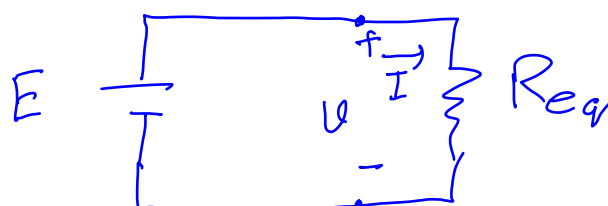



$$R_{eq} = R_1 + R_2$$

Parallel Resistances

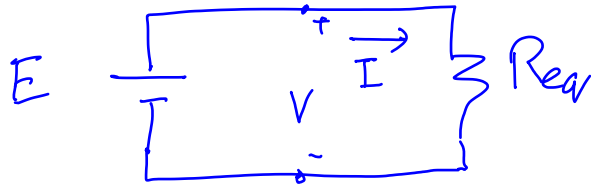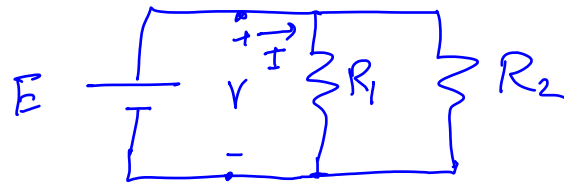

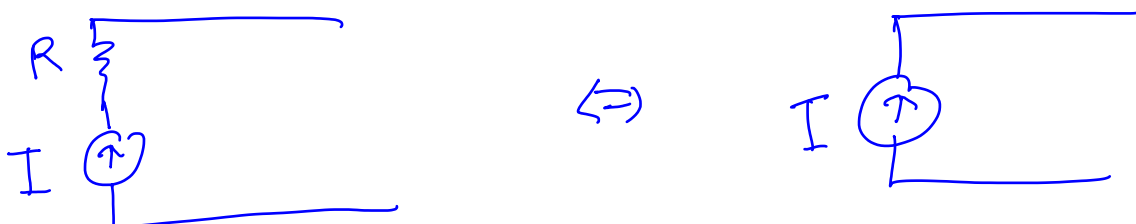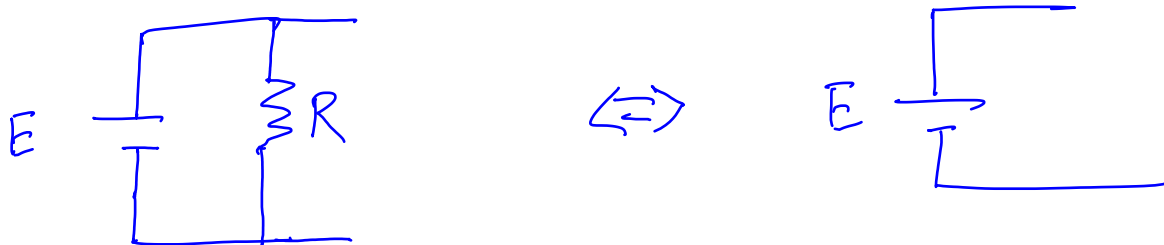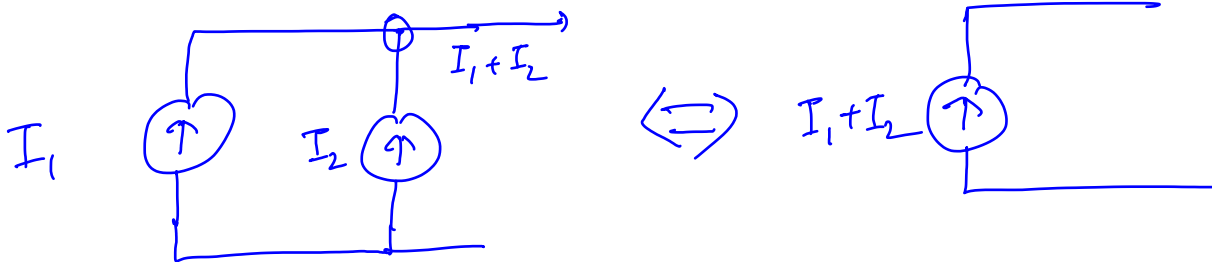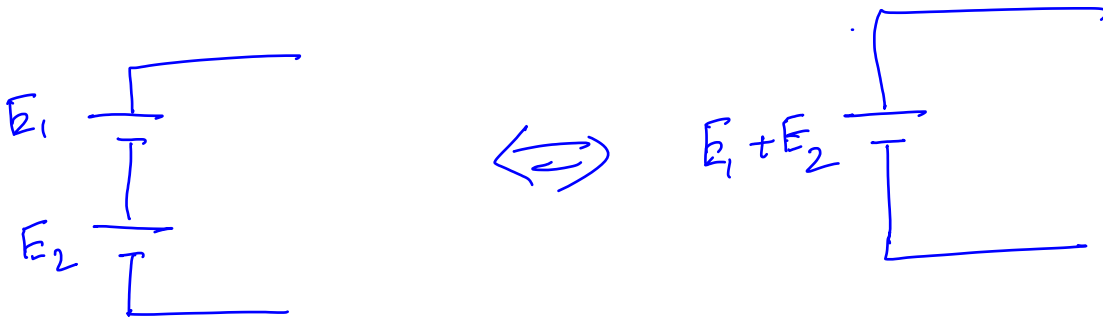
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



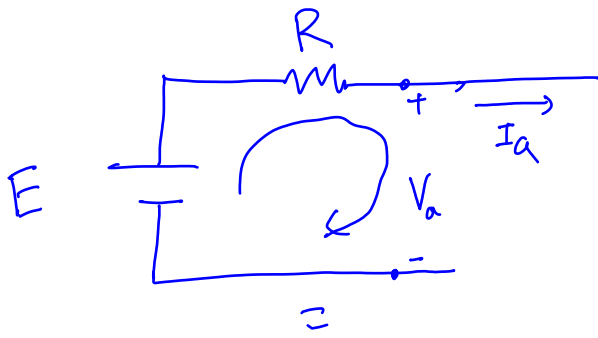




$$E = I_a R + V_a$$

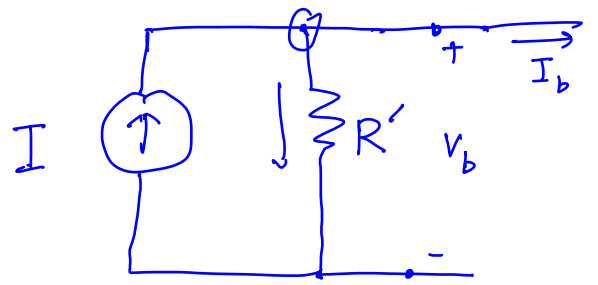

$$I = \frac{V_b}{R'} + I_b$$

For equivalence $I_a = I_b$ and $V_a = V_b$

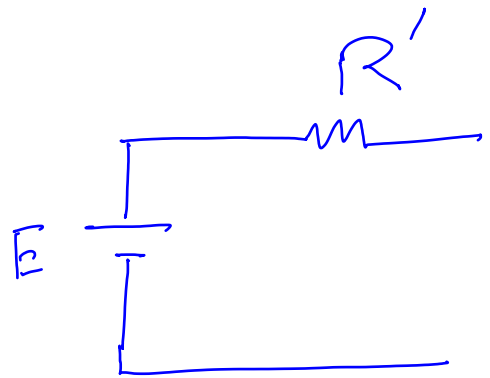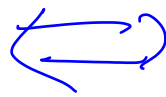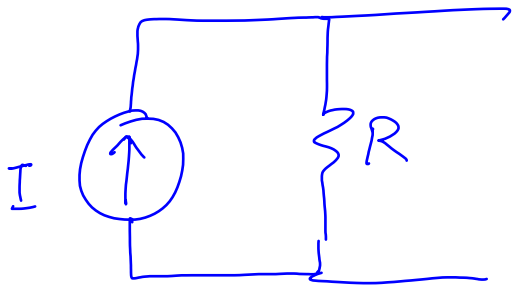
$$\left. \begin{aligned} I &= E/R \\ R' &= R \end{aligned} \right\}$$



$$R' = R$$


Superposition Principle

$$E = IR$$

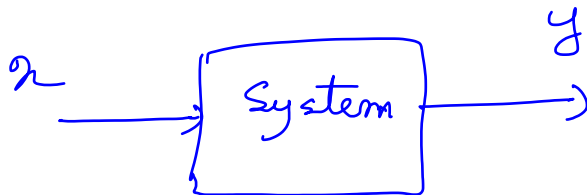

$$\left. \begin{aligned} x_1 &\longrightarrow y_1 \\ x_2 &\longrightarrow y_2 \end{aligned} \right\} \Rightarrow \alpha_1 x_1 + \alpha_2 x_2 \longrightarrow \alpha_1 y_1 + \alpha_2 y_2$$

The system is linear

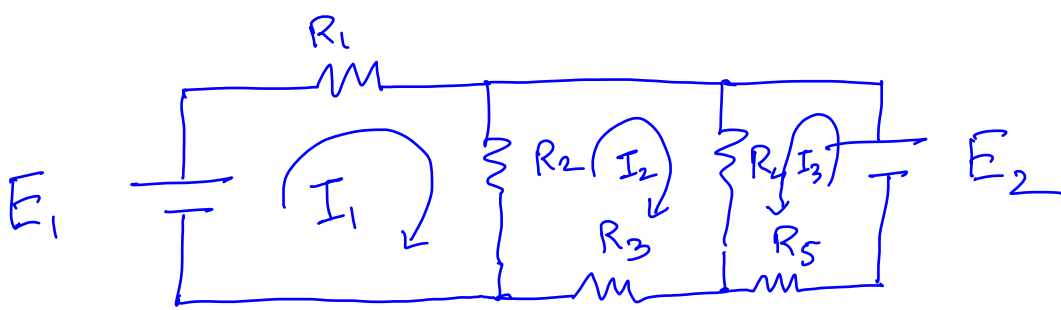

$$E_1 = I_1 R_1 + (I_1 - I_2) R_2$$

$$0 = -(I_1 - I_2) R_2 + (I_2 + I_3) R_4 + I_2 R_3$$

$$E_2 = (I_2 + I_3) R_4 + I_3 R_5$$

$$A x = b, \quad A \in \mathbb{R}^{3 \times 3}$$

$$x \in \mathbb{R}^{3 \times 1}$$

$$b \in \mathbb{R}^{3 \times 1}$$

$$x = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$A = \begin{bmatrix} R_1 + R_2 & -R_2 & 0 \\ -R_2 & R_2 + R_3 + R_4 & R_4 \\ 0 & R_4 & R_4 + R_5 \end{bmatrix} \quad b = \begin{bmatrix} E_1 \\ 0 \\ E_2 \end{bmatrix}$$

$$b = \begin{bmatrix} E_1 \\ 0 \\ E_2 \end{bmatrix} = \underbrace{\begin{bmatrix} E_1 \\ 0 \\ 0 \end{bmatrix}}_{b_1} + \underbrace{\begin{bmatrix} 0 \\ 0 \\ E_2 \end{bmatrix}}_{b_2}$$

$$A x = b = b_1 + b_2$$

$$x = \underbrace{A^{-1}b_1}_{x_1} + \underbrace{A^{-1}b_2}_{x_2} \left. \vphantom{\begin{matrix} A^{-1}b_1 \\ A^{-1}b_2 \end{matrix}} \right\} \begin{array}{l} \text{superposition} \\ \text{holds} \end{array}$$

\swarrow contribution from E_1 \swarrow contribution from E_2

$$Ax = b$$

there are "p" no. of independent sources.

$$b = \sum_{i=1}^p b_i$$

Example

$$b = \begin{pmatrix} E_1 - E_2 \\ 0 \\ E_3 \end{pmatrix} = \underbrace{\begin{pmatrix} E_1 \\ 0 \\ 0 \end{pmatrix}}_{b_1} - \underbrace{\begin{pmatrix} E_2 \\ 0 \\ 0 \end{pmatrix}}_{b_2} + \underbrace{\begin{pmatrix} 0 \\ 0 \\ E_3 \end{pmatrix}}_{b_3}$$

Superposition Theorem

Each branch current or voltage can be decomposed into contributions from individual independent current or voltage sources.

