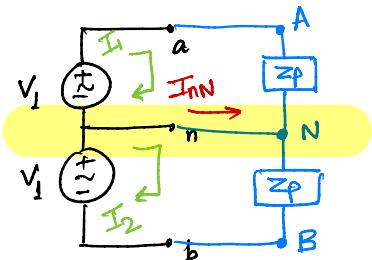


Review


Single-phase Three-wire sources (Two-phase)



$$V_1 = V_p \angle \theta^\circ$$

$$V_{an} = V_a - V_n = V_1 = V_p \angle \theta^\circ$$
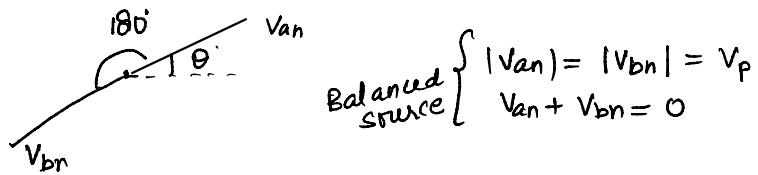
$$V_{bn} = -V_1 = -V_p \angle \theta^\circ = V_p \angle \theta^\circ - 180^\circ$$



$$I_{nN} = 0 \quad \leftarrow \text{when source and load are balance.}$$

Time-domain	freq. domain
$V_{an}(t) = V_p \cos(\omega t + \theta^\circ)$	$V_{an} = V_1 = V_p \angle \theta^\circ$
$V_{bn}(t) = V_p \cos(\omega t + \theta^\circ - 180^\circ)$	$V_{bn} = -V_1 = V_p \angle \theta^\circ - 180^\circ$



$$p(t) = V(t) i(t)$$

$$P_{avg} = V \cdot I \quad X$$

$$P_{avg} = \frac{1}{2} \operatorname{Re} \{ \underbrace{V \cdot I^*} \} \quad \checkmark$$

① Example : Consider $V_{12} = 9 \angle 30^\circ$, $V_{32} = 3 \angle 130^\circ$
 find $V_{21} = 9 \angle -150^\circ$, $V_{13} = V_{12} + V_{23}$

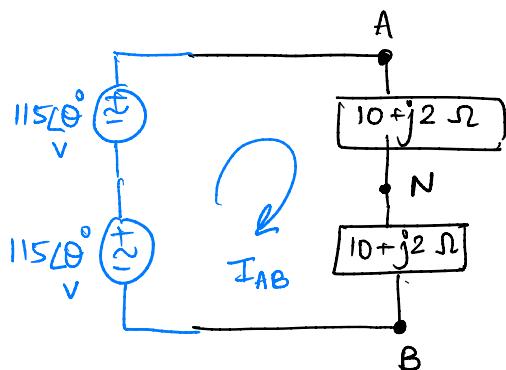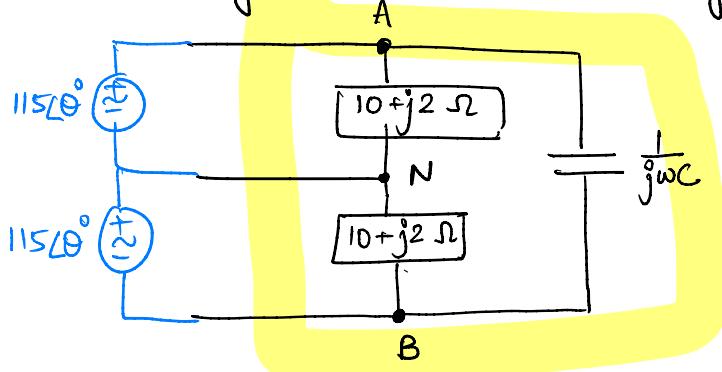② Consider a single-phase three-wire balanced source connected to a balanced load. $f = 50 \text{ Hz}$, $V_{an} = 115 \angle 0^\circ \text{ V}$
 → • Find power factor of the load if capacitor is omitted.
 • find value of C that will lead to a unity power factor of total load.



$$PF = \cos(\theta - \phi)$$


$$I_{AB} = \frac{115 \angle \theta^\circ + 115 \angle \theta^\circ}{2(10 + j2)} = \frac{230 \angle \theta^\circ}{2(10 + j2)}$$

$$= 11.27 \angle \theta^\circ - 11.3^\circ \text{ A}$$

$$\phi = \theta - 11.3^\circ$$

$$PF = \underbrace{\cos(\theta - \theta + 11.3^\circ)}_{\text{lagging}} = 0.98 \text{ lagging}$$
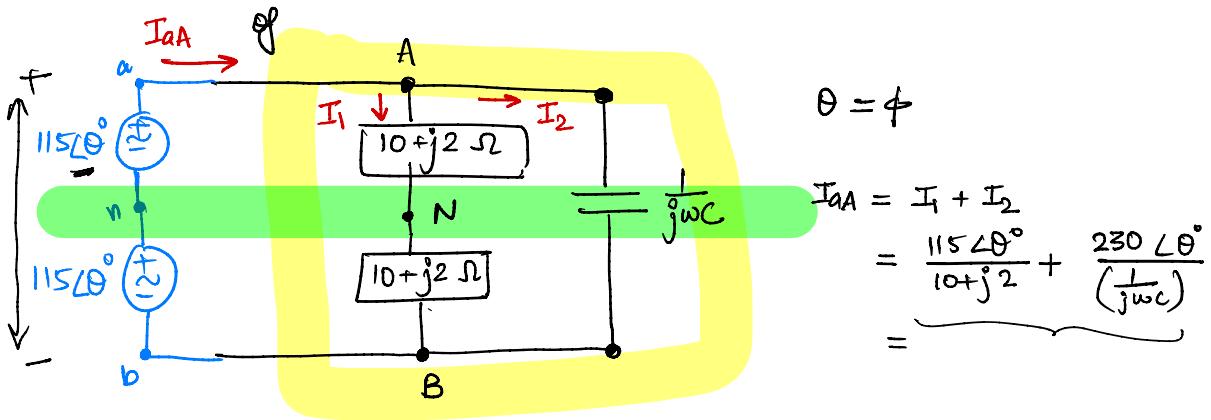
$$PF = 1 \Rightarrow \cos(\theta - \phi) = 1 \Rightarrow \theta - \phi = 0 \Rightarrow \theta = \phi$$



$$\theta = \phi$$

$$\begin{aligned} I_{AA} &= I_1 + I_2 \\ &= \frac{115 \angle 0^\circ}{10 + j2} + \frac{230 \angle 0^\circ}{(j\omega C)} \\ &= \underbrace{\quad}_{\text{ }} \end{aligned}$$

$$S = \text{Complex power of total load} = \frac{1}{2} VI^*$$

$$\text{PF} = \frac{\text{Re}\{S\}}{|S|} \Rightarrow \text{PF} = 1 \Rightarrow |S| = \text{Re}\{S\} \Rightarrow \boxed{\text{Im}\{S\} = 0}$$


$$\begin{aligned} S &= \frac{1}{2} V_{AN} I_{AN}^* + \frac{1}{2} V_{NB} I_{NB}^* + \frac{1}{2} V_{AB} I_{AB}^* \\ &= \frac{1}{2} V_{AN} \left(\frac{V_{AN}}{Z_p}\right)^* + \frac{1}{2} V_{NB} \left(\frac{V_{NB}}{Z_p}\right)^* + \frac{1}{2} V_{AB} \left(\frac{V_{AB}}{Z_c}\right)^* \\ &= \underbrace{\frac{1}{2} \frac{|V_{AN}|^2}{|Z_p|^2} Z_p}_{} + \underbrace{\frac{1}{2} \frac{|V_{NB}|^2}{|Z_p|^2} Z_p}_{} + \underbrace{\frac{1}{2} \frac{|V_{AB}|^2}{|Z_c|^2} Z_c}_{} \\ &= \frac{|V_{AN}|^2}{|Z_p|^2} Z_p + \frac{1}{2} \frac{|V_{AB}|^2}{|Z_c|^2} Z_c \end{aligned}$$

$Z_p = 10 + j2$
$Z_c = \frac{1}{j\omega C}$


$$S = \frac{115^2}{104} (10 + j2) + \frac{1}{2} \frac{(230)^2}{(j\omega C)^2} \left(\frac{-j}{\omega C}\right)$$

$$\text{Im}(S) = 0 \Rightarrow C = \frac{1}{\omega \times 104} = \frac{1}{100\pi \times 104} = 30.6 \mu F$$

Three-phase Sources

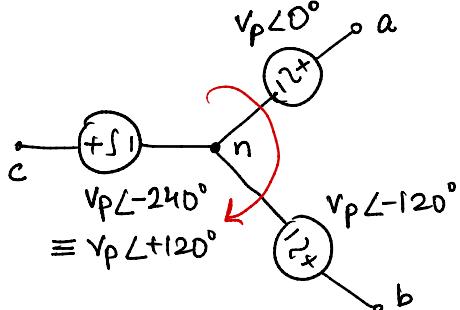

→ abc or positive sequence

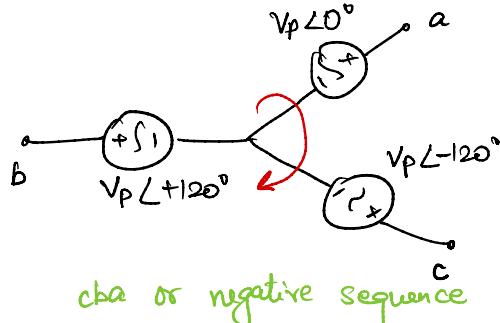

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle +120^\circ$$


$$\left\{ \begin{array}{l} |V_{an}| = |V_{bn}| = |V_{cn}| = V_p \\ V_{an} + V_{bn} + V_{cn} = 0 \end{array} \right.$$

Balanced source.

Balanced source

Phase voltages: V_{an} , V_{bn} , V_{cn}

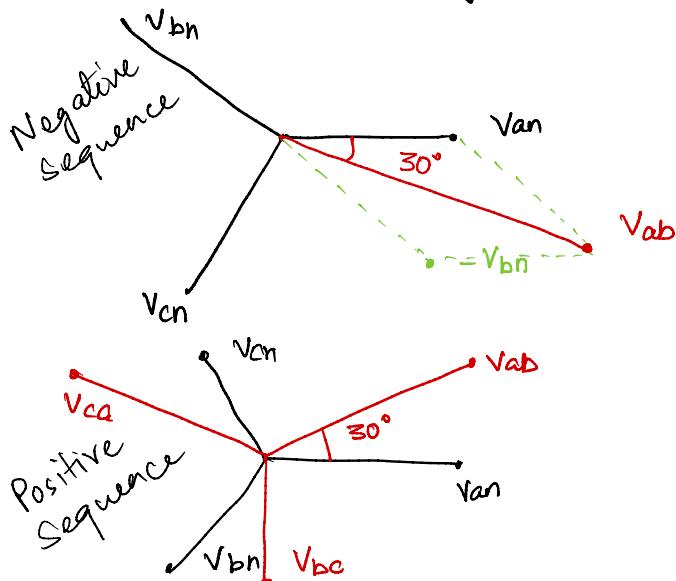Line-to-line or line voltages: V_{ab} , V_{bc} , V_{ca}





$$V_{ab} = V_{an} - V_{bn} = V_{an} + (-V_{bn})$$

$$V_L = \sqrt{3} V_p$$

$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} \\ &= V_{an} - V_{bn} \\ &= \sqrt{3} V_p \angle 30^\circ \end{aligned}$$
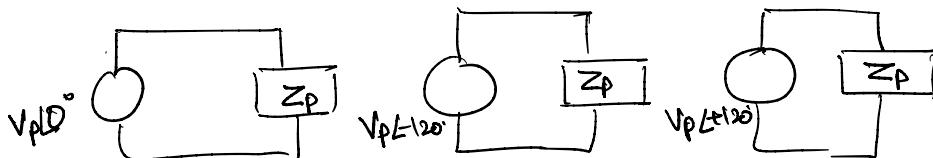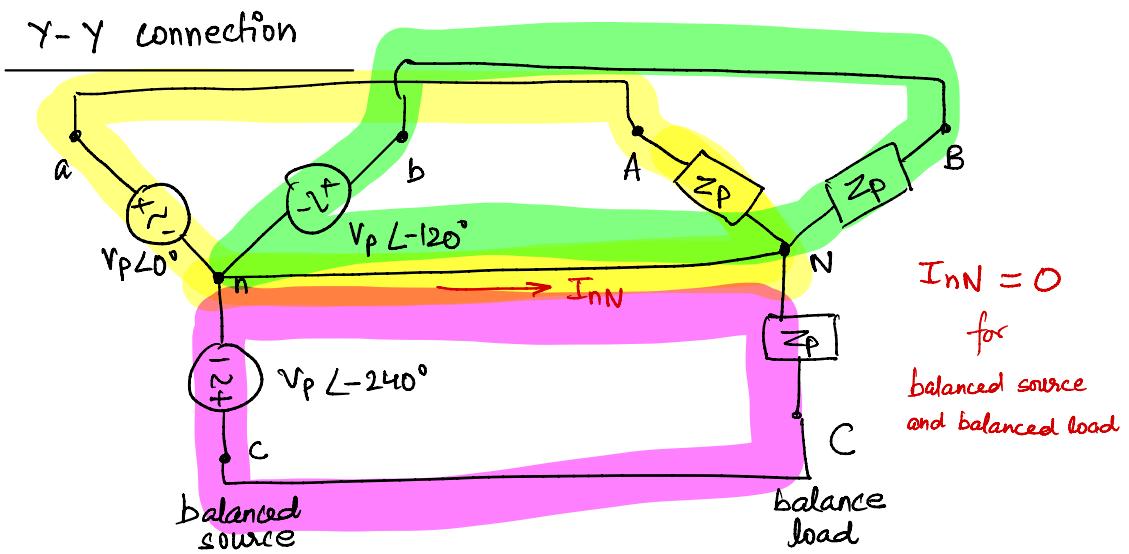
$$\begin{aligned} V_{bc} &= \sqrt{3} V_p \angle -90^\circ \\ V_{ca} &= \underbrace{\sqrt{3} V_p \angle -210^\circ}_{V_L} \end{aligned}$$



"per-phase" analyses

$$I_{AA} = \frac{V_{an}}{Z_p}$$

$$I_{BB} = \frac{V_{bn}}{Z_p} = \frac{V_{an} \angle -120^\circ}{Z_p} = I_{AA} \angle -120^\circ$$

$$I_{CC} = \frac{V_{cn}}{Z_p} = \frac{V_{an} \angle +120^\circ}{Z_p} = I_{AA} \angle +120^\circ$$

$$I_{nn} = I_{AA} + I_{BB} + I_{CC} = 0$$

$$V_{an} = V_p \angle 0^\circ$$

$$\begin{aligned} V_{bn} &= V_p \angle -120^\circ \\ &= V_{an} \angle -120^\circ \end{aligned}$$

$$= V_{an} (1 \angle -120^\circ)$$

Example : Consider three-phase balanced $\gamma - \gamma$ connected system.

$$V_{an} = 200 \angle 0^\circ \text{ V rms}$$

$$Z_p = 100 \angle 60^\circ \Omega$$

find phase and line voltages .

find phase and line currents.

find total average power delivered to load.

Phase Voltages :

$$V_{an} =$$

$$V_{bn} = 200 \angle -120^\circ \text{ Vrms}$$

$$V_{cn} = 200 \angle +120^\circ \text{ Vrms}$$

$$\text{line voltages: } V_{ab} = \sqrt{3} V_p \angle 30^\circ = 200\sqrt{3} \angle 30^\circ \text{ Vrms}$$

$$V_{bc} = 200\sqrt{3} \angle -90^\circ \text{ Vrms}$$

$$V_{ca} = 200\sqrt{3} \angle -210^\circ \text{ Vrms}$$

Line currents:


$$I_{aA} = \frac{V_{an}}{Z_p} = \frac{200 \angle 0^\circ}{100 \angle 60^\circ} = 2 \angle -60^\circ \text{ Arms}$$

$$I_{bB} = 2 \angle -120^\circ \text{ Arms}$$

$$I_{cC} = 2 \angle -300^\circ \text{ Arms}$$

Total Average power:

Average power in phase A

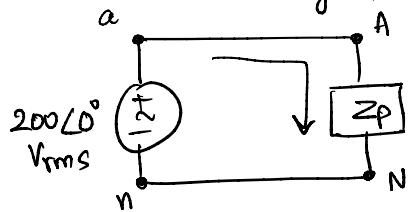

$$P_{avg, A} = \frac{1}{2} \operatorname{Re}\{VI^*\} = \operatorname{Re}\{V_{eff} I_{eff}^*\}$$

$$= \operatorname{Re}\{V_{an} I_{AN}\}$$

$$= \operatorname{Re}\{200 \angle 0^\circ \times 2 \angle -60^\circ\} \text{ W}$$

$$= \operatorname{Re}\{400 \angle -60^\circ\}$$

$$= 400 \cos(-60^\circ)$$

$$= 200 \text{ W}$$

$$P_{avg, B} = 200 \text{ W}$$

$$P_{avg, C} = 200 \text{ W}$$

$$P_{avg, \text{total}} = 600 \text{ W.}$$