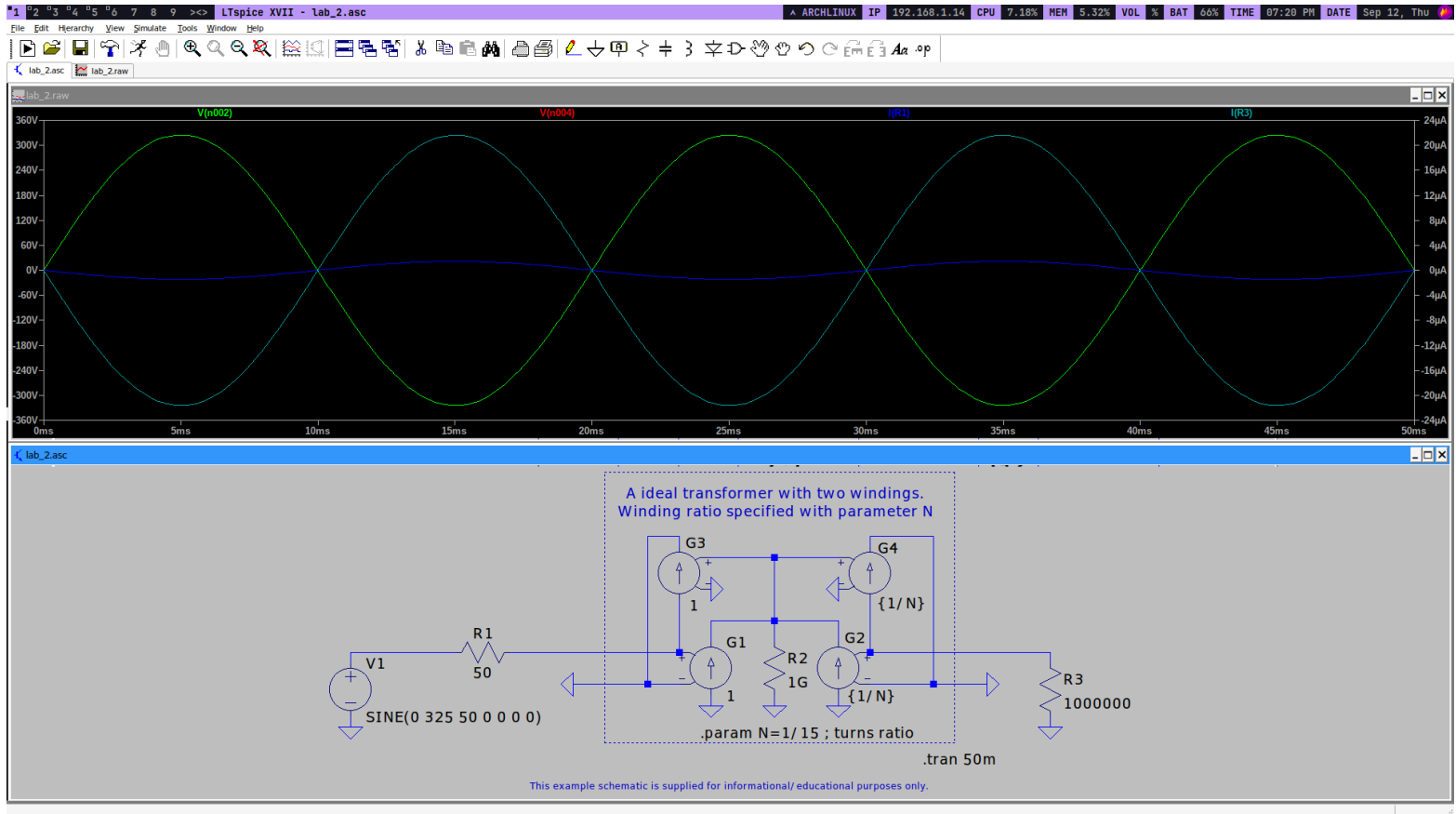


CTD LAB 2

Aditya Gautam 2023043

- Ideal Transformer (case 1)



- Non Ideal Transformer (case 2)

