
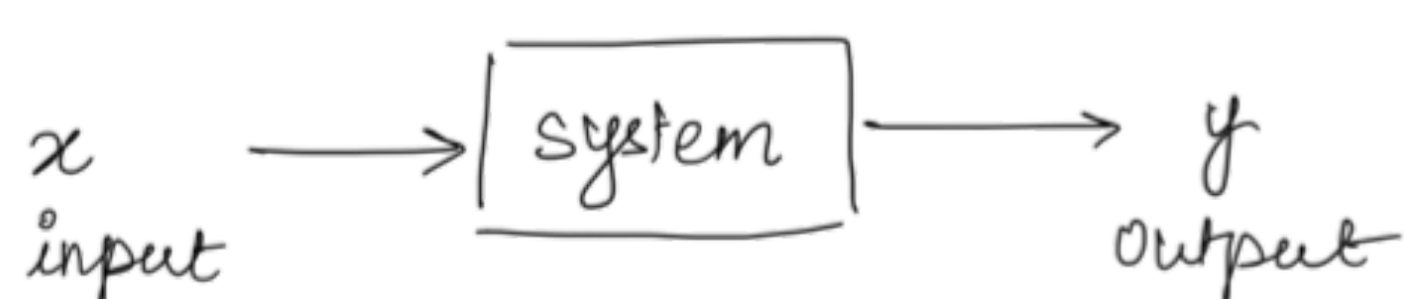


Linear Circuit

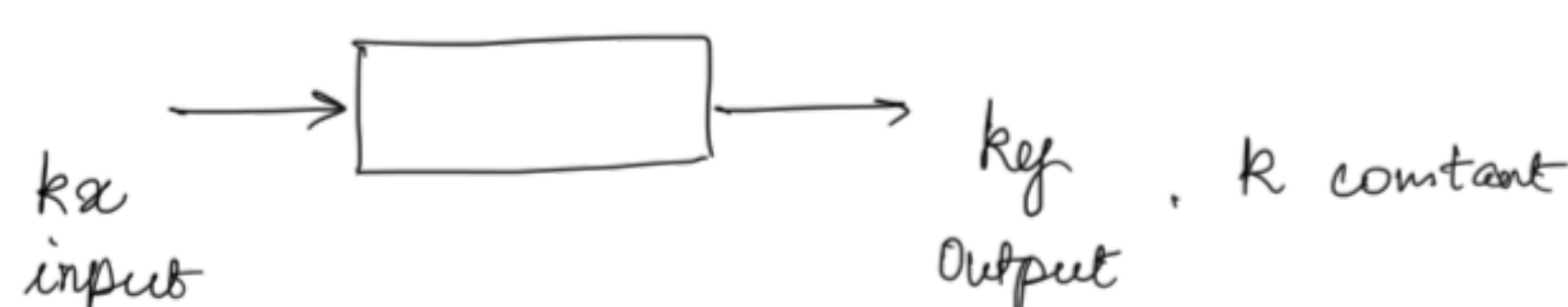

System is linear if



Resistor "R" : $v = iR$

Inductor "L" : $v = L \frac{di}{dt}$


Capacitor "C" : $i = C \frac{dv}{dt}$

$$\begin{pmatrix} v_1 & i_1 \\ kv_1 & ki_1 \end{pmatrix} \rightarrow v = A \left(\frac{di}{dt} \right)^2$$

Linear Electric Circuits

consists of

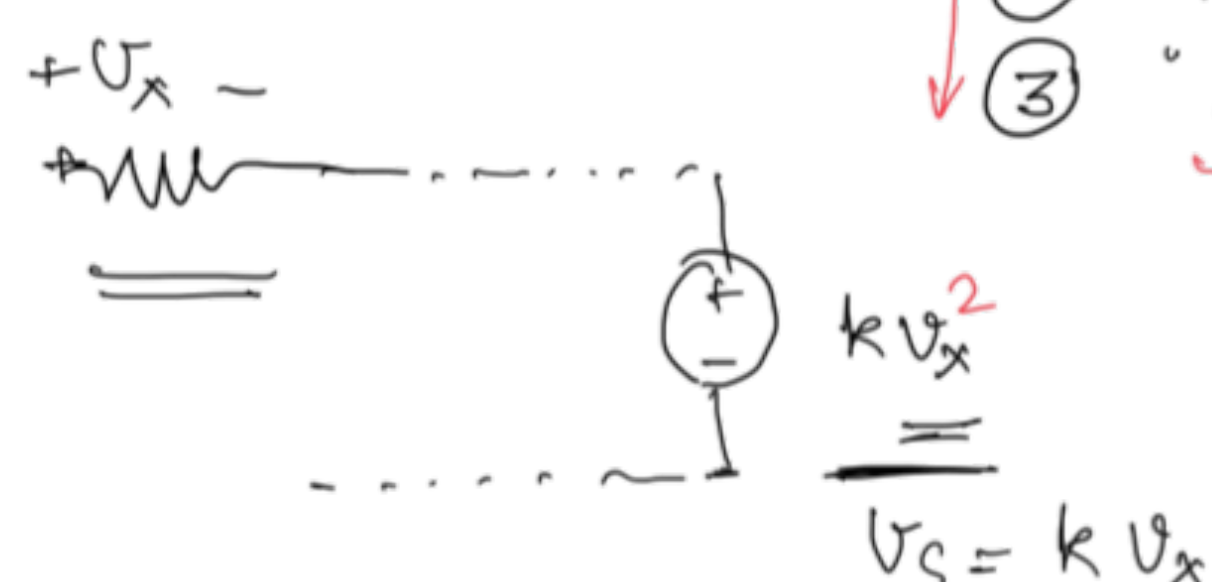
- ① R, L, C linear elements
- ② Independent voltage/current sources
- ③ "Linear" dependent sources.



Response of a linear circuit

→ full response = transient + steady-state

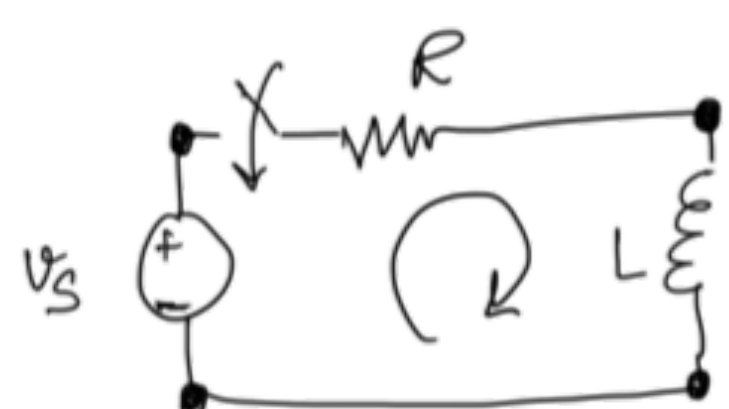- due to sudden change
- natural response
- R, L, C
- due to source
- forced response
- v_s, i_s



$$-v_s + iR + L \frac{di}{dt} = 0$$

$$i = i_{\text{transient}} + i_{\text{steady-state}}$$

$$t \rightarrow \infty \quad i = i_{\text{steady-state}}$$


Sinusoids and complex number

Sinusoidally varying voltage source

$$v_s(t) = V_m \cos(\omega t)$$

$$v_s(t) = V_m \sin(\omega t)$$

$$v_s(t) = V_m \sin(\omega t + \phi)$$

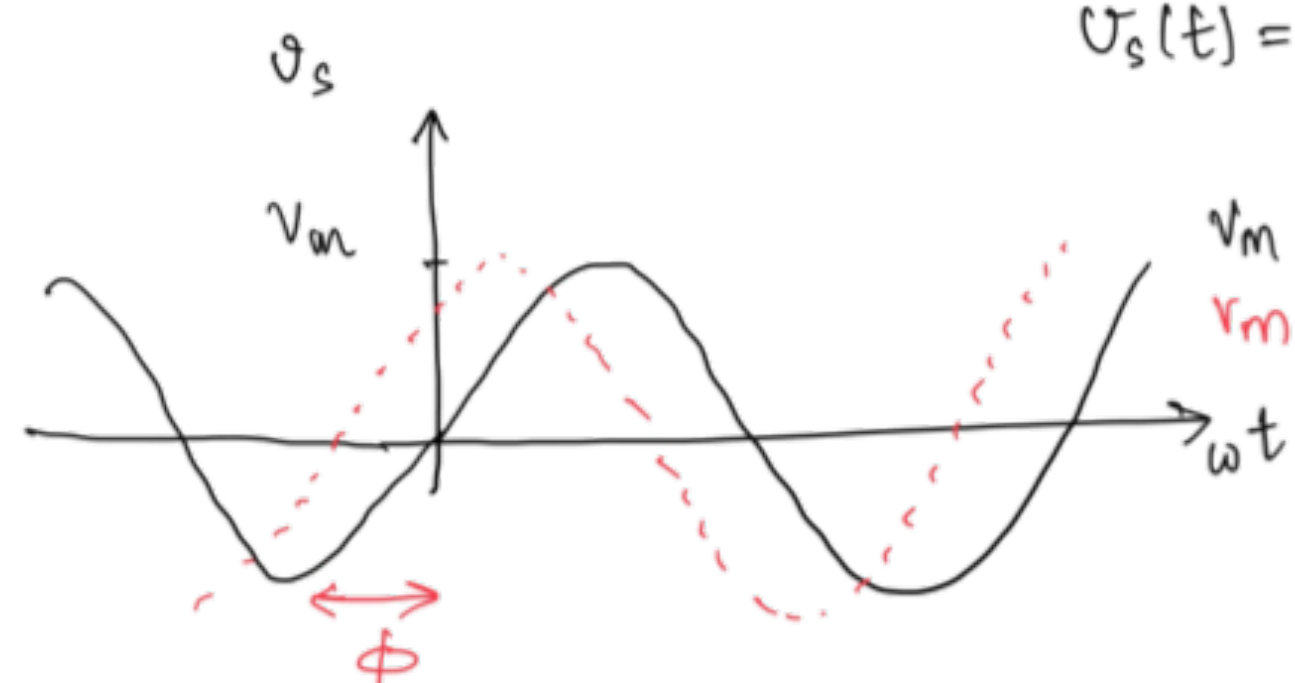

$V_m \sin(\omega t)$ is leading $V_m \sin(\omega t + \phi)$ by angle ϕ .
 $V_m \sin(\omega t + \phi)$ is lagging $V_m \sin(\omega t)$ by angle ϕ .

$$\sin(\omega t + 45^\circ) \xrightarrow{\times \frac{\pi}{180}} \sin(\omega t + \frac{\pi}{4}) \text{ radians}$$

$$\sin(-\theta) = -\sin \theta$$

$$\cos(-\theta) = +\cos \theta$$

$$\sin(A+B) = \sin A \cos B + \cos A \sin B$$

$$\cos(A+B) = \cos A \cos B - \sin A \sin B$$

sin +ve | All +ve
 tan +ve | cos +ve
 All silver tea cups

Complex Number

Real : x


Complex numbers : $x + jy \equiv x + jy$; $j = \sqrt{-1}$

rectangular form

$$\text{Euler's Identity: } e^{j\theta} = \underbrace{\cos \theta}_{\text{exp}} + \underbrace{j \sin \theta}_{\text{rect.}}$$

Complex No.

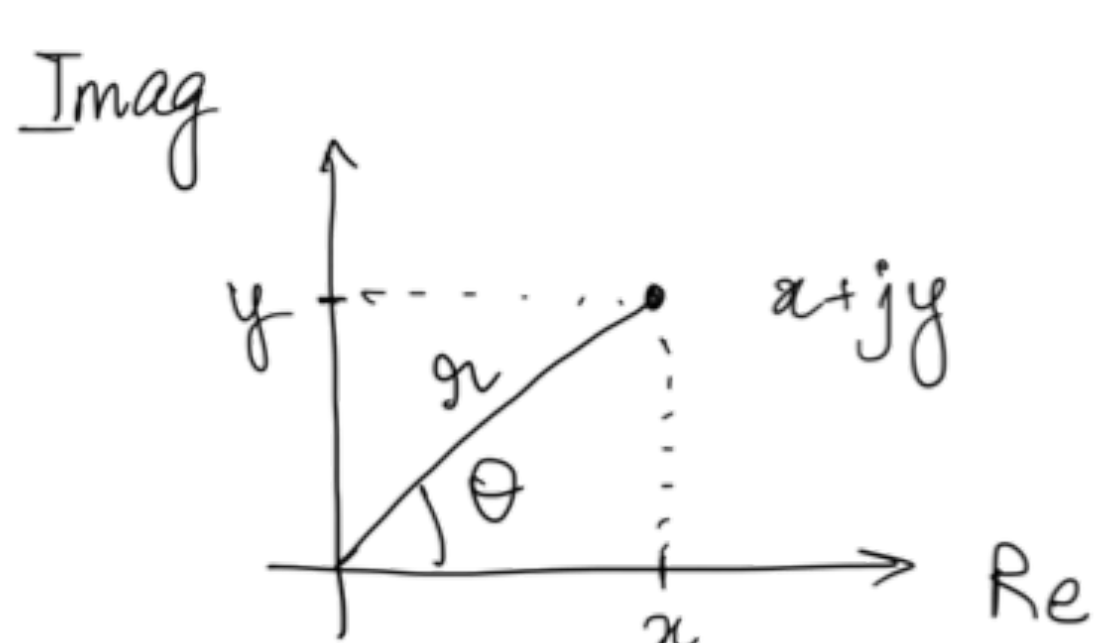rectangular: $x + jy$
 exponential: $x e^{j\theta}$
 (polar form: $x \angle \theta$)



$$r = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1}(y/x)$$

$$(r_1 e^{j\theta_1}) \times (r_2 e^{j\theta_2}) = (r_1 r_2) e^{j(\theta_1 + \theta_2)}$$


$$\frac{A + jB}{C + jD} \times \frac{C - jD}{C - jD} = \frac{(A + jB)(C - jD)}{C^2 + D^2}$$

Module 1

Sinusoidal steady-state Analysis

assuming transient has died out long back.

Consider

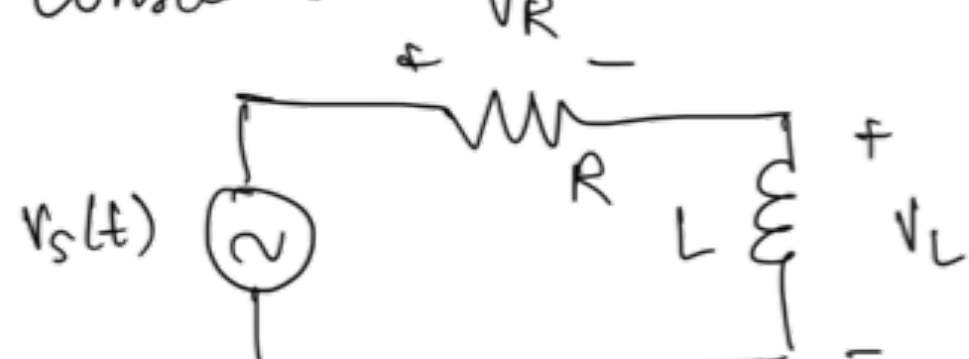

$$v_s(t) = V_m \cos(\omega t)$$

Find $i(t)$

$$v_s(t) = iR + L \frac{di}{dt}$$

$$\Rightarrow V_m \cos(\omega t) = iR + L \frac{di}{dt}$$

$$\text{General form solution: } i = I_1 \cos \omega t + I_2 \sin \omega t$$

$$\Rightarrow V_m \cos(\omega t) = (I_1 R + \omega L I_2) \cos \omega t + (R I_2 - \omega L I_1) \sin \omega t$$

$$\Rightarrow \underbrace{(I_1 R + \omega L I_2 - V_m)}_0 \cos \omega t + \underbrace{(R I_2 - \omega L I_1)}_0 \sin \omega t = 0$$

$$\left. \begin{aligned} I_1 R + \omega L I_2 - V_m &= 0 \\ R I_2 - \omega L I_1 &= 0 \end{aligned} \right\}$$