

tr5frbj

12/08/24

Circuit Theory and Devices

Lab: LT Spice (2nd week onwards)


Book: Engineering Circuit Analysis (9th edition)

Relative grading	Labs	20%
every 2 weeks	Quiz	20%
scientific calc	Mid sem End sem	30% 30%

Course: 9 modules (chapter 10 onwards)
(continuation of B3)

* Lecture: 1

⇒ Linear Circuits

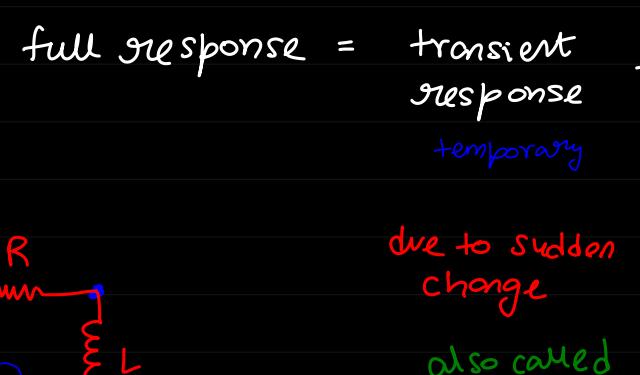

System is linear if

$$Kx \rightarrow \boxed{\text{sys}} \rightarrow Ky$$

where K is constant

"R" Resistor: linear element ✓
 $V = iR$

"L" Inductor: linear element ✓
 $V = L \frac{di}{dt}$

"C" Capacitor: linear element ✓
 $i = C \frac{dv}{dt}$


* Linear Electric Circuits:

consists of ⇒

① R, L, C → linear elements

② Independent voltage & current sources


③ linear dependent sources

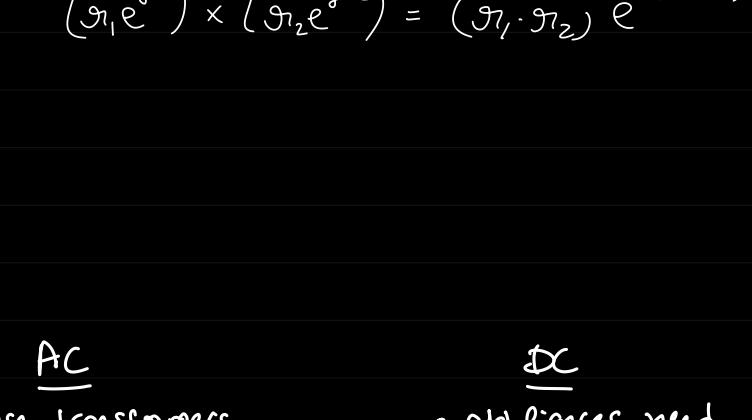

Note: diode and transistors are non-linear elements

* Response of a linear circuit

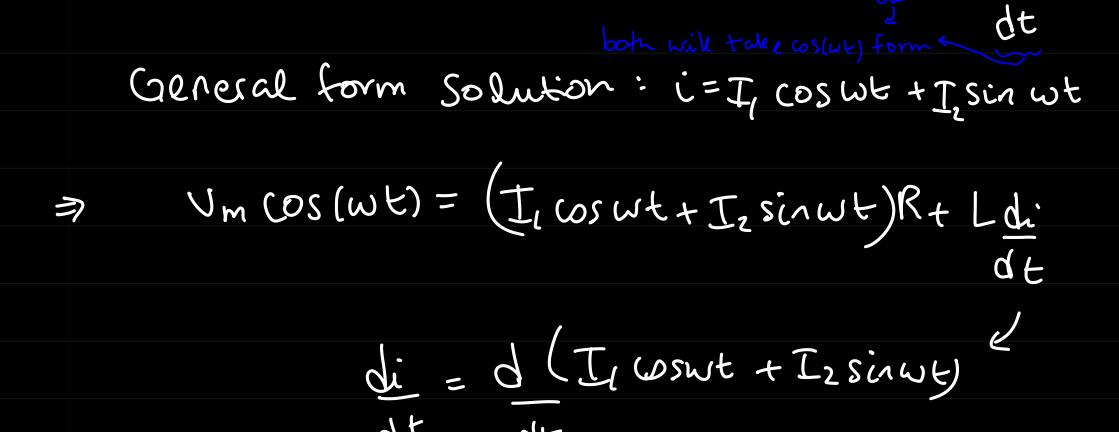① full response = transient response + steady state
transient persists $t \rightarrow \infty$



$$i_{\text{final}} = i_{\text{transient}} + i_{\text{steady state}}$$

$$\text{as } t \rightarrow \infty, i_{\text{final}} = i_{\text{steady state}}$$


* Sinusoids & complex numbers

Sinusoidally varying voltage source

$$V_s(t) = V_m \cos(\omega t)$$

$$V_s(t) = V_m \sin(\omega t)$$

$$V_s(t) = V_m \sin(\omega t + \phi)$$

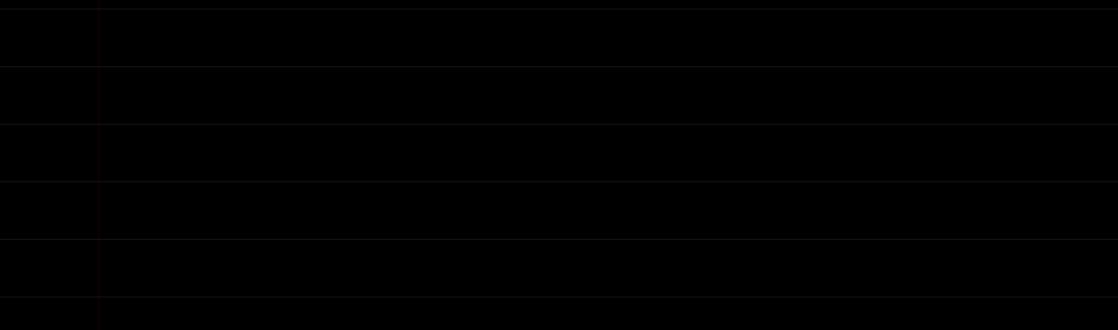

$$\Rightarrow \text{Euler's identity: } e^{j\theta} = \cos\theta + j\sin\theta$$

$$\text{rectangular form: } x + iy$$

$$\text{real part: } x, \text{ imaginary part: } y$$

$$y = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1}\left(\frac{y}{x}\right)$$

$$(i_1 e^{j\theta_1}) \times (i_2 e^{j\theta_2}) = (i_1 i_2) e^{j(\theta_1 + \theta_2)}$$

$$V_m \cos(\omega t) = (I_1 \cos\omega t + I_2 \sin\omega t) R + (I_2 \cos\omega t - I_1 \sin\omega t) L$$

$$\Rightarrow (I_1 R + I_2 L - V_m) \cos(\omega t) + (I_2 R - I_1 L) \sin(\omega t) = 0$$

$$\Rightarrow \cos\omega t \cdot (I_1 R + I_2 L - V_m) + \sin\omega t \cdot (I_2 R - I_1 L) = 0$$

$$\boxed{I_1 R + I_2 L = V_m}$$

$$\boxed{I_1 = I_2 \cdot \frac{R}{L}}$$