

$p(t)$

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) \quad \checkmark$$

$$P_{avg} = \operatorname{Re} \left\{ \frac{V I^*}{2} \right\}$$


$$v(t) = V_m \cos(\omega t + \theta)$$

$$v(t) = \operatorname{Re} \left\{ V_m e^{j\omega t + j\theta} \right\}$$

$$e^{j\omega t}$$

$$V = V_m \angle \theta$$


Example

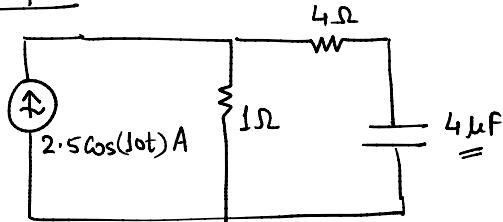

① Find power delivered to each element at $t = 0, 10, 20$ ms

② Find average power delivered to each element.

In frequency domain

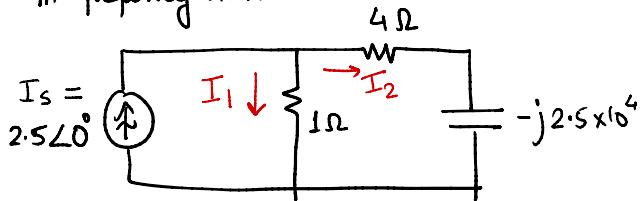

Power delivered to 1Ω

$$P_{1\Omega}(t) = V_{1\Omega}(t) i_{1\Omega}(t)$$

$$I_{1\Omega} = I_1 = I_S \frac{\frac{4-j2.5 \times 10^4}{1+4-j2.5 \times 10^4}}{\approx I_S \Rightarrow i_{1\Omega}(t) = 2.5 \cos(10t) A}$$

$$V_{1\Omega} = (I_1)(1\Omega) \Rightarrow V_{1\Omega}(t) = 2.5 \cos(10t) V$$

$$P_{1\Omega}(t) = 2.5 \cos(10t) \cdot 2.5 \cos(10t)$$

$$P_{1\Omega}(t) = 3.125 + 3.125 \cos(20t) \text{ Watts}$$

$$P_{1\Omega}(t=0) = 6.25 \text{ W}$$

$$P_{1\Omega}(t=10\text{ms}) = 6.1877 \text{ W}$$

$$P_{1\Omega}(t=20\text{ms}) = 6.0033 \text{ W}$$

Average power delivered to 1Ω

$$P_{avg, 1\Omega} = 3.125 \text{ W}$$

Power delivered to 4Ω :-

$$P_{4\Omega}(t) = V_{4\Omega}(t) \cdot i_{4\Omega}(t)$$

$$I_{4\Omega} = I_2 = I_s \frac{1}{S - j2.5 \times 10^4} = 10^4 \angle 90^\circ A \rightarrow i_{4\Omega}(t)$$

$$V_{4\Omega} = 4(I_{4\Omega}) = 4 \times 10^4 \angle 90^\circ V \rightarrow v_{4\Omega}(t)$$

$$P_{4\Omega}(t) = 2 \times 10^{-8} + 2 \times 10^{-8} \cos(20t) W$$

$$P_{4\Omega}(t=0) = 4 \times 10^{-8} W$$

$$P_{4\Omega}(t=10ms) = 3.96 \times 10^{-8} W$$

$$P_{4\Omega}(t=20ms) = 3.84 \times 10^{-8} W$$

$$P_{avg, 4\Omega} = 2 \times 10^{-8} W$$

Power delivered to capacitor :-

$$P_C(t) =$$

$$P_{avg, C} =$$

$$I_c = I_2 = 10^4 \angle 90^\circ A \leftarrow \rightarrow i_c(t) \Rightarrow p(t) = i_c(t)v_c(t) \checkmark$$

$$V_c = (j2.5 \times 10^4) I_2 = 2.5 V \rightarrow v_c(t)$$

$$\underbrace{i_c \times v_c}_{\text{Phasor of power}} \rightarrow p(t)$$

$$i_c(t) = 10^4 \cos(10t + 90^\circ)$$

$$v_c(t) = 2.5 \cos(10t)$$

$$P_C(t) = 1.25 \times 10^{-4} \cos(20t + 90^\circ) W$$


$$P_C(t=0) = 0 W$$

$$P_C(t=10ms) = 2.48 \times 10^{-5} W$$


$$P_C(t=20ms) = 4.86 \times 10^{-5} W$$

$$P_{avg, C} = 0$$

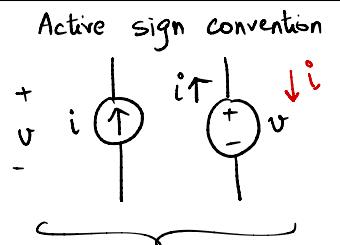
- ① $P_{1\Omega}(t) + P_{4\Omega}(t) + P_C(t) = \text{constant 1}$ X
- ② $P_{\text{avg}, 1\Omega} + P_{\text{avg}, 4\Omega} + P_{\text{avg}, C} = \text{constant 2}$ \checkmark $= P_{\text{avg, source}}$



$$v \cdot i = -20 \text{ W}$$

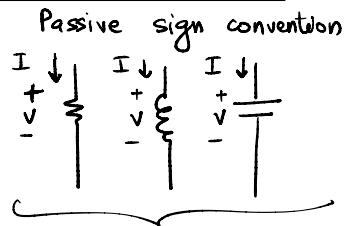



Maximum Power Transfer :

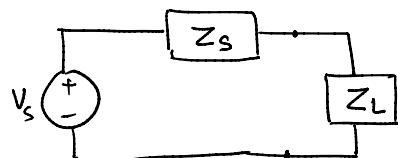

$$R_s = R_L$$

Max power delivered to load ,
when $Z_L = Z_s^*$

Impedance Matching :-

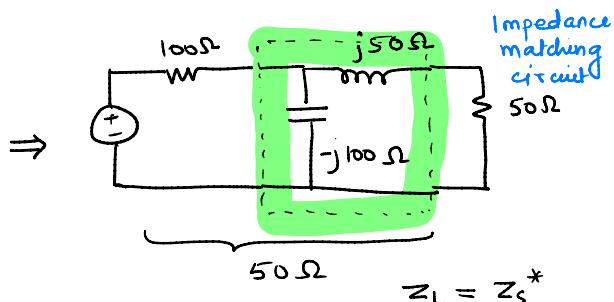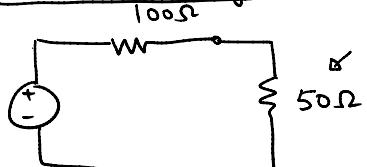

$$Z_L = Z_s^*$$

Effective value (RMS value) of voltage and current:-

$$v(t) \xrightarrow{i(t)} R \quad \xrightarrow{V_{\text{eff}}} \quad I_{\text{eff}} \xrightarrow{R}$$

$$v(t) \leftarrow P_{\text{avg}} = P_{\text{avg}}$$

$$\Rightarrow \frac{1}{T} \int_0^T i^2(t) R dt = I_{\text{eff}}^2 R = \frac{V_{\text{eff}}^2}{R}$$

$$\Rightarrow I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \text{Root mean square}$$

Sinusoidally varying sources

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \phi) dt}$$

$$I_{\text{eff}} = \frac{I_m}{\sqrt{2}}$$

$2 \cos^2 x = \cos 2x + 1$

$$T = \frac{2\pi}{\omega} = \frac{1}{f}$$

Suppose, $I = 10 \angle 90^\circ A$

$$\Rightarrow I = \underbrace{\frac{10}{\sqrt{2}}}_{\text{rms}} \angle 90^\circ A \text{ rms}$$

$$V_{\text{eff}} = \frac{V_m}{\sqrt{2}} \text{ rms value}$$

$$V_1 = 100 \angle -60^\circ V \text{ rms}$$

$$V_1 = 100\sqrt{2} \angle -60^\circ V$$

Apparent Power

$$P_{\text{apparent}} = I_{\text{eff}} V_{\text{eff}}$$

Power factor

$$\text{PF} = \frac{\text{average power}}{\text{apparent power}} = \frac{(V_m I_m / 2) \cos(\theta - \phi)}{V_{\text{eff}} I_{\text{eff}}} = \cos(\theta - \phi)$$

$$\text{PF} = \underbrace{\cos(\theta - \phi)}_{\text{Power factor angle}}$$