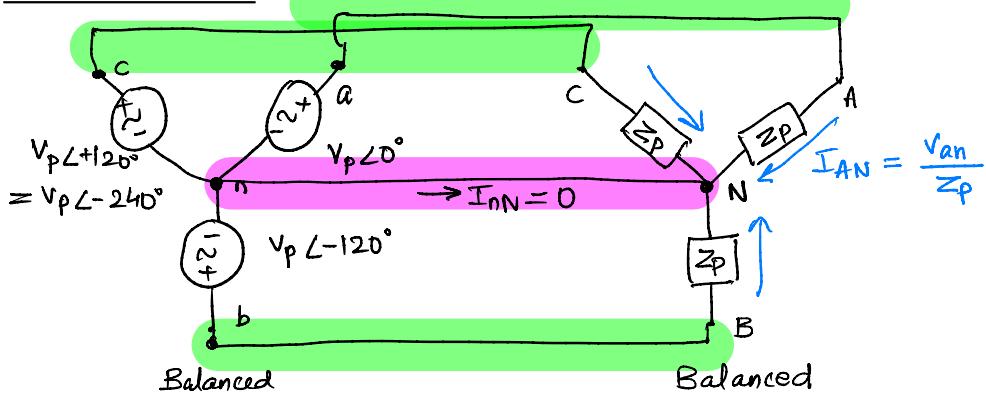


### Three phase systems

Y-Y connection

"star-star" connection



Phase Voltages :  $V_{AN} = V_{an}$ ,  $V_{BN} = V_{bn}$ ,  $V_{CN} = V_{cn}$

Line Voltages :  $V_{ab}$ ,  $V_{bc}$ ,  $V_{ca}$

Line Currents :  $I_{aA}$ ,  $I_{bB}$ ,  $I_{cC}$

Phase currents :  $I_{AN} = I_{aA}$ ,  $I_{BN} = I_{bB}$ ,  $I_{CN} = I_{cC}$

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle -240^\circ$$


phase voltages

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_p \angle 30^\circ$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_p \angle -90^\circ$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_p \angle -210^\circ$$

line voltages

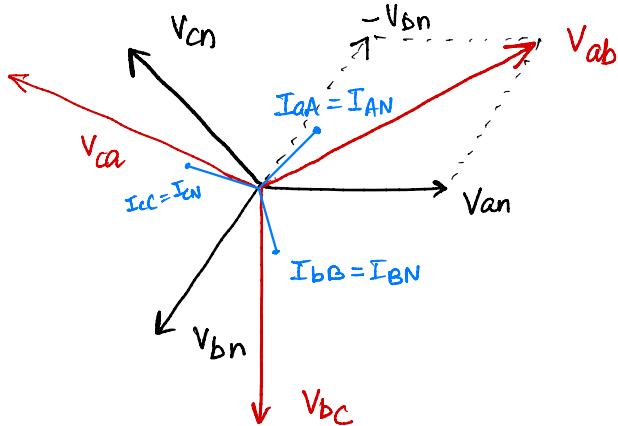

$V_p$  = magnitude of phase voltages =  $|V_{AN}| = |V_{BN}| = |V_{CN}| = V_p$   
 $V_L$  = magnitude of line voltages =  $|V_{ab}| = |V_{bc}| = |V_{ca}| = \sqrt{3}V_p$

$$V_L = \sqrt{3}V_p$$

Line currents = phase currents.

$$I_{aA} = I_{AN} = \frac{V_{AN}}{Z_p} = \frac{V_p}{Z_p}$$

$$I_{bB} = I_{BN} = \frac{V_{BN}}{Z_p}$$

$$I_{cC} = I_{CN} = \frac{V_{CN}}{Z_p}$$

$$\begin{aligned} Z_p &= \frac{V_{AN}}{I_{AN}} \\ &= \frac{V_p \angle \theta^\circ}{I_p \angle \phi^\circ} \\ &= \frac{V_p}{I_p} \angle \theta - \phi^\circ \end{aligned}$$

$I_p$  = magnitude of phase currents =  $|I_{AN}| = |I_{BN}| = |I_{CN}|$

$I_L$  = magnitude of line currents =  $|I_{aA}| = |I_{bB}| = |I_{cC}|$

$$I_p = I_L$$

$$\begin{aligned} P_{avg} \text{ for any phase} &= \frac{1}{2} \operatorname{Re} \{ V I^* \} & V_{AN} &= V_p \angle \theta^\circ \\ P_{avg, A} &= \frac{1}{2} \operatorname{Re} \{ V_{AN} I_{AN}^* \} & I_{AN} &= I_p \angle \phi^\circ \\ &= \frac{1}{2} \operatorname{Re} \{ V_p \angle \theta^\circ (I_p \angle \phi^\circ)^* \} \\ &= \frac{1}{2} V_p I_p \cos(\theta - \phi) \\ &= \frac{1}{2} \frac{1}{\sqrt{3}} V_L I_L \cos(\theta - \phi) \end{aligned}$$

$P_{avg}$  per phase =  $P_{avg}$  Aphase =  $P_{avg}$  Bphase =  $P_{avg}$  Cphase =  $\frac{1}{2} V_p I_p \cos(\theta - \phi)$

$$P_{avg} \text{ per phase} = \frac{V_L I_L}{\sqrt{3}} \cos(\theta - \phi), \text{ if } V_L, I_L \text{ are rms values.}$$

$$P_{avg} \text{ total} = \frac{3}{2} V_p I_p \cos(\theta - \phi)$$

$$= 3 V_p I_p \cos(\theta - \phi), \text{ if } V_p \& I_p \text{ are rms values.}$$

$$P_{avg} \text{ total} = \sqrt{3} V_L I_L \cos(\theta - \phi), \text{ if } V_L \& I_L \text{ are rms values.}$$

Total instantaneous power

$$P_{\text{total}}(t) = P_A(t) + P_B(t) + P_C(t)$$

$$P_A(t) = V_{AN}(t) i_{AN}(t)$$

$$V_{AN}(t) = V_p \cos(\omega t + \theta)$$

$$i_{AN}(t) = I_p \cos(\omega t + \phi)$$

$$P_A(t) = V_p I_p \cos(\omega t + \phi) \cos(\omega t + \theta)$$

$$= \frac{V_p I_p}{2} \left[ \underbrace{\cos(\theta - \phi)}_{\beta} + \underbrace{\cos(2\omega t + \theta + \phi)}_{\alpha} \right]$$

$$= \frac{V_p I_p}{2} [\cos \alpha + \cos \beta]$$

$$P_B(t) = V_{BN}(t) i_{BN}(t) = \frac{V_p I_p}{2} [\cos \beta + \cos(\alpha - 240^\circ)]$$

$$P_C(t) = \frac{V_p I_p}{2} [\cos \beta + \cos(\alpha + 240^\circ)]$$

$$P_{\text{total}}(t) = \frac{V_p I_p}{2} \left[ 3 \cos \beta + \cos \alpha + \underbrace{\cos(\alpha - 240^\circ)}_{\alpha} + \underbrace{\cos(\alpha + 240^\circ)}_{\alpha} \right]$$


$$P_{\text{total}}(t) = 3 \frac{V_p I_p}{2} \cos \beta = \frac{3 V_p I_p}{2} \cos(\theta - \phi) - \cos \alpha$$

$$P_{\text{avg}} = \frac{1}{T} \int_0^T P(t) dt$$

## Y-Δ Connections

Y-connected source

Δ-connected load (no neutral node)

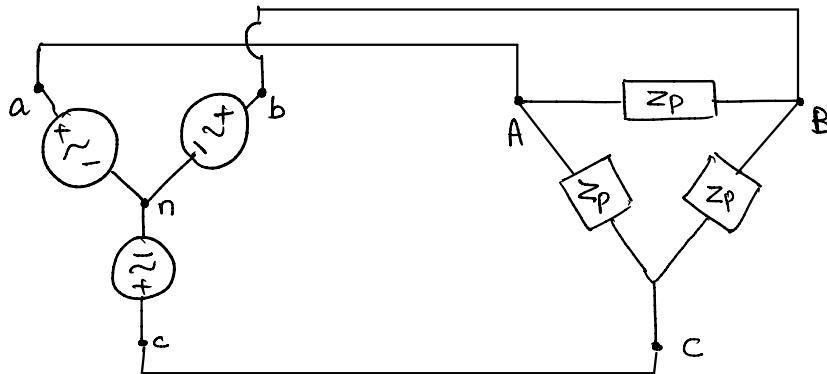

Phase voltages:  $V_{AB} = V_{ab}$ ,  $V_{BC} = V_{bc}$ ,  $V_{CA} = V_{ca}$

Line voltages:  $V_{ab}$ ,  $V_{bc}$ ,  $V_{ca}$  } ← same as phase voltages

$$\left. \begin{array}{l} V_{AB} = V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_{an} \angle 30^\circ \\ V_{BC} = V_{bc} = \sqrt{3} V_{an} \angle -90^\circ \\ V_{CA} = V_{ca} = \sqrt{3} V_{an} \angle -210^\circ \end{array} \right\} \begin{array}{l} \text{Line voltages} \\ = \text{phase voltages} \end{array}$$

$V_p$  = magnitude of phase voltage =  $|V_{AB}| = |V_{BC}| = |V_{CA}| = \sqrt{3} |V_{an}|$

$V_L$  = magnitude of line voltage =  $(V_{ab}) = |V_{bc}| = |V_{ca}| = \sqrt{3} |V_{an}|$

$$V_p = V_L$$

Line currents:  $I_{aA} = I_{AB} - I_{CA} = \sqrt{3} I_{AB} \angle -30^\circ$

$$I_{bB} = \sqrt{3} I_{BC} \angle -30^\circ$$

$$I_{cC} = \sqrt{3} I_{CA} \angle -30^\circ$$

Phase currents:  $I_{AB} = V_{AB} / Z_P$

$$I_{BC} = V_{BC} / Z_P$$

$$I_{CA} = V_{CA} / Z_P$$


$$\begin{aligned} Z_P &= \frac{V_{AB}}{I_{AB}} \\ &= \frac{V_p \angle \theta^\circ}{I_p \angle \phi^\circ} \\ &= \frac{V_p}{I_p} \angle \theta - \phi^\circ \end{aligned}$$

$I_p$  = magnitude of phase currents =  $|I_{AB}| = |I_{BC}| = |I_{CA}|$

$I_L$  = magnitude of line currents =  $|I_{aA}| = |I_{bB}| = |I_{cC}|$

$$\Rightarrow I_L = \sqrt{3} \underbrace{|I_{AB}|}_{I_p}$$

$$\Rightarrow I_L = \sqrt{3} I_p$$

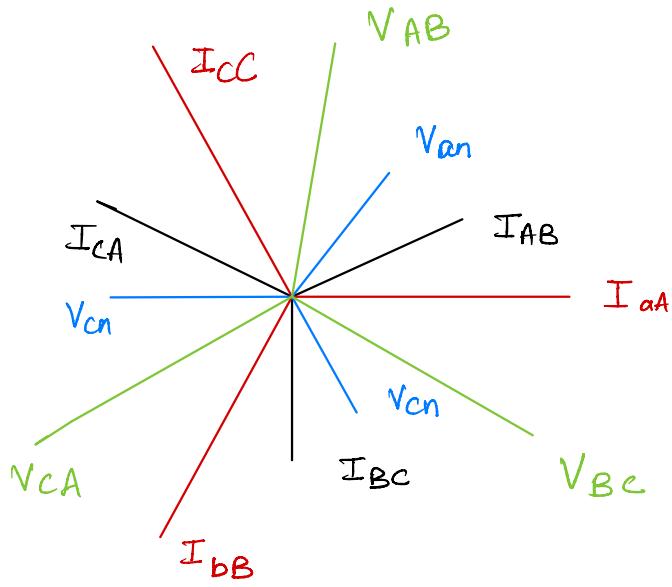

Similar to  $\Delta$ - $\Delta$  connection:

$$P_{avg \text{ per phase}} = \frac{1}{2} R_p \left\{ V_{AB} I_{AB}^* \right\} = \frac{1}{2} V_p I_p \cos(\theta - \phi)$$



$$P_{avg \text{ per phase}} = \frac{V_L I_L}{\sqrt{3}} \cos(\theta - \phi) , \text{ if } V_L, I_L \text{ are rms values.}$$

$$P_{avg \text{ total}} = \frac{3}{2} V_p I_p \cos(\theta - \phi)$$

$$= 3 V_p I_p \cos(\theta - \phi) , \text{ if } V_p \text{ & } I_p \text{ are rms values.}$$

$$P_{avg \text{ total}} = \sqrt{3} V_L I_L \cos(\theta - \phi) , \text{ if } V_L \text{ & } I_L \text{ are rms values.}$$

## Y-Y connection versus Y-Δ connection

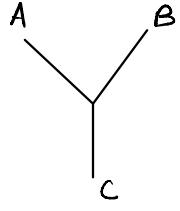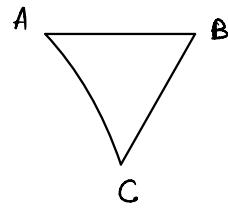		
Phase voltages Line voltages	$V_{AN}, V_{BN}, V_{CN}$ $V_{ab}, V_{bc}, V_{ca}$	$V_{AB}, V_{BC}, V_{CA} \rightarrow$ same $V_{ab}, V_{bc}, V_{ca} \leftarrow$ same
Phase currents Line currents	$I_{AN}, I_{BN}, I_{CN} \leftarrow$ same $I_{aA}, I_{bB}, I_{cC} \leftarrow$ same	$I_{AB}, I_{BC}, I_{CA}$ $I_{aA}, I_{bB}, I_{cC}$
	$V_L = \sqrt{3} V_p$ $I_L = I_p$	$V_L = V_p$ $I_L = \sqrt{3} I_p$
$Z_p$	$Z_p = \frac{V_p}{I_p} \angle \theta - \phi$	$Z_p = \frac{V_p}{I_p} \angle \theta - \phi$
Power per phase	$\frac{1}{2} V_p I_p \cos(\theta - \phi)$ $= \frac{1}{2} \frac{V_L I_L}{\sqrt{3}} \cos(\theta - \phi)$	$\frac{1}{2} V_p I_p \cos(\theta - \phi)$ $= \frac{1}{2} \frac{V_L I_L}{\sqrt{3}} \cos(\theta - \phi)$
Power total	$\frac{3}{2} V_p I_p \cos(\theta - \phi)$ $= \frac{1}{2} \frac{V_L I_L}{\sqrt{3}} \cos(\theta - \phi)$	$\frac{3}{2} V_p I_p \cos(\theta - \phi)$ $= \frac{1}{2} \frac{V_L I_L}{\sqrt{3}} \cos(\theta - \phi)$

Star to delta load transformation :-

