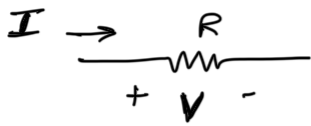


Phasor


$$i(t) = I_m \cos(\omega t + \phi) = \operatorname{Re}\{I_m e^{j\omega t + j\phi}\}$$

↓ Remove $\underline{e^{j\omega t}}$, $\underline{\operatorname{Re}\{}}$ ↑


$$\underbrace{I_m e^{j\phi}} = \underbrace{I_m \angle \phi}_{\text{phasor}}$$



$$V = IR$$

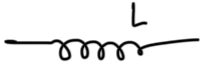

$$V = j\omega L I$$

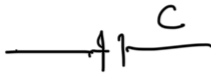

$$V = \frac{1}{j\omega C} I$$

$$Z_R = R$$

voltage & current in phase

$$Z_L = j\omega L$$

voltage leads current by 90°

$$Z_C = \frac{1}{j\omega C}$$

voltage lags current by 90°

Impedance

$$Z = \frac{V}{I} \quad \Omega$$

$$Z = \underbrace{X}_{\text{resistance}} + j \underbrace{Y}_{\text{reactance}}$$

Admittance


$$Y = \frac{1}{Z} \quad ; \quad \begin{aligned} \operatorname{Re}\{Y\} &= \text{conductance} \\ \operatorname{Im}\{Y\} &= \text{susceptance} \end{aligned}$$

Impedance Combinations

Series : $Z_{eq} = Z_1 + Z_2 + \dots + Z_N$


Parallel : $\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$

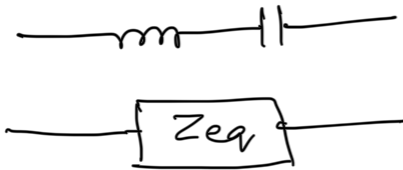Example: find impedance of a series combination of an inductor L ($L = 5 \text{ mH}$) and capacitor C ($C = 100 \text{ nF}$)
 $\omega = 10^4 \text{ rad/s}$




$$\begin{aligned} Z_{eq} &= Z_L + Z_C \\ &= j50 - j \\ &= j49 = 0 + j49 \\ &= 49 e^{j\pi/2} \end{aligned}$$

Example :-

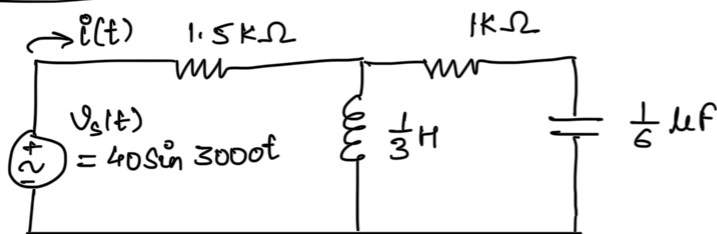

find $i(t)$

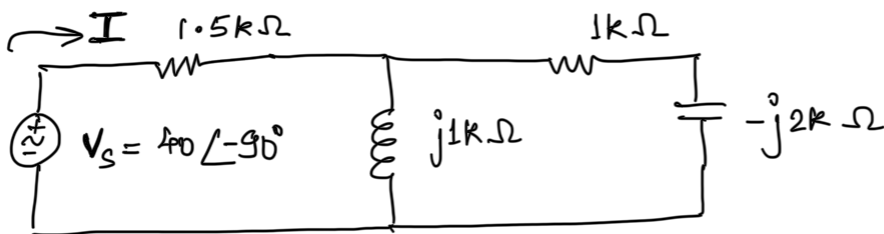
Step 1 Convert to freq. domain (write in terms of phasor & Z)



$$\begin{aligned} \sin \omega t &= \cos(90^\circ - \omega t) \\ &= \cos(\omega t - 90^\circ) \end{aligned}$$

$$\begin{aligned} Z_C &= \frac{1}{j\omega C} \\ &= \frac{1}{j 3000 \times 10^{-6}} \\ &= \frac{2 \times 10^6}{j \times 10^3} \\ &= -j2 \text{ k}\Omega \end{aligned}$$


Step 2

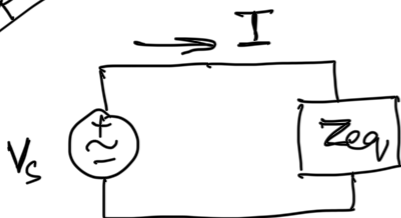

$$I = \frac{V_s}{Z_{eq}}$$

Find Z_{eq} .
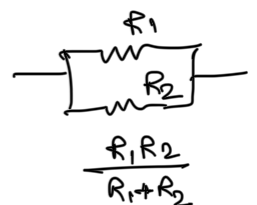
$$\begin{aligned} Z_{eq} &= 1.5 + \frac{(j1)(1-j2)}{1-j1} \text{ k}\Omega \\ &= 2.5 \angle 36.87^\circ \text{ k}\Omega \end{aligned}$$



$$I = \frac{V_s}{Z_{eq}} = \frac{40 \angle -90^\circ}{2.5 \times 10^3 \angle 36.87^\circ} = 16 \angle -126.87^\circ \text{ mA}$$

$$i(t) = \operatorname{Re} \{ 16 e^{-j126.87^\circ} e^{j\omega t} \}$$

$$= 16 \cos(\omega t - 126.87^\circ) \text{ mA}$$


$\hookrightarrow 3000$

Complex Number $\angle x + jy$
 $r \angle \theta$

$$r = \sqrt{x^2 + y^2} \quad , \quad x = r \cos \theta$$

$$\theta = \tan^{-1}(y/x) \quad , \quad y = r \sin \theta$$

Example

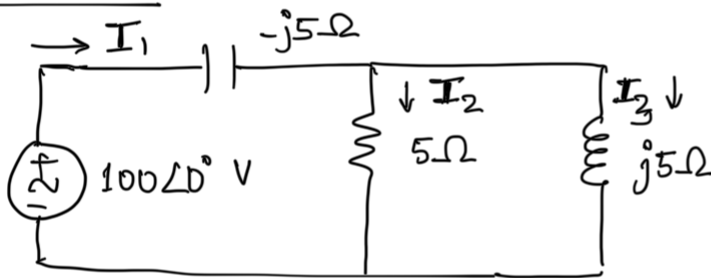

Find I_1, I_2, I_3 .




Review

Voltage Division

$$V_k = V \frac{R_k}{R_1 + \dots + R_N}$$


Current Division
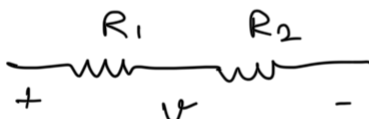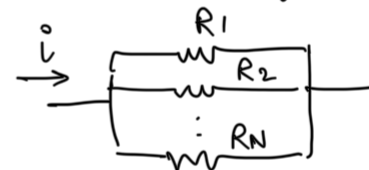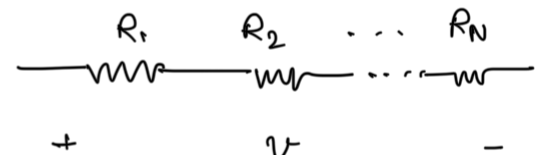
$$i_k = i \frac{1/R_k}{1/R_1 + 1/R_2 + \dots + 1/R_N}$$




$$V_1 = V \frac{R_1}{R_1 + R_2}$$

$$V_2 = V \frac{R_2}{R_1 + R_2}$$

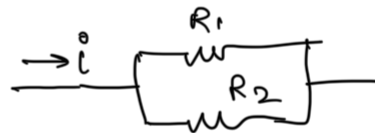

$$i_1 = i \frac{R_2}{R_1 + R_2}$$

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

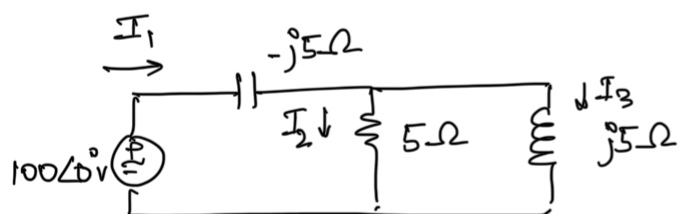


find I_1, I_2, I_3

$$I_1 = \frac{100 \angle 0^\circ}{Z_{eq.}}, \quad I_2 = I_1 \left(\frac{j5}{5+j5} \right), \quad I_3 = I_1 \left(\frac{5}{5+j5} \right)$$

$$Z_{eq.} = 3.53 \angle -45^\circ \Omega = 2.5 - j2.5 \Omega$$

$$I_1 = 28.3 \angle 45^\circ A$$

Nodal Analysis

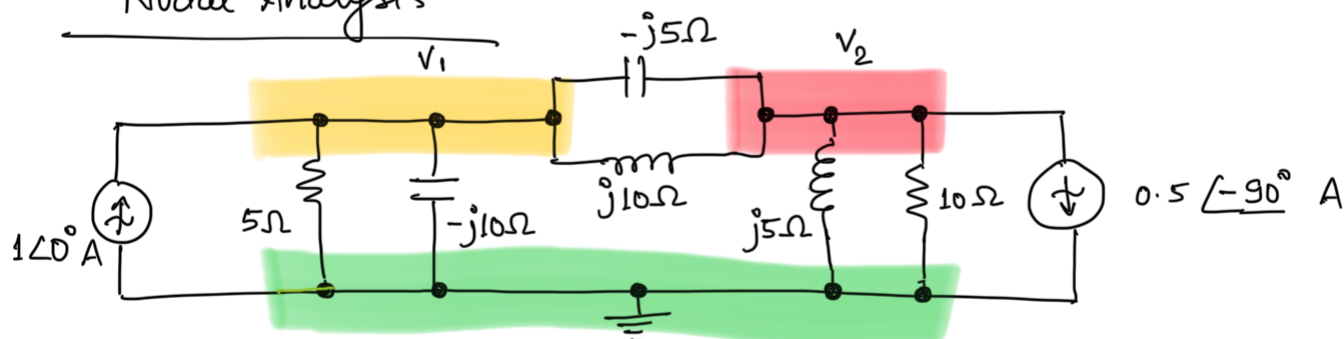

Find $V_1(t)$ and $V_2(t)$

at node 1 ;

$$1 \angle 0^\circ = \frac{V_1}{5} + \frac{V_1}{-j10} + \frac{V_1 - V_2}{-j5} + \frac{V_1 - V_2}{j10}$$

$$\Rightarrow (0.2 + j0.2)V_1 - j0.1V_2 = 1 \quad \text{--- ①}$$

at node 2 ;

$$-0.5 \angle -90^\circ = \frac{V_2}{10} + \frac{V_2}{j5} + \frac{V_2 - V_1}{-j5} + \frac{V_2 - V_1}{j10}$$

$$\Rightarrow -j0.1V_1 + (0.1 - j0.1)V_2 = j0.5 \quad \text{--- ②}$$


$$V_1 = 1 - j2 = 2.24 \angle -63.4^\circ V$$

$$V_2 = -2 + j4 = 4.47 \angle 116.6^\circ V$$

$$v_1(t) = 2.24 \cos(\omega t - 63.4^\circ) \text{ V}$$

$$v_2(t) = 4.47 \cos(\omega t + 116.6^\circ) \text{ V}$$

Mesh Analysis

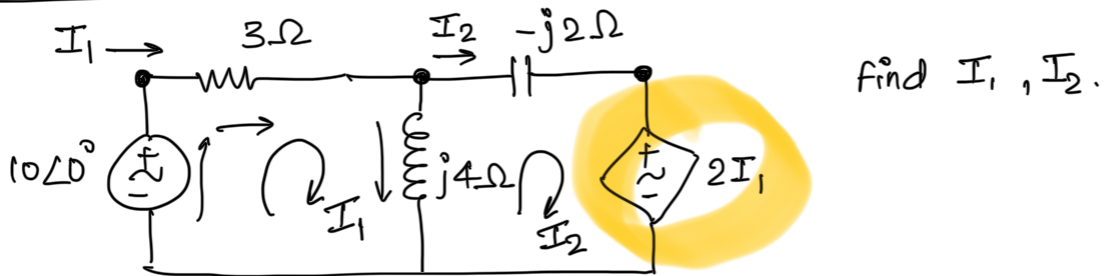

$$-10\angle 0^\circ + 3I_1 + (I_1 - I_2)j4 = 0$$

$$(I_2 - I_1)j4 + (-j2)I_2 + 2I_1 = 0$$

$$I_1 = 1.24 \angle 29.7^\circ \text{ A}$$

$$I_2 = 2.77 \angle 56.3^\circ \text{ A}$$

$$i_1(t) = 1.24 \cos(\omega t + 29.7^\circ) \text{ A}$$

$$i_2(t) = 2.77 \cos(\omega t + 56.3^\circ) \text{ A}$$