

tr5frbj 12/08/24

Circuit Theory and Devices

Lab: LT Spice (2nd week onwards)

book: Engineering Circuit Analysis (9th edition)

Relative grading


Labs	20%
Quiz	20%
Midsem	30%

Scientific calc

Course: 9 modules chapter 10 onwards
{continuation of BE3}

Lecture 1

⇒ Linear Circuits

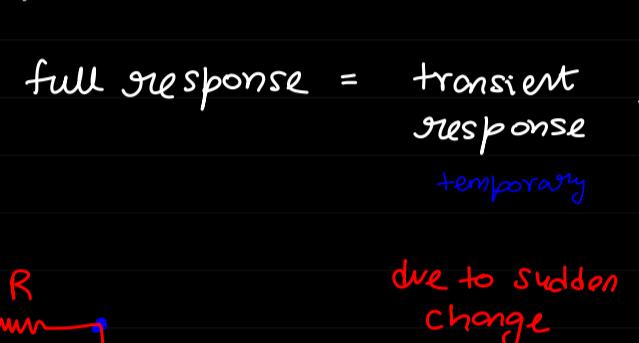

System is linear if

$$Kx \rightarrow [\text{sys}] \rightarrow Ky$$

where K is constant

"R" Resistor: linear element ✓
 $V = iR$

"L" Inductor: linear element ✓
 $V = L \frac{di}{dt}$


* Linear Electric Circuits:

consists of ⇒

① $R, L, C \rightarrow$ linear elements


② Independent voltage & current sources

③ Linear dependent sources

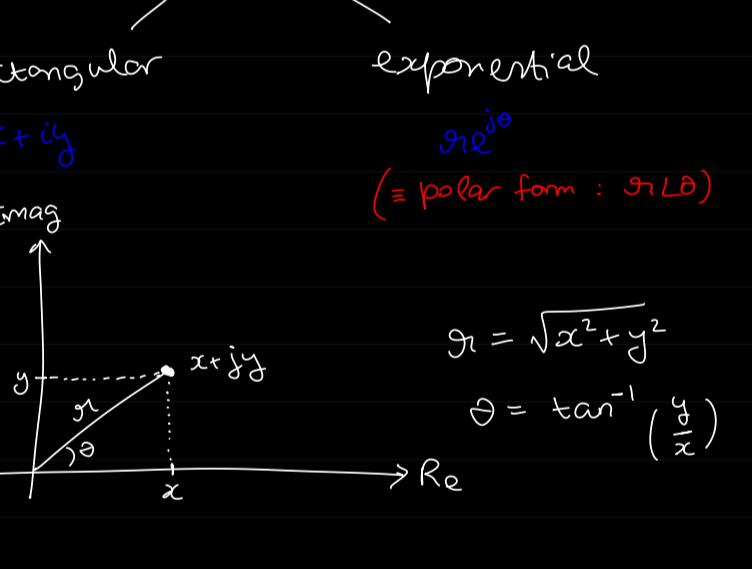

* Response of a linear circuit

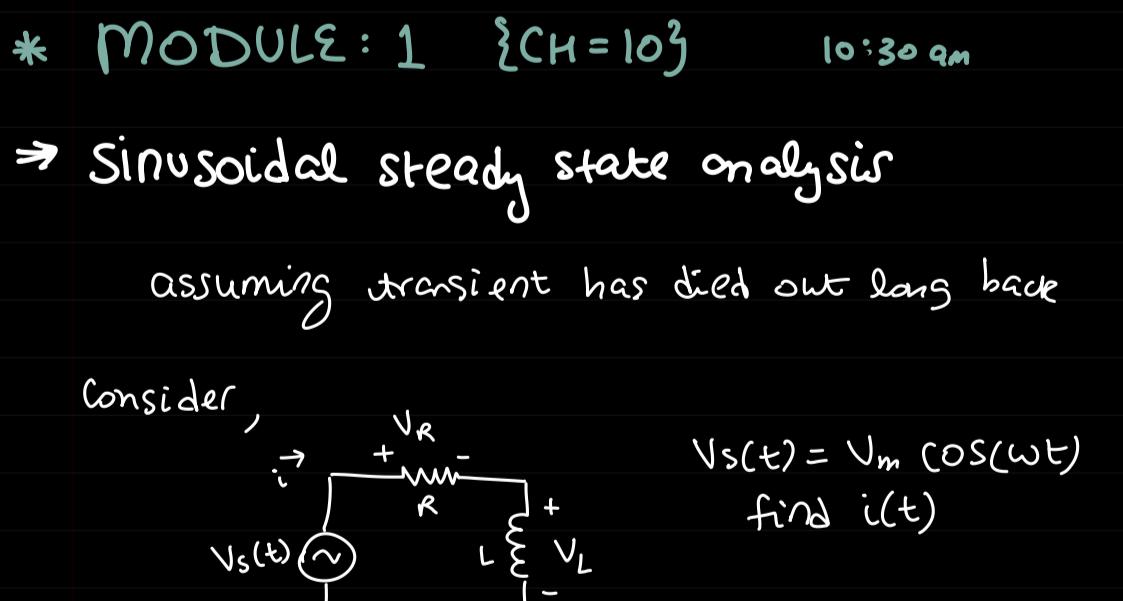① full response = transient response + steady state
transient temporary persists $t \rightarrow \infty$




* Complex Numbers

Sinusoidally varying voltage source

$$V_s(t) = V_m \cos(\omega t)$$

$$V_s(t) = V_m \sin(\omega t)$$

$$V_s(t) = V_m \sin(\omega t + \phi)$$

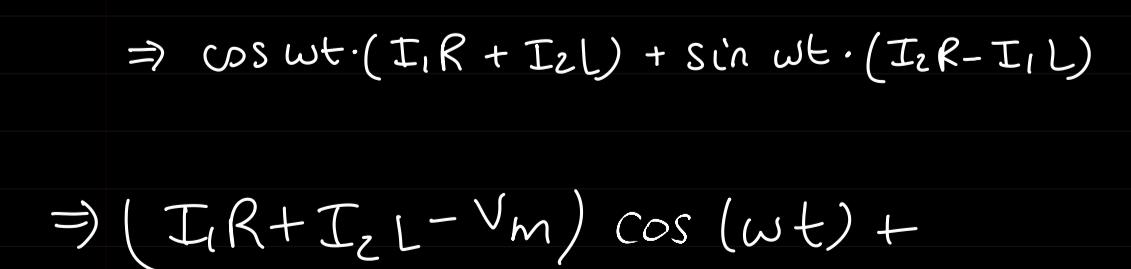

$$\Rightarrow \text{Euler's identity: } e^{j\theta} = \cos\theta + j\sin\theta$$

$$\frac{d}{dt} (I_1 e^{j\omega t}) = I_1 \omega e^{j\omega t}$$

$$\Rightarrow V_m \cos(\omega t) = iR + L \frac{di}{dt}$$

$$\Rightarrow V_m \cos(\omega t) = iR + L \frac{d}{dt} (I_1 \omega e^{j\omega t})$$

$$\Rightarrow V_m \cos(\omega t) = I_1 \omega (-\sin\omega t) + I_2 \cos\omega t$$

$$\Rightarrow V_m \cos(\omega t) = I_2 \cos\omega t - I_1 \sin\omega t$$

$$\Rightarrow \cos\omega t \cdot (I_1 R + I_2 L) + \sin\omega t \cdot (I_2 R - I_1 L) = 0$$

$$\Rightarrow (I_1 R + I_2 L - V_m) \cdot 1 + (I_2 R - I_1 L) \cdot 0 = 0$$

$$\boxed{I_1 R + I_2 L = V_m}$$

$$\Rightarrow I_1 = \frac{V_m - I_2 R}{L}$$

$$\boxed{I_1 = I_2 \cdot \frac{R}{L}}$$

$$\Rightarrow I_2 R + I_2 L = V_m \Rightarrow I_2 = \frac{V_m}{R + L}$$

* Section 10.1

(a) $Q_1 y \quad 5\sin(5t - 9^\circ)$

$$t=0 \Rightarrow 5\sin(-9^\circ) = -5\sin(9^\circ) = -0.782$$

$$t=0.01 \Rightarrow 5\sin(0.05 - 9^\circ) = -5\sin(8.95^\circ) \quad X$$

\Downarrow
radians

$$5\sin\left(\frac{0.05 \times 80}{\pi} - 9^\circ\right) = 5\sin(2.86^\circ - 9^\circ)$$

$$\Rightarrow -5\sin(6.14^\circ) = -0.534$$

$$t=0.1 \Rightarrow 5\sin(0.5 - 9^\circ) = 5\sin(28.64^\circ - 9^\circ) = 5\sin(19.64^\circ)$$

$$\Rightarrow 1.6805$$

(b) $4\cos 2t$

$$t=0 \Rightarrow 4\cos(0) = 4$$

$$t=1 \Rightarrow 4\cos(2) = 3.997$$

$$t=1.5 \Rightarrow 4\cos(3) = 3.994$$

(c) $3.2 \cos(6t + 15^\circ)$

$$t=0 \Rightarrow 3.2 \cos(15^\circ) = 3.09$$

$$t=0.01 \Rightarrow 3.2 \cos(0.06 + 15^\circ) = 3.2 \cos(3.43^\circ + 15^\circ)$$

$$\Rightarrow 3.2 \cos(18.43^\circ)$$

$$\Rightarrow 3.035$$

$$t=0.1 \Rightarrow 3.2 \cos(0.6 + 15^\circ) = 3.2 \cos(34.3^\circ + 15^\circ)$$

$$= 3.2 \cos(49.3^\circ)$$

$$= 2.086$$

Q2) (a) $300\sin(628t) \rightarrow 300 \cdot \cos(628t - 90^\circ)$


$$4\sin(3\pi t + 30^\circ) \rightarrow 4\cos(3\pi t - 60^\circ)$$

$$14\sin(50t - 8^\circ) - 10\cos 50t \rightarrow$$


Q3) $V_L = 10\cos(10t - 45^\circ)$

(a) $i_L = 5\cos 10t$

$$-45^\circ$$

 

⇒ AC Power Analysis {Module: 3}

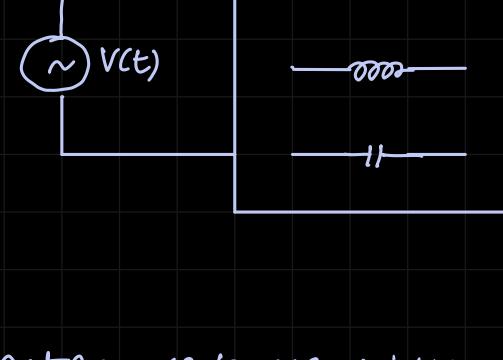

$$\cos(A) \cos(B) =$$

$$\frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

Instantaneous power: $p(t) = v(t) \cdot i(t)$

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$p(t) = V_m \cos(\omega t + \theta) \cdot I_m \cos(\omega t + \phi)$$

$$p(t) = \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{constant}} + \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)}_{\text{twice frequency (harmonic)}}$$

• Average Power

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(\theta - \phi) dt + \underbrace{\frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) dt}_{0}$$

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

* Avg. Power absorbed

• by a purely resistive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

here, phase diff = 0°




$$P_{avg} = \frac{V_m \cdot I_m}{2} = \frac{I_m^2 R}{2} = \frac{V_m^2}{2R}$$

• by a purely inductive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$


here, phase diff = 90°

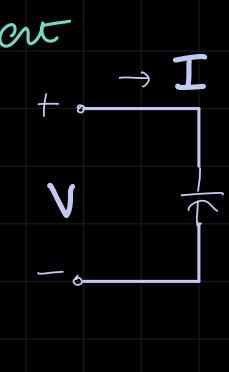

$$P_{avg} = 0 \text{ for inductor}$$

• by a purely capacitive element
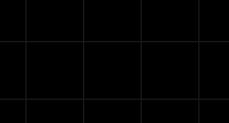
$$P_{avg} = \frac{V_m \cdot I_m}{2} \cos(-90^\circ)$$



$$P_{avg} = 0 \text{ for capacitor}$$

* Lecture: 6

$$v(t) = V_m \cos(\omega t + \phi) \quad \leftarrow \text{Revision}$$

$$\downarrow$$


$$v(t) = R \Re \{ V_m e^{j\omega t} e^{j\phi} \}$$

$\downarrow -e^{j\omega t}$

$$V_m e^{j\phi} = V_m \angle \phi$$

exponential polar

• eg)

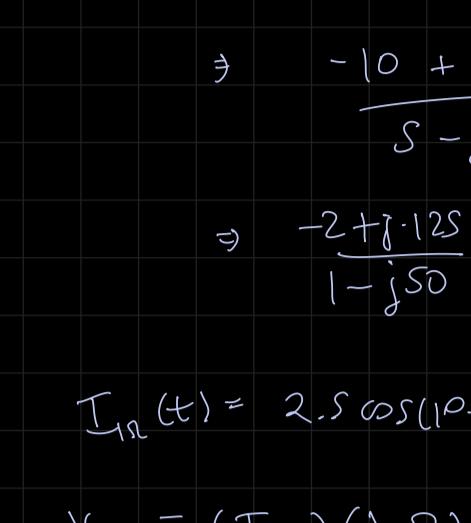


① find power delivered to each element at $t = 0, 10, 20 \text{ ms}$

② find P_{avg} to each element

(Ans) convert to freq. domain

$$V_{1\text{R}} = V_{u\text{R}} + V_c$$

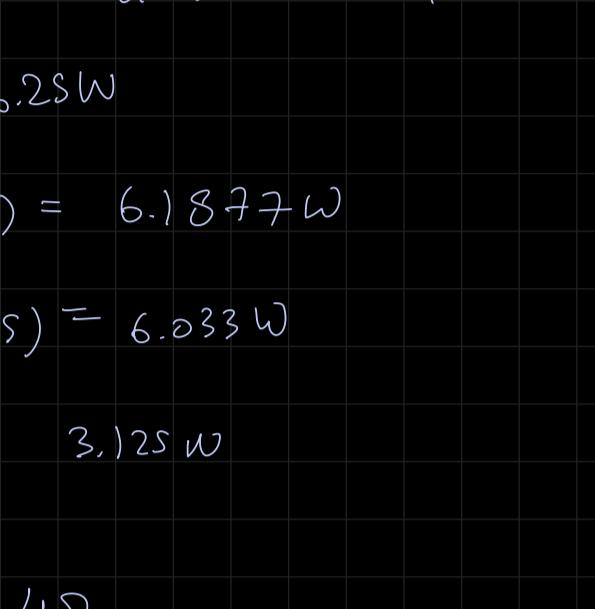

$$\textcircled{1} \quad P_{inst} = \underbrace{V_u I_m \cos(\theta - \phi)}_{2} + \underbrace{V_m I_m}_{2} \cos(2\omega t + \phi + \theta)$$

$$I_i = -2.5 \times \left(\frac{4 - j2.5 \times 10^4}{1 + j - j2.5 \times 10^4} \right) \simeq -2.5 \text{ A}$$

$$\Rightarrow \frac{-10 + j62.5 \times 10^4}{5 - j2.5 \times 10^4} \rightarrow \frac{-2 + j12.5}{1 - j50}$$

$$\Rightarrow \frac{-2 + j12.5}{1 - j50} \times \frac{1 + j50}{1 + j50} =$$

$$I_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$V_{1\text{R}} = (I_{1\text{R}})(2 \Omega) \Rightarrow V_{1\text{R}}(t) = 2.5 \cos(10t)$$

$$\cos^2(\theta) = \frac{1 + \cos(2\theta)}{2}$$

$$P_{1\text{R}}(t) = 2.5 \cos(10t) \cdot 2.5 \cos(10t) \text{ W}$$

$$P_{1\text{R}}(t=0) = 6.25 \text{ W}$$

$$P_{1\text{R}}(t=20 \text{ ms}) = 6.033 \text{ W}$$

$$(P_{avg})_{1\text{R}} = 3.125 \text{ W}$$

⇒ P delivered to 4Ω

$$P_{4\Omega}(t) = V_{u\text{R}}(t) \times I_{u\text{R}}(t)$$

$$\hookrightarrow I_{u\text{R}} = I_s \times \frac{1}{5 - j2.5 \times 10^4} = 10^{-4} \angle 90^\circ \text{ A}$$

$$V_{u\text{R}} = 4 \times I_{u\text{R}} = 4 \times 10^{-4} \angle 90^\circ \text{ V}$$

convert to time domain

$$P_{1\text{R}}(t) = 2 \times 10^{-8} + 2 \times 10^{-8} \cos(20t) \text{ W}$$

$$t=0^- \quad 4 \times 10^{-8} \text{ W}$$

$$t=10 \text{ ms} = 3.96 \times 10^{-8} \text{ W}$$

$$P_{avg}{}_{1\text{R}} = 2 \times 10^{-8} \text{ W}$$

⇒ P delivered to capacitor

$$P_c(t) = V_c(t) \cdot I_c(t)$$

$$\left(P_{avg} \right)_c = 0 \quad \text{since phase diff} = 90^\circ$$

$$I_c = I_2 = 10^{-4} \angle 90^\circ \text{ A} \Rightarrow I_c(t) = 10^{-4} \cos(20t + 90^\circ)$$

$$V_c = (-j2.5 \times 10^4) \times 10^{-4} \angle 90^\circ$$

$$-j2.5 \times 10^4 \times (+j10^{-4}) = 2.5 \text{ V}$$

$$P_c(t) = 1.25 \times 10^{-4} \cos(20t + 90^\circ) \text{ W}$$

$$t=0 \Rightarrow P = 0 \text{ W}$$

$$t=10 \text{ ms} \Rightarrow P = 2.48 \times 10^{-8} \text{ W}$$

$$(P_{avg})_c = 1.25 \times 10^{-8} \text{ W}$$

$$\text{Note: we cannot multiply } I_c \text{ and } V_c \text{ in phasor form and then convert to time domain for getting } P_c \text{ (power) because power does not have a phasor part. It is a real value.}$$

* Correct or not?

$$\text{depends on } \times \quad \textcircled{1} \quad P_{1\text{R}}(t) + P_{4\Omega}(t) + P_c(t) = \text{constant 1}$$

$$\checkmark \quad \textcircled{2} \quad P_{avg}{}_{1\text{R}} + P_{avg}{}_{4\Omega} + P_{avg}{}_c = \text{constant 2} \quad \text{= } P_{avg} \text{ source}$$

active sign convention

this instant power is given by $v \cdot i$ some $v = 20 \text{ V}$

passive sign convention

some $v = 20 \text{ V}$

* Maximum Power Transfer Theorem

maximum power delivered to load when

$$Z_L = Z_S^*$$

complex conjugate of Z_S



⇒ Impedance Matching

$$\text{impedance matching circuit}$$

$$100 \Omega \quad 100 \Omega \quad j50 \Omega \quad 50 \Omega$$

$$Z_L = Z_S^*$$

$$i(t) \xrightarrow{\text{square}} i^2(t) \xrightarrow{\text{mean}} \frac{1}{T} \int_0^T i^2(t) dt \xrightarrow{\text{sqrt}} \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$V_{eff} = \frac{V_m}{\sqrt{2}}$$

$$I_{eff} = \frac{I_m}{\sqrt{2}}$$

$$V_{eff} = \frac{V_m}{\sqrt{2}}$$

$$I_{eff} = \frac{I_m}{\sqrt{2}}$$
</div