

Quick Recap


RLC \rightarrow total response

$$V(t) = V_f(t) + V_n(t)$$

$$= V_{SS} + \underbrace{V_T(t)} \begin{cases} A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ A_1 t e^{s t} + A_2 e^{s t} \\ e^{-\alpha t} (A_d \sin \omega_d t + B_d \cos \omega_d t) \end{cases}$$

$$I_L(t) = I_L(t^+) \quad (V_L(t) \neq \infty)$$

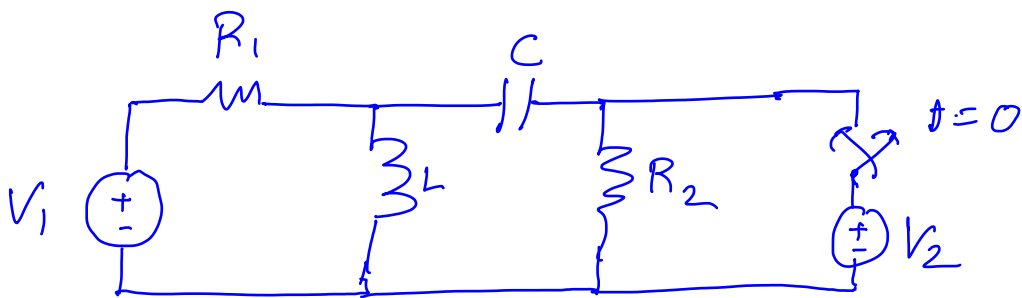
$$V_C(t^-) = V_C(t^+) \quad (I_C(t) \neq \infty)$$



$$I_L(0^-) = ?$$

$$V_C(0^-) = ?$$


at $t = 0^-$

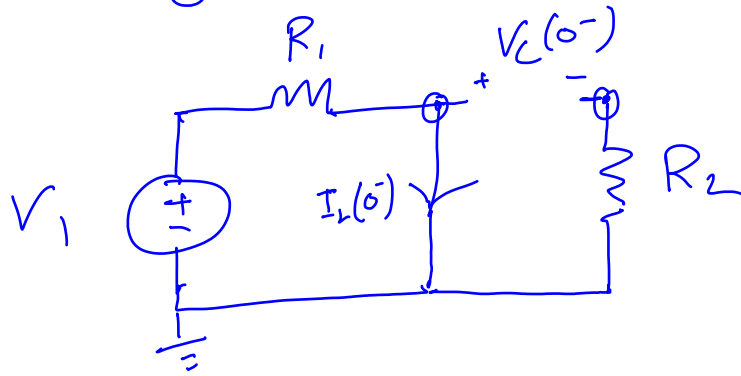


$$I_L(0^-) = \frac{V_1}{R_1}$$

$$V_C(0^-) = 0$$

open-loop OpAmp

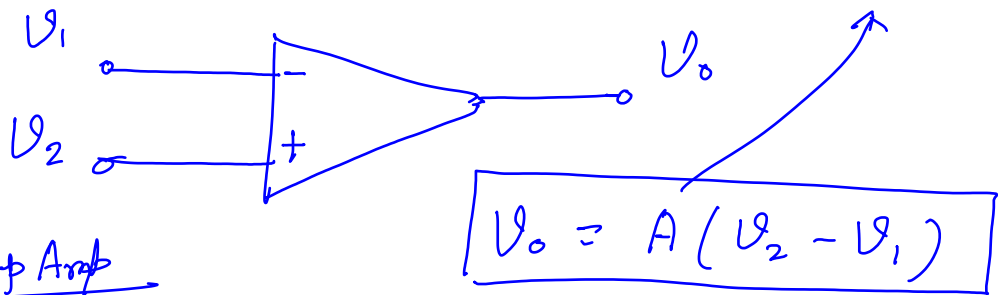

closed-loop OpAmp

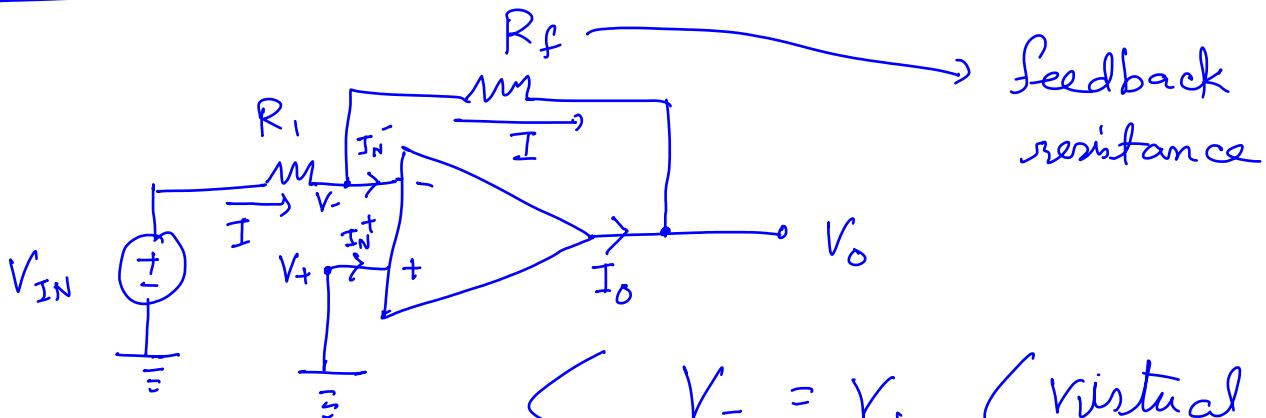

Ideal
OpAmp

$$\begin{cases} V_- = V_+ \text{ (virtual short)} \\ I_N^- = I_N^+ = 0 \end{cases}$$

$$\frac{V_{IN}}{R_1} = -\frac{V_0}{R_f} \Rightarrow V_0 = -\frac{R_f}{R_1} V_{IN}$$

$$I + I_0 = 0 \Rightarrow I_0 = -I = -\frac{V_{IN}}{R_1}$$

$I_{IN} = 0$, however, $I_0 \neq 0$. This is possible because of the power supplies ($+V_{CC}$, $-V_{CC}$). OpAmp is an active element.

Equivalent circuit of OpAmp ✓

Fundamental questions

$$\frac{0}{0} = ?$$


$$\infty \times 0 = ?$$

$$\frac{0}{0} = \underline{m} \Rightarrow 0 = m \times 0$$

any real number

$$\lim_{t \rightarrow \infty} \frac{e^{-pt}}{e^{-qt}} \left. \begin{array}{l} = 0 \quad \text{if } p > q \\ = \infty \quad \text{if } p < q \\ = 1 \quad \text{if } p = q \end{array} \right\}$$

Getting back to OpAmp

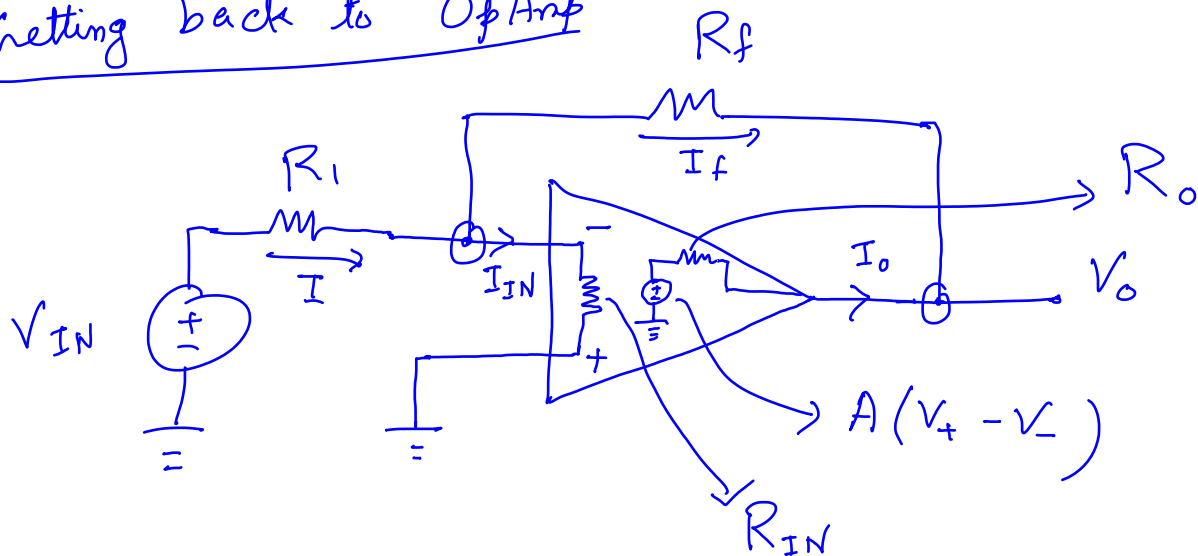

Ideal OpAmp

$$A = \infty$$

$$R_{IN} = \infty$$

$$R_O = 0$$

$$I = I_f + I_{IN} \quad \text{--- (I)}$$

$$I_f + I_O = 0 \quad \text{--- (II)}$$

$$\frac{V_{IN} - V^-}{R_i} = \frac{V^- - V_o}{R_f} + \frac{V^-}{R_{IN}} \quad \text{--- (I)}$$

$$\frac{V^- - V_o}{R_f} + \frac{A(V^+ - V^-) - V_o}{R_o} = 0 \quad \text{--- (II)}$$

$$\underline{V^+ = 0}$$

since $R_{IN} = \infty$

$$\Rightarrow \frac{V_{IN} - V^-}{R_i} = \frac{V^- - V_o}{R_f}$$


since $R_o = 0 \Rightarrow \boxed{A(V^+ - V^-) = V_o}$

$$A(V^+ - V^-) = V_o$$

$$A(0 - V^-) = V_o$$

since $A = \infty \Rightarrow V^- = 0$ and V_o is finite.
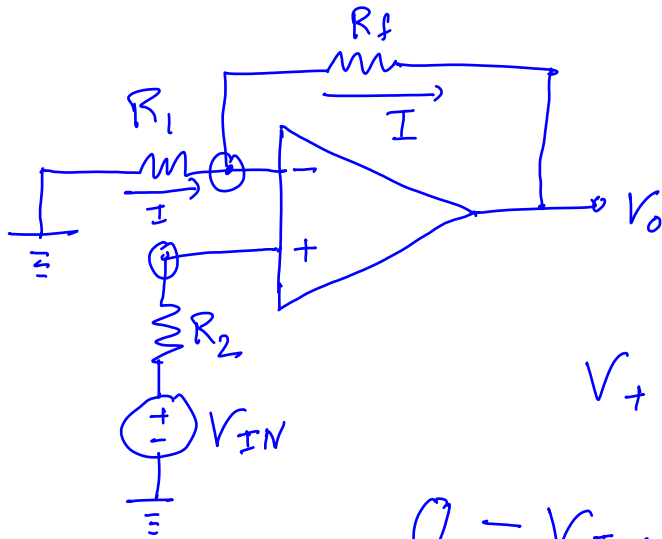
$$\Rightarrow \left. \begin{array}{l} V^+ = V^- (= 0) \\ I_{IN} = 0 \end{array} \right\} \begin{array}{l} - \\ - \end{array}$$



$$V_+ = V_- = V_{IN}$$

$$\frac{0 - V_{IN}}{R_1} = \frac{V_{IN} - V_O}{R_f}$$


\Rightarrow

$$\frac{V_O}{R_f} = \left(\frac{1}{R_1} + \frac{1}{R_f} \right) V_{IN}$$

\Rightarrow


$$V_O = \left(1 + \frac{R_f}{R_1} \right) V_{IN}$$

(non-inverting amplifiers)

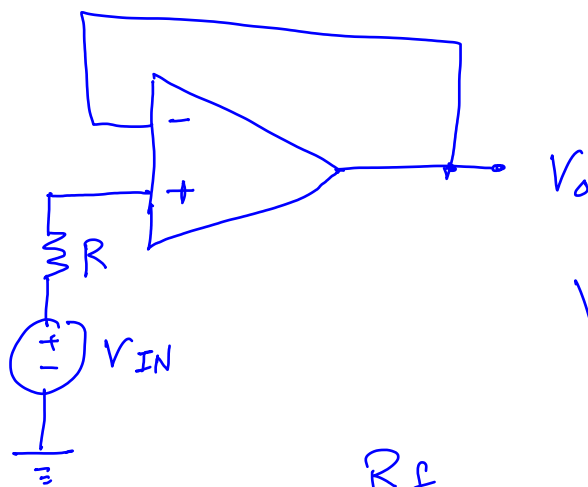

$$V_O = V_{IN}$$

(Buffer)

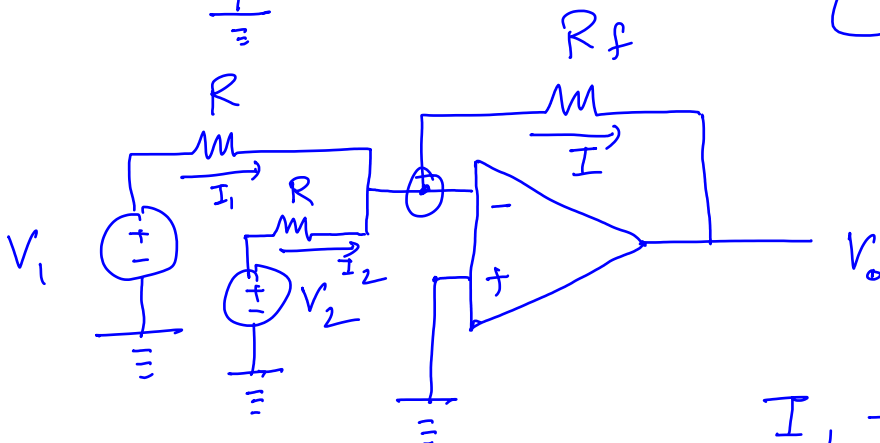


$$I_1 + I_2 = I$$

($V^+ = V^- = 0$)

$$\frac{V_1}{R} + \frac{V_2}{R} = - \frac{V_o}{R_f}$$

$$V_o = - \frac{R_f}{R} (V_1 + V_2)$$

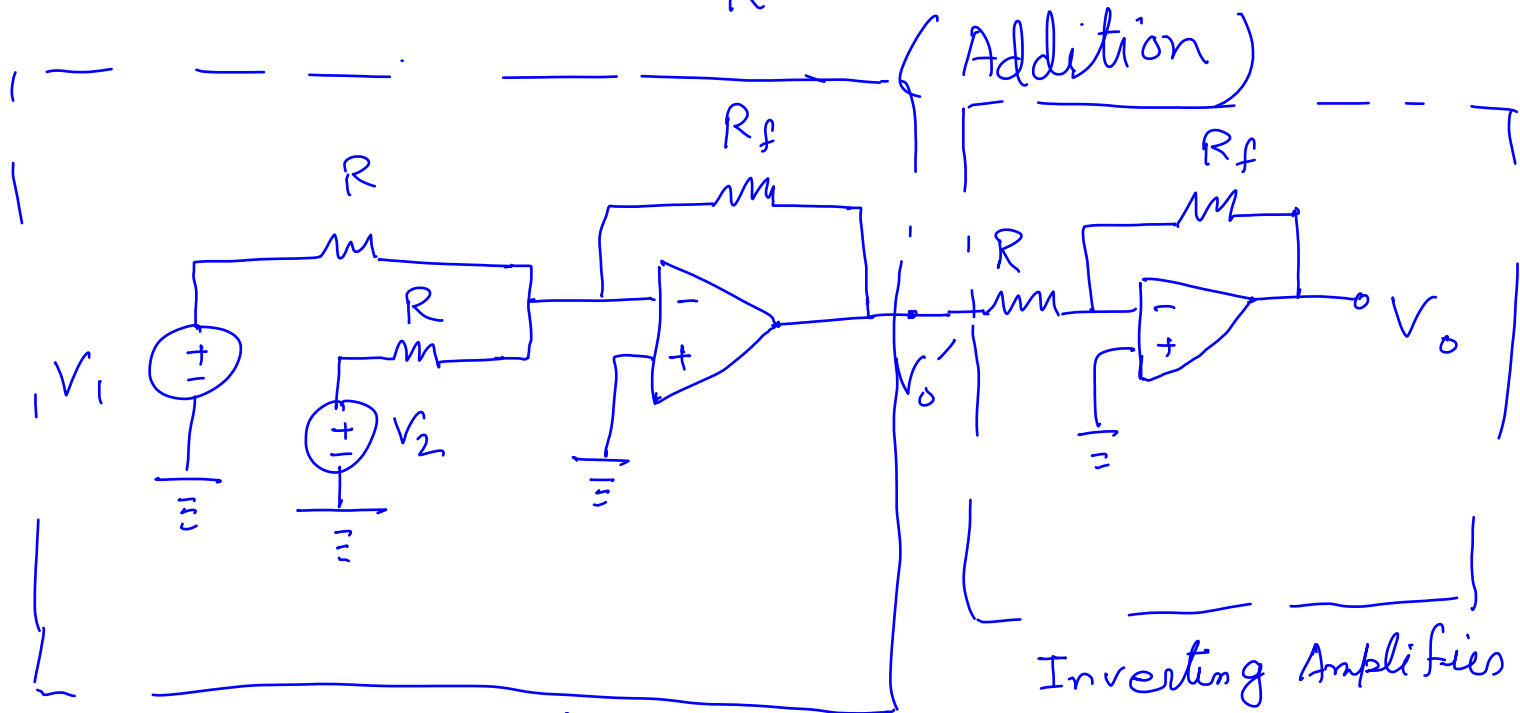

Inverting Adder

$$V_o' = - \frac{R_f}{R} (V_1 + V_2)$$

$$V_o = - \frac{R_f}{R} V_o' = + \frac{R_f^2}{R^2} (V_1 + V_2)$$

