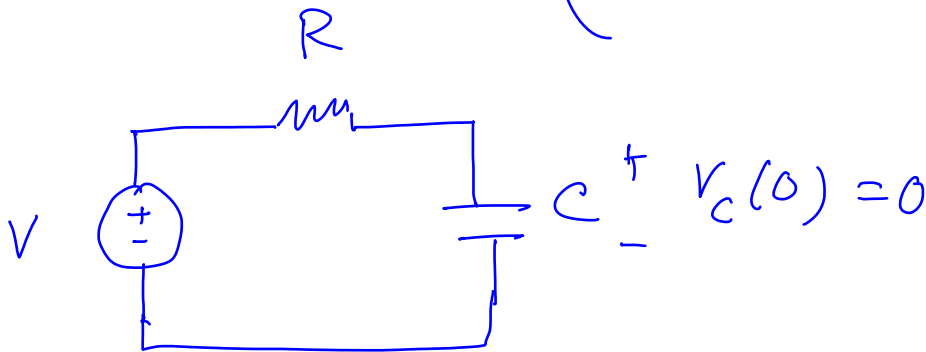


Quick Recap

RC circuit $\left\{ \begin{array}{l} \text{charging} \\ \text{discharging} \end{array} \right\}$

Unit step function

$$u(t) = \begin{cases} 0 & \forall t < 0 \\ 1 & \forall t \geq 0 \end{cases}$$



$$V_C(t) = V(1 - e^{-t/(RC)}) \quad \forall t \geq 0$$

time constant (T)



$$T = RC$$

at $t = T$,

$$V_C(t) \approx 66\% V$$


$$\left. \frac{dV_C}{dt} \right|_{t=0} = \frac{V}{RC} e^{-t/RC} \bigg|_{t=0} = \frac{V}{RC} = \frac{V}{T}$$

If the rate of change of V_C would have remained same as $\left. \frac{dV_C}{dt} \right|_{t=0}$ for $t > 0$, the capacitor voltage would have reached V at $t = T$.

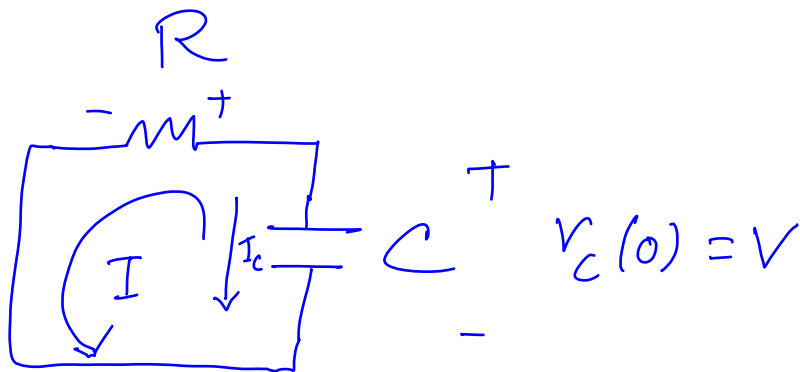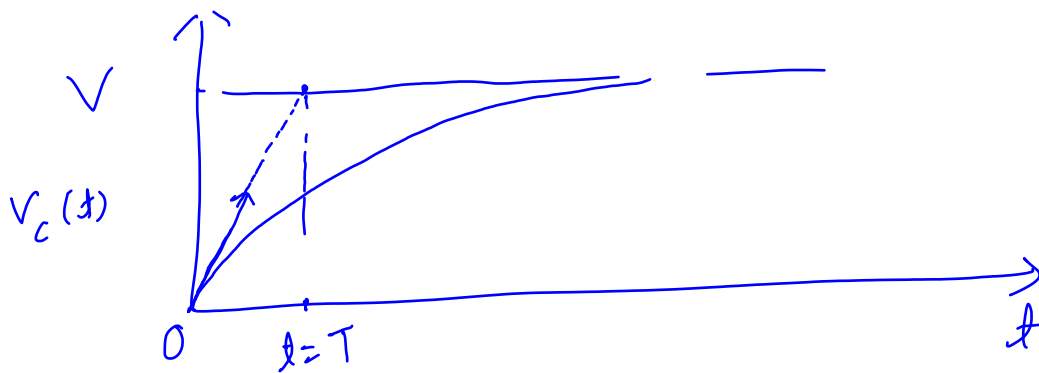


$$V_C(t) = V e^{-t/RC}$$

$$I_C = C \frac{dV_C}{dt} = -I$$

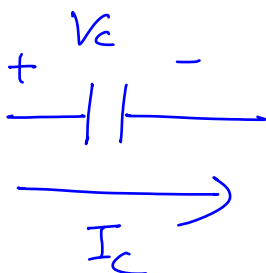

$$I_C = C \frac{dV_C}{dt}$$

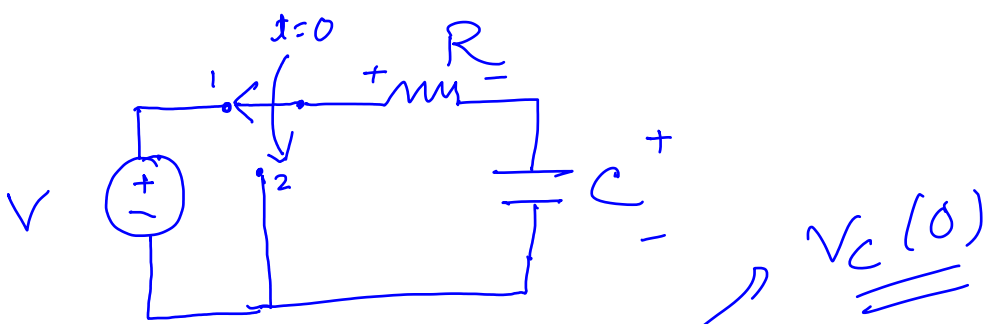


$$V_C(t) = \boxed{V} e^{-t/RC} \quad \forall t \geq 0$$

$$\underline{V_C(0^-) = V \Rightarrow V_C(0^+) = V} \quad \text{if } I_C \neq \infty$$

$$\lim_{\varepsilon \rightarrow 0} V_C(0-\varepsilon) = \lim_{\varepsilon \rightarrow 0} V_C(0+\varepsilon) \quad (\text{continuity property})$$

$$V_R(0^-) = 0 \quad V_R(0^+) = -V \quad (\text{discontinuous})$$

$t \geq 0$

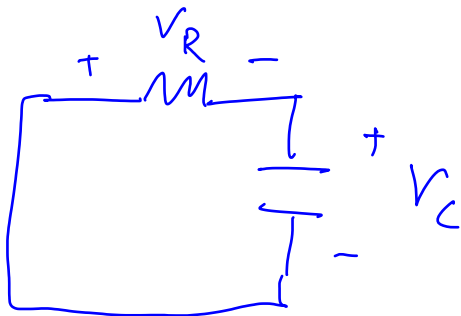


$$V_C(t) + V_R(t) = 0 \quad \forall t \geq 0$$

$$V_C(0) + V_R(0) = 0$$

$$\Rightarrow V_R(0) = -V_C(0)$$

$$= -V$$



Let's consider the following circuit,

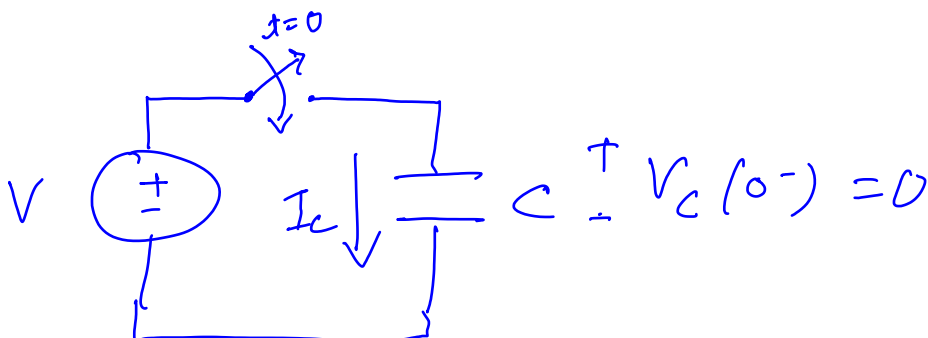

$$V_C(0^+) = V \quad (\text{using KVL})$$

$$I_C = C \frac{dV_C}{dt}$$

$$V_C(t) = V u(t)$$

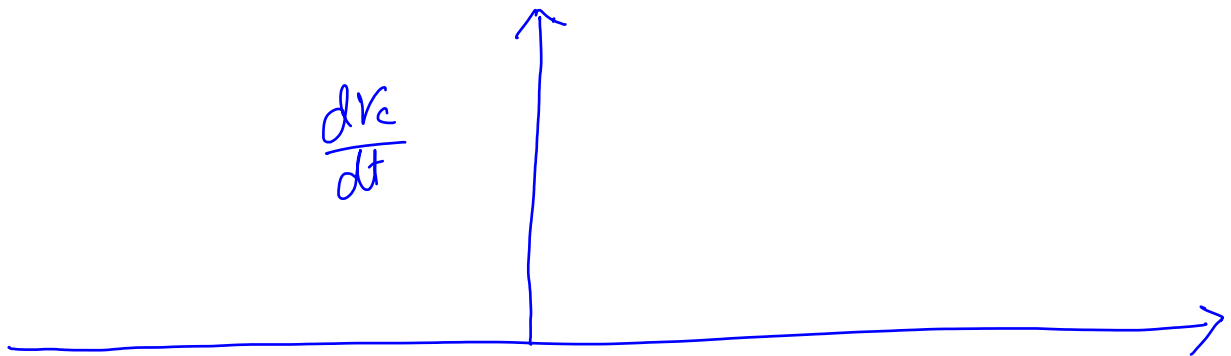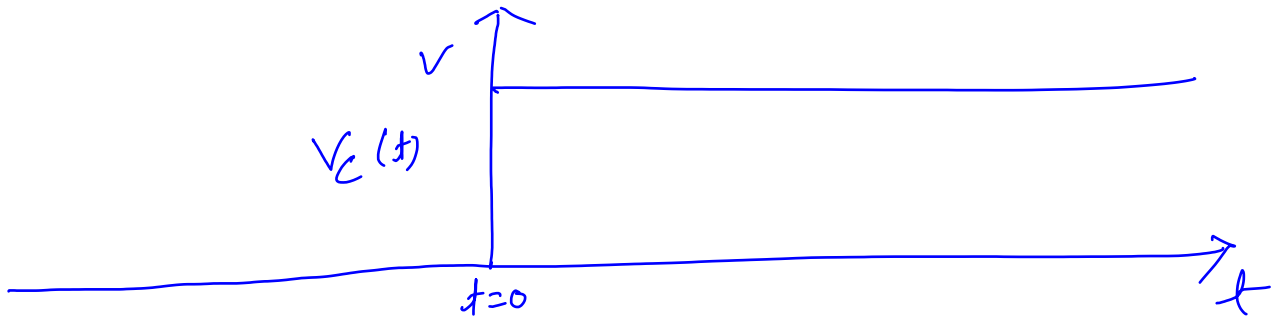


$$1) \quad \frac{dV_C}{dt} = 0 \quad \forall t \neq 0$$

$$2) \quad \frac{dV_C}{dt} \text{ is not defined at } t = 0$$

$$3) \quad \int_{-\infty}^{\infty} \frac{dV_C}{dt} dt = V$$

Dirac - delta function

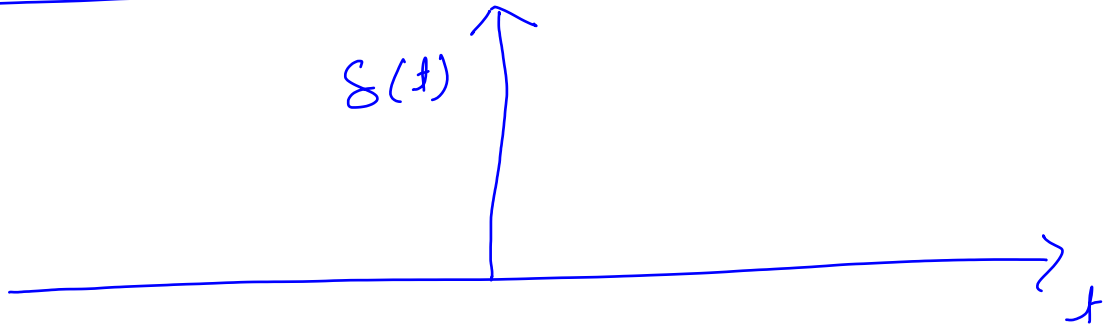

$$1) \quad \delta(t) = 0 \quad \forall t \neq 0$$

$$2) \quad \delta(t) \text{ is not defined at } t=0$$

$$3) \quad \int_{-\infty}^{\infty} \delta(t) dt = 1$$

$$\Rightarrow \quad \frac{d u(t)}{dt} = \delta(t)$$

$$u(t) = \int_{-\infty}^t \delta(t) dt$$

if $t < 0$,


$$u(t) = \int_{-\infty}^t \delta(t) dt = 0$$

if $t \geq 0$,

$$u(t) = \int_{-\infty}^t \delta(t) dt = \int_{-\infty}^{\infty} \delta(t) dt - \int_t^{\infty} \delta(t) dt$$

$$= 1 - 0 = 1$$

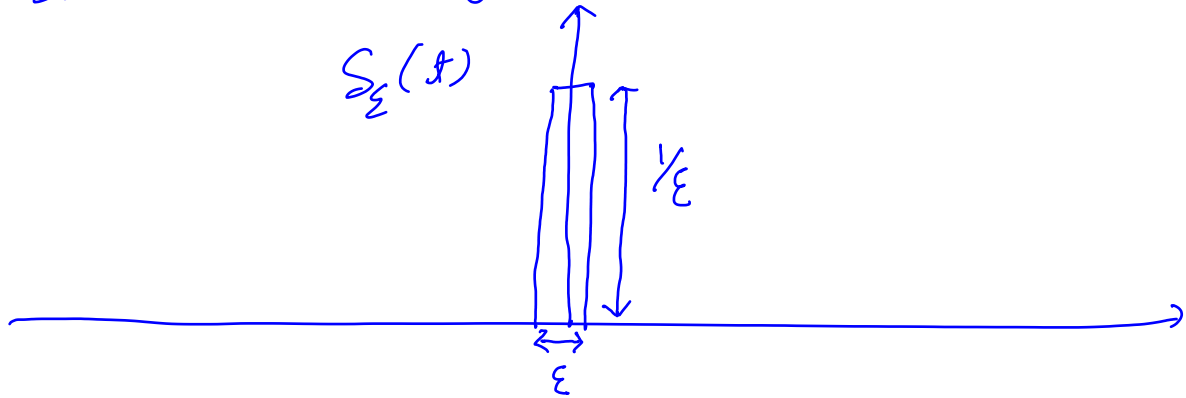
$$\int_{-\infty}^{+\infty} \delta(t) dt = \int_{0^-}^{0^+} \delta(t) dt = 1$$



$$S_\epsilon(t) = 0 \quad \forall t > \epsilon/2 \text{ and } \forall t < -\epsilon/2$$

$$= \frac{1}{\epsilon} \quad -\frac{\epsilon}{2} \leq t \leq \frac{\epsilon}{2}$$
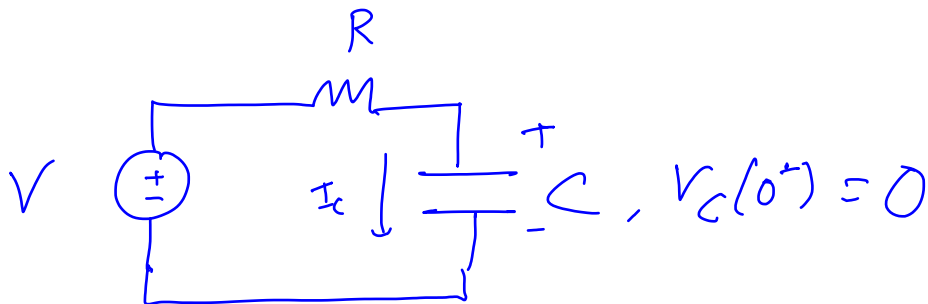
$$\delta(t) = \lim_{\epsilon \rightarrow 0} S_\epsilon(t)$$



$$V_c(t) = V (1 - e^{-t/RC}) \quad \forall t \geq 0$$

$$I_c(t) = C \frac{dV_c}{dt} = \frac{V}{R} e^{-t/RC}$$

U
 $R \rightarrow 0$

$$I_c(t) = S(t) \cdot C$$

(some constant)
Try to derive
the expression
of C ...

